
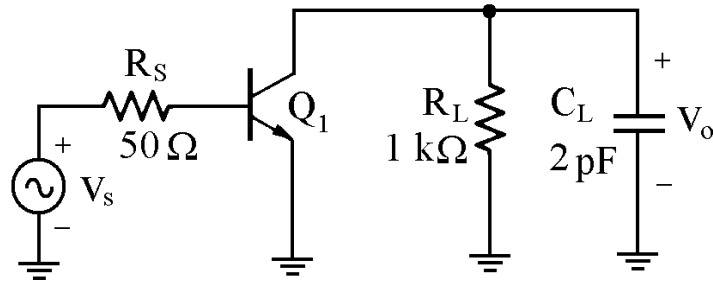


## EE4341 TUTORIAL 5 SOLUTION

1.

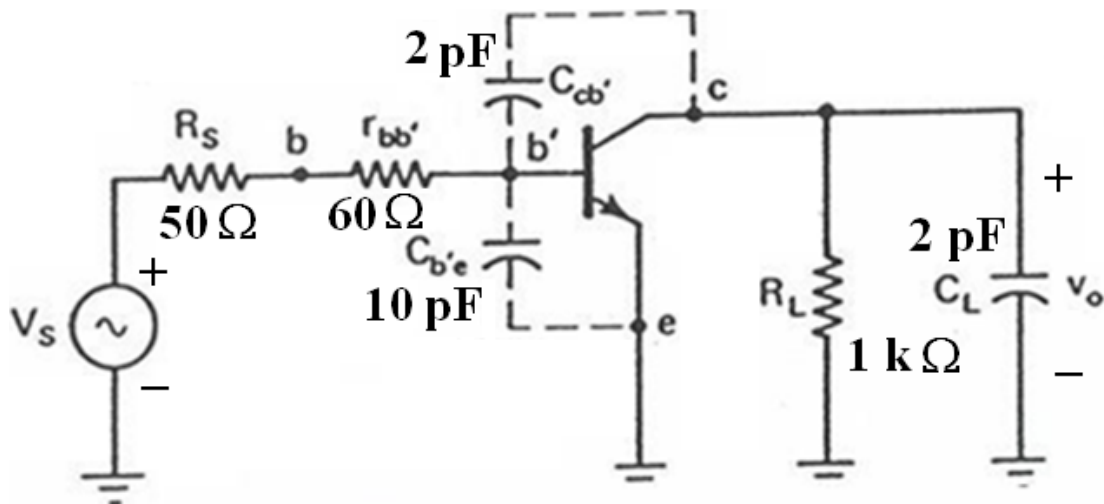

$Q_1$ :  $\beta = 60$ ,  $C_{cb'} = 2 \text{ pF}$ ,  $C_{b'e} = 10 \text{ pF}$  and  $r_{bb'} = 60 \text{ } \Omega$ ,  $V_T = 25 \text{ mV}$ .



Mid-band voltage gain  $v_o/v_s$  is given by:

$$v_o = -g_m v_s \left( \frac{r_\pi}{R_s + r_{bb'} + r_\pi} \right) R_L$$

$$- \frac{v_o}{v_s} = g_m R_L \left( \frac{r_\pi}{R_s + r_{bb'} + r_\pi} \right)$$

$$\therefore r_\pi = \frac{\beta}{g_m}$$

$$-\frac{v_o}{v_s} = \frac{\beta R_L}{R_s + r_{bb'} + \frac{\beta}{g_m}}$$

$$55 = \frac{60 \times 1k}{110 + \frac{60}{g_m}} \Rightarrow g_m = 61.2mS$$

$$I_c = g_m V_T = 61.2mS \times 25mV = 1.53mA$$

Two critical frequencies where roll-off of voltage gain happen:

$$f_1 = \frac{1}{2\pi[(R_s + r_{bb'}) // r_\pi]C_i}$$

$$C_i = C_{b'e} + C_{cb'}(1 + g_m R_L) = 10pF + 2pF(1 + 61.2) = 134.3pF$$


$$\therefore f_1 = \frac{1}{2\pi \times 99 \times 134.3p} = 12MHz$$

$$f_2 = \frac{1}{2\pi(R_L // r_o)C_o} \approx \frac{1}{2\pi R_L C_o}, \quad \because r_o \gg R_L$$

$$C_o = C_L + C_{cb'} \left( 1 + \frac{1}{g_m R_L} \right) = 2pF + 2pF \left( 1 + \frac{1}{61.2} \right) \approx 4pF$$


$$\therefore f_2 = \frac{1}{2\pi \times 1k \times 4p} = 40MHz$$
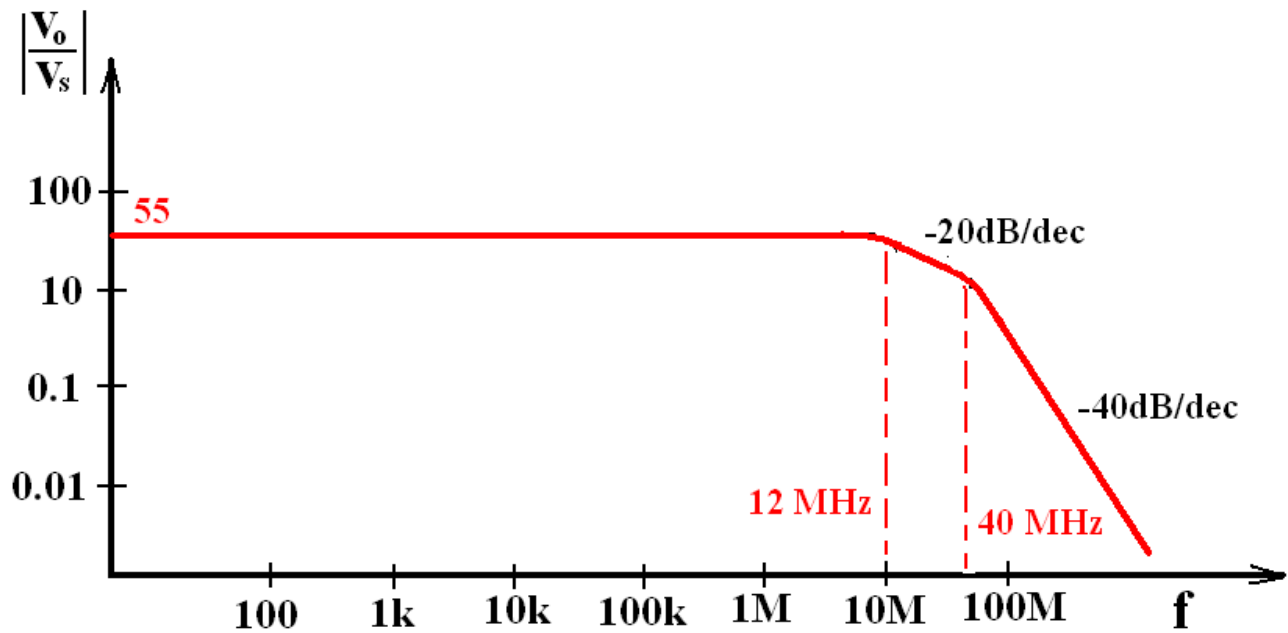
$$\frac{v_o}{v_s} = \frac{-55}{\left( 1 + \frac{jf}{f_1} \right) \left( 1 + \frac{jf}{f_2} \right)}$$



The -3dB bandwidth is dominated by  $f_1$ , which is about 12 MHz.

2.

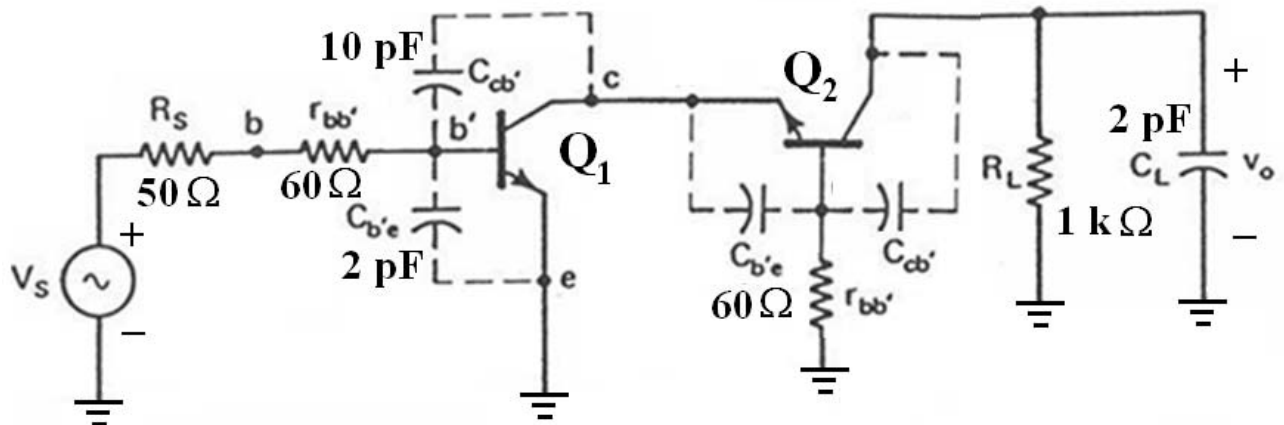

$$I_{C1} = I_{E2} = 1.53 \text{ mA}$$

$$r_{e2} = \frac{V_T}{I_{E2}} = \frac{1060}{61} = 16.3 \Omega$$

Mid-band voltage gain for the first stage:

$$A_{v1} = \frac{-v_{c1}}{v_s} = \left( \frac{-r_{\pi1}}{R_s + r_{bb'} + r_{\pi1}} \right) g_m r_{e2} = \left( \frac{-980}{110 + 980} \right) (61.2m \times 16.3) = -0.9$$

Mid-band voltage gain for the second stage:

$$A_{v2} = \frac{i_{c2} R_L}{i_{e2} r_{e2}} = \frac{\alpha R_L}{r_{e2}} = \left( \frac{60}{61} \right) \left( \frac{1k}{16.3} \right) = 60.2$$

Overall mid-band voltage gain:

$$A_v = \frac{v_o}{v_s} = A_{v1} \times A_{v2} = -0.9 \times 60.2 = -54.2$$

Three critical frequencies where roll-off of voltage gain happen:


$$C_i = C_{b'e} + C_{cb'} (1 + g_m r_{e2}) = 10pF + 2pF \times 2 \approx 14pF$$

$$\therefore f_1 = \frac{1}{2\pi[(R_s + r_{bb'}) // r_{\pi1}] C_i} = \frac{1}{2\pi \times 99 \times 14p} \approx 115MHz$$

$$f_2 = \frac{1}{2\pi r_{e2} \left[ C_{b'e} + C_{cb'} \left( 1 + \frac{1}{g_m r_{e2}} \right) \right]} = \frac{1}{2\pi r_{e2} (C_{b'e} + 2C_{cb'})} = \frac{1}{2\pi \times 16.3 \times 14p} \approx 700MHz$$


$$f_3 = \frac{1}{2\pi R_L \left[ C_L + C_{cb'} \left( 1 + \frac{1}{A_{v2}} \right) \right]} = \frac{1}{2\pi \times 1k \left[ 2p + 2p \left( 1 + \frac{1}{56.5} \right) \right]} \approx 40MHz$$
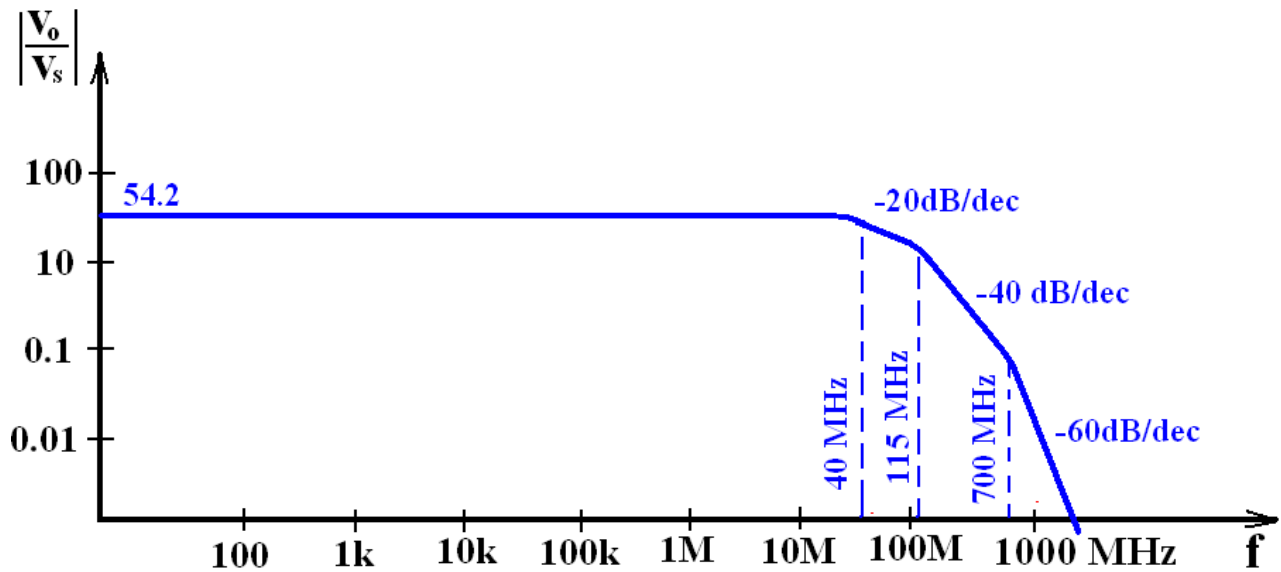
$$\frac{v_o}{v_s} = \frac{-54.2}{\left(1 + \frac{jf}{f_1}\right) \left(1 + \frac{jf}{f_2}\right) \left(1 + \frac{jf}{f_3}\right)}$$



The -3dB bandwidth is dominated by  $f_3$ , which is about 40 MHz.

3.

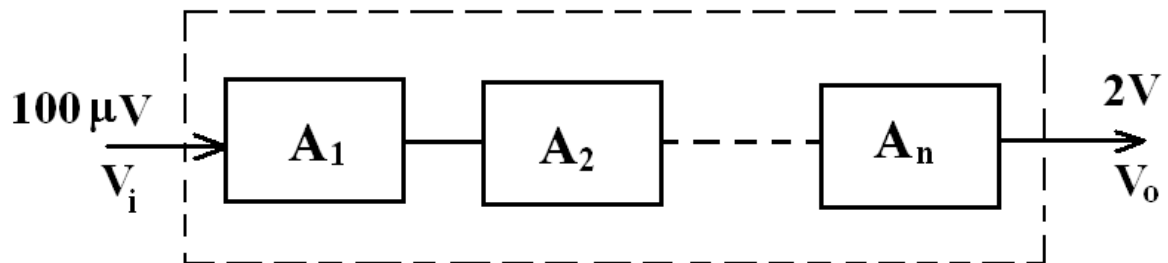

For n-stage of identical amplifiers, the overall gain response will be:

$$A_T = \frac{v_o}{v_i} = \frac{A^n}{\left(1 + \frac{jf}{f_p}\right)^n}$$

$$|A_T| = \frac{A^n}{\left( \sqrt{1 + \left( \frac{f}{f_p} \right)^2} \right)^n} = \frac{A^n}{\left( 1 + \left( \frac{f}{f_p} \right)^2 \right)^{\frac{n}{2}}}$$

If the -3dB bandwidth of the overall gain is  $f_1$ , then:

$$\begin{aligned} \frac{A^n}{\left( 1 + \left( \frac{f_1}{f_p} \right)^2 \right)^{\frac{n}{2}}} &= \frac{A^n}{2^{\frac{1}{2}}} \\ \therefore \left( 1 + \left( \frac{f_1}{f_p} \right)^2 \right)^n &= 2 \\ 1 + \left( \frac{f_1}{f_p} \right)^2 &= 2^{1/n} \Rightarrow f_1 = f_p \sqrt{2^{1/n} - 1} \end{aligned}$$

The required overall mid-band gain:

$$A_T = \frac{2V}{100\mu V} = 20,000$$

If  $n=2$ ,

$$f_p = \frac{f_1}{\sqrt{2^{1/n} - 1}} = \frac{30\text{MHz}}{\sqrt{2^{1/2} - 1}} = 46.6\text{MHz}$$

$$A = \frac{GBW}{f_p} = \frac{600}{46.6} = 12.9$$

$$\therefore A_T = (12.9)^2 = 166 < 20,000$$

If  $n = 4$ ,

$$f_p = \frac{f_1}{\sqrt{2^{1/n} - 1}} = \frac{30\text{MHz}}{\sqrt{2^{1/4} - 1}} = 69\text{MHz}$$

$$A = \frac{GBW}{f_p} = \frac{600}{69} = 8.7$$

$$\therefore A_T = (8.7)^4 = 5,728 < 20,000$$

If  $n = 5$ ,

$$f_p = \frac{f_1}{\sqrt{2^{1/n} - 1}} = \frac{30\text{MHz}}{\sqrt{2^{1/5} - 1}} = 78\text{MHz}$$

$$A = \frac{GBW}{f_p} = \frac{600}{78} = 7.7$$

$$\therefore A_T = (7.7)^5 = 27,280 > 20,000$$

Therefore, 5 stages are needed with 4 stages of identical gain = 7.7 and

the last stage gain = 5.7.