

# Small-Signal MOSFET Amplifiers

---

**E2002 Analog Electronics**

Prof. Zheng Yuanjin

Email: [yjzheng@ntu.edu.sg](mailto:yjzheng@ntu.edu.sg)

Office: S2.2-B2-16

Tel: 65927764

# Module Goals

---

Understanding of concepts related to:

- Biasing of Transistors (BJT and MOSFET)
  - dc and ac equivalent circuits for small-signal amplifier
  - Small-signal models of BJT and MOSFET
  - Amplifier characteristics such as voltage gain, input and output resistances
  - Analysis of three broad classes of single-stage amplifiers
    - Inverting amplifiers – common-emitter and common-source configurations
    - Followers – common-collector and common-drain configurations
    - Noninverting amplifiers – common-base and common-gate configurations
-

# References

---


## **Text Book**

1. Richard C. Jaeger and Travis N. Blalock,  
“Microelectronic Circuit Design”, 4th Edition, McGraw  
Hill, 2011, Chapters 4, 5, 13 and 14.


## **References**

1. Allan R. Hambley, “Electronics”, 2<sup>nd</sup> Edition, Prentice  
Hall, 2000
  2. Donald A. Neamen, “Electronic Circuit Analysis and  
Design”, 2<sup>nd</sup> Edition, McGraw-Hill, 2002
-

# MOSFET Regions of Operation

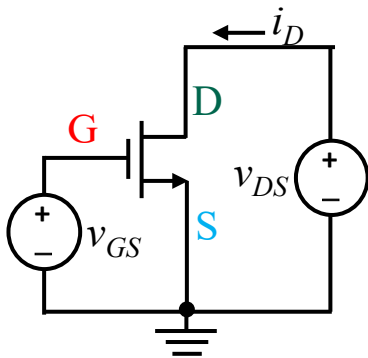

$V_{TN}$ : Threshold Voltage of NMOS

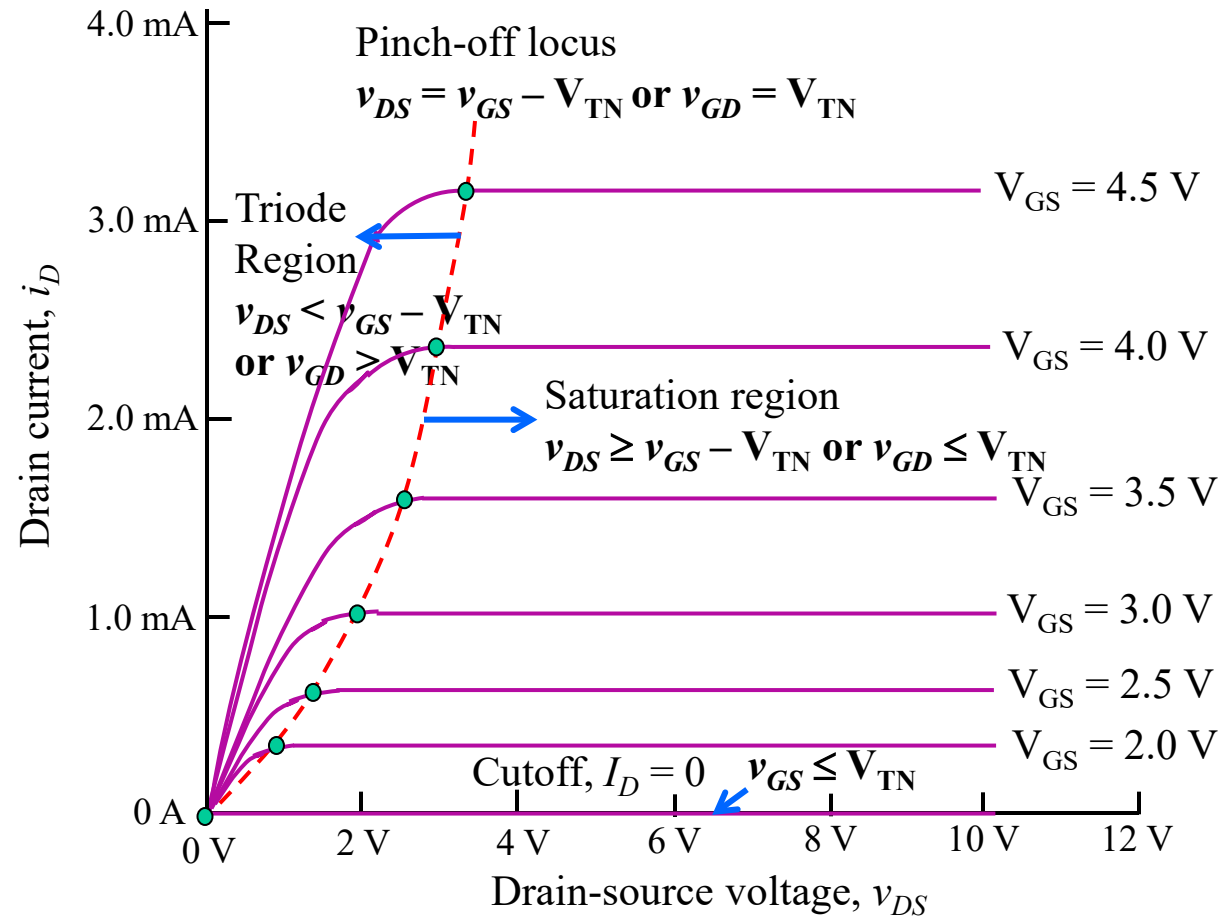

# MOSFET Biasing for Different Regions of Operation

In EE2002, only enhancement mode MOSFET is considered.

Region	NMOS	PMOS
Cutoff	$V_{GS} < V_{TN}$ $I_D = 0$	$ V_{GS}  <  V_{TP} $ $I_D = 0$
Triode	$V_{DS} < V_{GS} - V_{TN}$ $I_D = K_n \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$	$ V_{DS}  <  V_{GS}  -  V_{TP} $ $I_D = K_p \left(  V_{GS}  -  V_{TP}  - \frac{ V_{DS} }{2} \right)  V_{DS} $
Saturation	$V_{DS} \geq V_{GS} - V_{TN}$ $I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2$	$ V_{DS}  \geq  V_{GS}  -  V_{TP} $ $I_D = \frac{K_p}{2} ( V_{GS}  -  V_{TP} )^2$

$$K_n = \mu_n C_{ox} \left( \frac{W}{L} \right) \text{ and } K_p = \mu_p C_{ox} \left( \frac{W}{L} \right)$$

# MOSFET Bias Analysis Approach


---

- Assume saturation region (unless operation region is obvious)
- Use circuit analysis to find  $V_{GS}$
- Use  $V_{GS}$  to calculate  $I_D$ , and  $I_D$  to find  $V_{DS}$
- Check validity of operation region assumption
- Change assumption and analyze again if required.

NOTE: An enhancement-mode MOSFET with  $V_{DS} = V_{GS}$  is always in saturation because  $|V_{DS}|$  always greater than  $(|V_{GS}| - |V_{TX}|)$ , where  $X$  is  $N$  or  $P$  for threshold voltage of NMOS or PMOS, respectively.

---

# MOSFET Bias Analysis: Triode Region

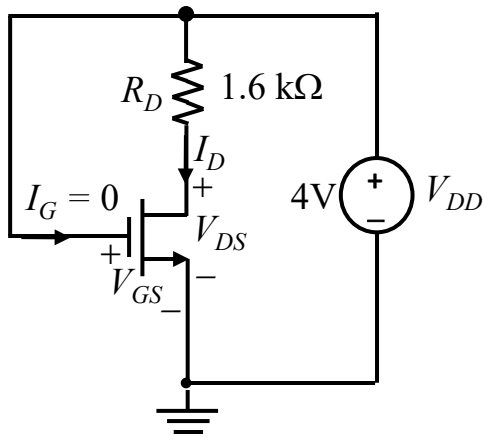

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{250\mu}{2} (4 - 1)^2 = 1.13 \text{ mA}$$

$$V_{DD} = I_D R_D + V_{DS}$$

$$V_{DS} = 4 - 1.6 \times 1.13 = 2.19 \text{ V}$$

But  $V_{DS} = 2.19 < V_{GS} - V_{TN} = 4 - 1 = 3$ ,  
Saturation region assumption is incorrect.

$$K_n = 250 \mu\text{A/V}^2$$

$$V_{TN} = 1 \text{ V}$$

Assume transistor is  
saturated,

$$V_{GS} = V_{DD} = 4 \text{ V.}$$


Using triode region equation,  $I_D = K_n \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$

$$V_{DS} = 4 - 1600 \times 250\mu (4 - 1 - V_{DS}/2) V_{DS}$$

$$V_{DS} = \mathbf{2.3 \text{ V}} \text{ and } I_D = \mathbf{1.06 \text{ mA}}$$

$V_{DS} = 2.3 < V_{GS} - V_{TN} = 3$ , transistor is in triode region.
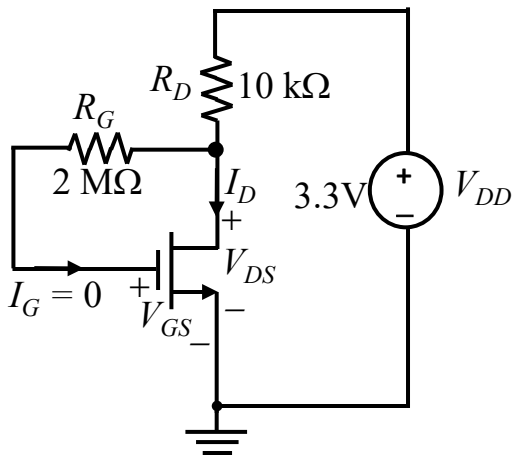
# MOSFET Bias Analysis: nMOS Two-Resistor Biasing



$$K_n = 260 \mu\text{A}/\text{V}^2$$

$$V_{TN} = 1 \text{ V}$$

Since  $I_G = 0$ ,  $V_{DS} = V_{GS}$   
Transistor is saturated

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{GS} = 3.3 - \frac{260\mu}{2} (V_{GS} - 1)^2 \times 10000 = 3.3 - 1.3(V_{GS} - 1)^2$$

$$1.3V_{GS}^2 - 1.6V_{GS} - 2 = 0$$

$$V_{GS} = \frac{1.6 \pm \sqrt{1.6^2 - 4 \times 1.3 \times -2}}{2 \times 1.3}$$

$$V_{GS} = -0.77 \text{ V or } 2 \text{ V}$$


$V_{GS} = -0.77 \text{ V}$  implies MOSFET is cutoff and contradict the observation.

$$V_{GS} = 2 \text{ V and } V_{DS} = V_{GS} = 2 \text{ V.}$$

$$I_D = 130\mu \times (2 - 1)^2 = 130 \mu\text{A.}$$


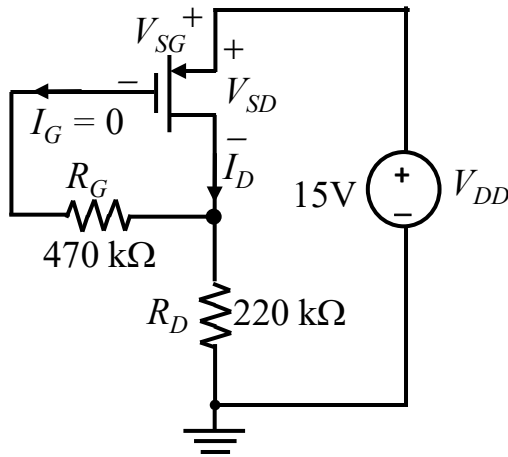
# MOSFET Bias Analysis: pMOS Two-Resistor Biasing



$$K_p = 50 \mu\text{A}/\text{V}^2$$

$$V_{TP} = -2 \text{ V}$$

Since  $I_G = 0$ ,  $V_{SD} = V_{SG}$   
Transistor is saturated

$$V_{SD} = V_{DD} - I_D R_D$$

$$|V_{GS}| = 15 - \frac{50\mu}{2} (|V_{GS}| - |V_{TP}|)^2 \times 220k = 15 - 5.5 (|V_{GS}| - 2)^2$$

$$5.5|V_{GS}|^2 - 10|V_{GS}| - 11 = 0$$

$$|V_{GS}| = \frac{10 \pm \sqrt{10^2 - 4 \times 5.5 \times -11}}{2 \times 5.5}$$

$$|V_{GS}| = 0.37 \text{ V or } 3.45 \text{ V}$$

Since  $|V_{GS}| = 0.37 \text{ V} < |V_{TP}| = 2 \text{ V}$ ,

$$|V_{GS}| = 3.45 \text{ V or } V_{SG} = 3.45 \text{ V}$$

$$I_D = 25\mu \times (3.45 - 2)^2 = 52.5 \mu\text{A}$$


$$V_{SD} = V_{SG} = 3.45 \text{ V}$$

# Introduction to Amplifiers

---

- BJT is an excellent amplifier when biased in forward-active region
  - MOSFET can be used as amplifier when biased in saturation region.
  - In these regions, transistors can provide high voltage, current and power gains.
  - Bias refers to setting the ‘quiescent’ (idle) current when there is no signal presence. It sets the transistor in the desired operation region.
  - Q-point (determined by DC analysis) also determines
    - Small-signal parameters of transistor
    - Voltage gain, input resistance, output resistance
    - Maximum input and output signal amplitudes
    - Power consumption
    - Efficiency (o/p signal power vs DC i/p power)
-

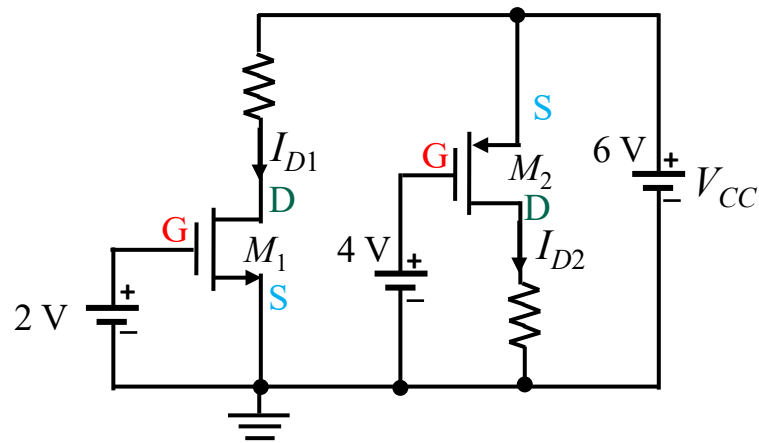
# Biasing MOSFET for linear amplification



MOSFET is biased in **saturation region** (corresponding to the forward-active of BJT) for small-signal amplifier.

pMOS behaves like nMOS with all the polarities reversed.



nMOS	pMOS
$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2$	$I_D = \frac{K_p}{2} ( V_{GS}  -  V_{TP} )^2$
with <b>channel length modulation</b> :	with <b>channel length modulation</b> :
$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$	$I_D = \frac{K_p}{2} ( V_{GS}  -  V_{TP} )^2 (1 + \lambda  V_{DS} )$

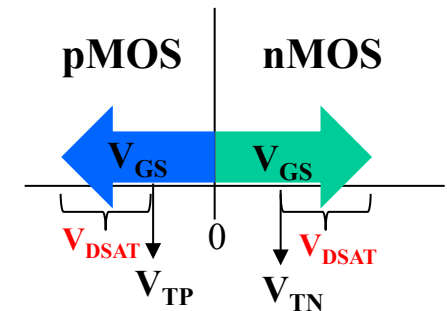

$$V_{SAT} = |V_{GS}| - |V_{TX}| > 0$$

$$X = N \text{ or } P$$

# MOSFET Amplifier

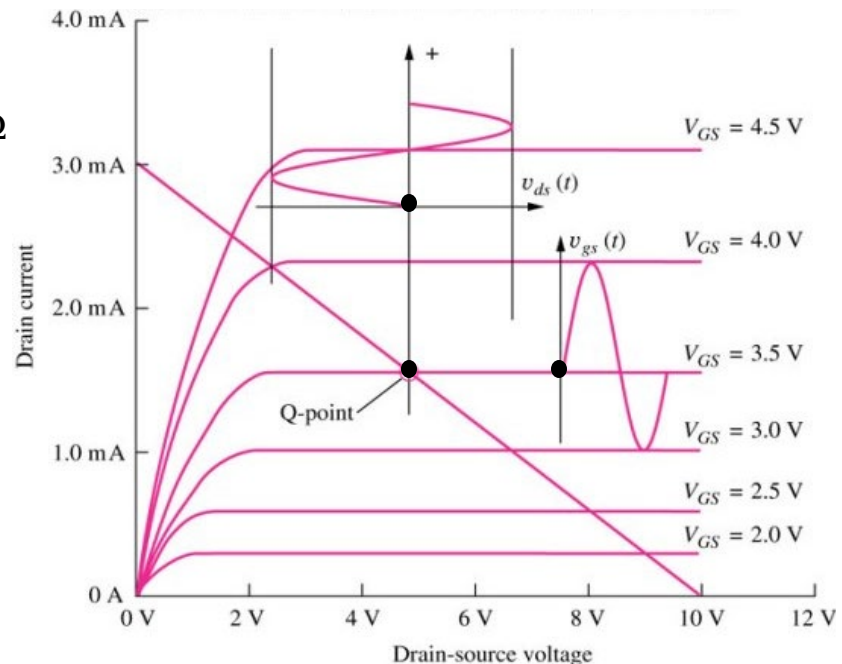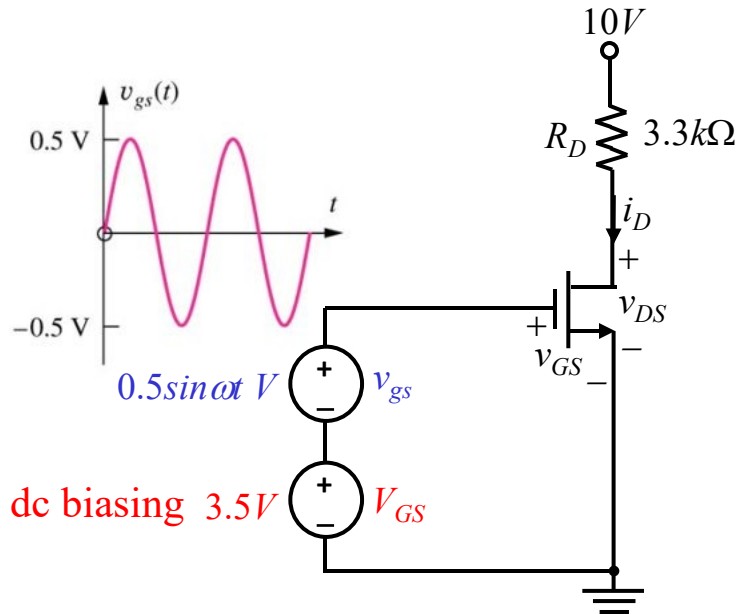

Q-point is set at  $(I_D, V_{DS}) = (1.56 \text{ mA}, 4.8 \text{ V})$  with  $V_{GS} = 3.5 \text{ V}$ .

Total gate-source voltage is:  $v_{GS} = V_{GS} + v_{gs}$

1 V *p-p* change in  $v_{GS} \Rightarrow 1.25 \text{ mA } p\text{-}p$  change in  $i_D \Rightarrow 4 \text{ V } p\text{-}p$  change in  $v_{DS}$ .


# DC and AC Analysis

---

- DC analysis:
  - Obtain dc equivalent circuit by replacing all capacitors by open circuits and inductors by short circuits. ac voltage sources by ground connections and ac current sources by open circuits.
  - Find Q-point from dc equivalent circuit by using appropriate large-signal transistor model.
- AC analysis:
  - Obtain ac equivalent circuit by replacing all capacitors by short circuits, inductors by open circuits, dc voltage sources by ground connections and dc current sources by open circuits.
  - Replace transistor by small-signal model
  - Use small-signal ac equivalent to analyze ac characteristics of amplifier.
- Combine end results of dc and ac analysis to yield total voltages and currents in the network.


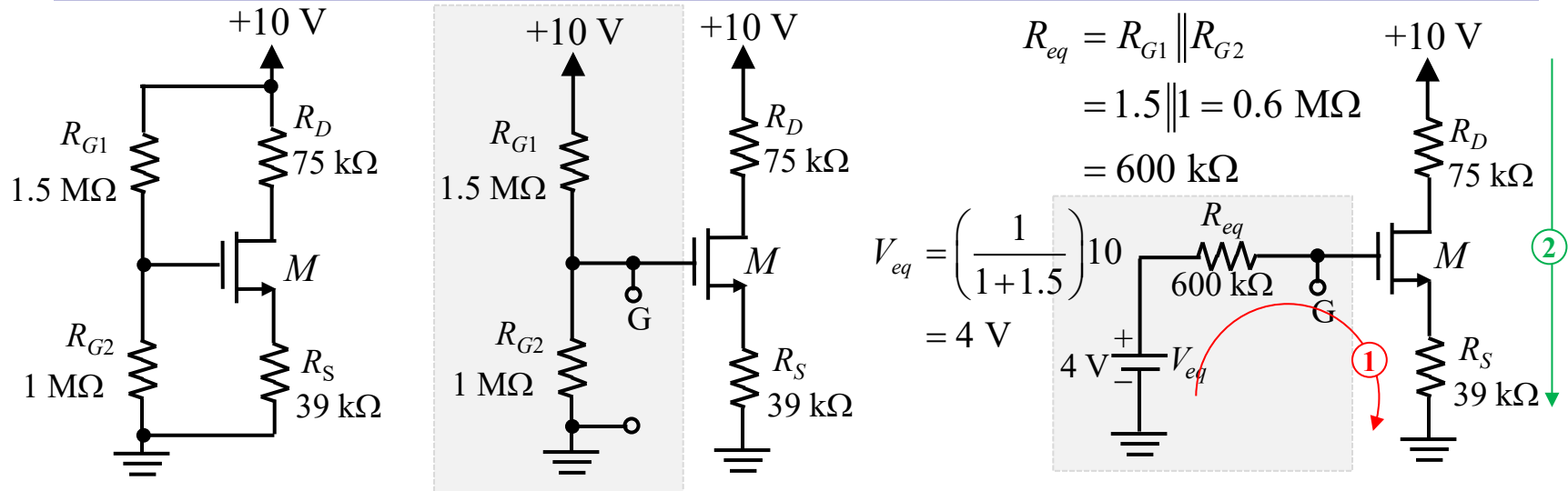
# DC Analysis Example: Four-Resistor MOSFET Biasing Circuit



**KVL 1:** Since  $I_G = 0$ ,  $V_{eq} = V_{GS} + I_D R_S$   
 $4 = V_{GS} + 0.5 \times 25 \mu (\text{V}_{GS} - 1)^2 \times 39 \text{ k}$   
 $V_{GS}^2 + 0.05 V_{GS} - 7.21 = 0$   
 $V_{GS} = -2.71 \text{ or } 2.66 \text{ V}$   
 Since  $V_{GS} = -2.71 < V_{TN} = 1$ ,  
 $V_{GS} = 2.66 \text{ V}$ .


$$I_D = (4 - 2.66) / 39 \text{ k} = \mathbf{34.4 \mu A}$$

**KVL 2:**  $V_{DS} = 10 - I_D R_D - I_S R_S$   
 $V_{DS} = 10 - 0.0344 \times (75 + 39) = \mathbf{6.08 \text{ V}}$   
 Since  $V_{DS} > V_{GS} - V_{TN} = 1.66$ ,  
 $M$  is in saturation region.


# DC and AC Equivalents for MOSFET Amplifier

$$X_L = \omega L$$


$$\omega = 0 \text{ rad/s}, X_L = 0$$

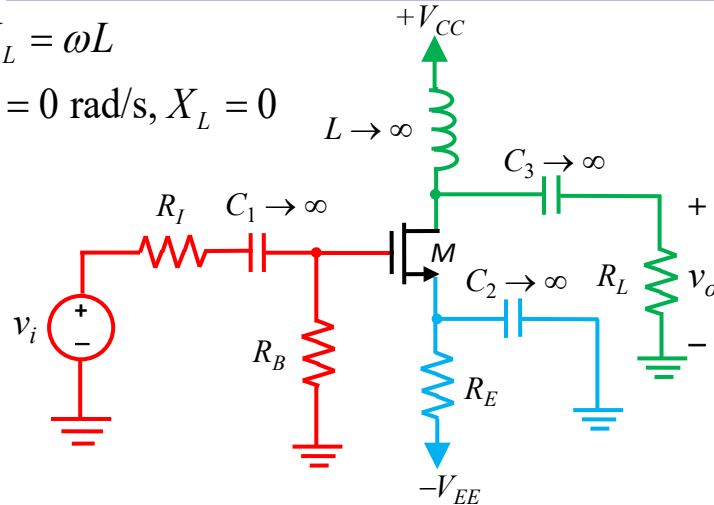


dc equivalent

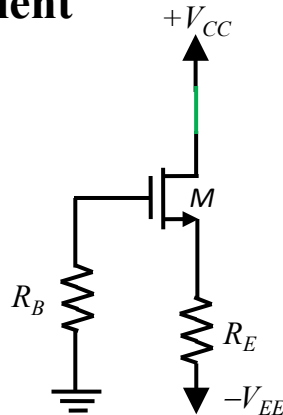


ac equivalent

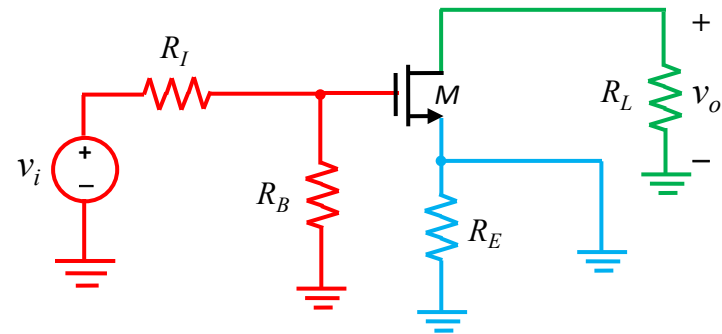

Simplified ac equivalent

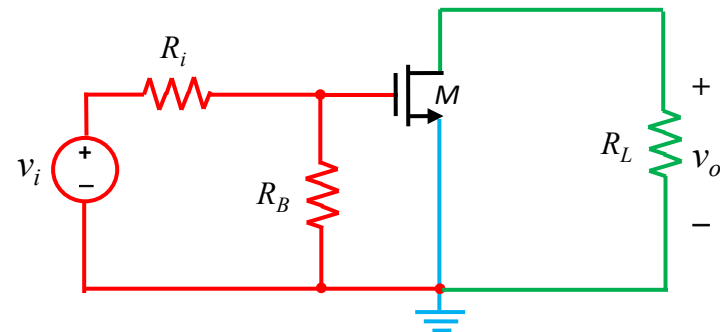

# Small Signal Parameters of MOSFET

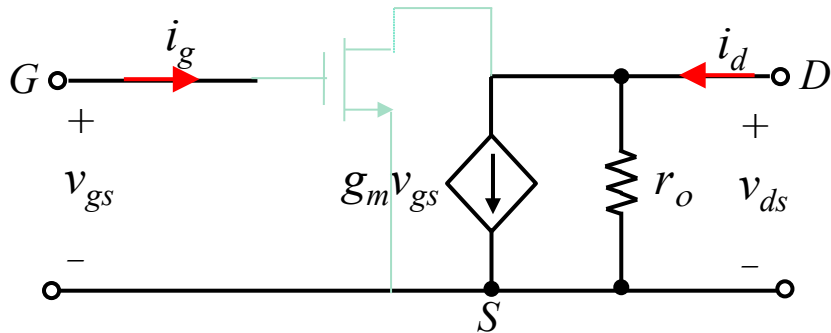

- Since gate is insulated from channel by gate-oxide input resistance =  $\infty$ .
- Small-signal parameters are controlled by the Q-point.
- For same operating point, MOSFET has lower transconductance than BJT. MOSFET transconductance is geometry dependent.

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{Q-pt} = K_n (V_{GS} - V_{TN}) (1 + \lambda V_{DS})$$

$$\text{where } K_n = \mu_n C_{OX} \left( \frac{W}{L} \right)$$

$$g_m = \frac{I_D}{\frac{V_{GS} - V_{TN}}{2}} = \sqrt{2K_n I_D}$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \cong \frac{1}{\lambda I_D}$$



# Small Signal Operation of MOSFET

---

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 \quad \text{for } v_{DS} \geq v_{GS} - V_{TN}$$

$$i_D = \frac{K_n}{2} (V_{GS} + v_{gs} - V_{TN})^2 = \frac{K_n}{2} \left[ (V_{GS} - V_{TN})^2 + 2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2 \right]$$

$$i_d = i_D - I_D = \frac{K_n}{2} \left[ 2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2 \right]$$


For linearity,  $i_d$  should be proportional to  $v_{gs}$

$$v_{gs} \ll 2(V_{GS} - V_{TN}) \Rightarrow v_{gs} \leq 0.2(V_{GS} - V_{TN})$$

Since MOSFET can be biased with  $(V_{GS} - V_{TN})$  equal to several volts, it can handle much larger values of  $v_{gs}$  than corresponding values of  $v_{be}$  for BJT.




# Small-Signal Model for PMOS

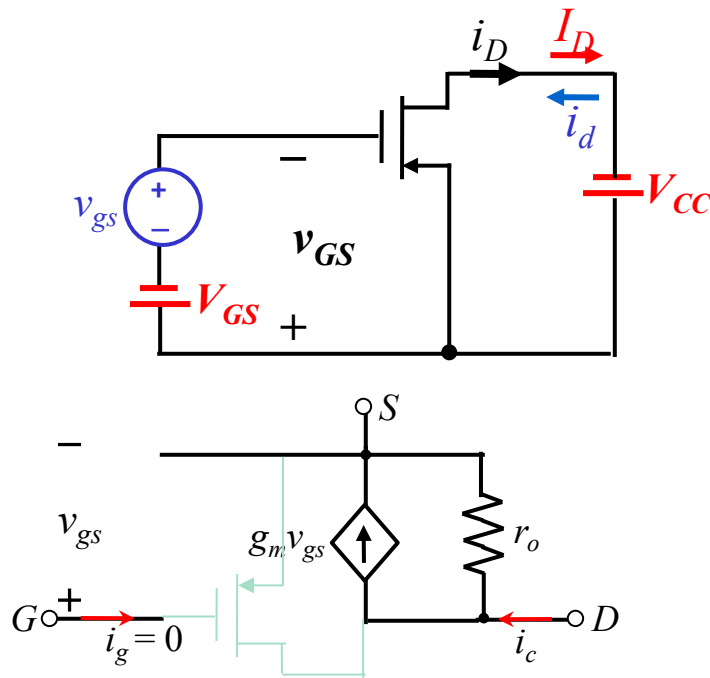

$$\downarrow v_{GS} = V_{GS} - v_{gs} \uparrow$$

$$\downarrow i_D = I_D - i_d \uparrow$$

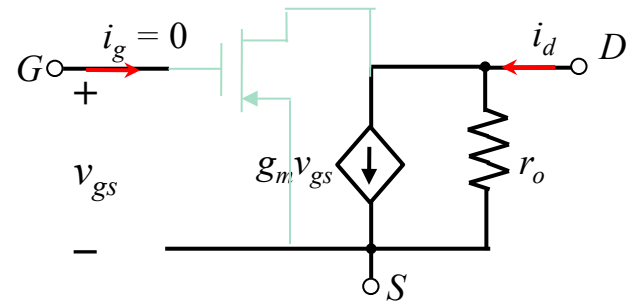


The small signal model for  $p$ MOS is exactly IDENTICAL to that of  $n$ MOS. This is not a mistake because the current direction is taken care of by the polarity of  $V_{GS}$ .



# Summary of Small Signal Parameters

Parameter	BJT	$n$ -MOSFET
$g_m$	$\frac{I_C}{V_T}$	$\frac{2I_D}{V_{GS} - V_{TN}}$ $K_n (V_{GS} - V_{TN})(1 + \lambda V_{DS}) \approx K_n (V_{GS} - V_{TN})$ $\sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$
$r_\pi$	$\frac{\beta}{g_m} = \frac{\beta V_T}{I_C}$	$\infty$
$r_o$	$\frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$	$\frac{1}{\lambda} + V_{DS} \approx \frac{1}{\lambda I_D}$
Small-signal requirement	$v_{be} \leq 0.005 \text{ V}$	$v_{gs} \leq 0.2 (V_{GS} - V_{TN})$

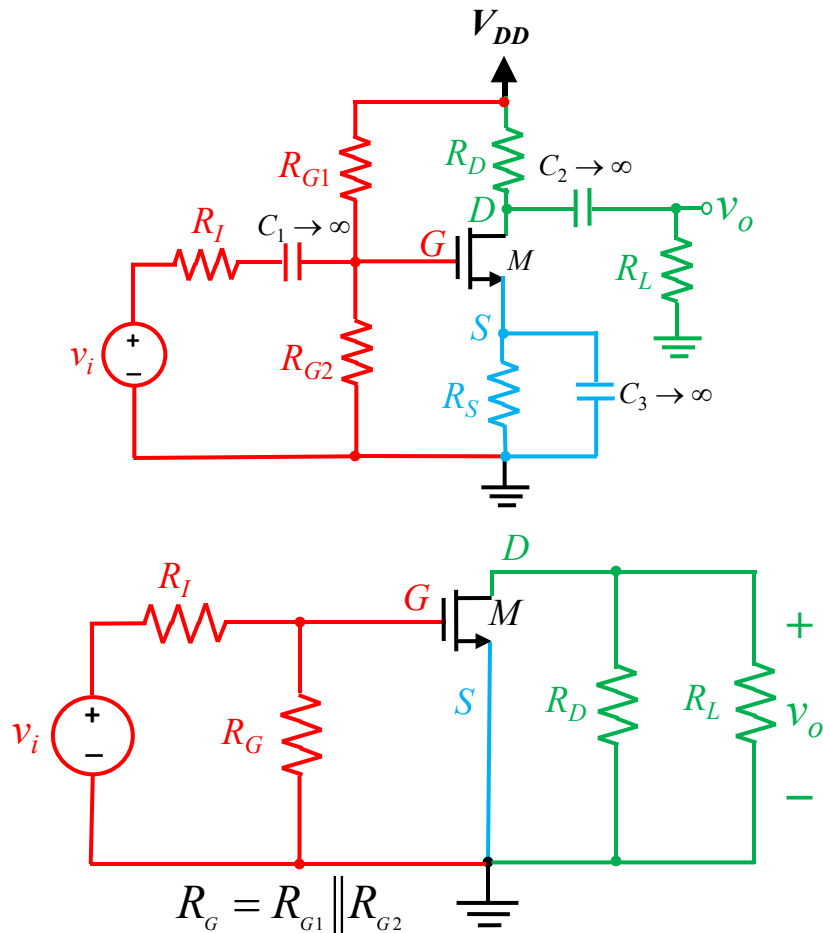
# Small Signal Analysis of Fully Bypass C-S Amplifier



- AC equivalent circuit is constructed by assuming that all capacitances have zero impedance at signal frequency and dc voltage sources represent ac grounds.
- The small signal parameters,  $g_m$  and  $r_o$  of the MOSFET is calculated at the Q-point,  $I_D$  and  $V_{DS}$ .


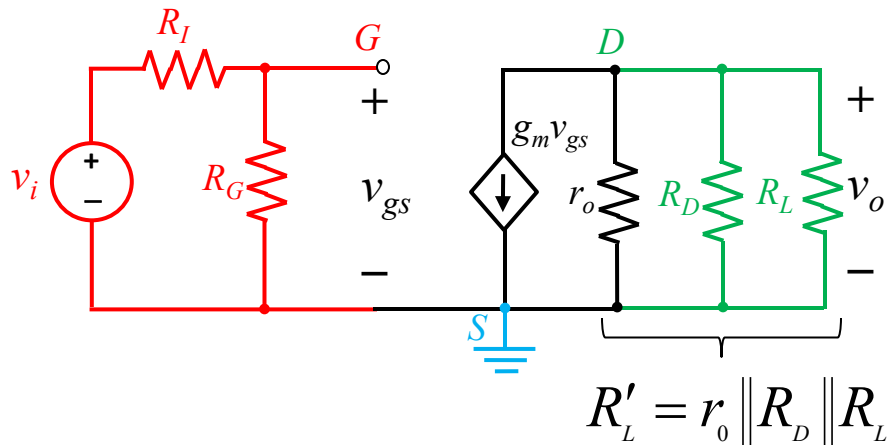
# Fully Bypass C-S Amplifier: Voltage Gain



Overall voltage gain from source  $v_i$  to output voltage across  $R_L$  is:



$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_g} \times \frac{v_g}{v_i} = A_{vt} \times \frac{v_g}{v_i}$$

$$= -g_m R'_L \left( \frac{R_G}{R_I + R_G} \right)$$

**Terminal voltage gain** between gate and drain is:

$$A_{vt} = \frac{v_d}{v_g} = \frac{-g_m v_{gs} R'_L}{v_{gs}} = -g_m R'_L$$
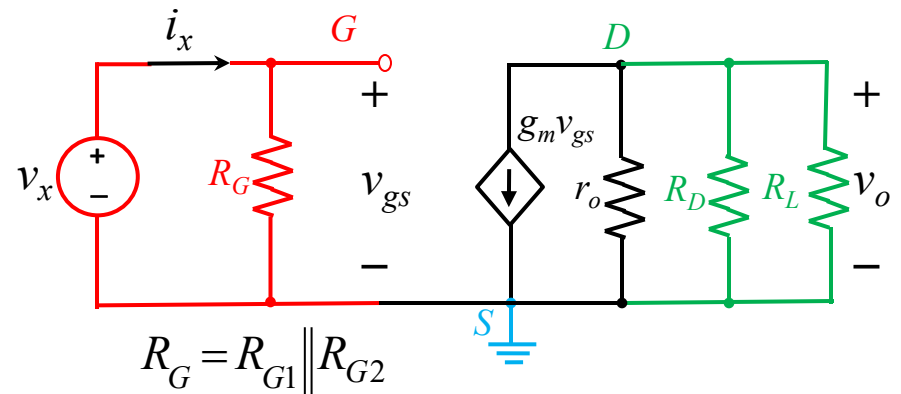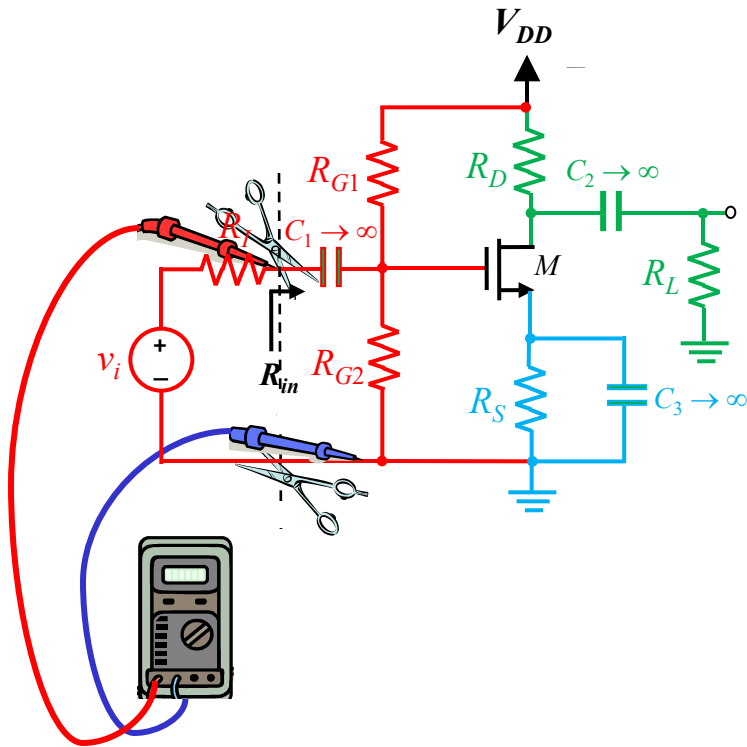
# Fully Bypass C-S Amplifier Input Resistance




$$v_x = i_x R_G$$

$$R_{in} = \frac{v_x}{i_x} = R_G$$



# Fully Bypass C-S Amplifier

## Output Resistance

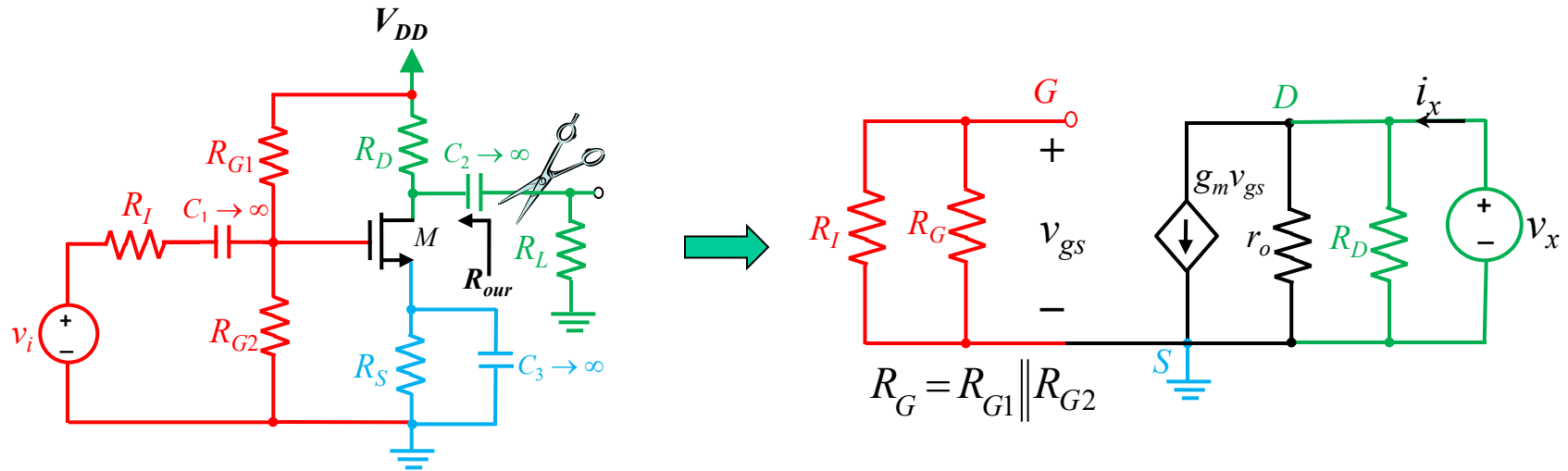

Since  $v_{gs} = 0$ ,  $g_m v_{gs} = 0$ .


$$v_x = i_x (R_D \parallel r_o)$$

$$R_{out} = \frac{v_x}{i_x} = R_D \parallel r_o$$

$$R_{out} \approx R_D \text{ if } r_o \gg R_D$$




# Fully Bypass C-S Amplifier Example

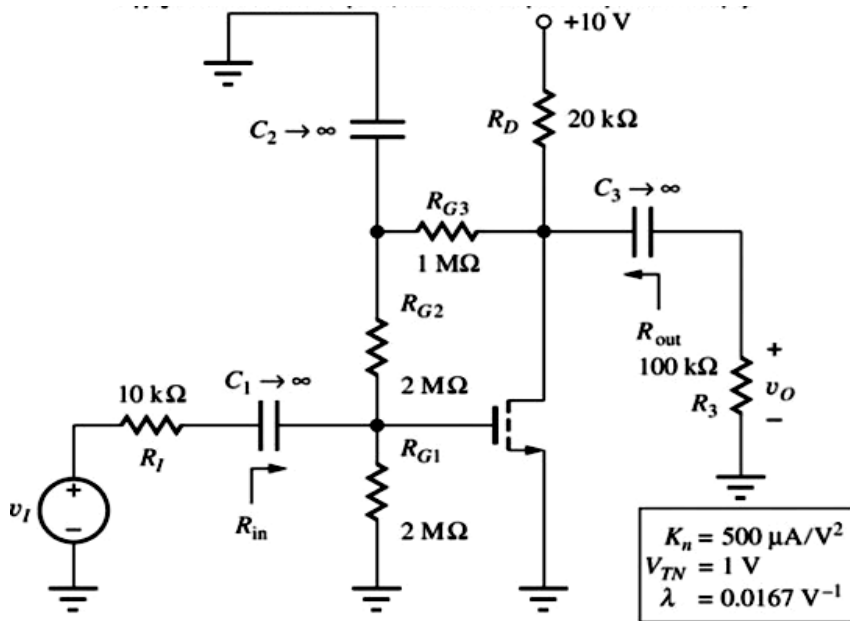

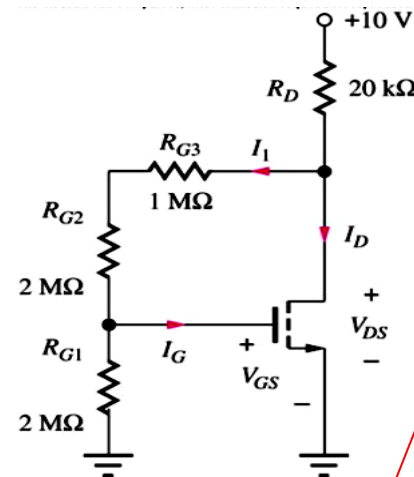**Problem:** Find voltage gain, input and output resistances.

**Given**  $K_n = 500 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 1\text{V}$ ,  
 $\lambda = 0.0167 \text{ V}^{-1}$



DC Analysis:

$$I_1 = \frac{V_{DS}}{5 \times 10^6}$$

$$V_{GS} = I_1 \times 2 \times 10^6 = 0.4 V_{DS}$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \dots\dots (1)$$


$$V_{DS} = 10 - 20 \times 10^3 (I_D + I_1) \text{ L L } (2)$$

$$\therefore V_{DS} = 5\text{V}, V_{GS} = 2\text{V}, I_D = 250 \mu\text{A}$$



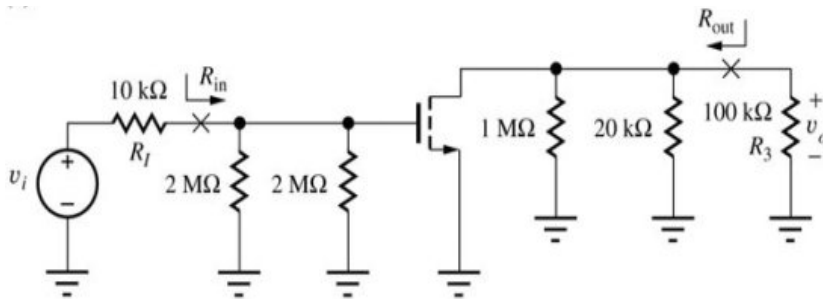
# Fully Bypass C-S Amplifier Example (contd.)

Construct the ac equivalent and simplify it.




$$g_m \approx \sqrt{2K_n I_D} = 5.20 \times 10^4 \text{ S}$$
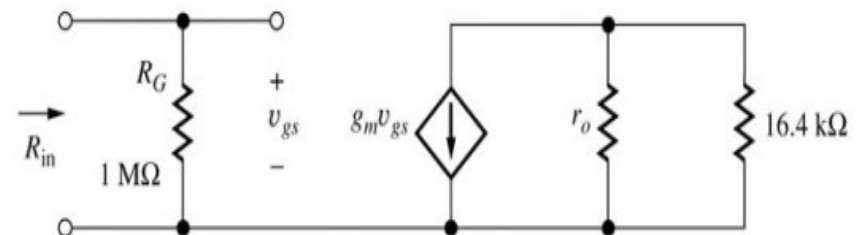
$$r_o = \frac{1}{\lambda} \frac{V_{DS}}{I_D} = 260 \text{ k}\Omega$$


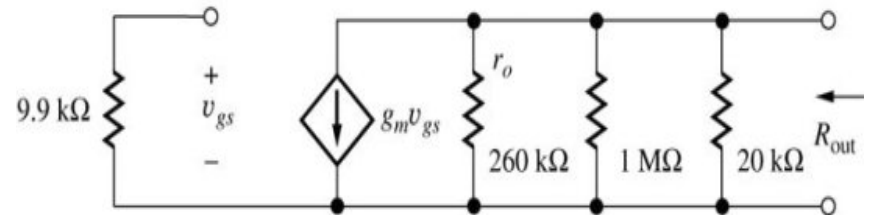
$$R_{in} = R_G = R_{G1} \parallel R_{G2} = 1 \text{ M}\Omega$$





$$R_{out} = r_o \parallel R_D \parallel R_{G3} = 18.2 \text{ k}\Omega$$

$$A_v = \frac{v_o}{v_i} = -g_m (R_{out} \parallel R_3) \left[ \frac{R_{in}}{R_I + R_{in}} \right] = -7.93$$

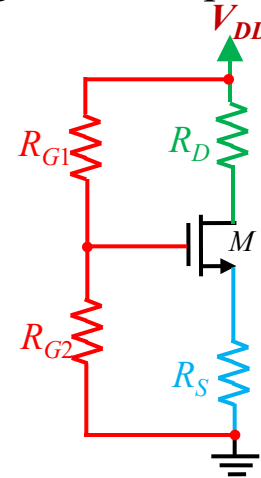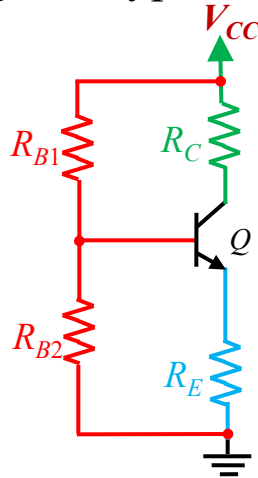
# Amplifier Families

- Constraints for signal injection and extraction yield three families of amplifiers
  - Common-Emitter (C-E)/Common- Source (C-S)
  - Common-Base (C-B)/Common- Gate (C-G)
  - Common-Collector (C-C)/Common- Drain (C-D)
- All circuit examples here use the four-resistor bias circuits to establish Q-point of the various amplifiers
- Coupling and bypass capacitors are used to change the ac equivalent circuits.


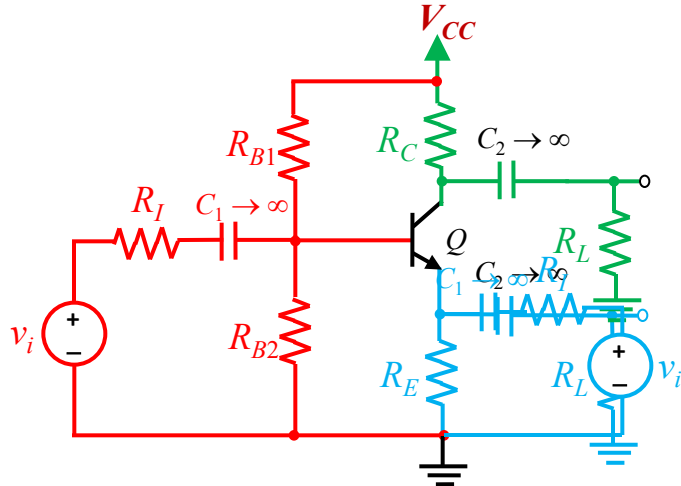
# Amplifier Family

$$i_e \approx i_c \approx I_s \exp\left(\frac{v_b - v_e}{V_T}\right)$$




C-E: i/p at **B**, o/p at **C**

C-C: i/p at **B**, o/p at **E**

C-B: i/p at **E**, o/p at **C**
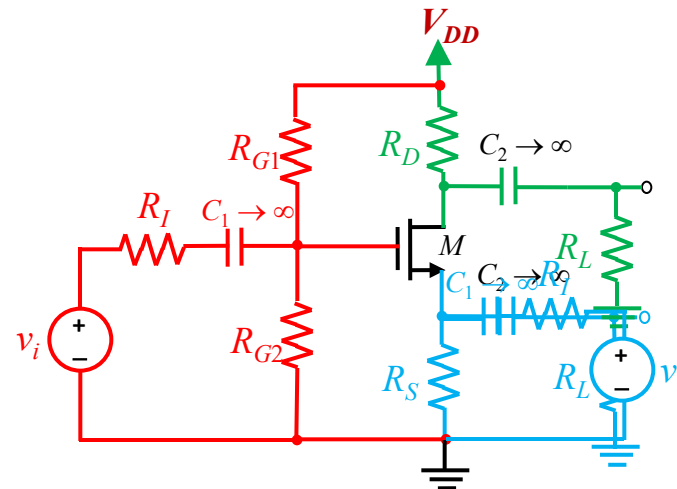
$$i_s = i_d \approx \frac{K_n}{2} (v_g - v_s - V_{TN})^2$$




C-S: i/p at **G**, o/p at **D**

C-D: i/p at **G**, o/p at **S**

C-G: i/p at **S**, o/p at **D**


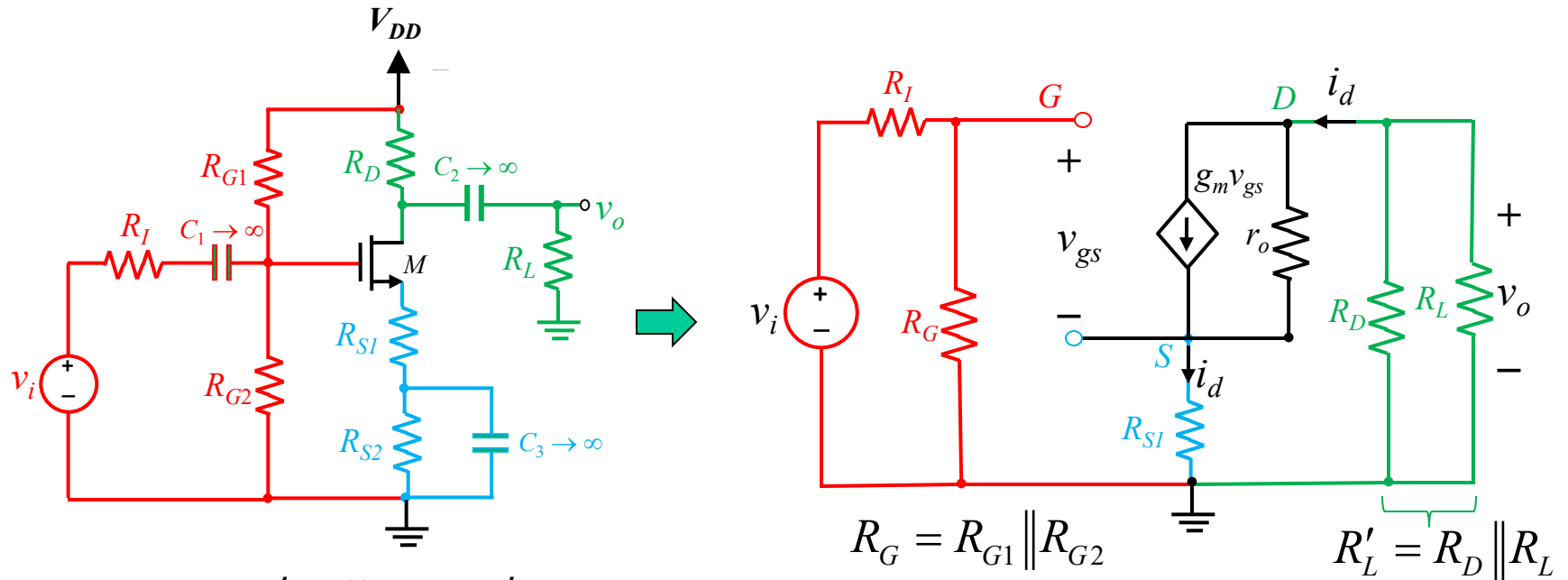
# C-S Amplifier (Inverting Amplifier): Terminal Voltage Gain





$$\because i_{r_o} \ll g_m v_{gs}, i_d \approx g_m v_{gs}$$

$$A_{vt} = \frac{v_d}{v_g} = \frac{-i_d R'_L}{v_{gs} + i_d R_{S1}} \approx \frac{-g_m v_{gs} R'_L}{v_{gs} + g_m v_{gs} R_{S1}} = \frac{-g_m R'_L}{1 + g_m R_{S1}}$$



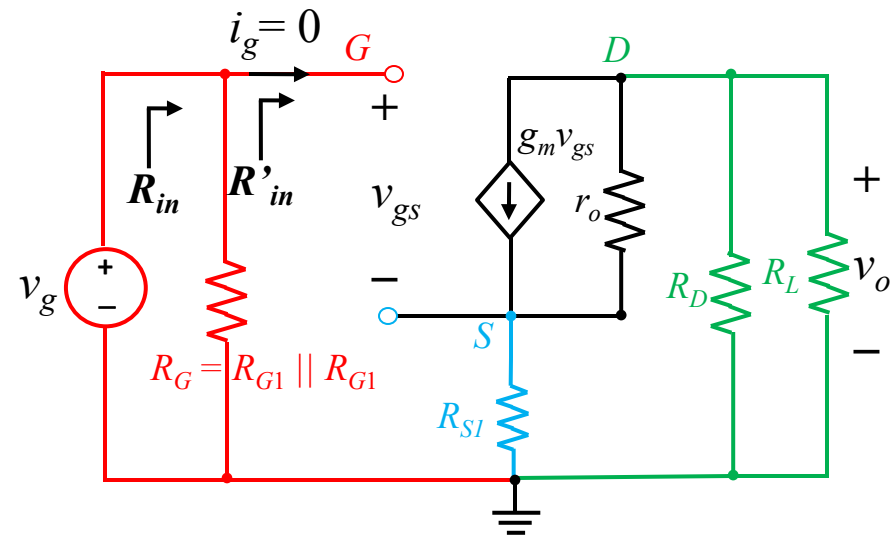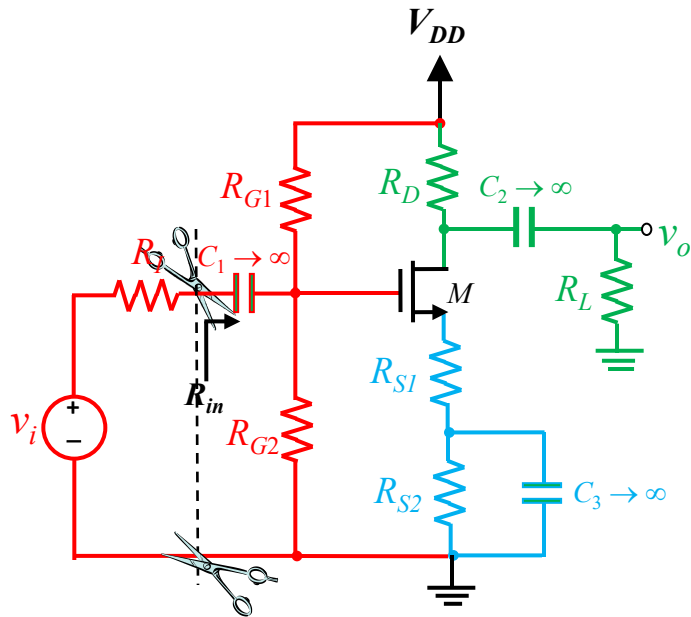
# C-S Amplifier (Inverting Amplifier): Input Resistance




$$\because i_g = 0, R_{in}' = \frac{v_g}{i_g} = \infty \quad \Rightarrow \quad R_{in} = R_{in}' \parallel R_G = R_G$$


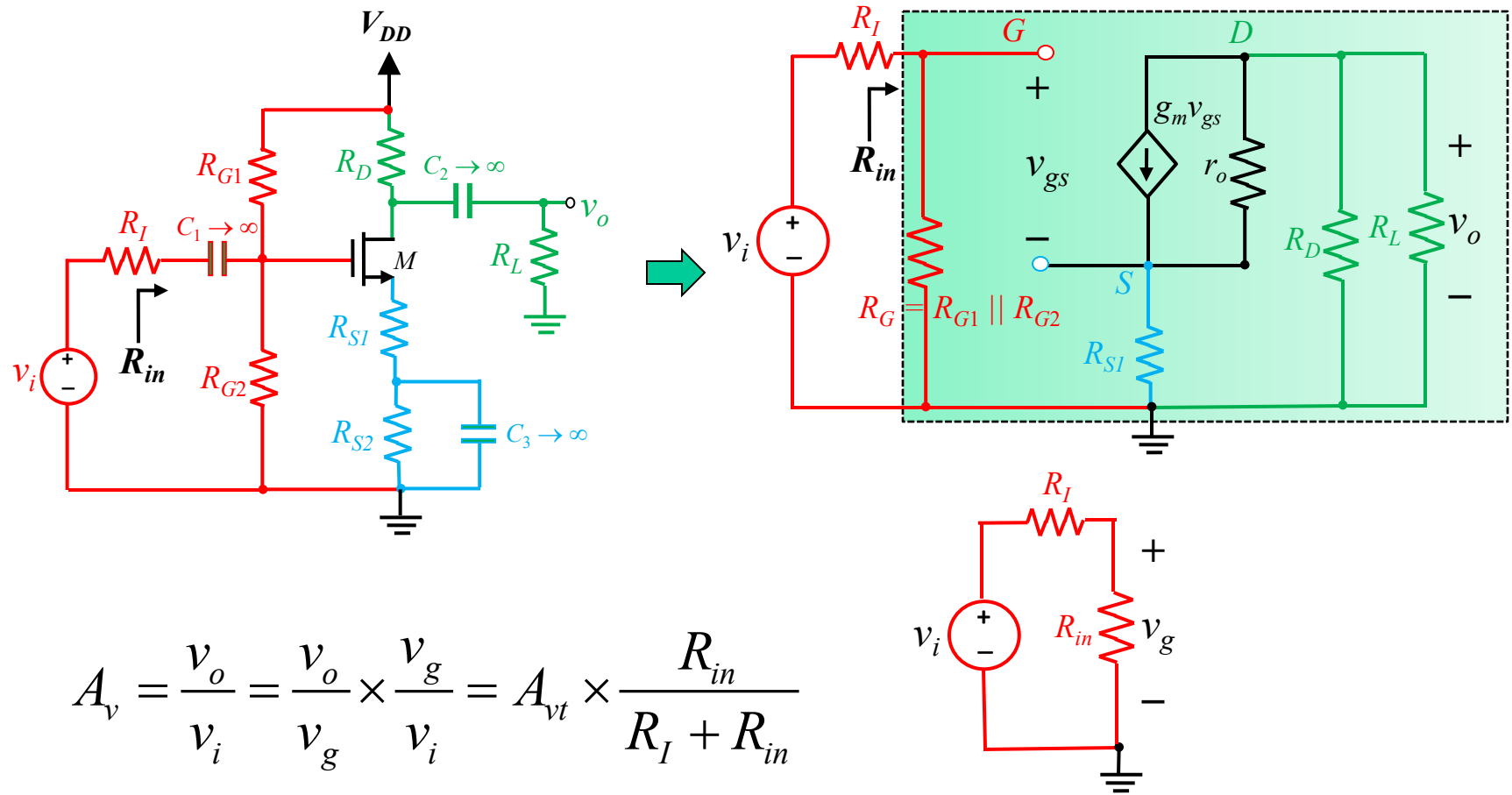
# C-S Amplifier (Inverting Amplifier): Overall Voltage Gain



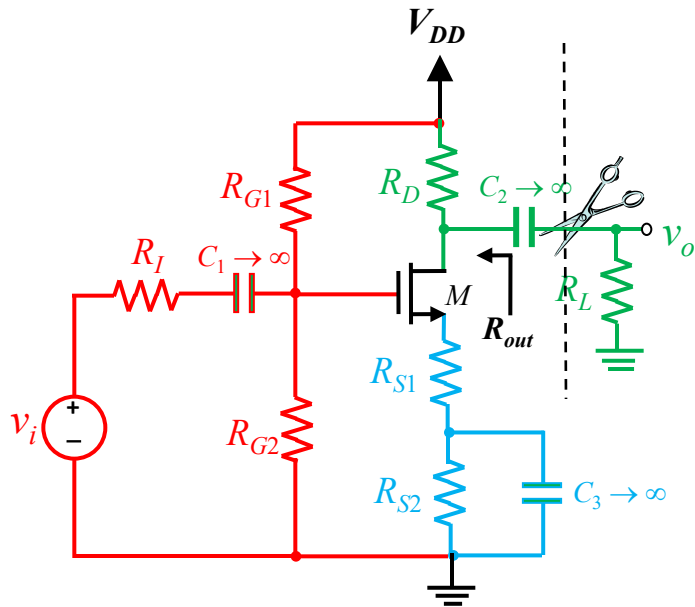
# C-S Amplifier (Inverting Amplifier): Output Resistance



$$v_x = (i_x - g_m v_{gs}) r_o + v_s$$

$$v_s = i_x R_{S1}$$
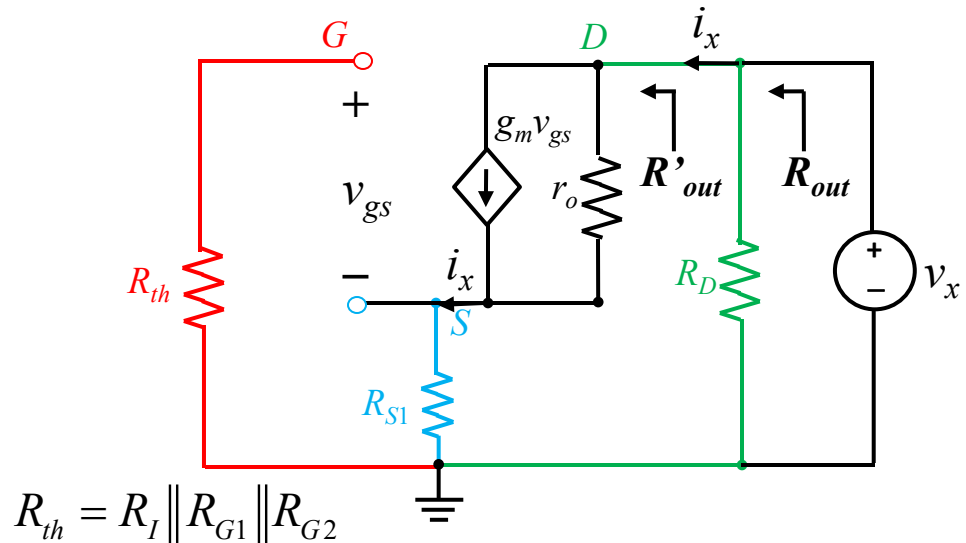
$$\because v_g = 0, v_{gs} = -v_s = -i_x R_{S1}$$



$$R_{th} = R_I \parallel R_{G1} \parallel R_{G2}$$

$$v_x = (i_x + g_m i_x R_{S1}) r_o + i_x R_{S1}$$

$$R'_{out} = \frac{v_x}{i_x} \approx (1 + g_m R_{S1}) r_o$$

$$R_{out} = R'_{out} \parallel R_D$$



# C-S Amplifier (Inverting Amplifier): Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ . 

$$v_{gs} = v_g - v_s \approx v_g - g_m v_{gs} R_{S1}$$


$$v_{gs} = \frac{v_g}{1 + g_m R_{S1}}$$

$$|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_g| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_{S1})$$

$$\because v_g = \left( \frac{R_{in}}{R_I + R_{in}} \right) v_i \Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_{S1}) \left( \frac{R_I + R_{in}}{R_{in}} \right)$$

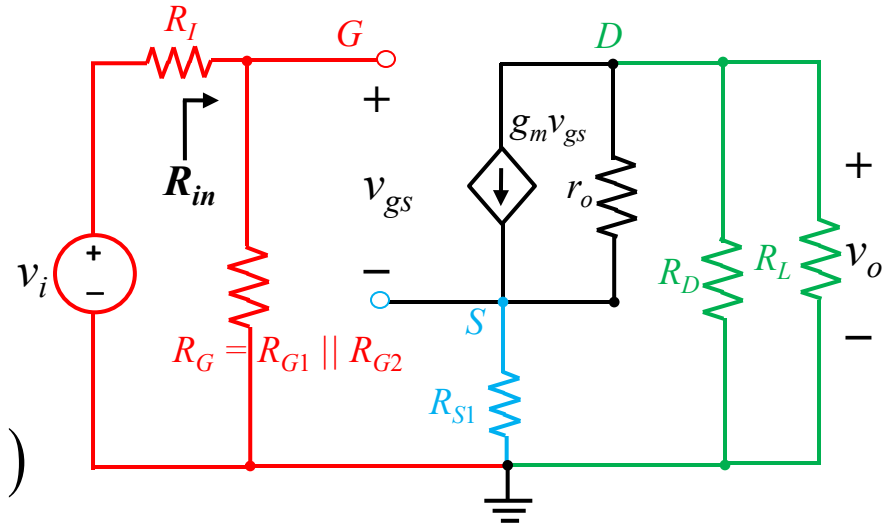Presence of  $R_{S1}$  increase permissible value of  $v_i$ .







# Summary: C-E and C-S

<div> <div><b>Parameter</b></div> <div><b>Amplifier</b></div> </div>		Terminal Voltage Gain $A_{vt}$	Input Resistance $R'_{in}$	Output Resistance $R'_{out}$
BJT	C-E	$\frac{-g_m R'_L}{1 + g_m R_{E1}}$	$r_\pi + (\beta + 1) R_{E1}$	$\left(1 + \frac{\beta R_{E1}}{r_\pi + R_{th} + R_{E1}}\right) r_o$
MOSFET	C-S	$\frac{-g_m R'_L}{1 + g_m R_{S1}}$	$\infty$	$(1 + g_m R_{S1}) r_o$
BJT	C-C	$\frac{g_m R'_L}{1 + g_m R'_L}$	$r_\pi + (\beta + 1) R'_L$	$r_o \left\  \left( \frac{r_\pi + R_{th}}{\beta + 1} \right) \right.$
MOSFET	C-D	$\frac{g_m R'_L}{1 + g_m R'_L}$	$\infty$	$r_o \left\  \frac{1}{g_m} \right.$
BJT	C-B	$g_m R'_L$	$\frac{1}{g_m}$	$\left[1 + g_m (r_\pi \parallel R_{th})\right] r_o$
MOSFET	C-G	$g_m R'_L$	$\frac{1}{g_m}$	$(1 + g_m R_{th}) r_o$

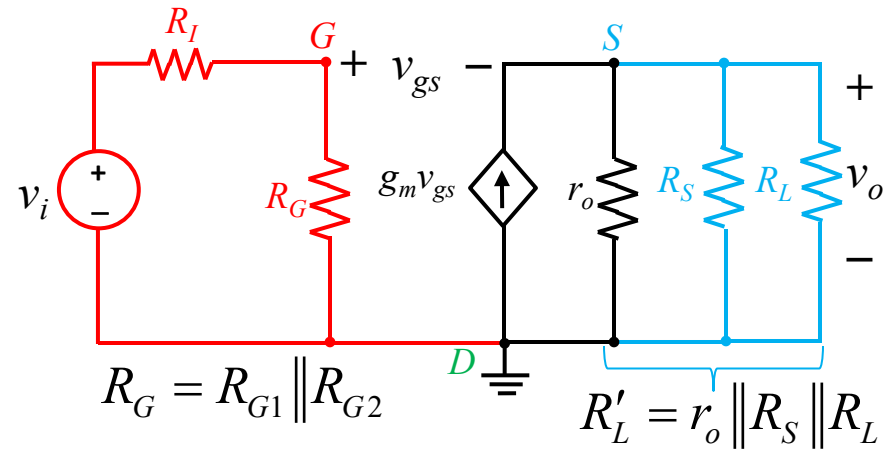
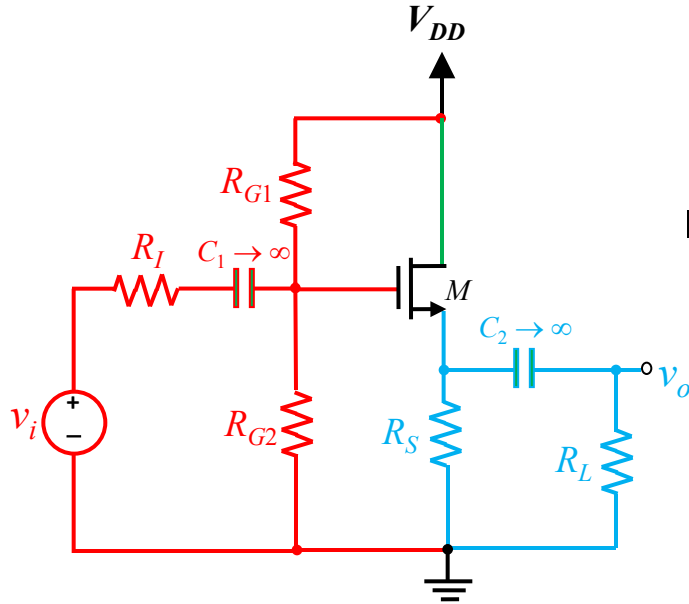
# C-D Amplifier (Voltage Follower): Terminal Voltage Gain



$$A_{vt} = \frac{v_s}{v_g} = \frac{g_m v_{gs} R'_L}{v_{gs} + g_m v_{gs} R'_L} = \frac{g_m R'_L}{1 + g_m R'_L}$$

$$\text{If } g_m R'_L \gg 1, A_{vt} \approx 1 \Rightarrow v_o \approx v_g$$

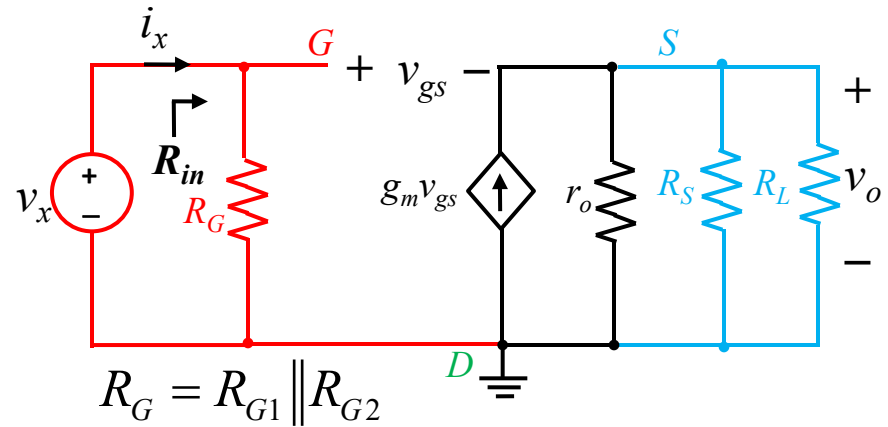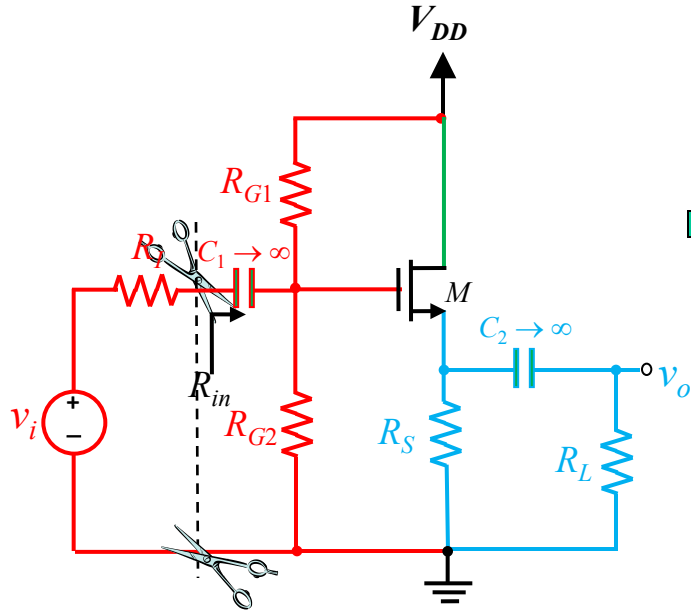
# C-D Amplifier (Voltage Follower): Input Resistance



$$v_x = i_x R_G \quad \Rightarrow \quad R_{in} = \frac{v_x}{i_x} = R_G$$



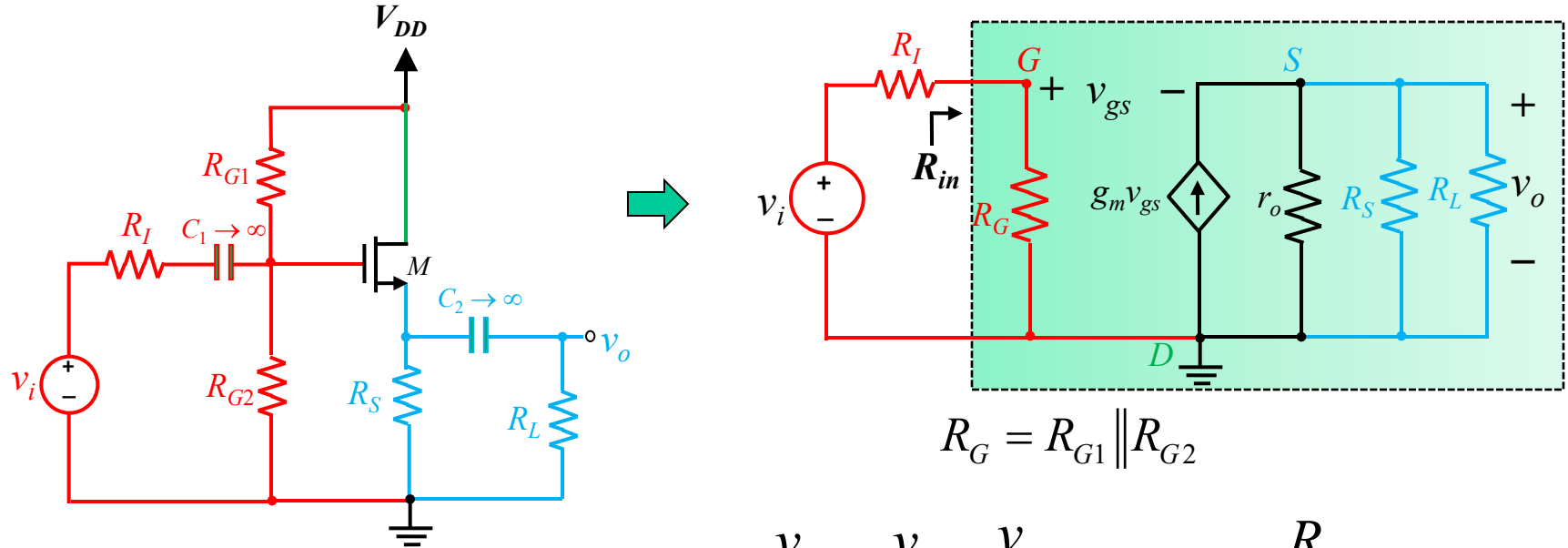
# C-D Amplifier (Voltage Follower): Overall Voltage Gain



$$R_G = R_{G1} \parallel R_{G2}$$


$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_g} \times \frac{v_g}{v_i} = A_{vt} \times \frac{R_G}{R_I + R_G}$$
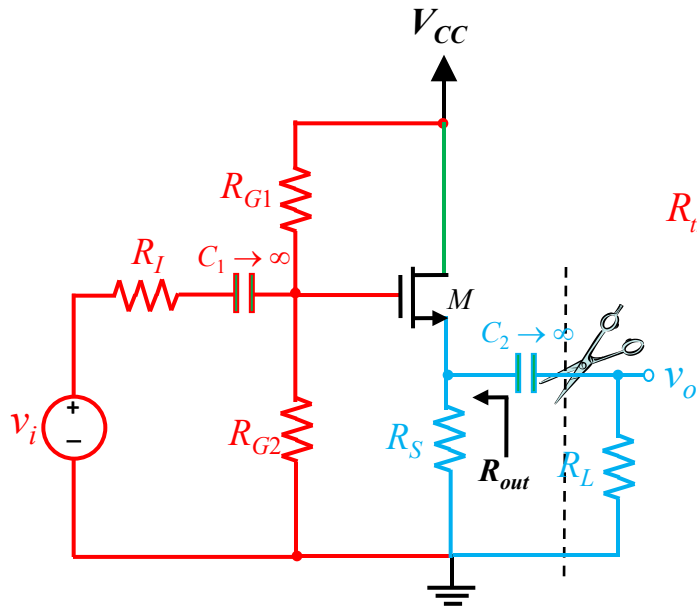
# C-D Amplifier (Voltage Follower): Output Resistance



$$i_x = \frac{v_x}{R_S} + \frac{v_x}{r_o} - g_m v_{gs}$$

$$v_{gs} = -v_x$$

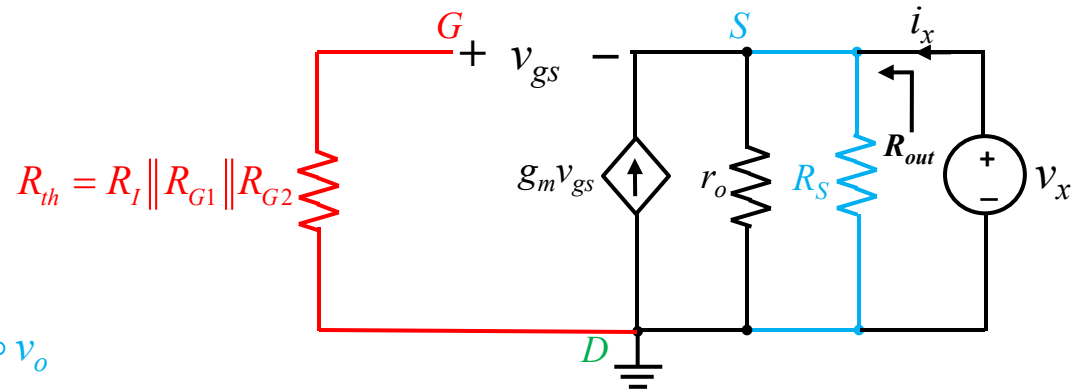

$$i_x = \frac{v_x}{R_S} + \frac{v_x}{r_o} + g_m v_x = \left( \frac{1}{R_S} + \frac{1}{r_o} + g_m \right) v_x$$

$$R_{out} = \frac{v_x}{i_x} = \left( \frac{1}{R_S} + \frac{1}{r_o} + g_m \right)^{-1} = R_S \parallel r_o \parallel \frac{1}{g_m} \approx R_S \parallel \frac{1}{g_m}$$



# C-D Amplifier (Voltage Follower): Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ .


$$v_{gs} = v_g - v_s \approx v_g - g_m v_{gs} R'_L$$

$$v_{gs} = \frac{v_g}{1 + g_m R'_L}$$

$$|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_g| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R'_L)$$


$$\because v_g = \left( \frac{R_G}{R_I + R_G} \right) v_i \Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R'_L) \left( \frac{R_I + R_G}{R_G} \right)$$

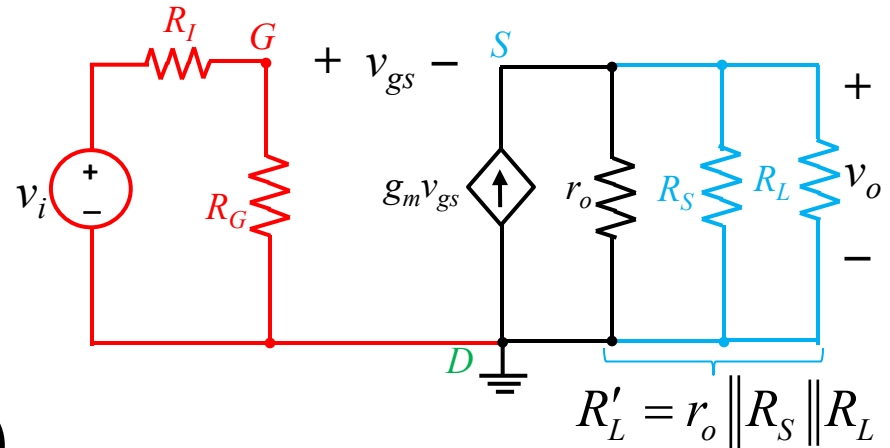

# Summary: C-C and C-D

<div> <div><b>Parameter</b></div> <div><b>Amplifier</b></div> </div>		Terminal Voltage Gain $A_{vt}$	Input Resistance $R'_{in}$	Output Resistance $R'_{out}$
BJT	C-E	$\frac{-g_m R'_L}{1 + g_m R_{E1}}$	$r_\pi + (\beta + 1) R_{E1}$	$\left(1 + \frac{\beta R_{E1}}{r_\pi + R_{th} + R_{E1}}\right) r_o$
MOSFET	C-S	$\frac{-g_m R'_L}{1 + g_m R_{S1}}$	$\infty$	$(1 + g_m R_{S1}) r_o$
BJT	C-C	$\frac{g_m R'_L}{1 + g_m R'_L}$	$r_\pi + (\beta + 1) R'_L$	$r_o \left\  \left( \frac{r_\pi + R_{th}}{\beta + 1} \right) \right.$
MOSFET	C-D	$\frac{g_m R'_L}{1 + g_m R'_L}$	$\infty$	$r_o \left\  \frac{1}{g_m} \right.$
BJT	C-B	$g_m R'_L$	$\frac{1}{g_m}$	$\left[1 + g_m (r_\pi \parallel R_{th})\right] r_o$
MOSFET	C-G	$g_m R'_L$	$\frac{1}{g_m}$	$(1 + g_m R_{th}) r_o$
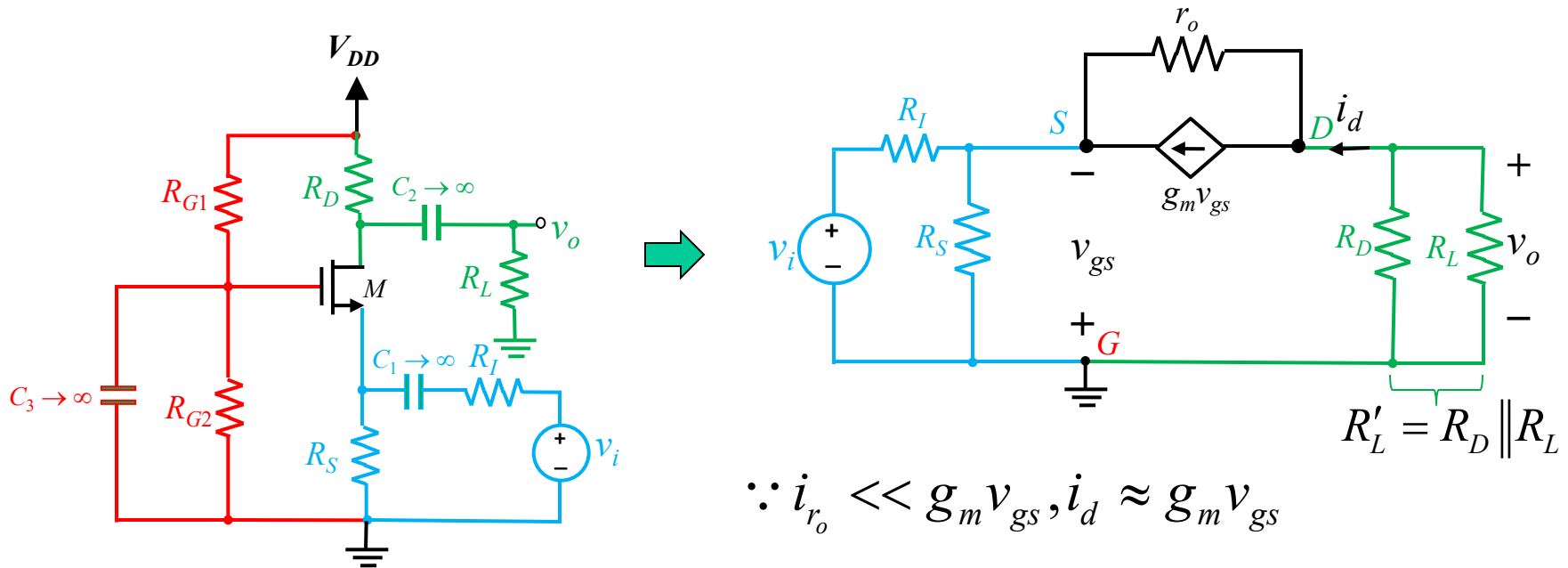
# C-G Amplifier (Noninverting Amplifier): Terminal Voltage Gain



$$\because i_{r_o} \ll g_m v_{gs}, i_d \approx g_m v_{gs}$$


$$v_s = -v_{gs}$$

$$A_{vt} = \frac{v_d}{v_s} = \frac{-i_d R'_L}{-v_{gs}} \approx \frac{-g_m v_{gs} R'_L}{-v_{gs}} = g_m R'_L$$





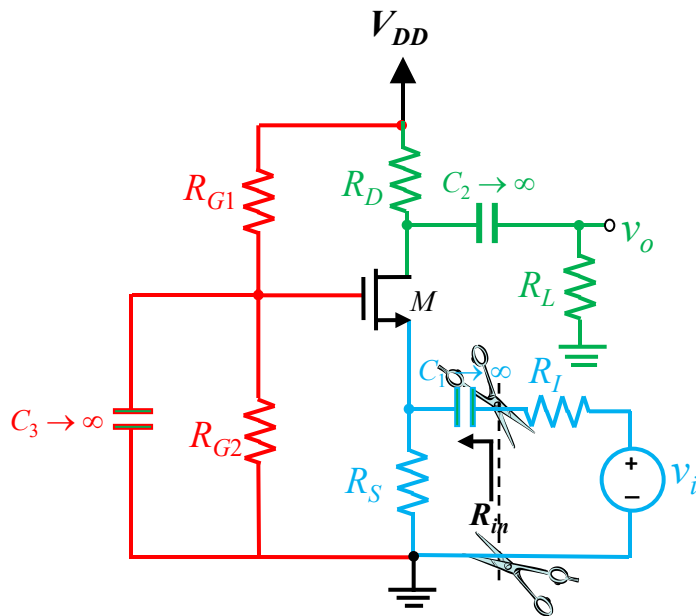
# C-G Amplifier (Noninverting Amplifier): Input Resistance



$$i_x = -g_m v_{gs} + \frac{v_{sd}}{r_o}$$

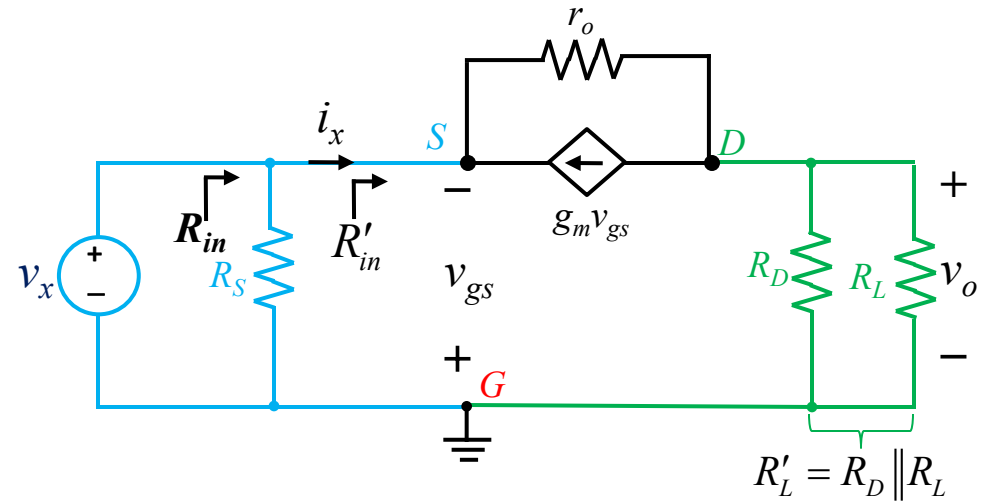This current can be ignored due to large  $r_o$




$$\because v_{gs} = -v_x, i_x \approx g_m v_x$$

$$R'_{in} = \frac{v_x}{i_x} \approx \frac{1}{g_m}$$


$$R_{in} = R'_{in} \parallel R_S = \frac{R_S}{1 + g_m R_S}$$


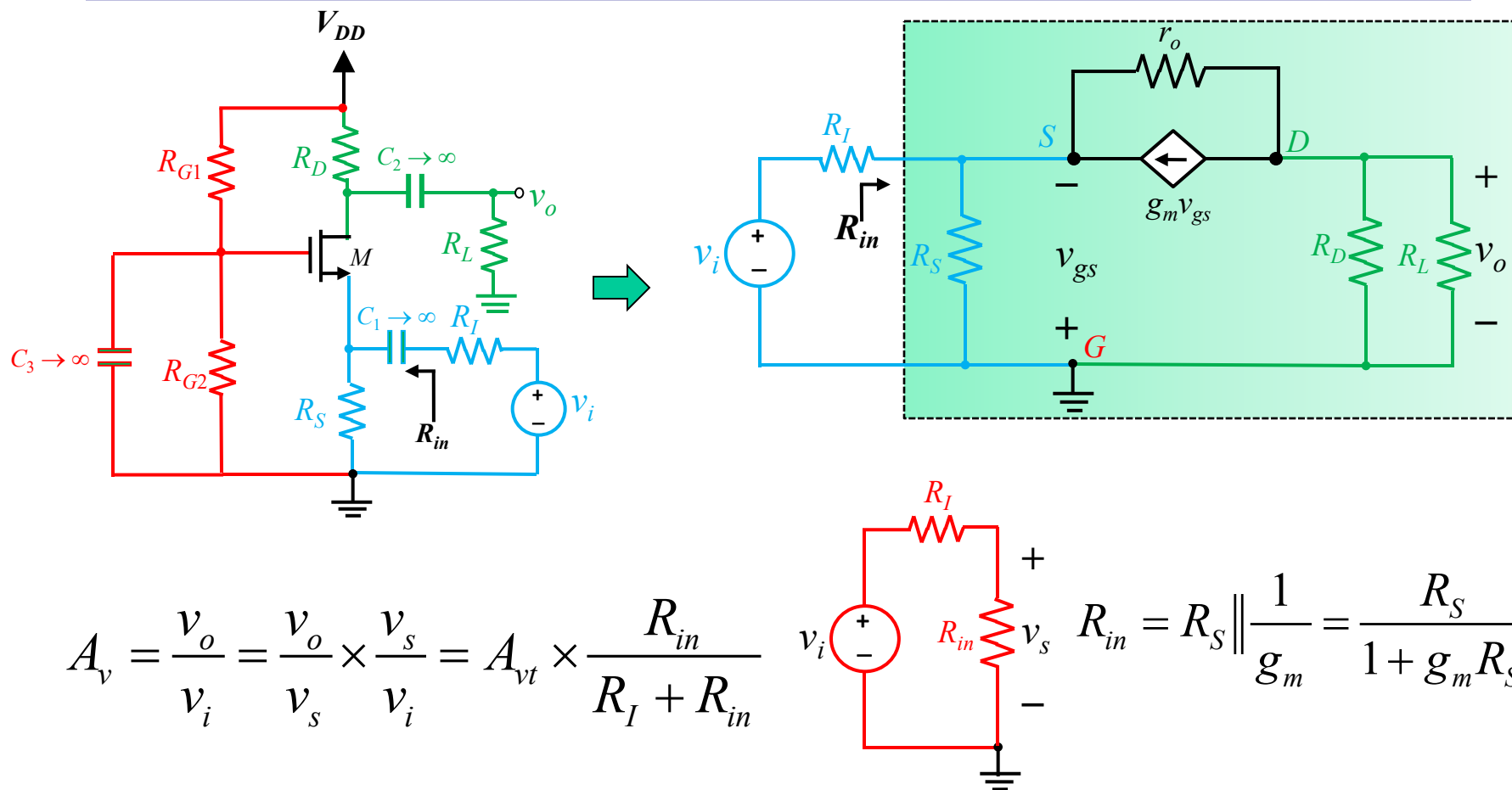
# C-G Amplifier (Noninverting Amplifier): Overall Voltage Gain



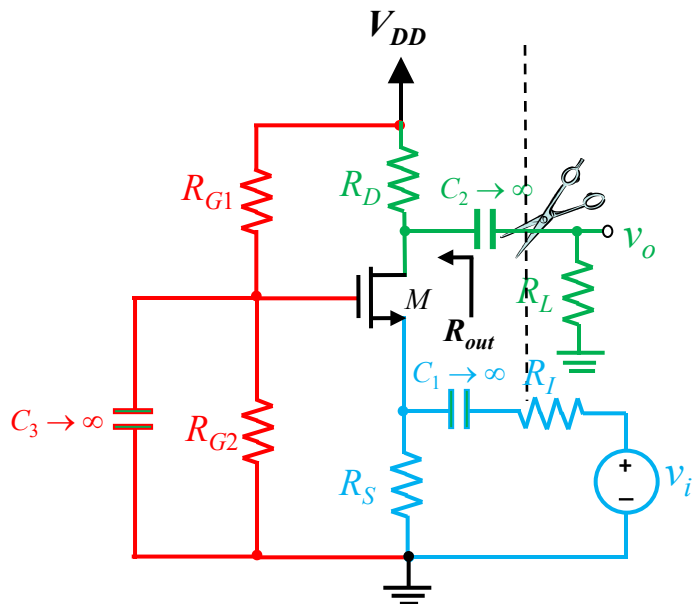
# C-G Amplifier (Noninverting Amplifier): Output Resistance



$$v_x = (i_x - g_m v_{gs}) r_o + v_s$$

$$v_s = i_x R_{th}$$

$$v_{gs} = -v_s = -i_x R_{th}$$

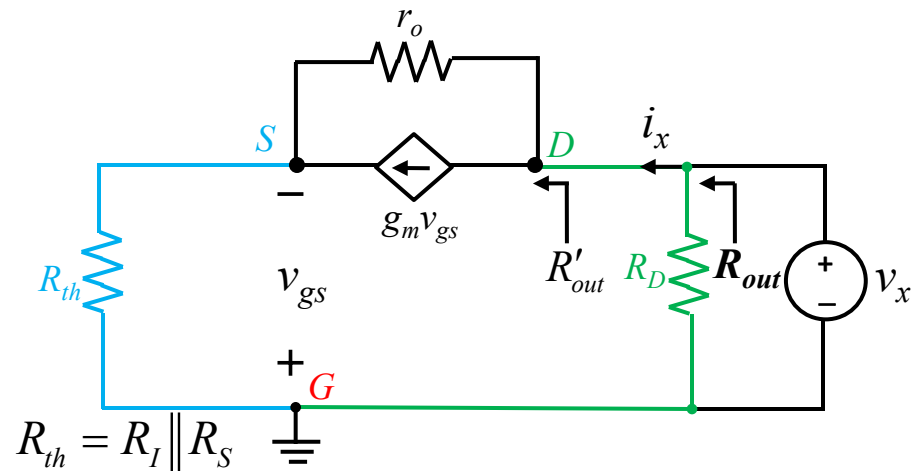

$$v_x = (i_x + g_m i_x R_{th}) r_o + i_x R_{th}$$

$$\approx (1 + g_m R_{th}) i_x r_o$$

$$R'_{out} = \frac{v_x}{i_x} \approx (1 + g_m R_{th}) r_o$$

$$R_{out} = R'_{out} \parallel R_D$$



# C-G Amplifier (Noninverting Amplifier): Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ .


$$v_{gs} = -\left(\frac{R_{in}}{R_I + R_{in}}\right)v_i$$

$$|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN})\left(\frac{R_I + R_{in}}{R_{in}}\right)$$

$$\because R_{in} = \frac{R_S}{1 + g_m R_S} \Rightarrow \frac{R_I + R_{in}}{R_{in}} = 1 + g_m R_I + \frac{R_I}{R_S}$$


$$\text{If } R_S \gg R_I, |v_i| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_I)$$

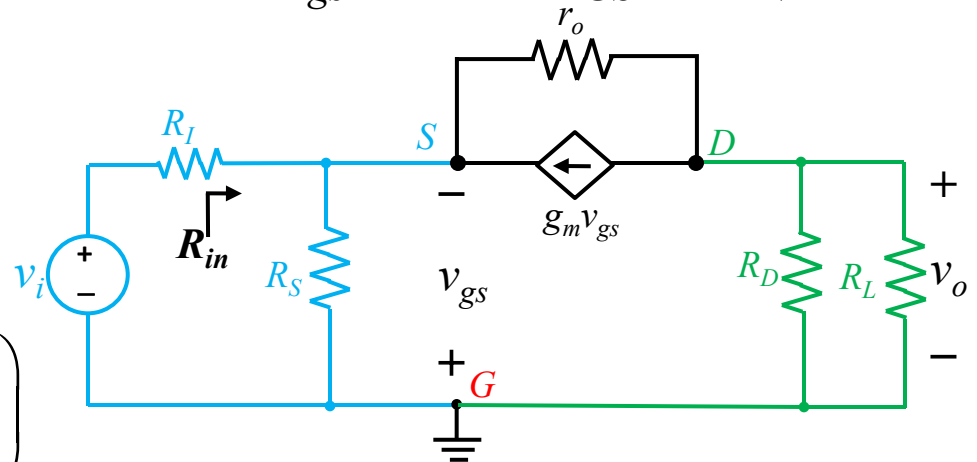

# Summary: C-B and C-G

<div> <div><b>Parameter</b></div> <div><b>Amplifier</b></div> </div>		Terminal Voltage Gain $A_{vt}$	Input Resistance $R'_{in}$	Output Resistance $R'_{out}$
BJT	C-E	$\frac{-g_m R'_L}{1 + g_m R_{E1}}$	$r_\pi + (\beta + 1) R_{E1}$	$\left(1 + \frac{\beta R_{E1}}{r_\pi + R_{th} + R_{E1}}\right) r_o$
MOSFET	C-S	$\frac{-g_m R'_L}{1 + g_m R_{S1}}$	$\infty$	$(1 + g_m R_{S1}) r_o$
BJT	C-C	$\frac{g_m R'_L}{1 + g_m R'_L}$	$r_\pi + (\beta + 1) R'_L$	$r_o \left\  \left( \frac{r_\pi + R_{th}}{\beta + 1} \right) \right.$
MOSFET	C-D	$\frac{g_m R'_L}{1 + g_m R'_L}$	$\infty$	$r_o \left\  \frac{1}{g_m} \right.$
BJT	C-B	$g_m R'_L$	$\frac{1}{g_m}$	$\left[1 + g_m (r_\pi \parallel R_{th})\right] r_o$
MOSFET	C-G	$g_m R'_L$	$\frac{1}{g_m}$	$(1 + g_m R_{th}) r_o$

# Current Gain

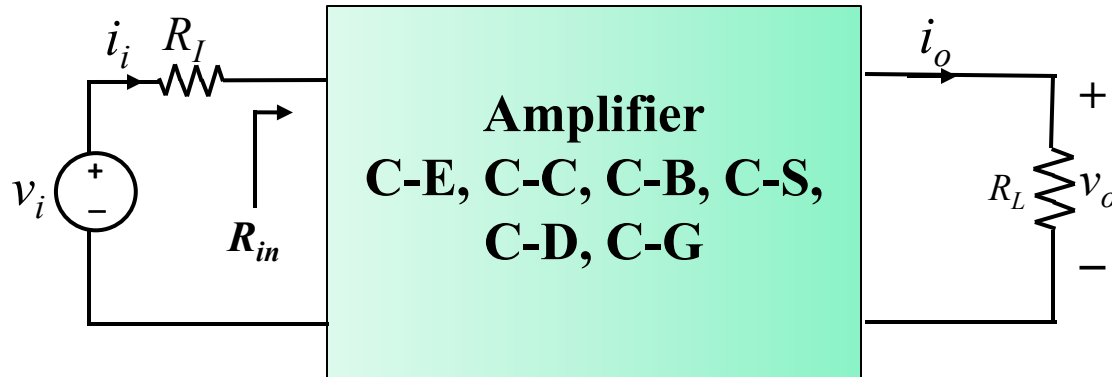

$$A_i = \frac{i_o}{i_i} = \frac{\frac{v_o}{R_L}}{\frac{v_i}{R_I + R_{in}}} = \frac{v_o}{v_i} \times \frac{R_I + R_{in}}{R_L} = A_v \times \frac{R_I + R_{in}}{R_L}$$