

NANYANG TECHNOLOGICAL UNIVERSITY  
SCHOOL OF ELECTRICAL & ELECTRONIC ENGINEERING  
EE4341/EE6341 ADVANCED ANALOG CIRCUITS  
TUTORIAL 11

- Design a DC-DC Cuk Converter as shown in Fig. 1 with specifications: input = 10 V, load resistance = 10  $\Omega$  and load power = 20 W. The switching frequency  $f_s = 60$  kHz. Specify the values of inductors and capacitors. The change in current for both inductors is kept at 15% of their average values. The output ripple voltage must be < 1% and the voltage ripple across  $C_1$  must be < 5%. Assuming that all the components are ideal.

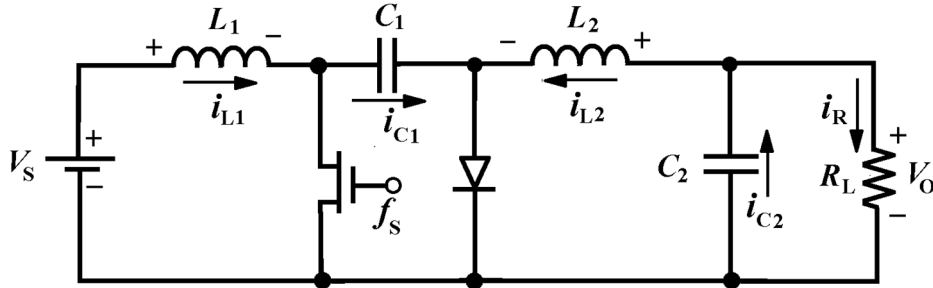


Figure 1

- For the given Buck Converter shown in Fig. 2, determine:
  - The output voltage when the duty ratio is 0.2.
  - The output voltage when the duty ratio is 0.6.

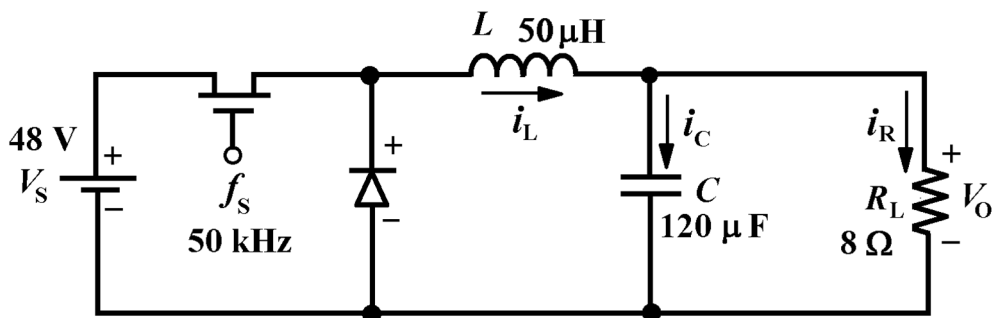


Figure 2