

# EE4341/EE6341

# Advanced Analog Circuits

## Tutorial 6

Dr See Kye Yak  
Associate Professor  
School of EEE  
Office: S2-B2C-112

Q1. Fig. 1 shows a class-A power amplifier with a capacitor coupled load  $R_L = 100\ \Omega$ . The BJT has a current gain  $\beta = 50$ . The power supply  $V_{CC} = +12\text{ V}$  and the BJT is to be biased at  $V_{CEQ} = 6\text{ V}$ . Assume  $V_{BE} = 0.7\text{ V}$  and  $V_{CE,sat} \approx 0\text{ V}$  for your calculation. Ignore the output resistance of the BJT and the reactance of coupling capacitors.

- Determine the value of  $R_C$  for maximum possible conversion efficiency.
- Calculate the DC biasing collector current  $I_{CQ}$  and the value of  $R_B$  to provide the biasing.
- Calculate the peak load voltage and current, and the conversion efficiency.


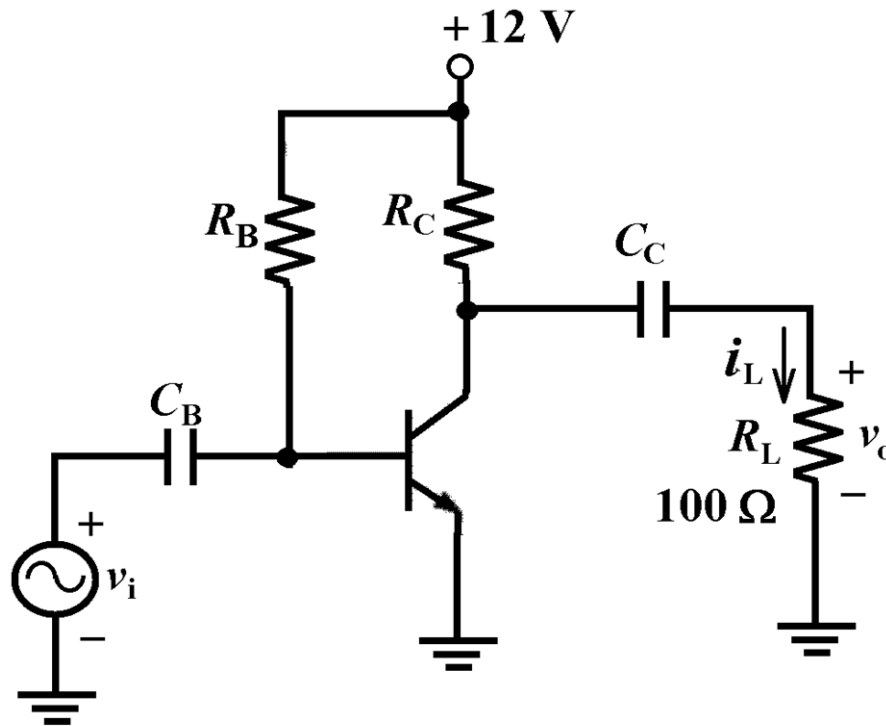


Figure 1

(a) DC load line:

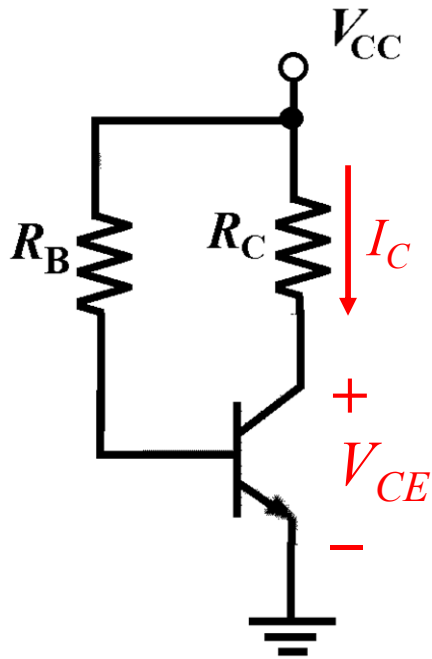


$$V_{CC} = I_C R_C + V_{CE}$$



When  $I_C = 0$ :  $V_{CE} = V_{CC}$

When  $V_{CE} = 0$ :  $I_C = \frac{V_{CC}}{R_C}$

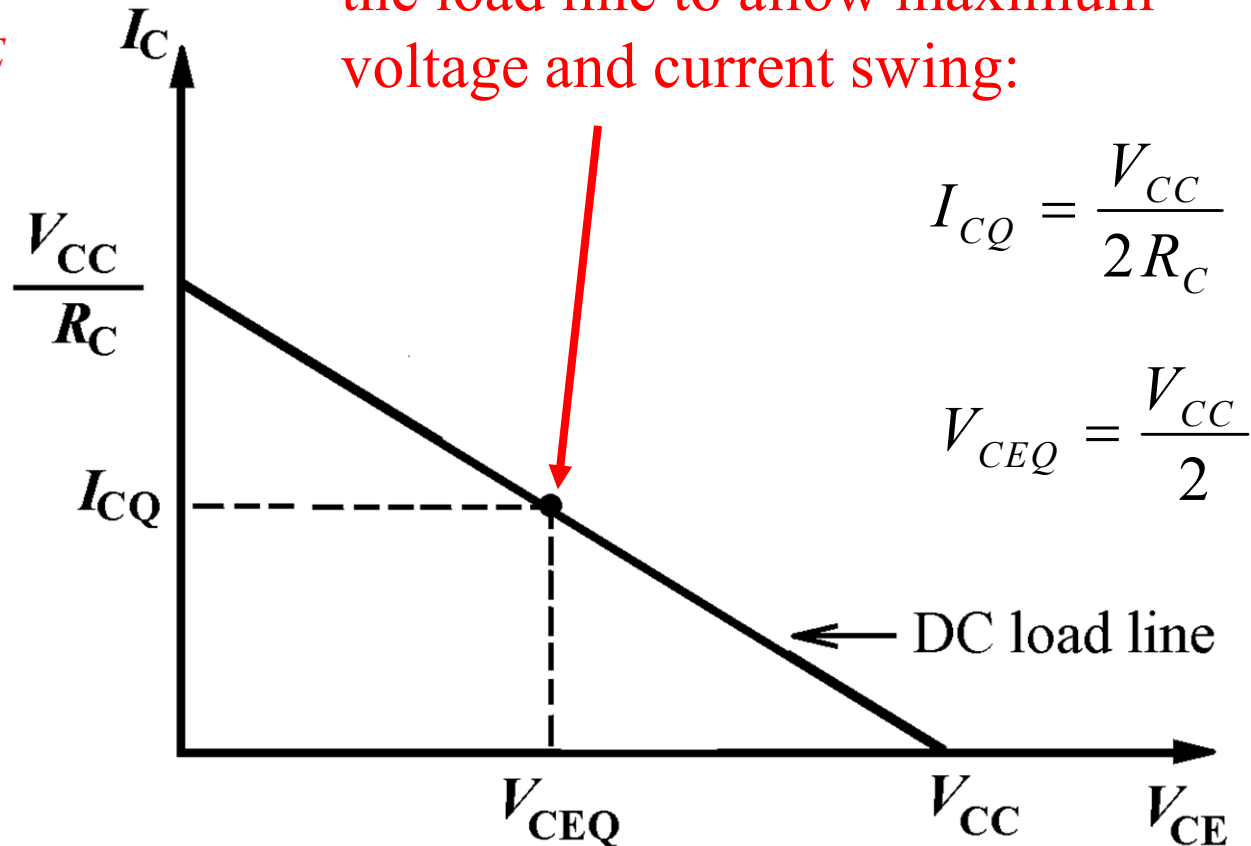Q-point is selected at mid-point of the load line to allow maximum voltage and current swing:



(a) AC load line:

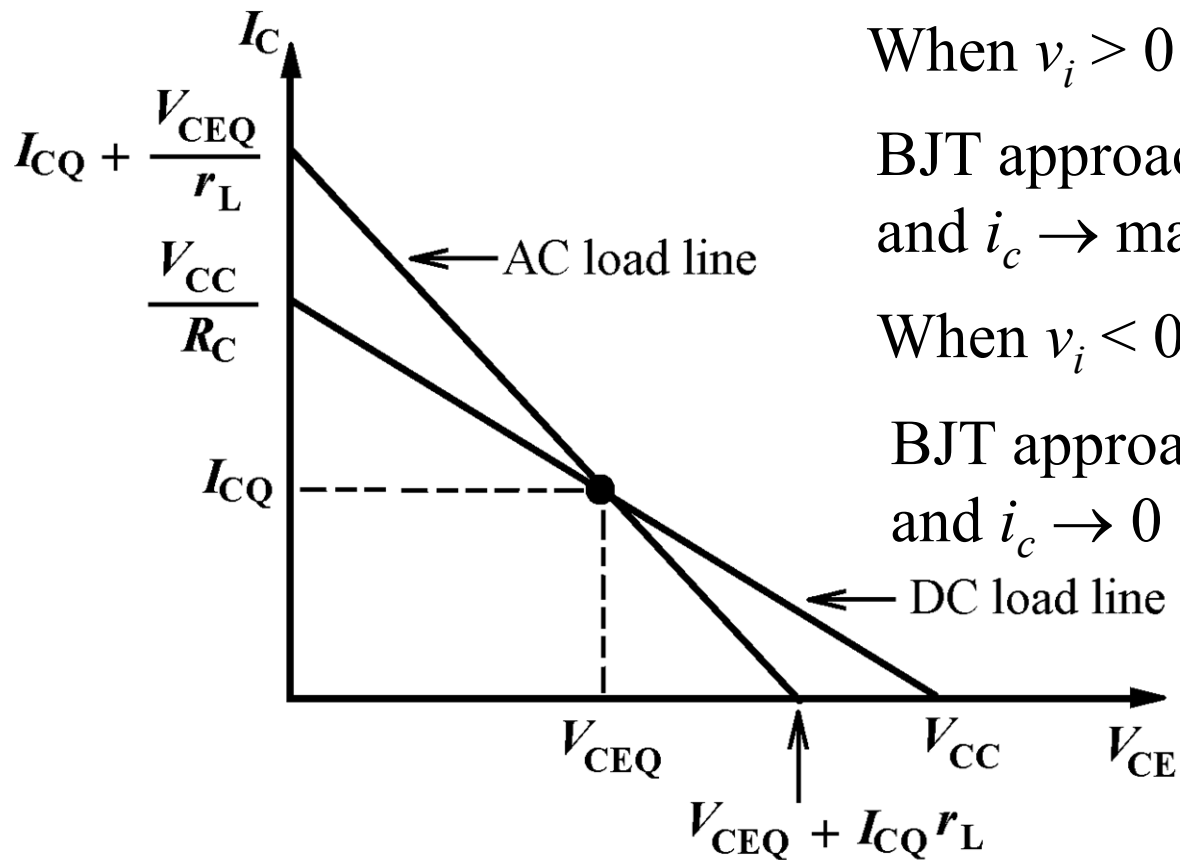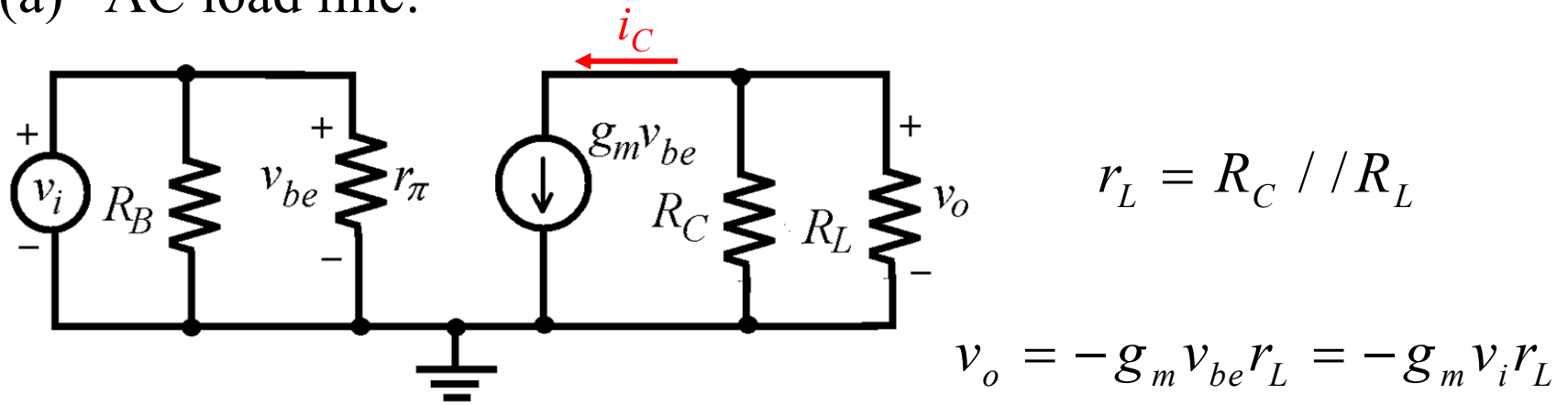


When  $v_i > 0$ :  $v_{CE} = V_{CEQ} - g_m v_i r_L$

BJT approaches saturation  $v_{CE} \rightarrow 0$   
and  $i_c \rightarrow \max$

When  $v_i < 0$ :  $v_{CE} = V_{CEQ} + g_m v_i r_L$

BJT approaches cut-off  $v_{CE} \rightarrow \max$   
and  $i_c \rightarrow 0$

(a)

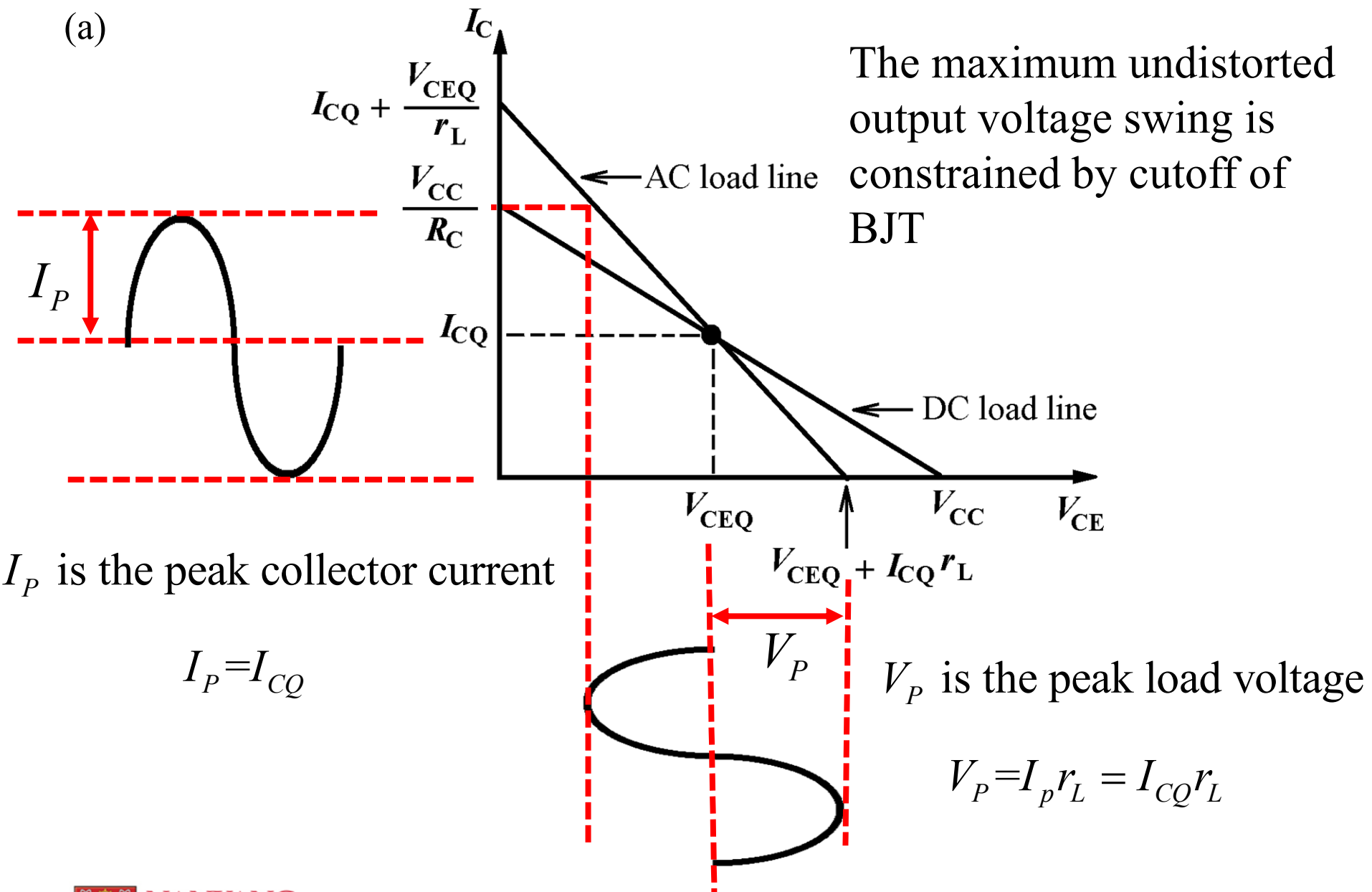

Average power to the load:

$$\bar{P}_L = \frac{V_P I_P}{2} = \frac{V_P^2}{2R_L} = \frac{(I_{CQ} r_L)^2}{2R_L} \quad I_{CQ} = \frac{V_{CC}}{2R_C}$$

$$\therefore \bar{P}_L = \frac{(I_{CQ} r_L)^2}{2R_L} = \frac{V_{CC}^2 r_L^2}{8R_C^2 R_L}$$

Average power from the power supply (ignore the current in  $R_B$  first):

$$\bar{P}_S = V_{CC} I_{CQ} = \frac{V_{CC}^2}{2R_C}$$

$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{V_{CC}^2 r_L^2}{8R_C^2 R_L} \times \frac{2R_C}{V_{CC}^2} = \frac{r_L^2}{4R_C R_L}$$

$$\eta = \frac{r_L^2}{4R_C R_L} \quad r_L = R_C // R_L = \frac{R_C R_L}{R_C + R_L}$$

$$\therefore \eta = \frac{R_C^2 R_L^2}{(R_C + R_L)^2} \times \frac{1}{4R_C R_L} = \frac{R_C R_L}{4(R_C + R_L)^2}$$

To find  $R_C$  for maximum conversion efficiency:

$$\frac{\partial \eta}{\partial R_C} = \frac{4(R_C + R_L)^2 R_L - R_C R_L \times 8(R_C + R_L)}{16(R_C + R_L)^4}$$


$$= \frac{R_L}{4(R_C + R_L)^2} - \frac{R_C R_L}{2(R_C + R_L)^3} = 0$$

$$\frac{1}{4} = \frac{R_C}{2(R_C + R_L)} \Rightarrow 2R_C + 2R_L = 4R_C \Rightarrow R_L = R_C$$

$$R_C = R_L = 100 \, \Omega$$

$$\eta = \frac{r_L^2}{4R_C R_L} = \frac{50^2}{4 \times 100 \times 100} = 0.0625 \, (6.25\%)$$

(b) DC biasing:

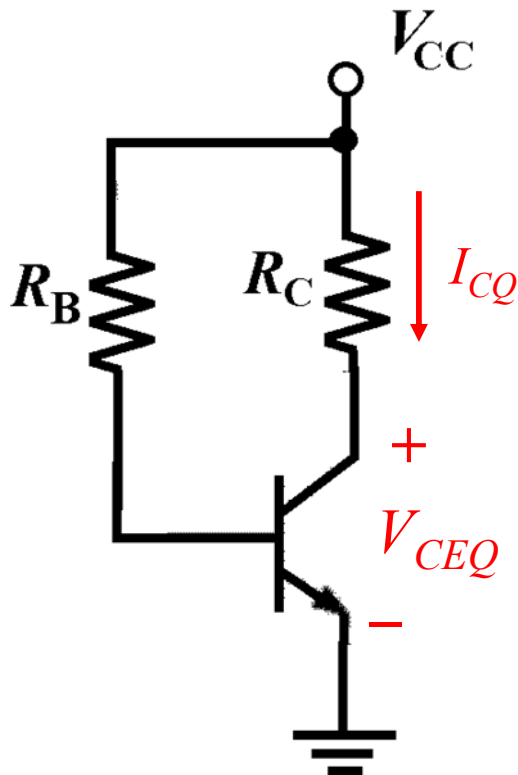

$$V_{CC} = I_{CQ} R_C + V_{CEQ}$$

$$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C} = \frac{12 - 6}{100} = 60 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{60 \text{ mA}}{50} = 1.2 \text{ mA}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_{BQ}} = \frac{12 - 0.7}{1.2 \text{ mA}} = 9.42 \text{ k}\Omega$$



(c) The peak load voltage:


$$V_P = I_{CQ} r_L = 60 \text{ mA} \times 50 \Omega = 3 \text{ V} \quad I_P = \frac{V_P}{R_L} = \frac{3}{100} = 30 \text{ mA}$$


$$\bar{P}_L = \frac{V_P I_P}{2} = \frac{3 \text{ V} \times 30 \text{ mA}}{2} = 45 \text{ mW}$$

$$\bar{P}_S = V_{CC} (I_{CQ} + I_{BQ}) = 12 \text{ V} \times 61.2 \text{ mA} = 734.4 \text{ mW}$$

$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{45}{734.4} \times 100 = 6.13\%$$

(c)

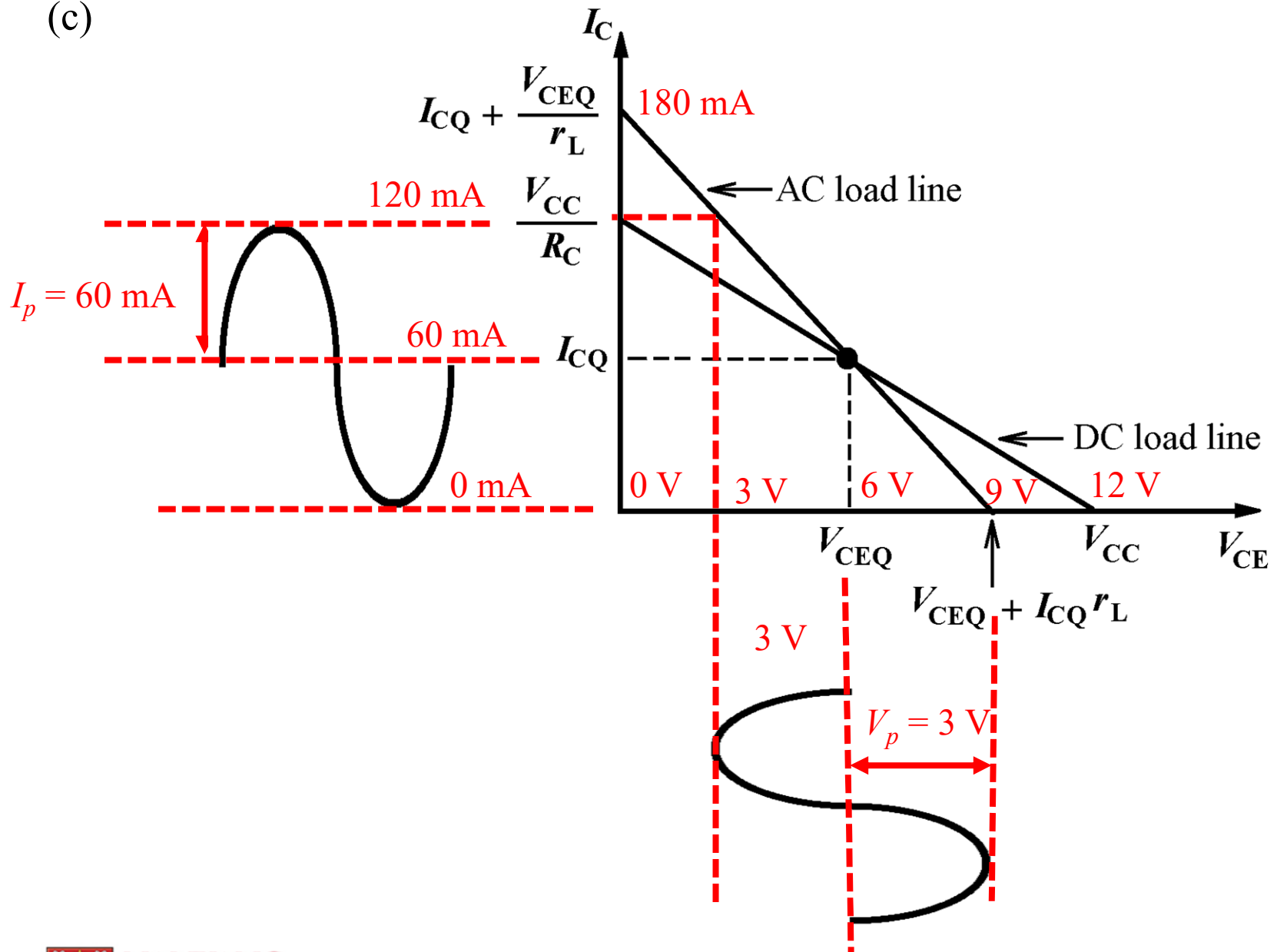

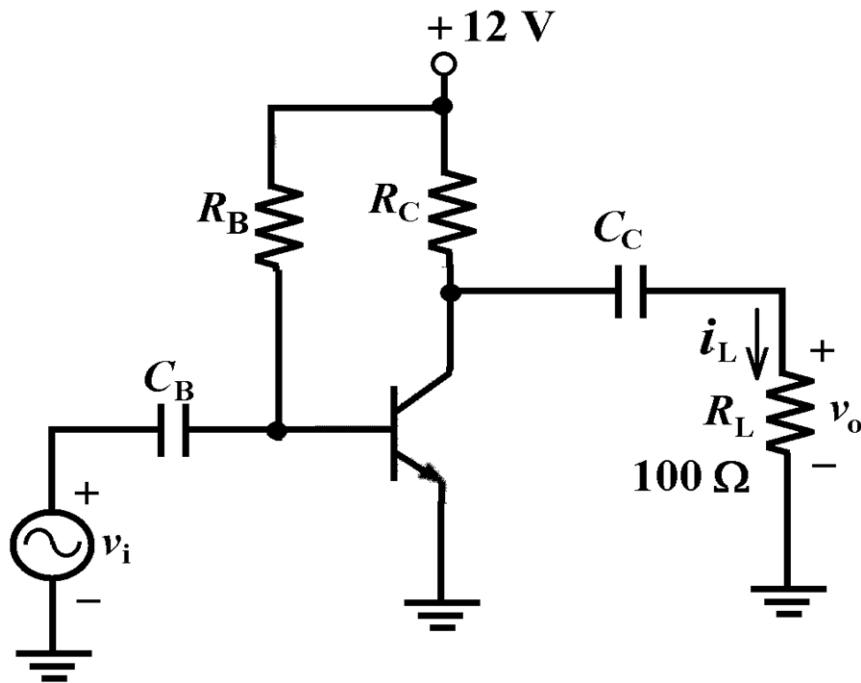

The classical class A amplifier has very poor efficiency and not suitable to be used as a power amplifier .

A power amplifier requires two stages:

- First stage provides the maximum voltage swing with negligible current
- Second stage (also known as output stage) delivers sufficient current to the load while maintaining full voltage swing.

2. An emitter follower power amplifier with a load  $R_L = 1\text{ k}\Omega$  is shown in Fig. 2. The transistor parameters are:  $\beta = 200$ ,  $V_{BE} = 0.7\text{ V}$  and  $V_{CE(sat)} = 0.2\text{ V}$ .
- (a) Determine the value of  $R$  that will produce maximum possible output signal swing.
- (b) What are the value of  $I_Q$  and the maximum and minimum values of  $i_{E1}$  and  $i_L$ ?
- (c) Calculate the conversion efficiency.

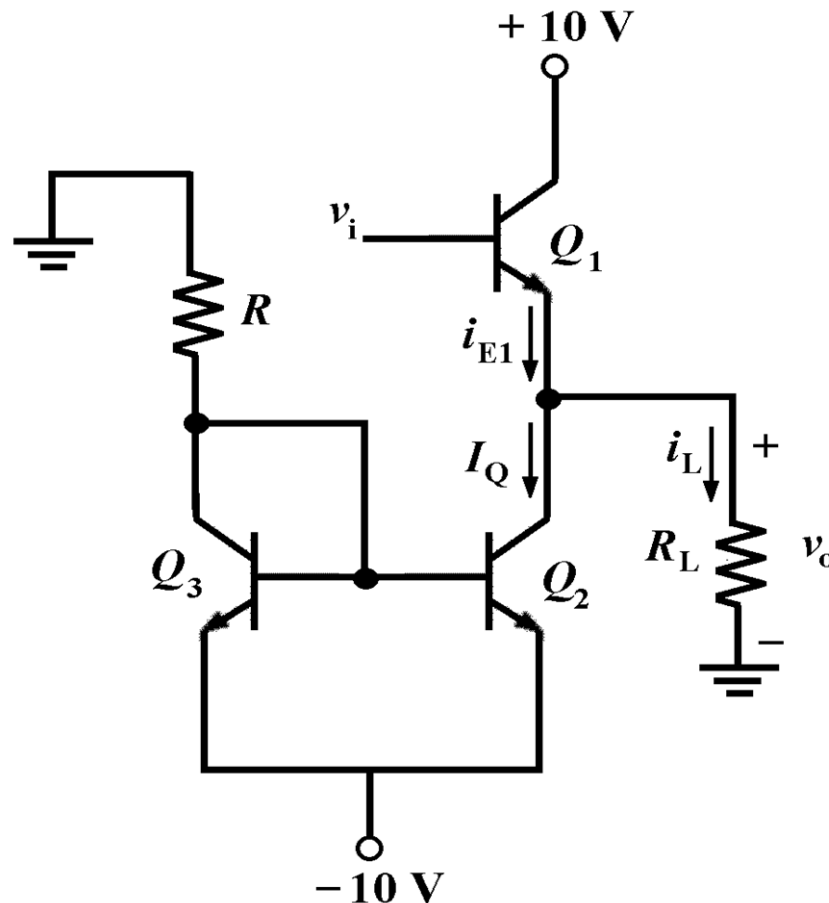


Figure 2


(a)

$$v_o = v_i - V_{BE1}$$

$$v_{BE1} = \frac{kT}{q} \ln \left( \frac{i_{C1}}{I_S} \right)$$

$$i_{C1} \approx i_{E1} = I_Q + i_L = I_Q + \frac{v_o}{R_L}$$
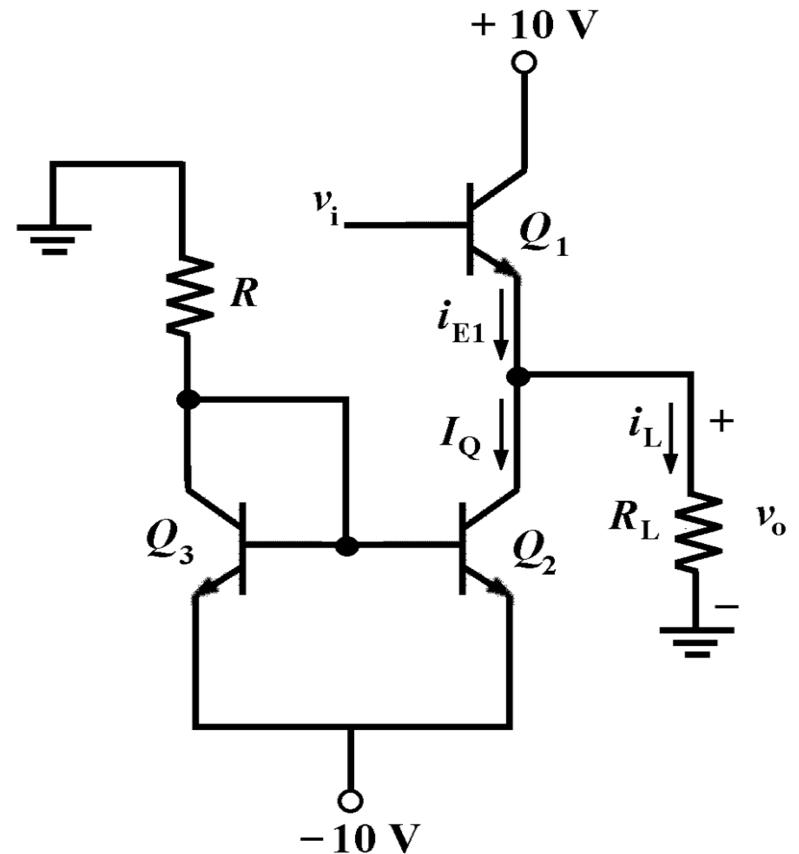
$$v_o = v_i - \frac{kT}{q} \ln \left( \frac{I_Q + \frac{v_o}{R_L}}{I_S} \right)$$



When  $v_i > 0$ , the maximum voltage swing is when  $Q_1$  is saturated:

$$v_o = V_{CC} - V_{CEsat1}$$



When  $v_i < 0$ , the output voltage swing is when  $Q_1$  reaches cut-off, i.e.  $i_{c1} = 0$ :

$$i_{c1} \approx i_{E1} = I_Q + i_L = 0 \quad \text{Note: } i_L \text{ is -ve, as } v_i < 0$$

$$I_Q + \frac{v_o}{R_L} = 0 \quad \therefore v_o = -I_Q R_L$$

Hence, depending on  $I_Q$ , the output is either:
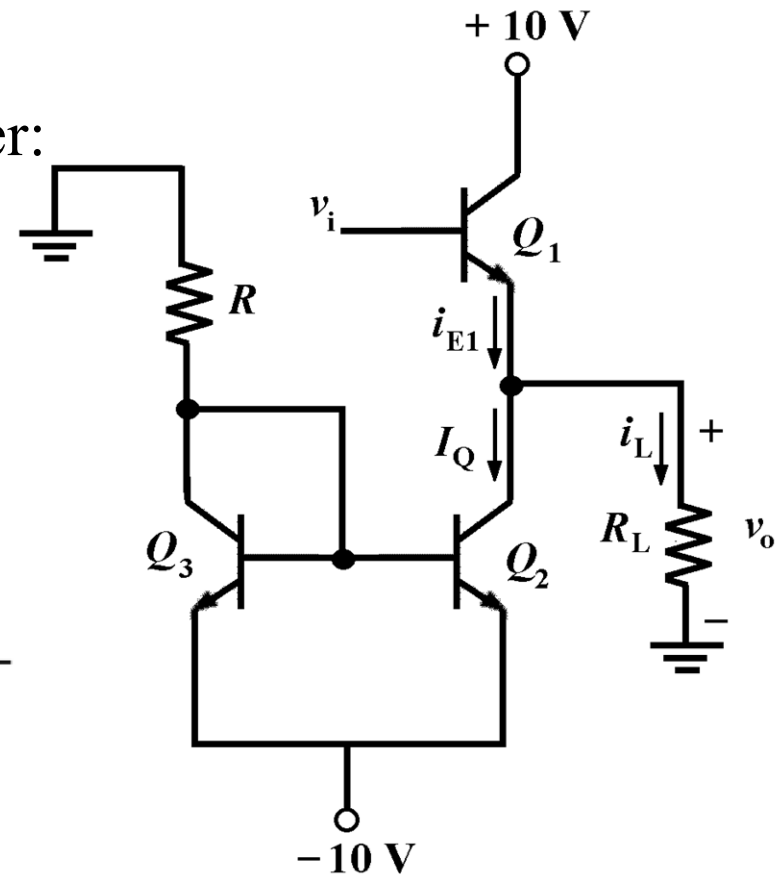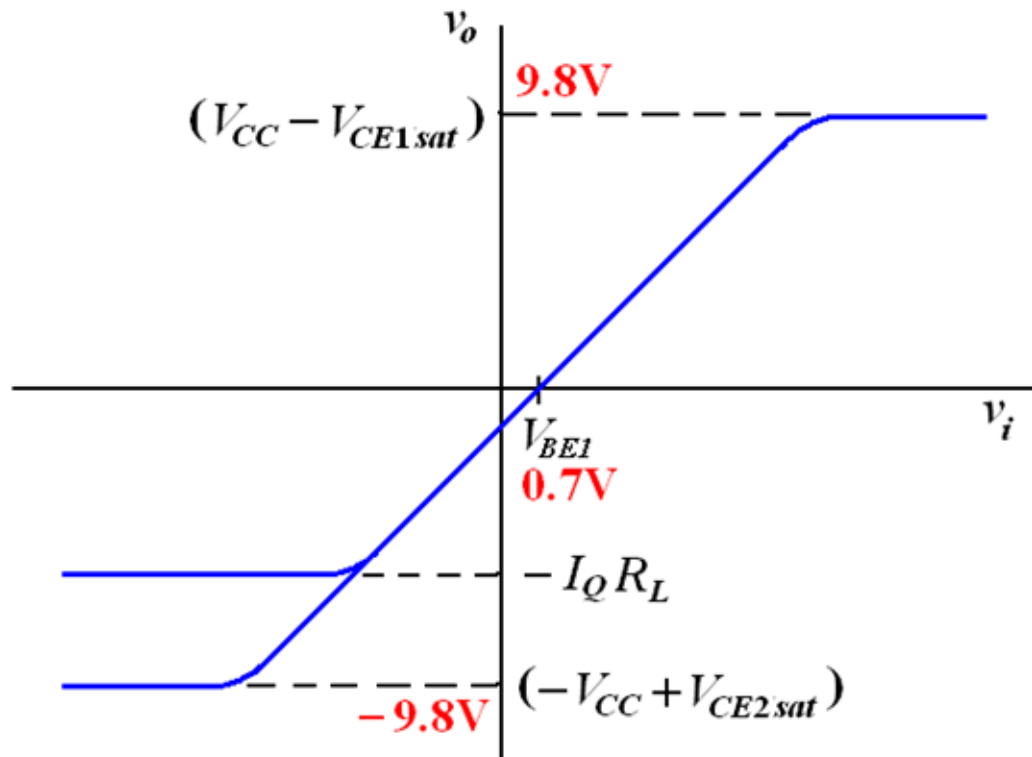
$$v_o = -I_Q R_L \text{ or } -V_{CC} + V_{CEsat2}$$



To achieve maximum negative output voltage of  $-V_{CC} + V_{CEsat2}$


The required minimum biasing:

$$I_Q \geq \frac{|-V_{CC} + V_{CEsat2}|}{R_L}$$

$I_Q$  must fulfill the following condition:

$$I_Q = \frac{|-V_{CC} + V_{CEsat2}|}{R_L} = \frac{10 - 0.2}{1k} = 9.8 \text{ mA}$$
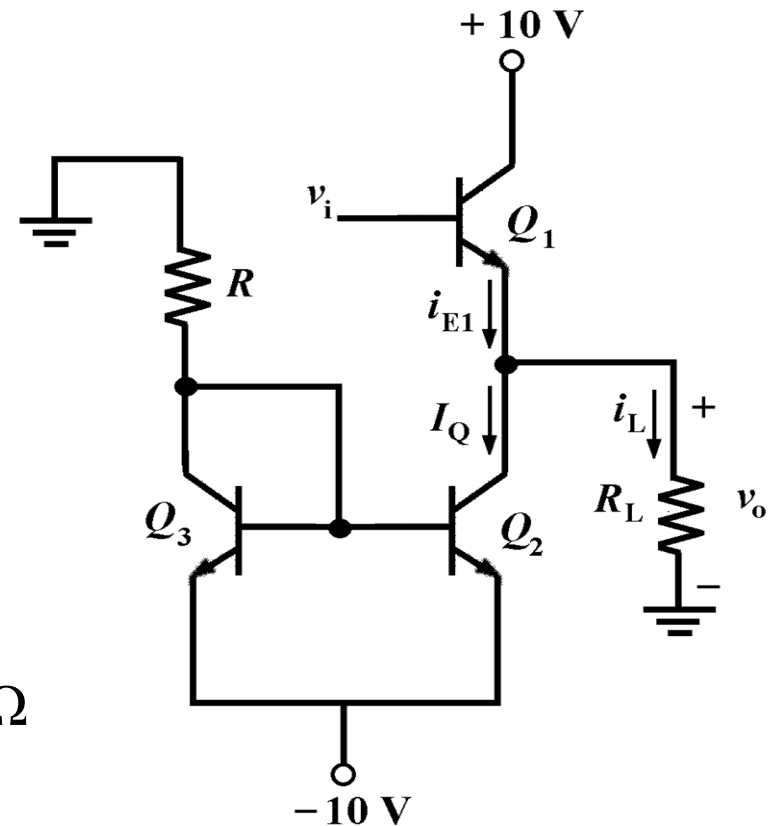
$$\therefore R = \frac{0 - V_{BE3} - (-V_{CC})}{I_Q} = \frac{0 - 0.7 + 10}{9.8m} = 950 \Omega$$




(b) With  $R = 950 \, \Omega$ ,  $I_Q = 9.8 \, \text{mA}$

$$i_{L,max} = \frac{v_{o,max}}{R_L} = \frac{V_{CC} - V_{CE1sat}}{R_L} = \frac{10 - 0.2}{1k} = 9.8 \, \text{mA}$$

$$i_{L,min} = \frac{v_{o,min}}{R_L} = \frac{-V_{CC} + V_{CE2sat}}{R_L} = \frac{-10 + 0.2}{1k} = -9.8 \, \text{mA}$$

$$i_{E1,max} = I_Q + i_{L,max} = 9.8\text{mA} + 9.8\text{mA} = 19.6 \, \text{mA}$$
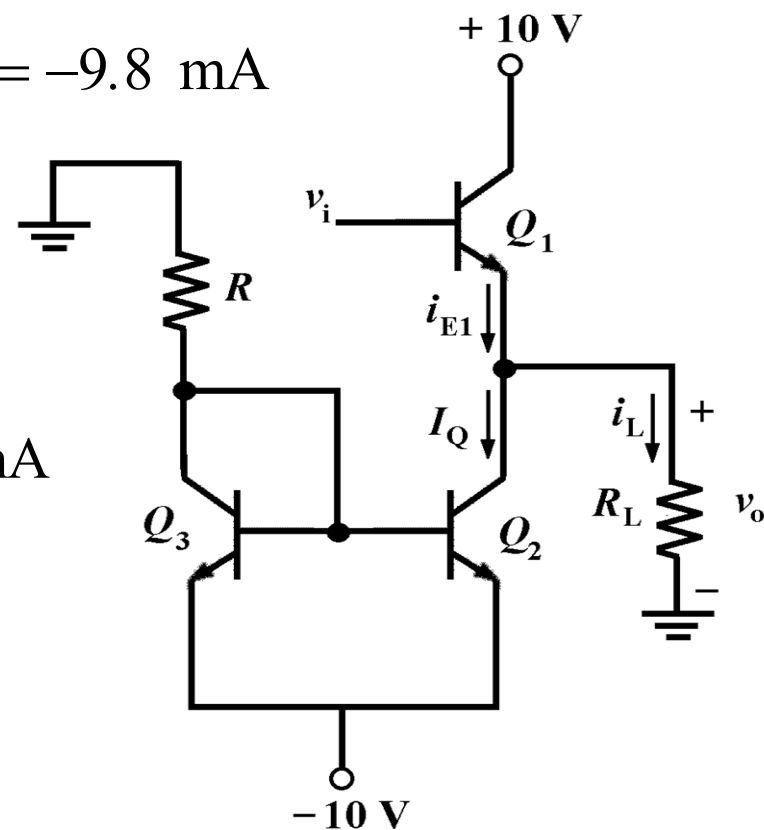
$$i_{E1,min} = I_Q + i_{L,min} = 9.8\text{mA} - 9.8\text{mA} = 0$$





(c)

Average power to the load:


$$\overline{P_L} = \frac{V_p I_p}{2} = \left( \frac{v_{o,max}^2}{2R_L} \right) = \frac{1}{2} \times \frac{9.8^2}{1k} = 48 \text{ mW}$$

The biasing currents for  $Q_1$ ,  $Q_2$  and  $Q_3$  are  $I_Q$ :

Average power from the power supply:

$$\begin{aligned} \overline{P_S} &= I_Q V_{CC} + I_Q [V_{CC} - (-V_{CC})] \\ &= 3I_Q V_{CC} = 3 \times 9.8 \text{ m} \times 10 = 294 \text{ mW} \end{aligned}$$
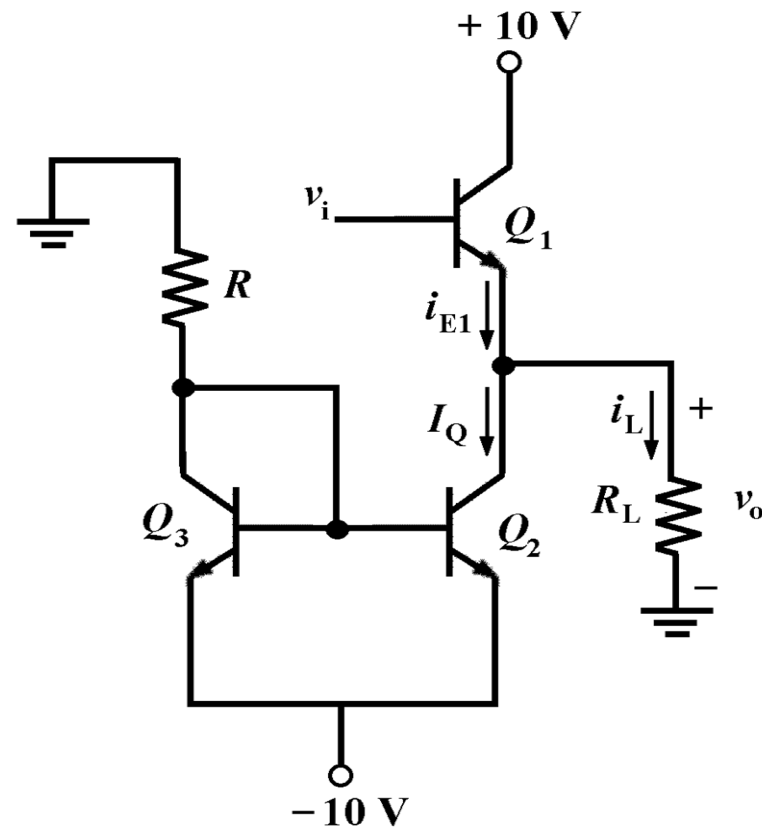
$$\eta = \frac{\overline{P_L}}{\overline{P_S}} \times 100 = \frac{48}{294} \times 100 = 16.32 \%$$



3. Consider a BiCMOS follower amplifier circuit shown in Fig. 3. The BJT parameters are:  $V_{BE} = 0.7$  V and  $V_{CE(sat)} = 0.2$  V. The MOSFET parameters are:  $V_{TN} = -1.8$  V and  $K_n = \frac{1}{2} k'_n \left( \frac{W}{L} \right) = 12$  mA/V<sup>2</sup>.

(a) Determine the maximum and minimum values of output voltage and the corresponding values of input voltage for the amplifier to operate in the linear region when: (i)  $R_L$  is removed (open-circuit) (ii)  $R_L = 500 \Omega$

(b) Determine the smallest possible value of  $R_L$  if a 2 V peak sine wave is produced at output. What is the corresponding conversion efficiency?

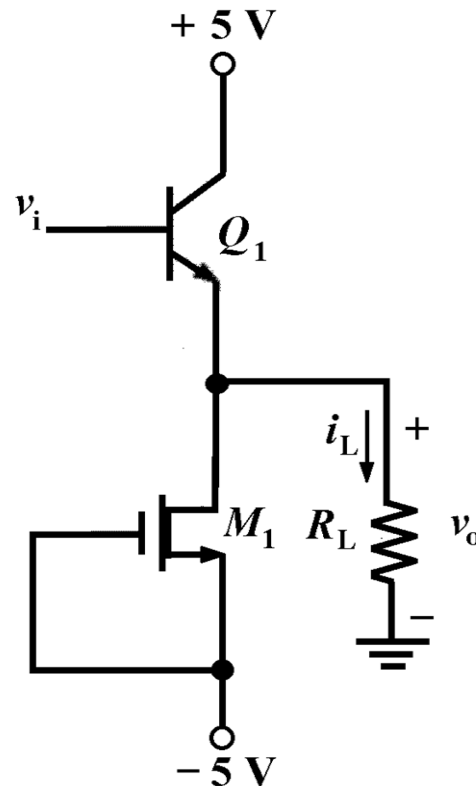


Figure 3

Note: The MOSFET is a depletion NMOS as

$V_{TN}$  is -ve.

$$I_{DQ} = K_n (v_{GS} - V_{TN})^2 = 12m[0 - (-1.8)]^2 = 38.9 \text{ mA}$$

The MOSFET must be kept in saturation mode so that it maintains as a constant current source:

$$V_{DS} \geq V_{GS} - V_{TN}$$


$$V_{DS} \geq 0 - (-1.8)$$

$$V_{DS} \geq 1.8 \text{ V}$$

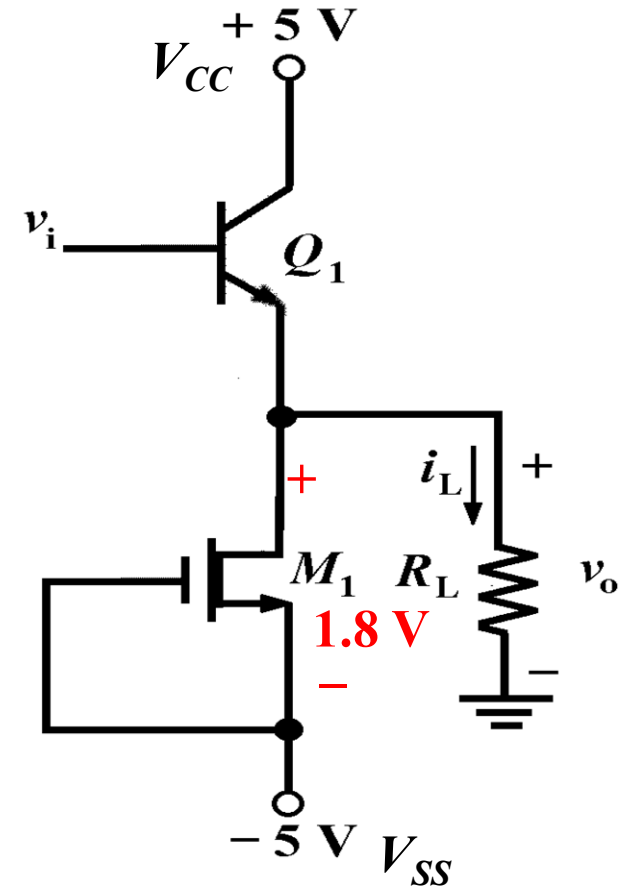(a)  $R_L = \infty$  (open-circuit)


$$v_{o,\max} = V_{CC} - v_{CEsat} = 5 - 0.2 = 4.8 \text{ V}$$


$$v_{o,\min} = V_{SS} + v_{DS,\min} = -5 + 1.8 = -3.2 \text{ V}$$



$$v_{i,\max} = v_{o,\max} + V_{BE} = 4.8 + 0.7 = 5.5 \text{ V}$$
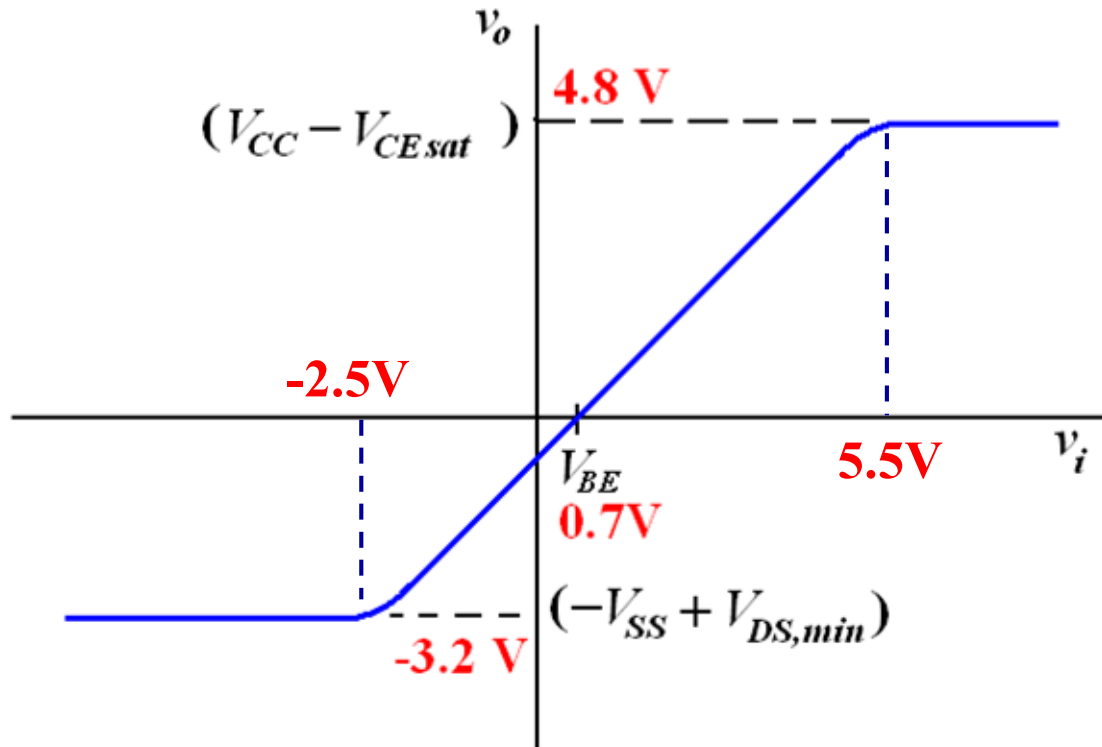
$$v_{i,\min} = v_{o,\min} + V_{BE} = -3.2 + 0.7 = -2.5 \text{ V}$$



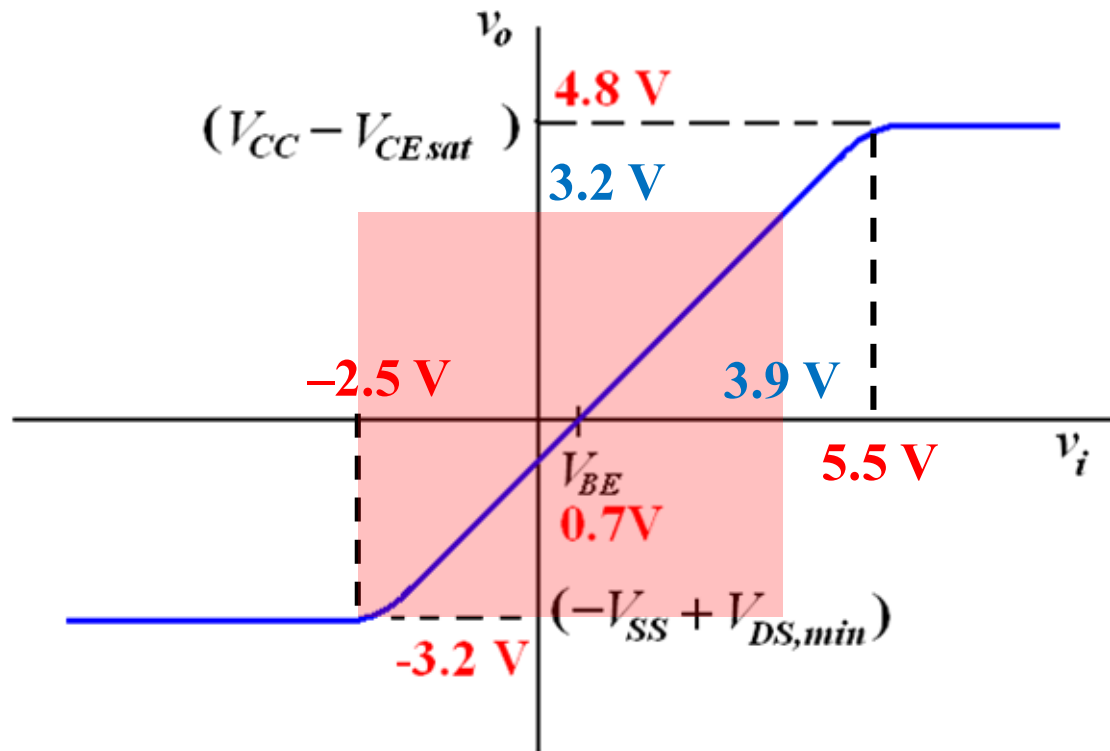

To obtain maximum output voltage swing without clipping:

$$-3.2\text{ V} \leq v_o \leq 3.2\text{ V}$$

The corresponding input voltage swing:

$$-2.5\text{ V} \leq v_i \leq 3.9\text{ V}$$

(b)  $R_L = 500 \, \Omega$

$$v_{o,\min} = -I_{DQ}R_L = -38.9\text{m} \times 500 = -19.45 \text{ V} \text{ or } -3.2 \text{ V}$$


$$\therefore v_{o,\min} = -3.2 \text{ V}$$

Similarly, to obtain maximum output voltage swing without clipping:

$$-3.2 \text{ V} \leq v_o \leq 3.2 \text{ V}$$

The corresponding input voltage swing:
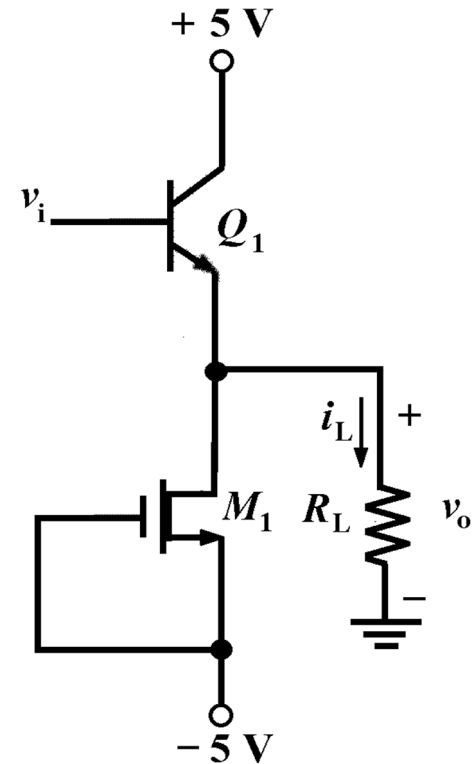
$$-2.5 \text{ V} \leq v_i \leq 3.9 \text{ V}$$



$$-2 \text{ V} \leq v_o \leq 2 \text{ V}$$

The negative swing sets the limit,  $v_o = -2\text{V}$ .

$$v_{o,\min} = -I_{DQ}R_L = -2 \text{ V}$$

$$\therefore R_L = \frac{v_{o,\min}}{I_{DQ}} = \frac{2}{38.9\text{m}} = 51.4 \text{ } \Omega$$

$$\therefore v_{i,\min} = -2 + 0.7 = -1.3 \text{ V}$$

$$\overline{P_L} = \frac{1}{2} \left( \frac{V_p^2}{R_L} \right) = \frac{1}{2} \times \frac{2^2}{51.4} = 38.9\text{mW}$$

$$\overline{P_S} = I_{DQ} [V_{CC} - (-V_{SS})] = 38.9\text{m} \times 10 = 389 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} \times 100 = \frac{38.9}{389} \times 100 = 10 \%$$

