

# Wideband Amplifiers

## EE4341: Advanced Analog Circuits

Professor Zheng Yuanjin

School of Electrical and Electronic Engineering

Email: [YJZHENG@ntu.edu.sg](mailto:YJZHENG@ntu.edu.sg)

# Learning Objectives

By the end of this section, you should be able to:

- Exactly know how to draw the frequency response and the relationship between unity gain frequency and -3 dB frequency of an amplifier.

- Fully master how to analyse a C-E amplifier frequency response using the miller capacitor splitting technique.

- Understand how to analyse a CE-CB amplifier frequency response.

- Understand the concept of feedback technique extending the amplifier bandwidth, and calculating cascaded system's bandwidth.



# Wideband Amplifiers

## Topic 1: Amplifier Frequency Response

### EE4341: Advanced Analog Circuits


Professor Zheng Yuanjin

School of Electrical and Electronic Engineering


Email: [YJZHENG@ntu.edu.sg](mailto:YJZHENG@ntu.edu.sg)
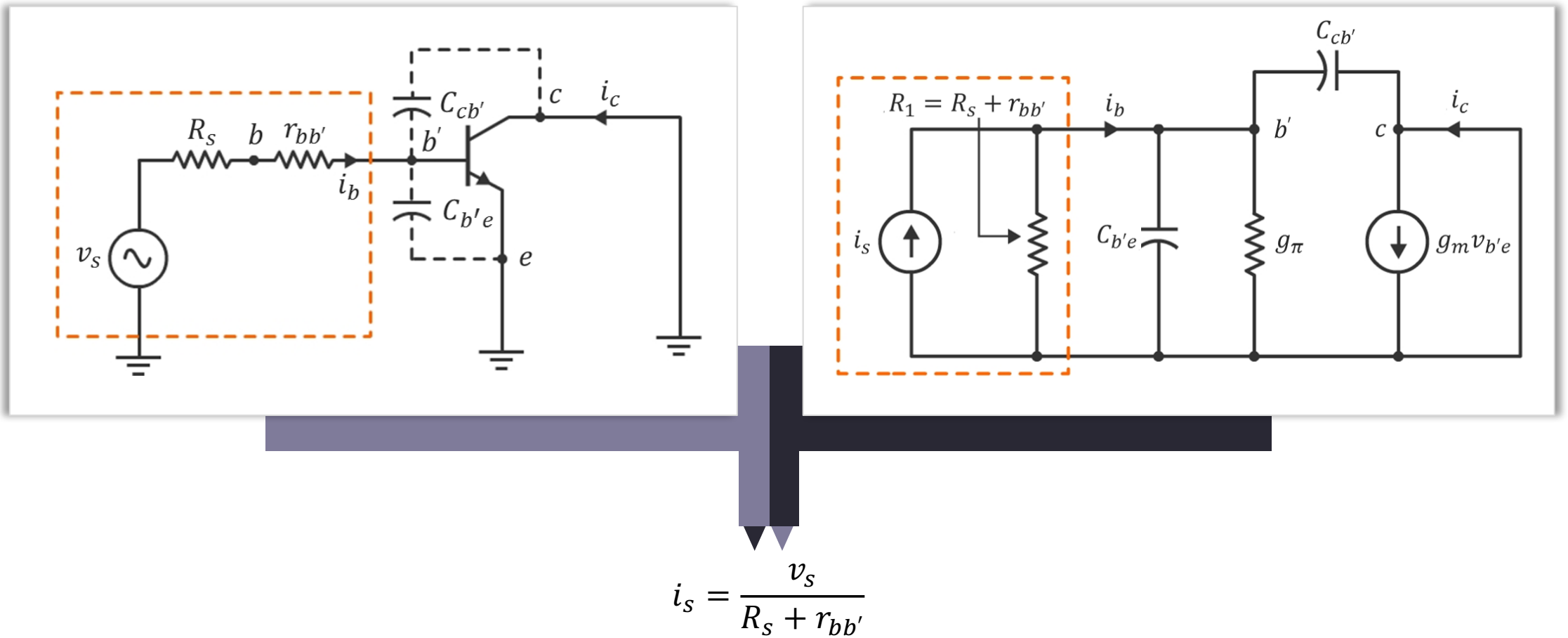
# Unity Gain Frequency of BJT

The short-circuit current gain is determined with output shorted.



# Unity Gain Frequency of BJT

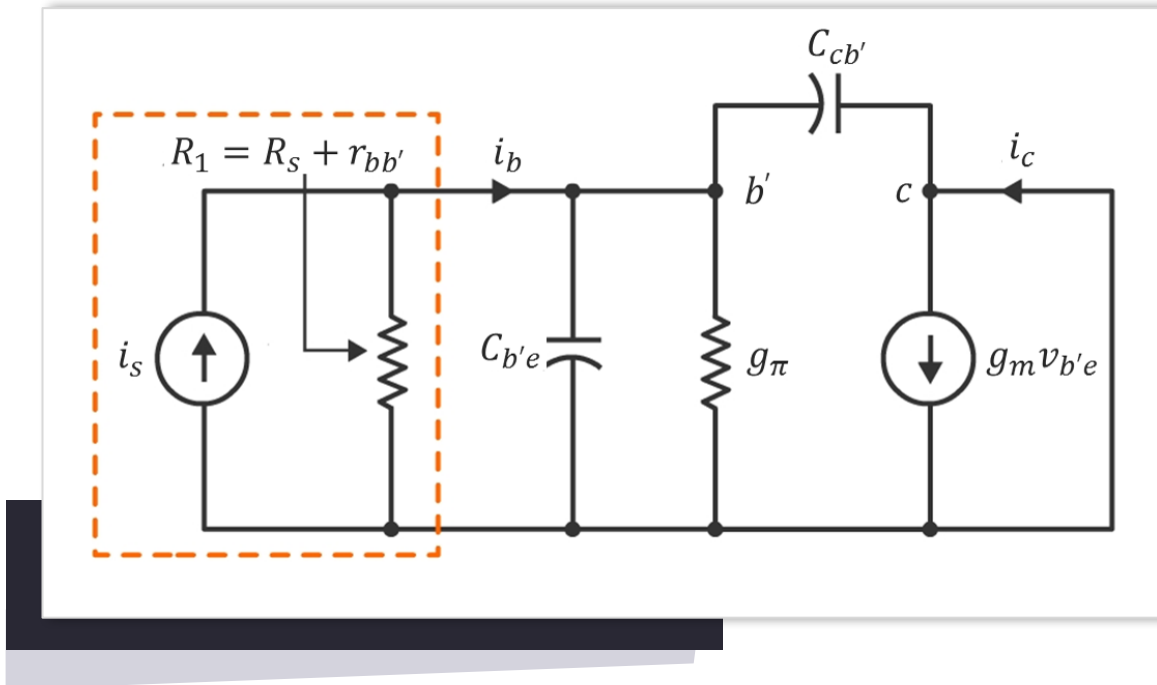

$$i_c = g_m v_{b'e}$$

Apply KCL at node  $b'$  :


$$\begin{aligned} i_b &= g_\pi v_{b'e} + j\omega C_{b'e} v_{b'e} + j\omega C_{cb'} (v_{b'e} - v_{ce}) \\ &= g_\pi v_{b'e} + j\omega C_{b'e} v_{b'e} + j\omega C_{cb'} v_{b'e} \\ &= [g_\pi + j\omega (C_{b'e} + C_{cb'})] v_{b'e} \end{aligned}$$

$$g_\pi = \frac{1}{r_\pi}$$

$$\begin{aligned} A_{i(sc)} = \frac{i_c}{i_b} &= \frac{g_m}{g_\pi + j\omega (C_{b'e} + C_{cb'})} \\ &= \left( \frac{g_m}{g_\pi} \right) \left[ \frac{1}{1 + j\omega (C_{b'e} + C_{cb'}) / g_\pi} \right] \end{aligned}$$

$$\therefore \frac{g_m}{g_\pi} = \frac{I_C}{V_T} \times \frac{V_T}{I_B} = \beta$$

# Unity Gain Frequency of BJT

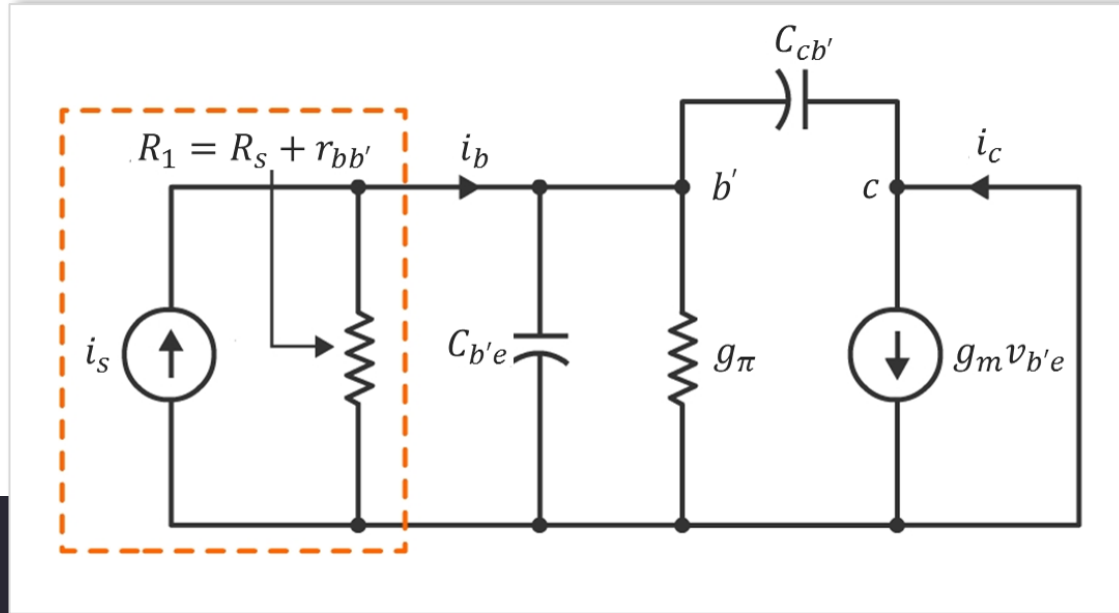

$$\therefore A_{i(sc)} = \frac{\beta}{1 + j\omega(C_{b'e} + C_{cb'})\beta/g_m}$$

By definition, unity gain frequency  $f_T$  occurs when:


$$|A_{i(sc)}| = \left| \frac{\beta}{1 + j\omega_T(C_{b'e} + C_{cb'})\beta/g_m} \right| = 1$$

$$\therefore \omega_T(C_{b'e} + C_{cb'})\beta/g_m \gg 1$$

$$\therefore \frac{\beta}{\frac{\omega_T(C_{b'e} + C_{cb'})\beta}{g_m}} \approx 1$$


$$\omega_T \approx \frac{g_m}{C_{b'e} + C_{cb'}} \Rightarrow f_T = \frac{g_m}{2\pi(C_{b'e} + C_{cb'})}$$

# Unity Gain Frequency of BJT

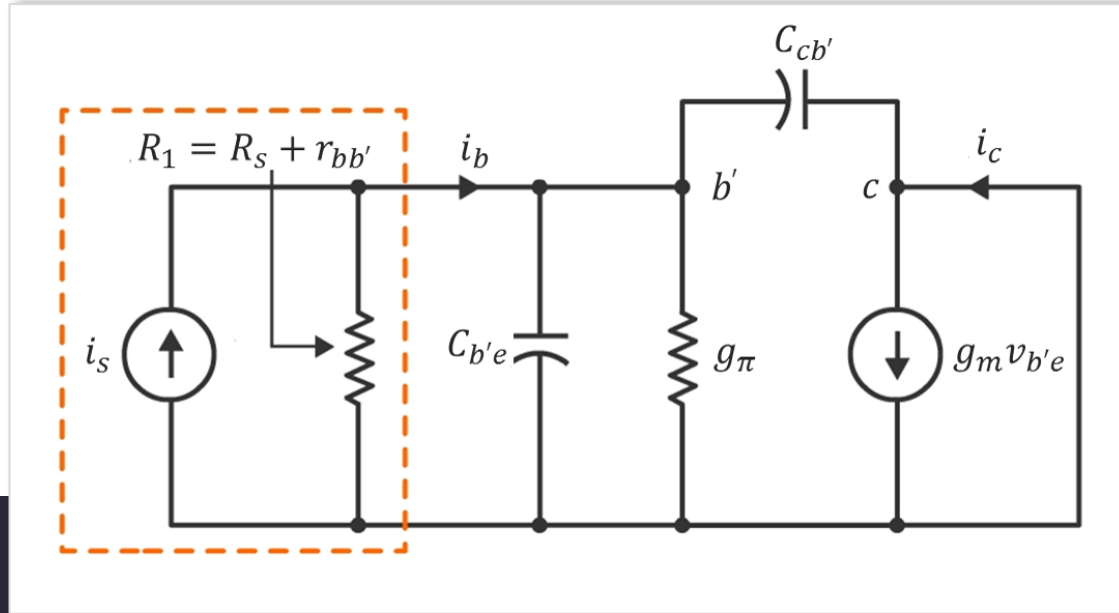

**Note:** The above expression shows that  $f_T$  is independent of  $\beta$  but is dependent on the biasing point (that determines  $g_m$ ) and the inherent parasitic capacitances of the device. As a general rule, to design a wideband amplifier with a -3 dB bandwidth of  $BW_{3dB}$ , the BJT must have a  $f_T > 5$  to 10 times  $BW_{3dB}$ .

# Unity Gain Frequency of BJT

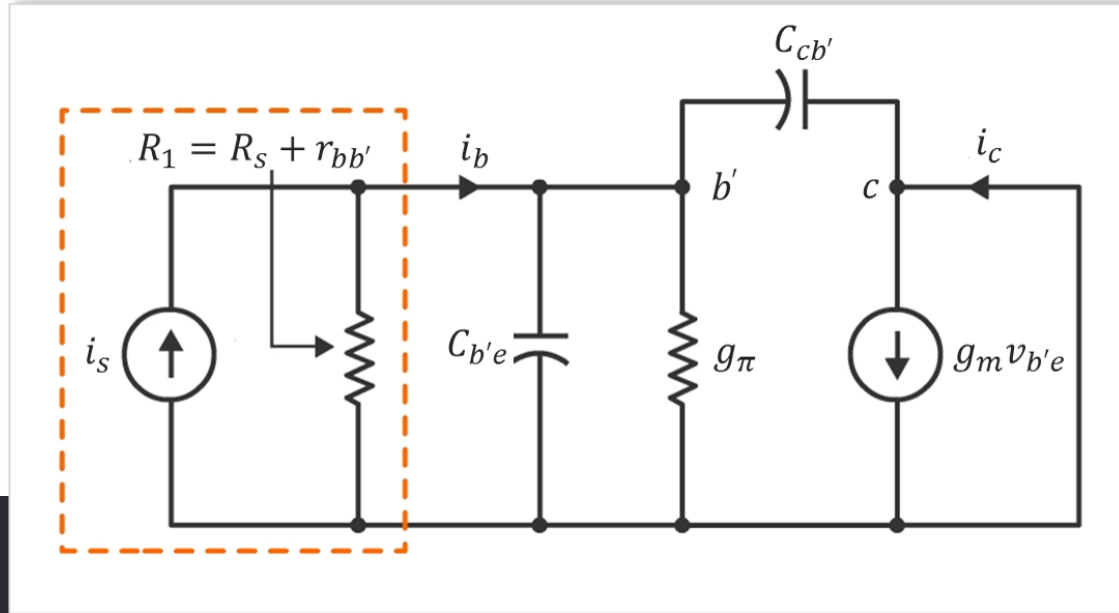

$$A_{i(sc)}(j\omega) = \frac{\beta}{1 + j\omega(C_{b'e} + C_{cb'})\beta/g_m}$$

$$\therefore \omega_T = \frac{g_m}{C_{b'e} + C_{cb'}}$$

$$\therefore A_{i(sc)}(j\omega) = \frac{\beta}{1 + j\left(\frac{\beta\omega}{\omega_T}\right)}$$

$$A_{i(sc)}(jf) = \frac{\beta}{1 + j\left(\frac{\beta f}{f_T}\right)}$$




# Unity Gain Frequency of BJT



$$A_{i(sc)} = \frac{\beta}{1 + j\left(\frac{\beta f}{f_T}\right)} = \frac{\beta}{1 + j\left(\frac{f}{f_\beta}\right)}$$

Where,  $f_\beta = \frac{f_T}{\beta}$  is the -3 dB frequency.

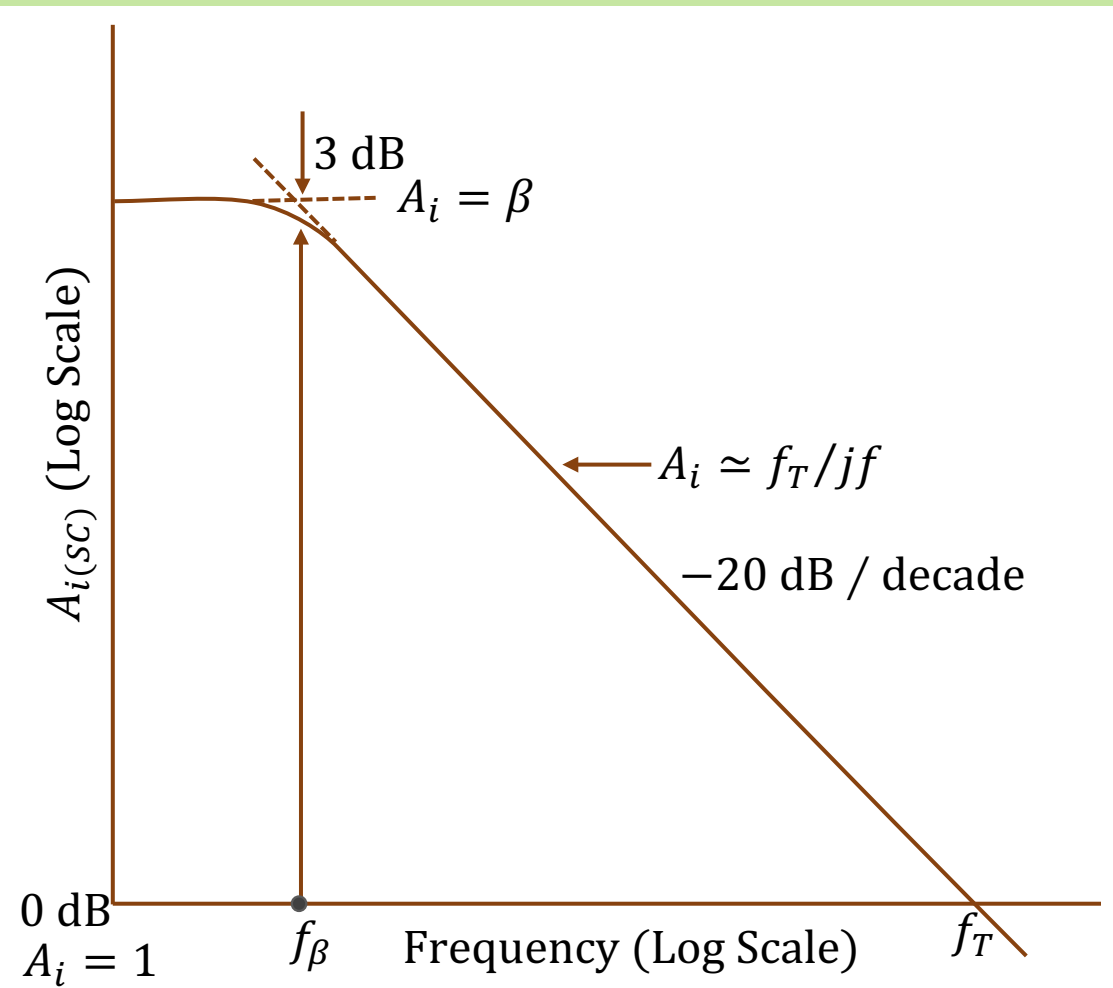
$$A_{i(sc)} \approx \frac{\beta}{j\left(\frac{f}{f_\beta}\right)} = \frac{\beta f_\beta}{jf} = \frac{f_T}{jf} \text{ for } f > 3f_\beta$$



# Frequency Response of CE Amplifier

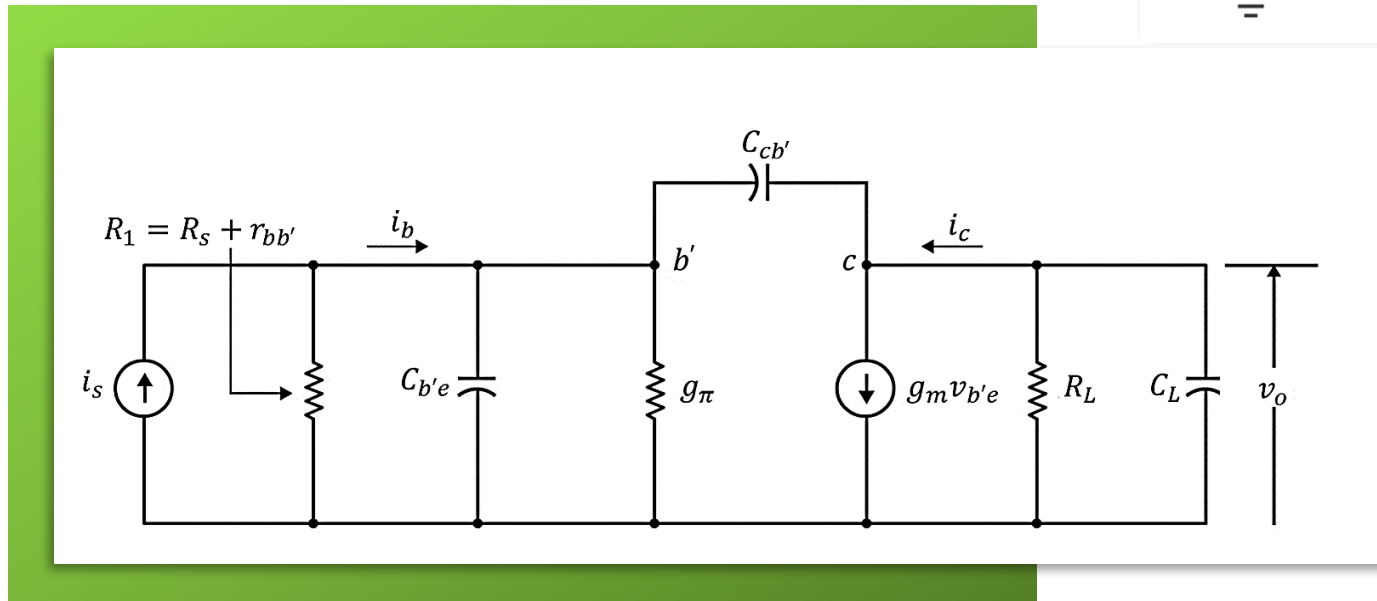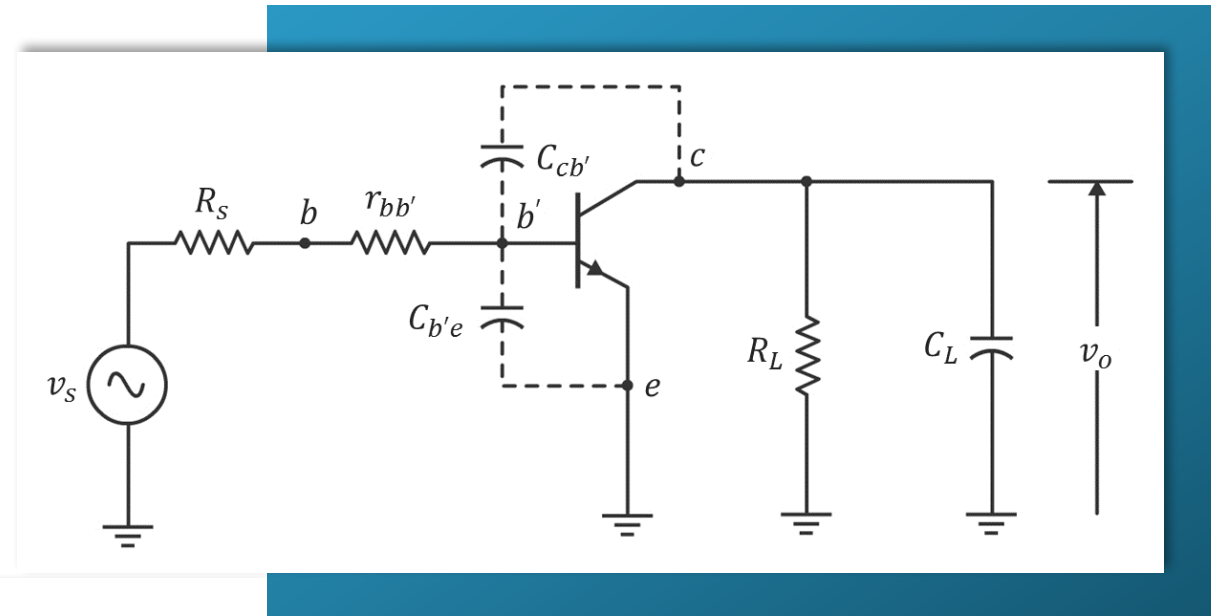

# Frequency Response of CE Amplifier

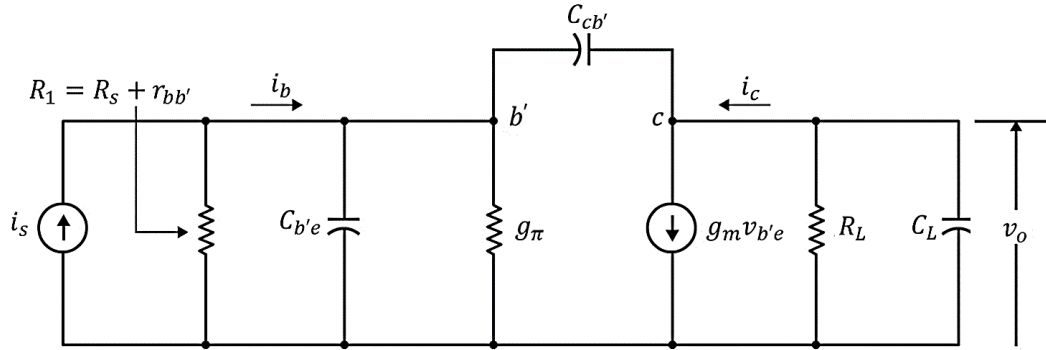

Apply KCL at node  $b'$ :

$$v_{b'e}(G_1 + g_\pi + j\omega C_{b'e}) = i_s + (v_o - v_{b'e})j\omega C_{cb'}$$

$$v_{b'e}[G_1 + g_\pi + j\omega(C_{b'e} + C_{cb'})] - j\omega C_{cb'}v_o = i_s \text{ ----- (1)}$$

Substitute (2) into (1):

$$v_{b'e} \left[ G_1 + g_\pi + j\omega(C_{b'e} + C_{cb'}) + \frac{j\omega C_{cb'}(g_m - j\omega C_{cb'})}{G_L + j\omega(C_{cb'} + C_L)} \right] = i_s$$

$$G_1 = \frac{1}{R_S + r_{bb'}} \quad G_L = \frac{1}{R_L}$$


Apply KCL at node c:

$$v_o(G_L + j\omega C_L) + g_m v_{b'e} = (v_{b'e} - v_o)j\omega C_{cb'}$$

$$v_o[G_L + j\omega(C_L + C_{cb'})] + g_m v_{b'e} = j\omega C_{cb'}v_{b'e}$$

$$v_o = \frac{-(g_m - j\omega C_{cb'})v_{b'e}}{G_L + j\omega(C_L + C_{cb'})} \text{ ----- (2)}$$

# Frequency Response of CE Amplifier

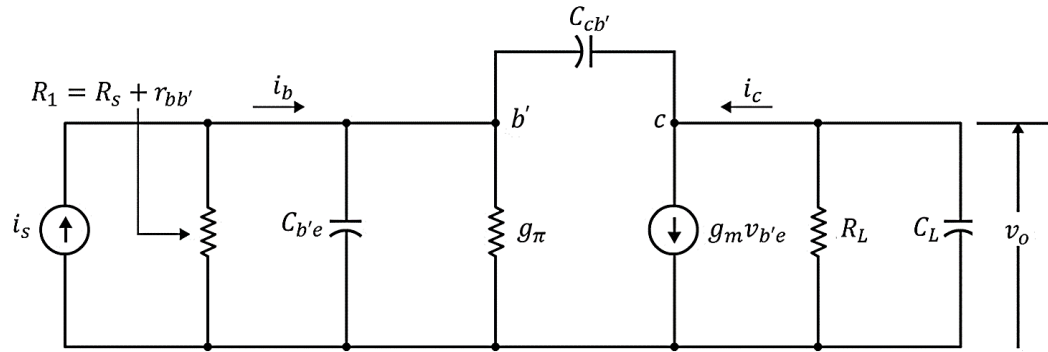


$$v_{b'e} = \frac{i_s}{G_1 + g_\pi + j\omega(C_{b'e} + C_{cb'}) + \frac{j\omega C_{cb'}(g_m - j\omega C_{cb'})}{G_L + j\omega(C_{cb'} + C_L)}} \text{ -----(3)}$$

Substitute (3) into (2):

$$\therefore v_o = \left[ \frac{-(g_m - j\omega C_{cb'})}{G_L + j\omega(C_{cb'} + C_L)} \right] \frac{i_s}{G_1 + g_\pi + j\omega(C_{b'e} + C_{cb'}) + \frac{j\omega C_{cb'}(g_m - j\omega C_{cb'})}{G_L + j\omega(C_{cb'} + C_L)}}$$

$$i_s = \frac{v_s}{R_S + r_{bb'}} = v_s G_1$$

# Frequency Response of CE Amplifier

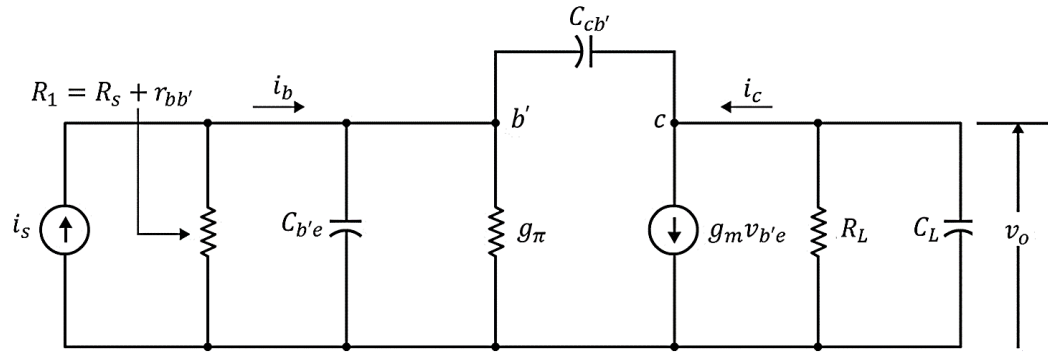

$$A_v = \frac{v_o}{v_s} = \frac{-(g_m - j\omega C_{cb'})G_1}{[G_L + j\omega(C_{cb'} + C_L)] \left[ G_1 + g_{\pi} + j\omega(C_{b'e} + C_{cb'}) + \frac{j\omega C_{cb'}(g_m - j\omega C_{cb'})}{G_L + j\omega(C_{cb'} + C_L)} \right]}$$

In the frequency range of interest ( $f$  in the MHz range):


$$g_m (\text{in the range of } 10^{-3}) \gg \omega C_{cb'} (\text{in the range of } 10^6 \times 10^{-12} \approx 10^{-6})$$

$$\therefore (g_m - j\omega C_{cb'})G_1 \approx g_m G_1$$

$$G_1 (\text{in the range of } 10^{-2}) \gg g_{\pi} (\text{in the range of } 10^{-4})$$

$$\therefore G_1 + g_{\pi} \approx G_1$$

# Frequency Response of CE Amplifier

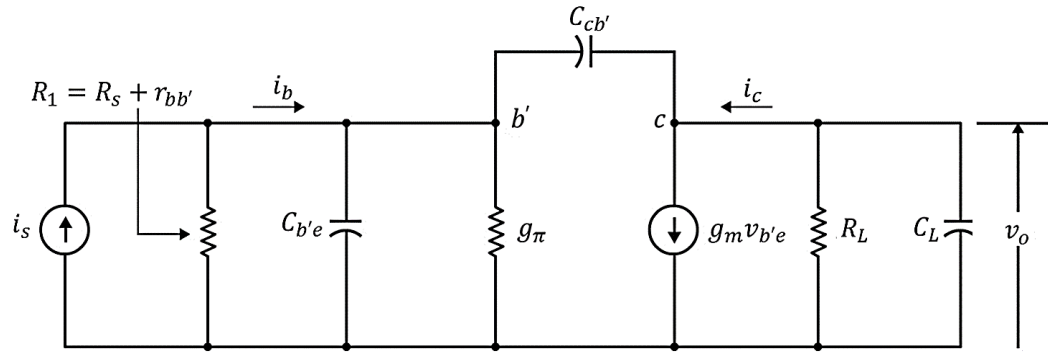


$G_L$  (in the range of  $10^{-3}$ )  $\gg \omega(C_{cb'} + C_L)$  (in the range of  $10^6 \times 10^{-12} \approx 10^{-6}$ )

$$\therefore G_L + j\omega(C_{cb'} + C_L) \approx G_L$$


$$A_v \approx \frac{-g_m G_1}{[G_L + j\omega(C_{cb'} + C_L)] \left[ G_1 + j\omega(C_{b'e} + C_{cb'}) + \frac{j\omega C_{cb'} g_m}{G_L} \right]}$$

# Frequency Response of CE Amplifier

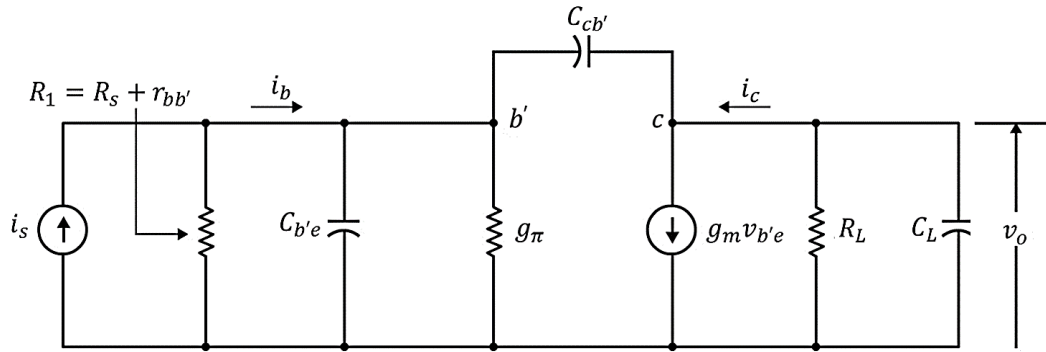

$$\begin{aligned}
 A_v &= \frac{-g_m G_1}{[G_L + j\omega(C_{cb'} + C_L)][G_1 + j\omega(C_{b'e} + C_{cb'} + g_m R_L C_{cb'})]} \\
 &= \frac{-g_m G_1}{G_L G_1 \left[1 + \frac{j\omega(C_{cb'} + C_L)}{G_L}\right] \left[1 + \frac{j\omega(C_{b'e} + C_{cb'} + g_m R_L C_{cb'})}{G_1}\right]} \\
 &= \frac{-g_m R_L}{\left[1 + \frac{j\omega(C_{b'e} + C_{cb'} + g_m R_L C_{cb'})}{G_1}\right] \left[1 + \frac{j\omega(C_{cb'} + C_L)}{G_L}\right]} \\
 &= \frac{-g_m R_L}{(1 + j\omega/\omega_1)(1 + j\omega/\omega_2)}
 \end{aligned}$$

# Frequency Response of CE Amplifier

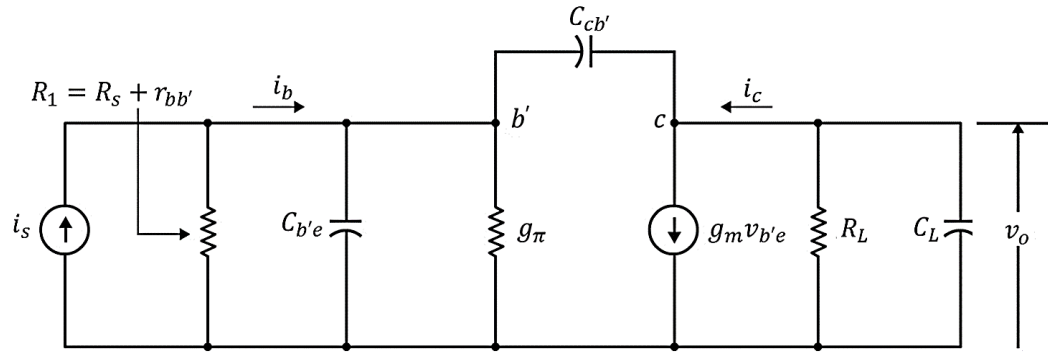

The two break frequencies:

$$\omega_1 = \frac{G_1}{C_{b'e} + C_{cb'}(1 + g_m R_L)} = \frac{1}{(R_S + r_{bb'})[C_{b'e} + C_{cb'}(1 + g_m R_L)]}$$

$$\therefore f_1 = \frac{1}{2\pi(R_S + r_{bb'})C_i} \quad \text{where, } C_i = C_{b'e} + (1 + g_m R_L)C_{cb'}$$

$$\omega_2 = \frac{G_L}{C_{cb'} + C_L} = \frac{1}{R_L(C_{cb'} + C_L)}$$


$$\therefore f_2 = \frac{1}{2\pi R_L(C_{cb'} + C_L)}$$

**Note:** The effective input capacitance is equal to  $C_{cb'}$  multiplied by  $(1 + g_m R_L)$ .

This is known as the Miller effect.



# Miller Effect

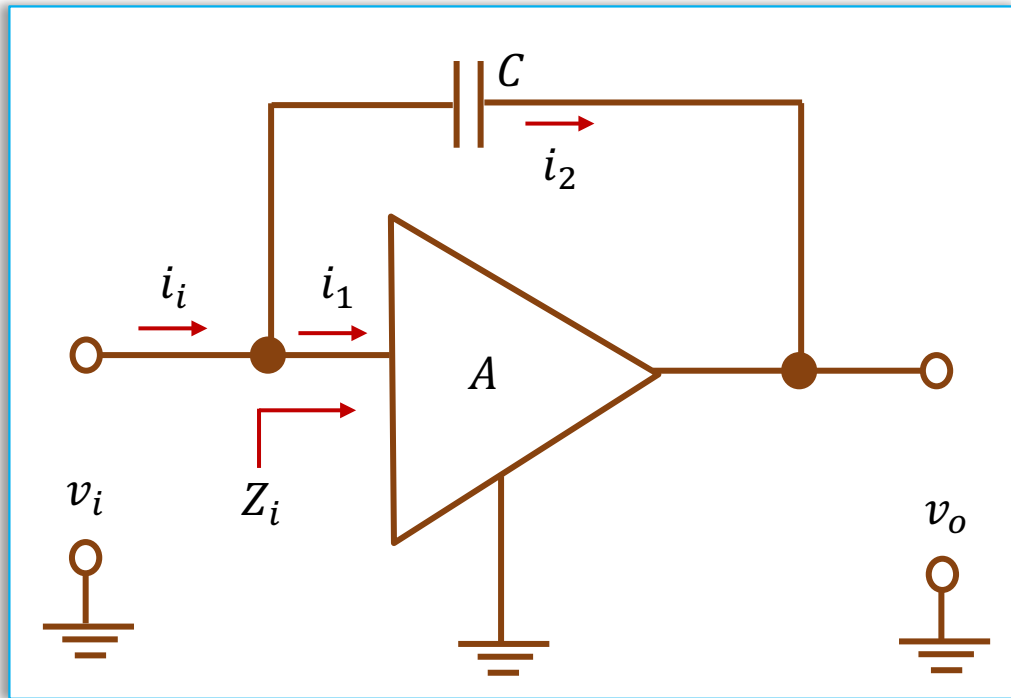

$$i_i = i_1 + i_2$$

$$i_i = \frac{v_i}{Z_i} + \frac{v_i - v_o}{1/j\omega C}$$

$$i_i = \frac{v_i}{Z_i} + j\omega C(v_i - v_o)$$

$$\therefore A = \frac{v_o}{v_i}$$

$$\therefore i_i = \frac{v_i}{Z_i} + j\omega C(v_i - Av_i)$$



# Miller Effect

$$i_i = \frac{v_i}{Z_i} + j\omega C(v_i - Av_i)$$

$$i_i = v_i \left[ \frac{1}{Z_i} + j\omega C(1 - A) \right]$$

The above expression shows that the effective input impedance is basically  $Z_i$  in parallel with a capacitance  $C(1-A)$ .

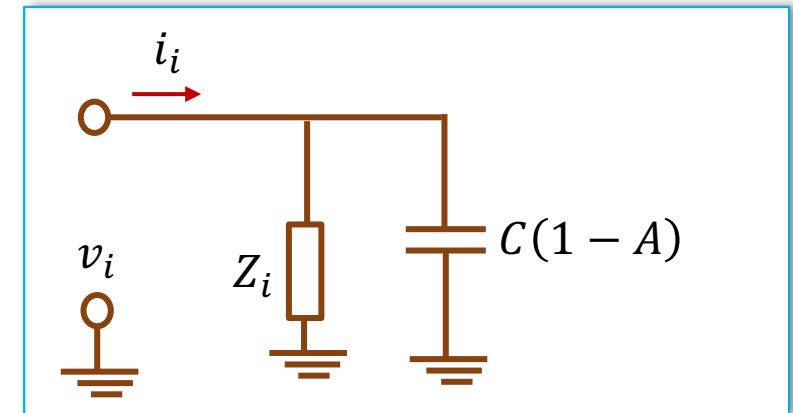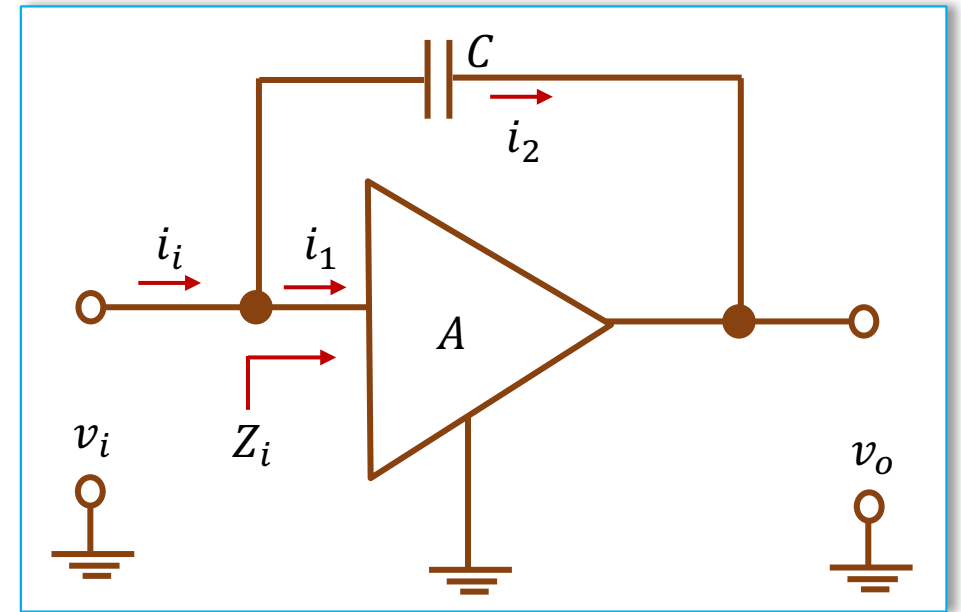The magnification of the capacitance  $C$  at the input of an amplifier is called the 'Miller Effect'.



# Miller Effect: Example

The BJT device parameters are:

$$r_{bb'} = 60 \, \Omega$$

$$R_s = 40 \, \Omega$$


$$C_{cb'} = 1.5 \, \text{pF}$$

$$f_T = 1.6 \, \text{GHz}$$

Load capacitance:  $C_L = 1 \, \text{pF}$

The BJT is biased at 2.5 mA.

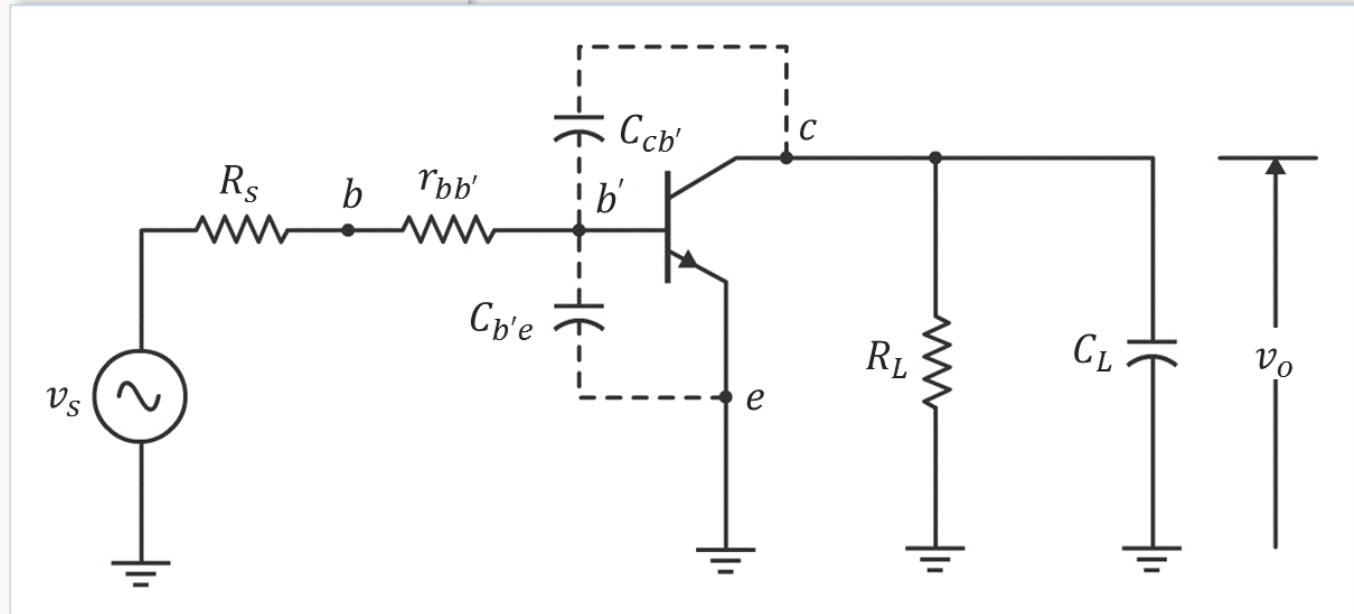Determine the voltage gain frequency response for different values of  $R_L$  varying from  $30 \, \Omega$  to  $10 \, \text{k}\Omega$ .



# Miller Effect: Example


$$\omega_T = 2\pi \times 1.6 \times 10^9 = 1.005 \times 10^{10} \text{ rad/s}$$

$$g_m = \frac{I_C}{V_T} = \frac{2.5 \text{ mA}}{26 \text{ mV}} = 0.096 \text{ S}$$

$$C_{b'e} + C_{cb'} = \frac{g_m}{\omega_T} = \frac{0.096}{1.005 \times 10^{10}} = 9.6 \text{ pF}$$

$$|A_{v(MID)}| = g_m R_L = (0.096) R_L$$
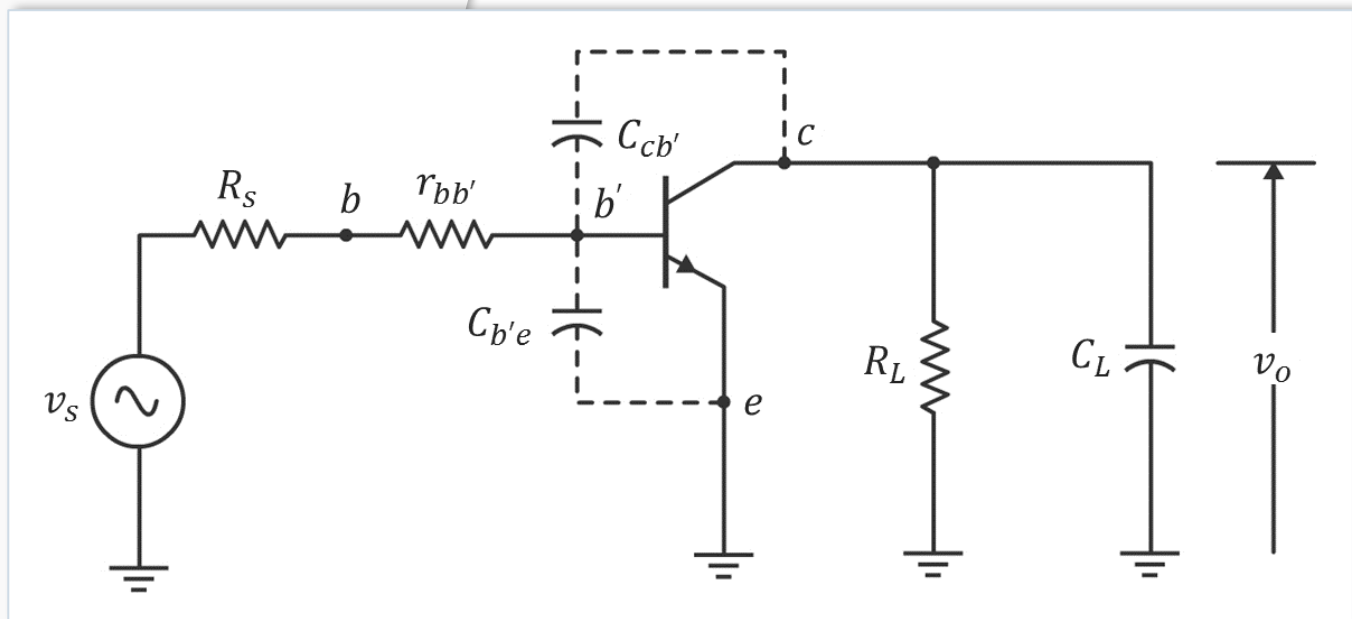
$$\begin{aligned} f_1 &= \frac{1}{2\pi(R_s + r_{bb'})(C_{b'e} + C_{cb'} + g_m R_L C_{cb'})} \\ &= \frac{1}{2\pi(100)(9.6 + 0.096 \times R_L \times 1.5) \times 10^{-12}} \\ &= \frac{1}{6.28 \times 10^{-10}(11.1 + 0.144 R_L)} \end{aligned}$$




# Miller Effect: Example

If  $R_L = 1 \text{ k}\Omega$ ,  $f_1 = 10.26 \text{ MHz}$

$$\begin{aligned} f_2 &= \frac{1}{2\pi \times R_L (C_{cb'} + C_L)} \\ &= \frac{1}{2\pi \times R_L (2.5 \times 10^{-12})} \\ &= \frac{1}{1.57 \times 10^{-11} \times R_L} \end{aligned}$$

If  $R_L = 1 \text{ k}\Omega$ ,  $f_2 = 63.7 \text{ MHz}$

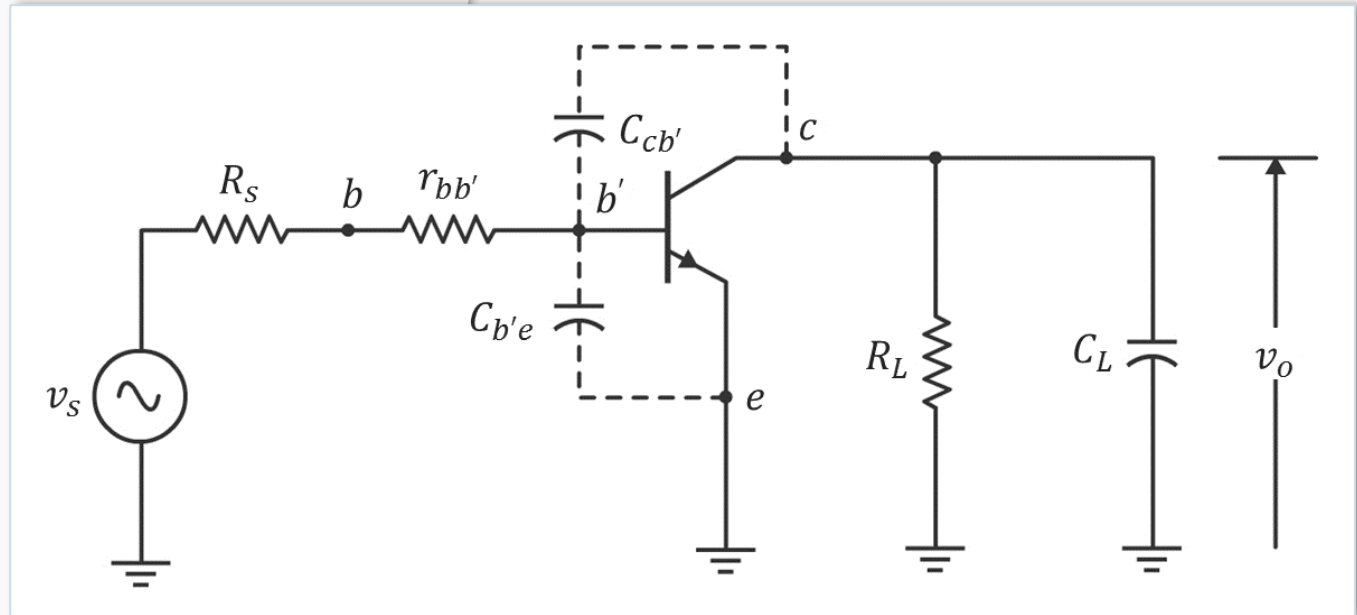Both  $f_1$  and  $f_2$  can be calculated for different load  $R_L$ .



# Miller Effect: Example



From the calculations, we have:

| $R_L (\Omega)$ | $f_1$ (MHz) | $f_2$ (MHz) | $BW$ (MHz) | $A_{V(MID)}$ | $A_{V(MID)} \times BW$ (MHz) |
|----------------|-------------|-------------|------------|--------------|------------------------------|
| 30             | 110         | 2,122       | 110        | 3            | 330                          |
| 100            | 64          | 637         | 64         | 10           | 640                          |
| 300            | 29          | 212         | 28         | 30           | 868                          |
| 1,000          | 10          | 64          | 10         | 100          | 1,000                        |
| 3,000          | 3.5         | 21          | 3.5        | 300          | 1,038                        |
| 10,000         | 1.05        | 6.4         | 1.04       | 1,000        | 1,040                        |

$f_1 \ll f_2$  for all load resistance values. Therefore,  $f_1$  is the primary factor that determines the -3dB BW of the amplifier.

Larger  $R_L$  gives larger mid-band gain but at the expense of reduction in BW.
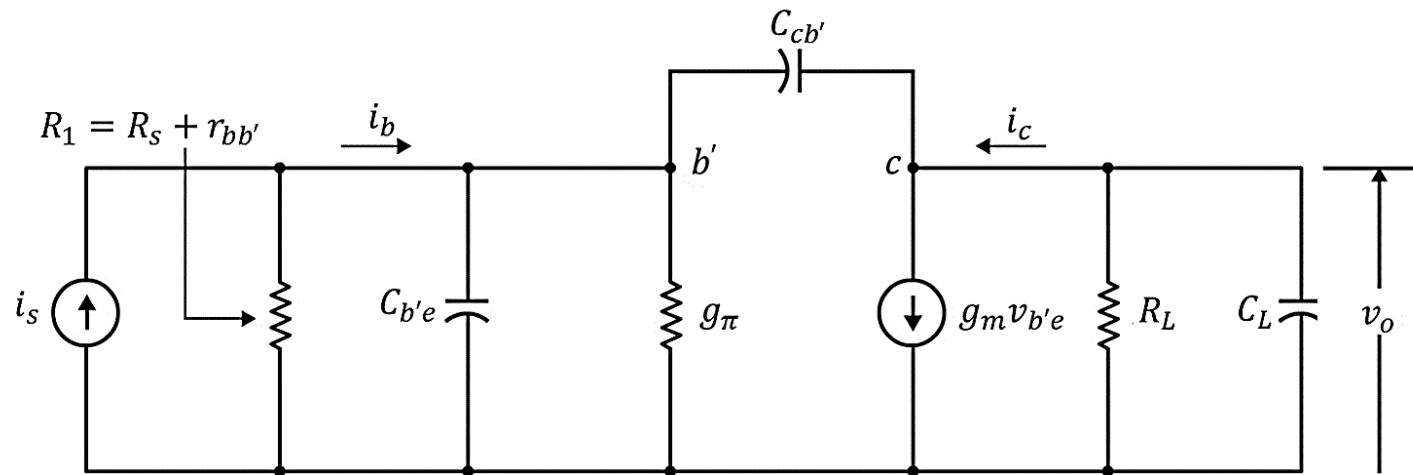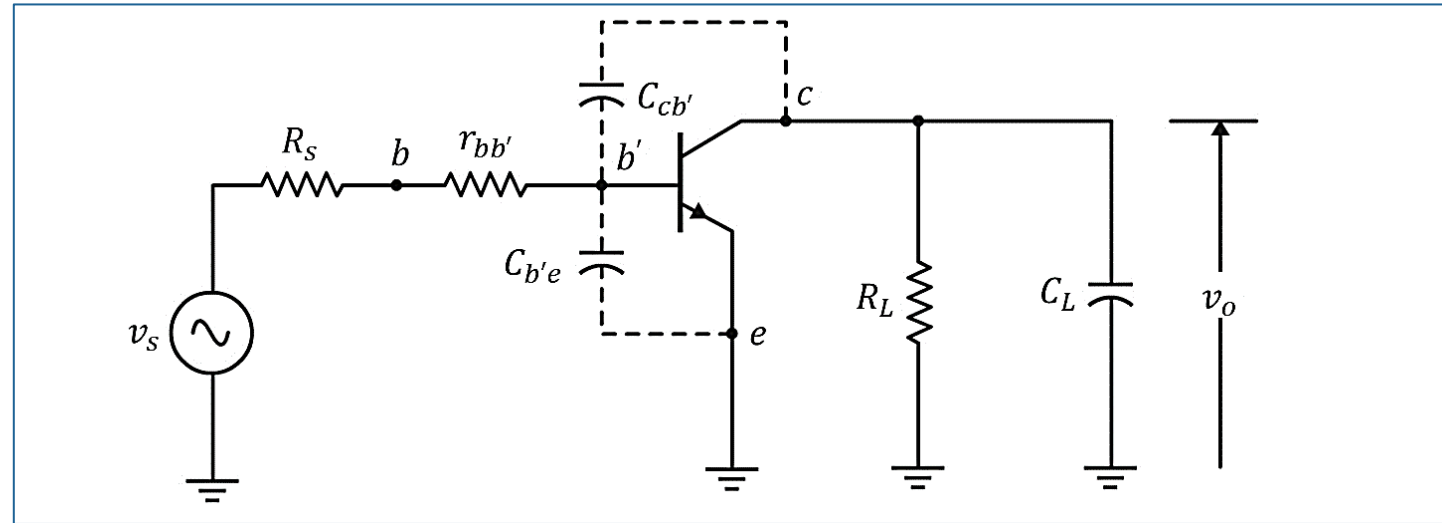
# Summary: C-E Amplifier Frequency Analysis using Miller Effect





Miller capacitor splitting

$A_{vt}$  : Terminal voltage gain

$$A_{vt} = -g_m R_L$$
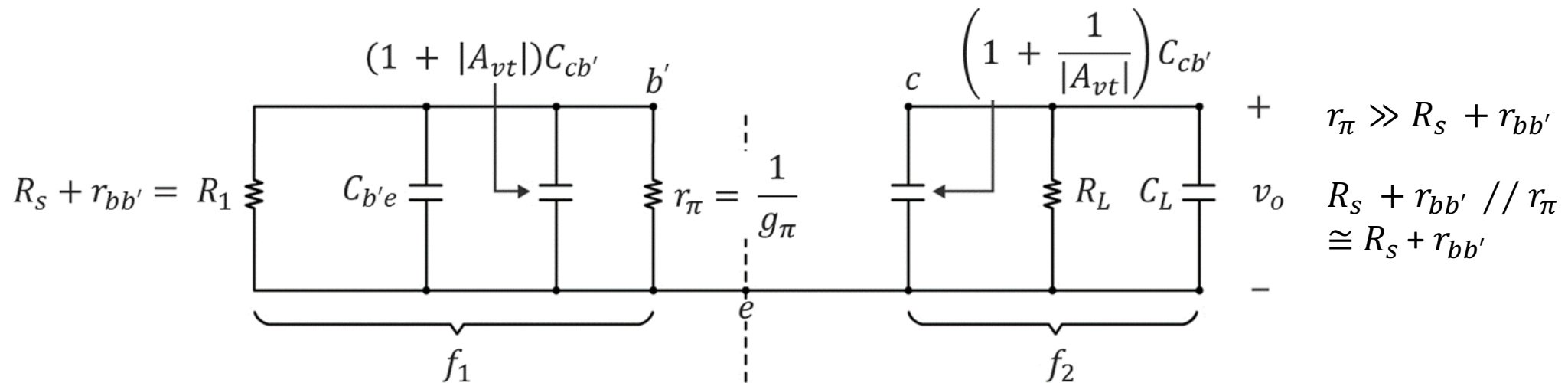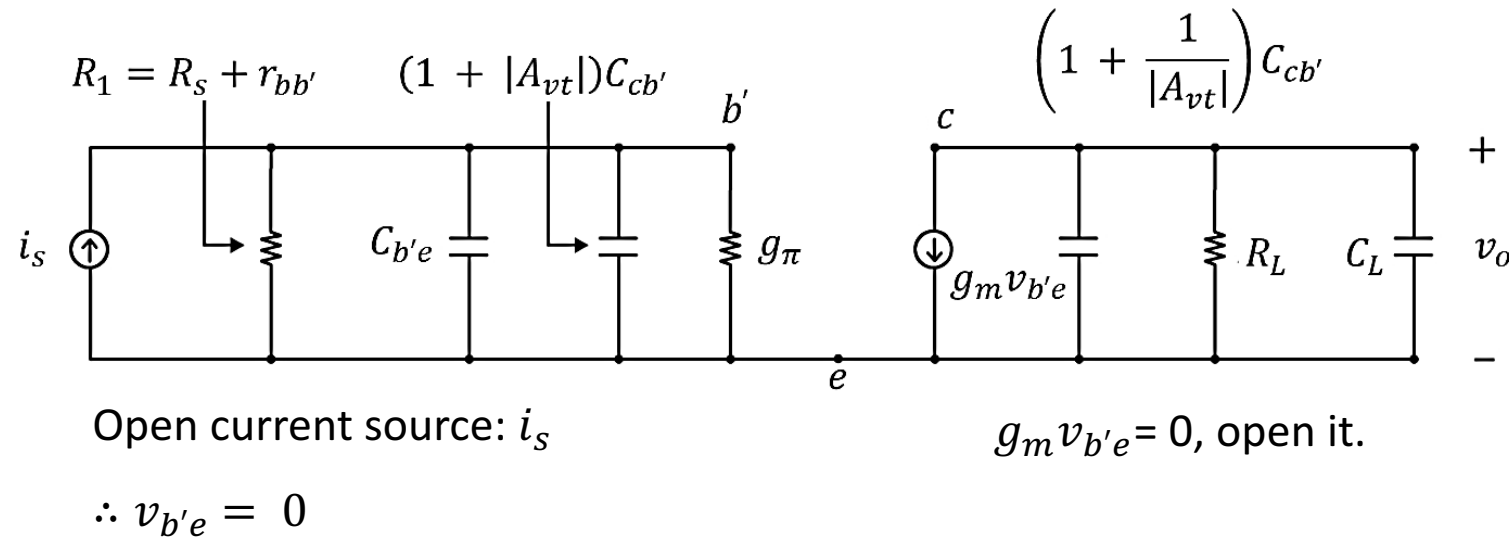
# Summary: C-E Amplifier Frequency Analysis using Miller Effect






# Summary: C-E Amplifier Frequency Analysis using Miller Effect


Calculate break frequency  $f_1$  and  $f_2$ .

$$f_1 = \frac{1}{2\pi[(R_s + r_{bb'}) // r_\pi][C_{b'e} + (1 + g_m R_L)C_{cb'}]}$$
$$\cong \frac{1}{2\pi[(R_s + r_{bb'})][C_{b'e} + (1 + g_m R_L)C_{cb'}]}$$
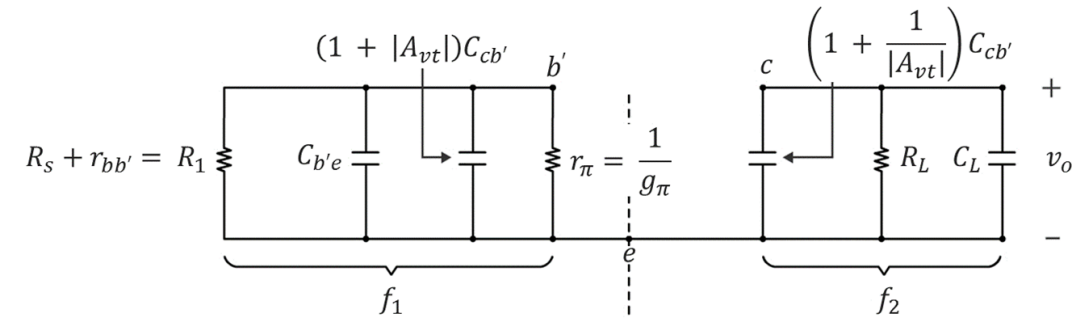
$$f_2 = \frac{1}{2\pi R_L \left[ \left(1 + \frac{1}{g_m R_L}\right) C_{cb'} + C_L \right]}$$
$$\cong \frac{1}{2\pi R_L (C_{cb'} + C_L)}$$


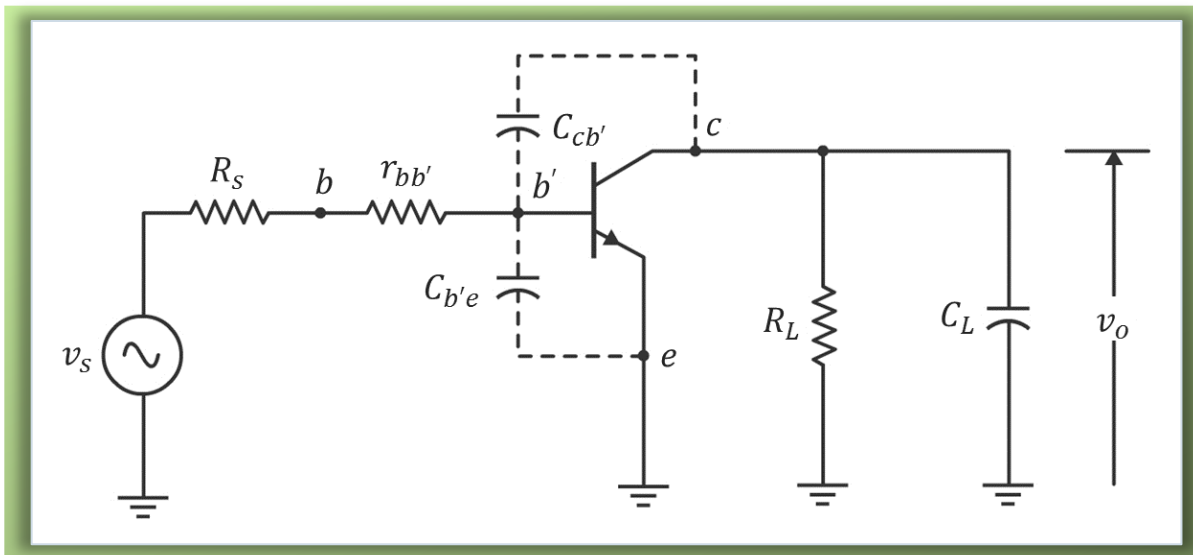
# Limitation of CE Stage for Wideband Application




$$|A_{v(MID)}| = g_m R_L$$

$$f_1 = \frac{1}{2\pi(R_s + r_{bb'})C_i}$$




$$\text{Where, } C_i = C_{b'e} + (1 + |A_{v(MID)}|)C_{cb'}$$
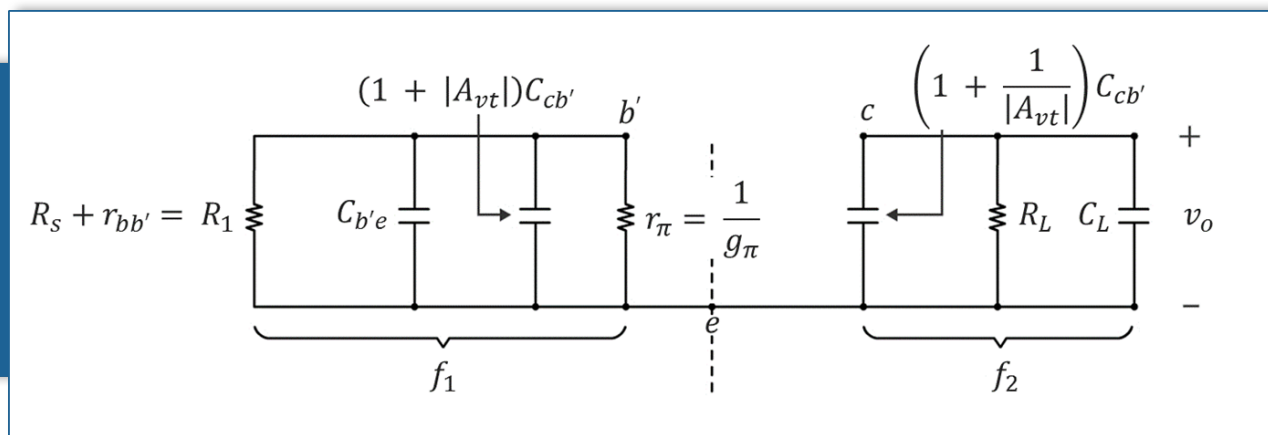
$$f_2 = \frac{1}{2\pi R_L(C_{cb'} + C_L)}$$



The BW is determined by  $f_1$  and  $C_i$  is large due to **Miller effect**. Hence, CE amplifier alone is not suitable for wideband application.

# BJT Models

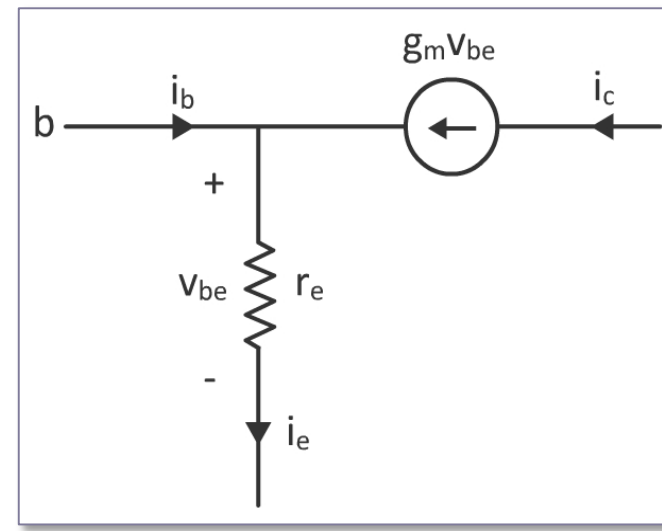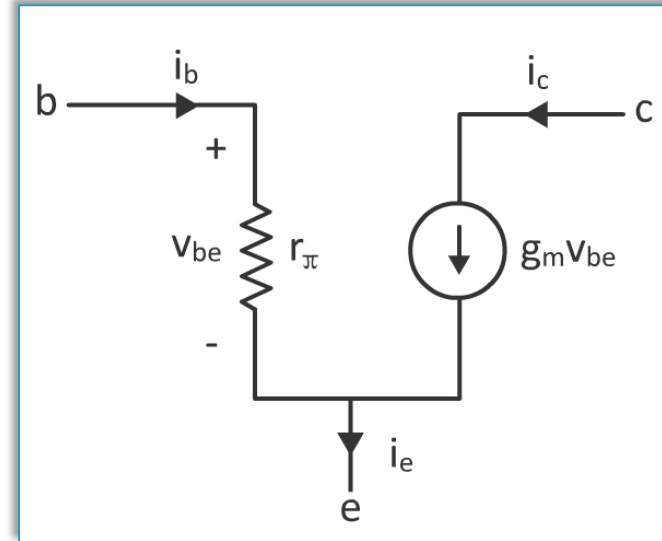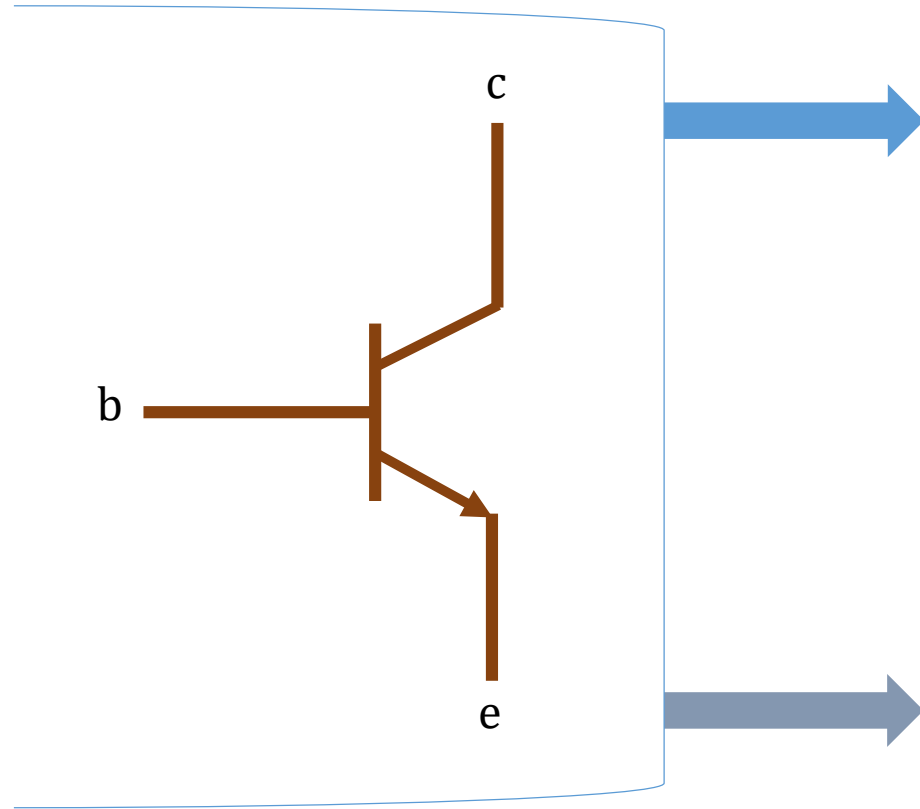

$$r_\pi = \frac{V_T}{I_B}$$

$$i_c = g_m v_{be}$$

$$v_{be} = i_b r_\pi$$

$$i_e = i_b + i_c$$

$$r_e = \frac{r_\pi}{(\beta+1)} \approx \frac{r_\pi}{g_m r_\pi} = \frac{1}{g_m}$$

$$r_e = \frac{V_T}{I_E}$$

$$v_{be} = i_e r_e = i_b (\beta + 1) r_e$$

$$r_\pi = (\beta + 1) r_e$$


$$i_e = i_b + i_c$$

# CE-CB Configuration (Cascode Amplifier)


The term **cascode** means cascading triode (it has been used since 1939).

$$r_e = \frac{(r_\pi + r_{bb'})}{(\beta + 1)} \approx \frac{r_\pi}{(\beta + 1)} \because r_\pi \gg r_{bb'}$$
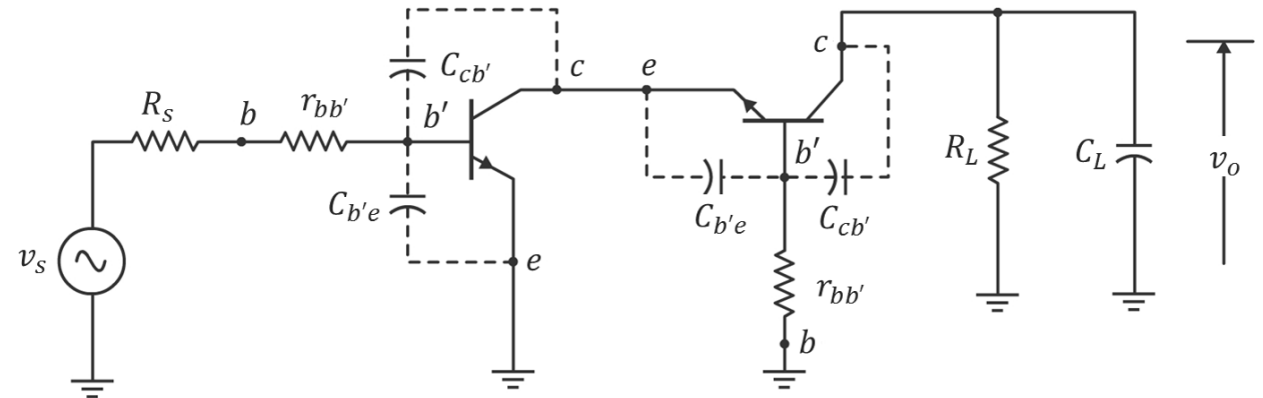
$$\approx \frac{r_\pi}{\beta} = \frac{r_\pi}{g_m r_\pi} = \frac{1}{g_m}$$



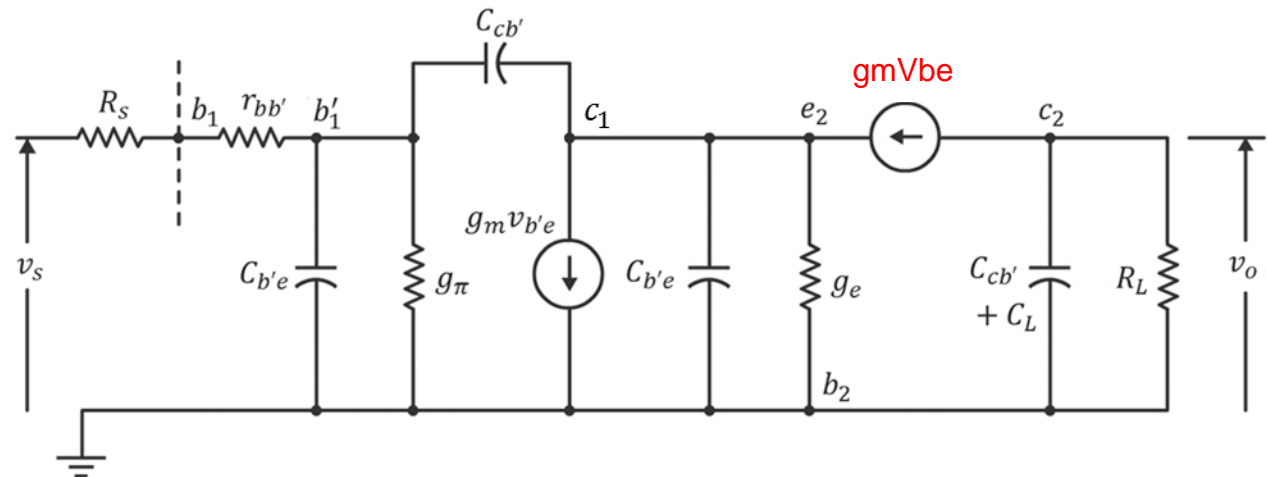For CB amplifier, the effect of  $r_{bb'}$  can be neglected.



# CE-CB Configuration (Cascode Amplifier)

$$Y_{L(CE)} \approx g_e + j\omega(C_{b'e} + C_{cb'})$$


$$= \frac{I_Q}{V_T} + j\omega(C_{b'e} + C_{cb'})$$

Where,  $g_e = \frac{1}{r_{e2}} = \frac{I_{E2}}{V_T}$ ,  $I_Q = I_{E2} = I_{C1}$ ,  $g_e = g_m$

$$Y_{L(CE)} = g_m + j\omega(C_{b'e} + C_{cb'}) = g_m \left[ 1 + \frac{j\omega(C_{b'e} + C_{cb'})}{g_m} \right] = g_m \left( 1 + \frac{j\omega}{\omega_T} \right)$$

$$Y_{L(CE)} = g_m \left( 1 + \frac{jf}{f_T} \right) \text{ For } f \ll f_T, Y_{L(CE)} \approx g_m$$

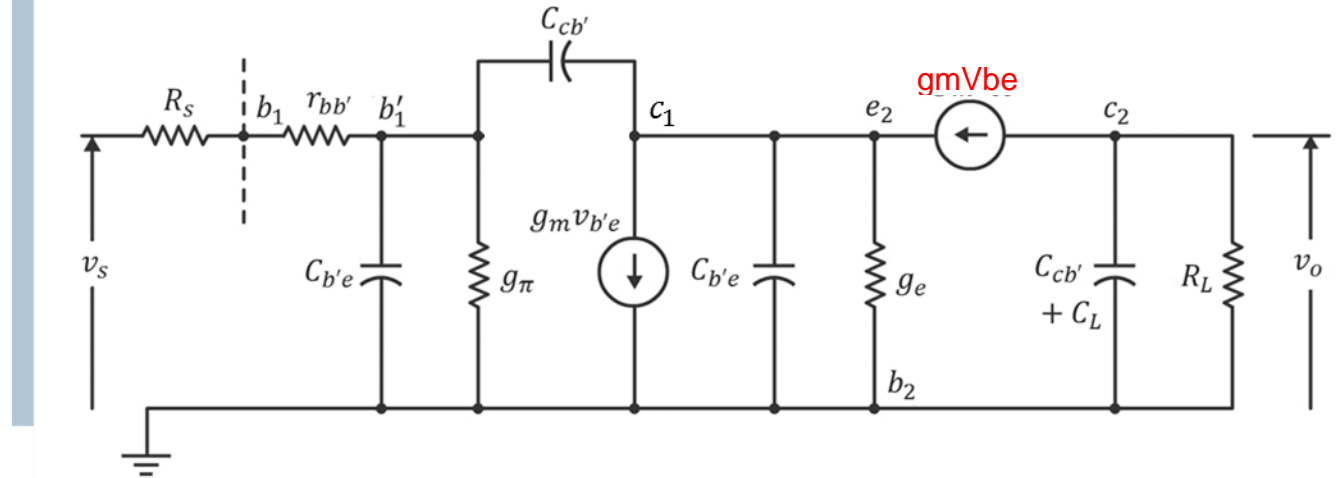The voltage gain for CE stage is:  $A_{v(CE)} = -g_m \left( \frac{1}{Y_{L(CE)}} \right) = -\frac{g_m}{g_m} = -1$



# CE-CB Configuration (Cascode Amplifier)

$$\omega_1 = \frac{1}{(R_S + r_{bb'})[C_{b'e} + C_{cb'}(1 + |A_{v(CE)}|)]}$$

$$= \frac{1}{(R_S + r_{bb'})(C_{b'e} + 2C_{cb'})}$$

$$\because C_{b'e} \gg C_{cb'}$$


$$\therefore C_{b'e} + 2C_{cb'} \approx C_{b'e} + C_{cb'} \approx \frac{g_m}{\omega_T}$$

$$\omega_1 = \frac{\omega_T}{g_m(R_S + r_{bb'})} \Rightarrow f_1 = \frac{f_T}{g_m(R_S + r_{bb'})}$$

**Note:** Now,  $f_1$  is independent of  $R_L$ .

The second break frequency  $\omega_2$  is: 
$$\omega_2 = \frac{g_e}{C_{b'e} + C_{cb'} \left(1 + \frac{1}{|A_{v(CE)}|}\right)} \approx \frac{g_m}{C_{b'e} + 2C_{cb'}} \approx \omega_T \Rightarrow f_2 \approx f_T$$

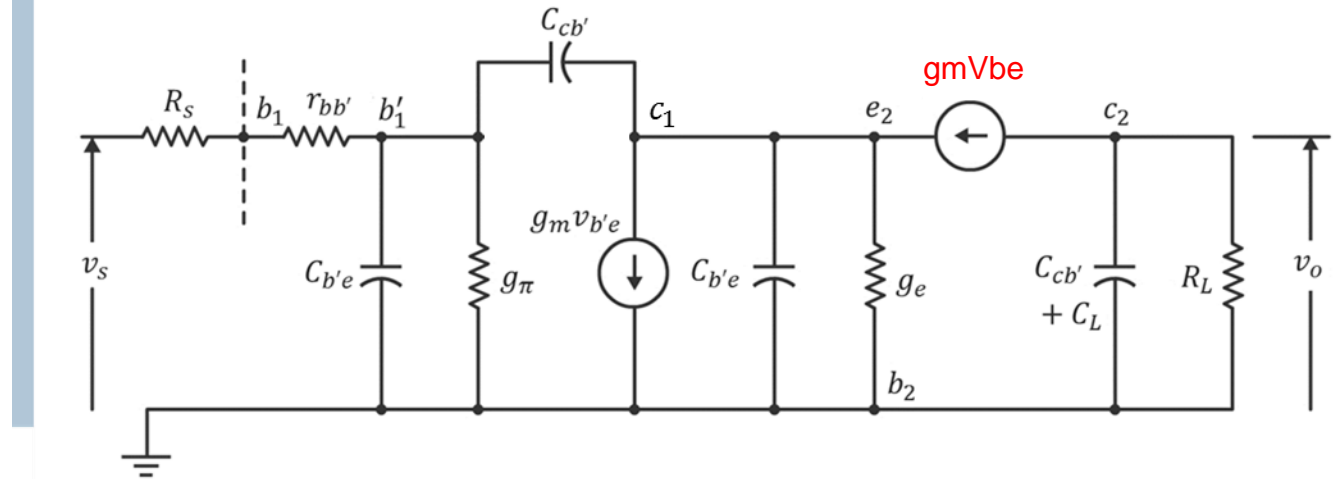$\omega_2$  will not have any significant effect in finding the overall BW.



# CE-CB Configuration (Cascode Amplifier)


The third break frequency  $\omega_3$  is:

$$\omega_3 = \frac{1}{R_L(C_{cb'} + C_L)} \Rightarrow f_3 = \frac{1}{2\pi R_L(C_{cb'} + C_L)}$$


$$A_{v(CB)} = \frac{\alpha R_L}{r_e} \approx g_m R_L \quad \textbf{Note: } \alpha \approx 1 \text{ and } r_e \approx \frac{1}{g_m}$$

The overall mid-band gain:
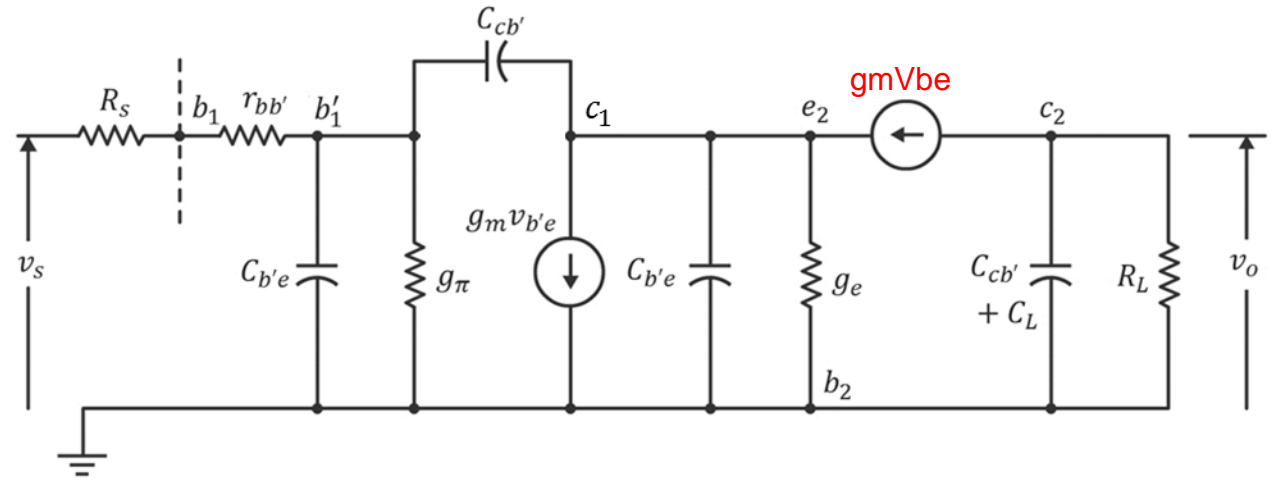
$$A_{V(MID)} = A_{v(CE)} A_{v(CB)} = (-1)(g_m R_L) = -g_m R_L$$


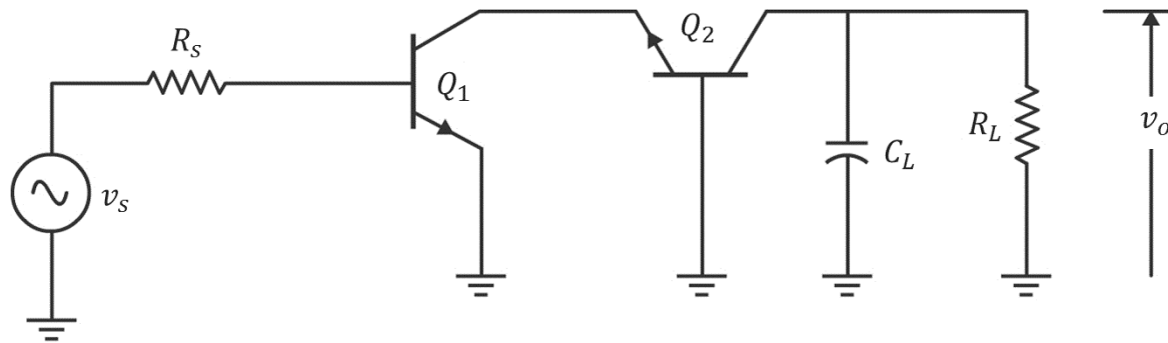
# CE-CB Configuration (Cascode Amplifier): Example



Two identical transistors  $Q_1$  and  $Q_2$  are configured as a Cascode Amplifier (CE-CB):

The BJT device parameters are:

$$r_{bb'} = 60 \, \Omega$$

$$R_s = 40 \, \Omega$$

$$C_{cb'} = 1.5 \, \text{pF}$$

$$f_T = 1.6 \, \text{GHz}$$


$$\text{Load capacitance: } C_L = 1 \, \text{pF}$$

The BJT is biased at 2.5 mA.

Determine the overall voltage gain frequency response for different values of  $R_L$  varying from 30  $\Omega$  to 10 k $\Omega$ .


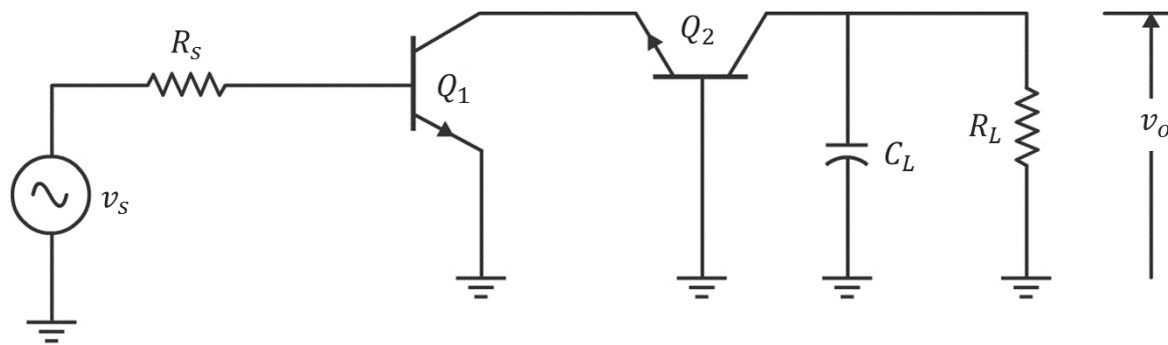
# CE-CB Configuration (Cascode Amplifier): Example



$$A_{v(MID)} = -g_m R_L = -0.096 R_L$$

$$f_1 = \frac{f_T}{g_m(R_s + r_{bb'})} = \frac{1.6 \times 10^9}{0.096(100)} \approx 160 \text{ MHz}$$

$$f_2 \approx f_T \approx 1.6 \text{ GHz}$$

$$f_3 = \frac{1}{2\pi R_L(C_{cb'} + C_L)} = \frac{1}{2\pi R_L(2.5 \times 10^{-12})}$$

# CE-CB Configuration (Cascode Amplifier): Example

From the calculations, we have:

| $R_L (\Omega)$ | $f_1(\text{MHz})$ | $f_2 (\text{MHz})$ | $f_3 (\text{MHz})$ | $BW(\text{MHz})$ | $A_{V(\text{MID})}$ | $A_{V(\text{MID})} \times BW(\text{MHz})$ |
|----------------|-------------------|--------------------|--------------------|------------------|---------------------|---|
| 30             | 160               | 1,600              | 2,122              | 160              | 3                   | 480                                       |
| 100            | 160               | 1,600              | 637                | 160              | 10                  | 1,600                                     |
| 300            | 160               | 1,600              | 212                | 128              | 30                  | 3,831                                     |
| 1,000          | 160               | 1,600              | 64                 | 59               | 100                 | 5,900                                     |
| 3,000          | 160               | 1,600              | 21                 | 21               | 300                 | 6,305                                     |
| 10,000         | 160               | 1,600              | 6.4                | 6.4              | 1,000               | 6,400                                     |

# CE and Cascode Comparison

| $R_L (\Omega)$ | $f_1$ (MHz) | $f_2$ (MHz) | $BW$ (MHz) | $A_{V(MID)}$ | $A_{V(MID)} \times BW$ (MHz) | CE Stage |
|----------------|-------------|-------------|------------|--------------|------------------------------|----------|
| 30             | 110         | 2,122       | 110        | 3            | 330                          |          |
| 100            | 64          | 637         | 64         | 10           | 640                          |          |
| 300            | 29          | 212         | 28         | 30           | 868                          |          |
| 1,000          | 10          | 64          | 10         | 100          | 1,000                        |          |
| 3,000          | 3.5         | 21          | 3.5        | 300          | 1,038                        |          |
| 10,000         | 1.05        | 6.4         | 1.04       | 1,000        | 1,040                        |          |

| $R_L (\Omega)$ | $f_1$ (MHz) | $f_2$ (MHz) | $f_3$ (MHz) | $BW$ (MHz) | $A_{V(MID)}$ | $A_{V(MID)} \times BW$ (MHz) |
|----------------|-------------|-------------|-------------|------------|--------------|------------------------------|
| 30             | 160         | 1,600       | 2,122       | 160        | 3            | 480                          |
| 100            | 160         | 1,600       | 637         | 160        | 10           | 1,600                        |
| 300            | 160         | 1,600       | 212         | 128        | 30           | 3,831                        |
| 1,000          | 160         | 1,600       | 64          | 59         | 100          | 5,900                        |
| 3,000          | 160         | 1,600       | 21          | 21         | 300          | 6,305                        |
| 10,000         | 160         | 1,600       | 6.4         | 6.4        | 1,000        | 6,400                        |

For  $R_L = 1\text{ k}\Omega$  , mid-band gain is 100 in both the cases but  $BW = 10\text{ MHz}$  for CE and  $BW \approx 60\text{ MHz}$  for the cascode stage which is nearly six times wider in BW.

# Wideband Amplifiers

## Topic 2: Amplifier Feedback Analysis


### EE4341: Advanced Analog Circuits

A/P Zheng Yuanjin

School of Electrical and Electronic Engineering

Email: [YJZHENG@ntu.edu.sg](mailto:YJZHENG@ntu.edu.sg)

# Applying Feedback to Broaden BW

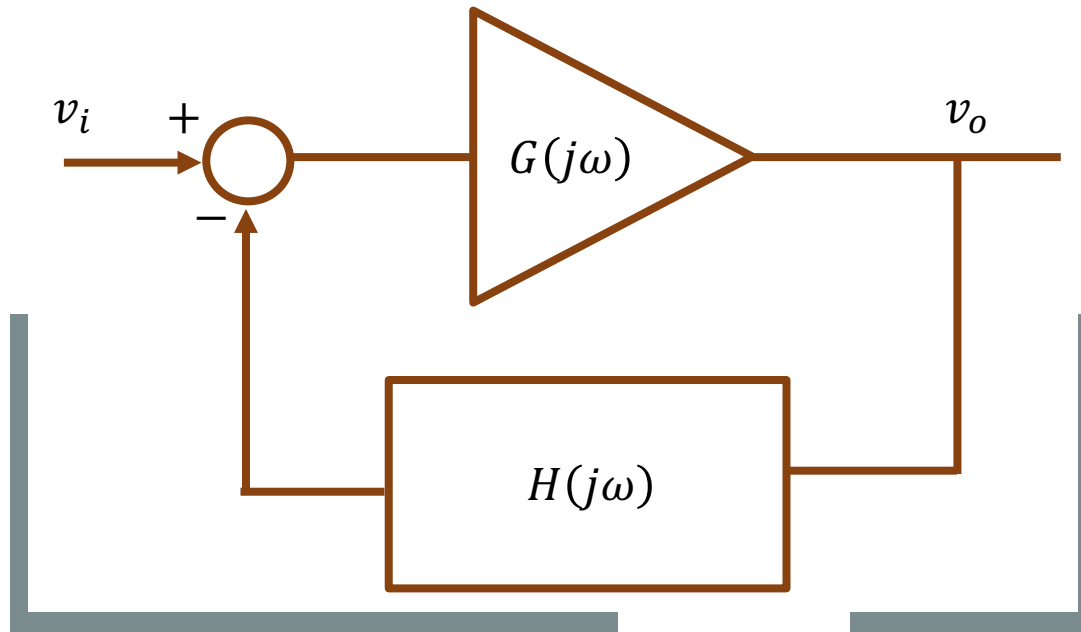


$$G(j\omega) = \frac{A_o}{1 + j\omega/\omega_o}$$

$$A_v(j\omega) = \frac{G(j\omega)}{1 + G(j\omega)H(j\omega)}$$

As the bandwidth of a transistor is restricted by its device parameters, negative feedback technique can be employed to broaden the amplifier's bandwidth. It would be at the expense of lower gain.

# Applying Feedback to Broaden BW

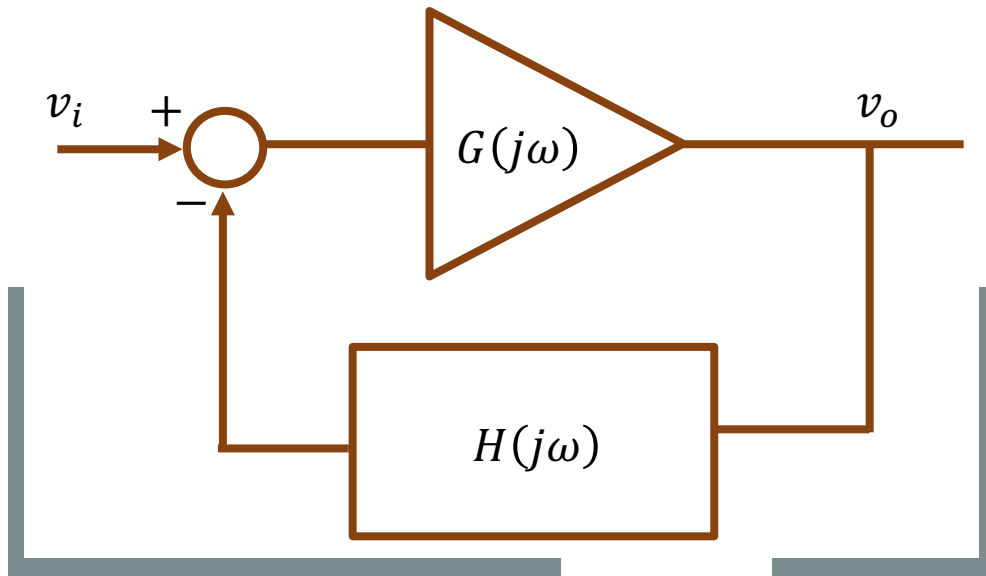

$G(j\omega)$  is the voltage transfer function of the amplifier and  $H(j\omega)$  is the negative feedback network.




If  $H(j\omega)$  is frequency-independent in the frequency of interest that is  $H(j\omega) = H$ .

$$A_v(j\omega) = \frac{G(j\omega)}{1 + G(j\omega)H}$$

$$A_v(j\omega) = \frac{\frac{A_o}{1 + j\omega/\omega_o}}{1 + \frac{A_o H}{1 + j\omega/\omega_o}} = \frac{A_o}{1 + j\omega/\omega_o + A_o H}$$

$$= \frac{A_o}{1 + A_o H} \left( \frac{1}{1 + \frac{j\omega}{\omega_o(1 + A_o H)}} \right) = \frac{A_o}{1 + A_o H} \left( \frac{1}{1 + j\omega/\omega_L} \right)$$

# Applying Feedback to Broaden BW

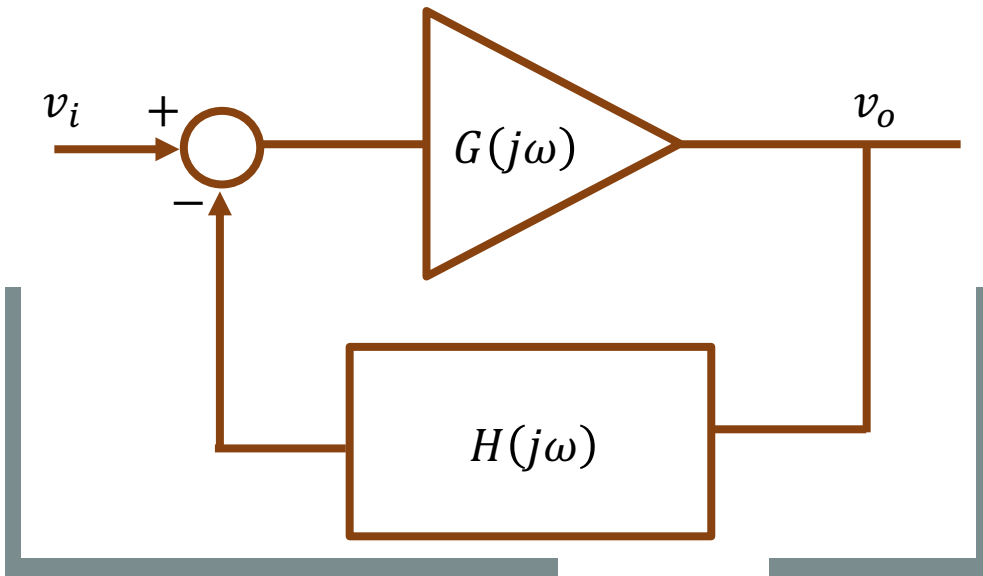

$$A_v(j\omega) = \frac{A_o}{1 + A_o H} \left( \frac{1}{1 + \frac{j\omega}{\omega_o(1 + A_o H)}} \right) = A_{v(MID)} \left( \frac{1}{1 + j\omega/\omega_L} \right)$$

The mid-band gain of the amplifier with feedback is:

$$A_{v(MID)} = \frac{A_o}{1 + A_o H} \quad \because A_o H \gg 1 \quad \therefore A_{v(MID)} \approx \frac{1}{H}$$

$\therefore$  The mid-band gain is controlled by the feedback network.

Now, the bandwidth of the amplifier with feedback has been broadened by a factor of  $(1 + A_o H)$ :

$$\omega_L = \omega_o(1 + A_o H)$$

# Summary of Feedback Configurations

| Feedback Configuration | Input   | Output  | Transfer Function          |
|------------------------|---------|---------|----------------------------|
| Shunt-Shunt            | Current | Voltage | Transresistance Amplifier  |
| Shunt-Series           | Current | Current | Current Amplifier          |
| Series-Shunt           | Voltage | Voltage | Voltage Amplifier          |
| Series-Series          | Voltage | Current | Transconductance Amplifier |

To sample the output voltage, measure the voltage with a voltmeter. Hence, voltage sampling at output is a 'shunt' connection.

To sample the output current, measure the current with an amp-meter. Hence, current sampling at output is a 'series' connection.

To feedback a voltage at the input, it needs to be in 'series' with the voltage signal source (think of the Thevenin equivalent model).

To feedback a current at the input, it needs to be in 'shunt' with the current signal source (think of the Norton equivalent model).



# Feedback Configuration


$$i_{out} = -i_c \approx -i_e$$

$$v_{in} = v_{be} + i_e R_E$$

$$\approx -i_{out}(r_e + R_E) \approx -i_{out}R_E$$

$$\because R_E \gg r_e$$
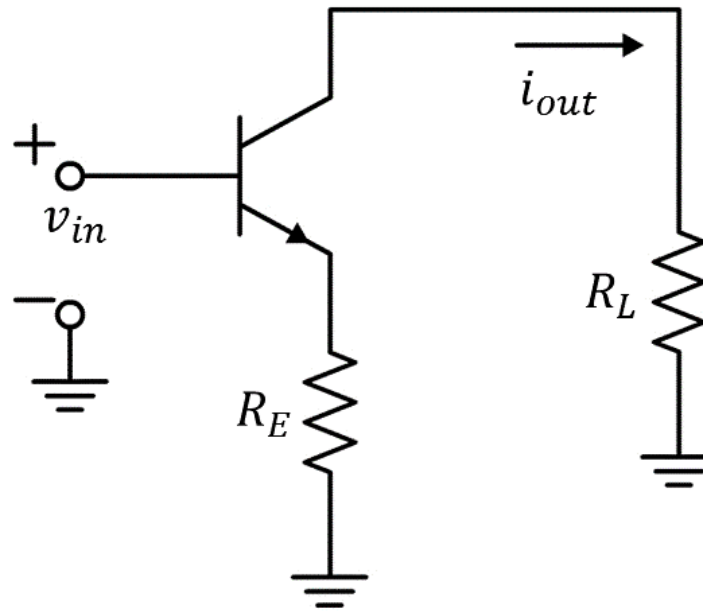
$$\therefore \frac{i_{out}}{v_{in}} = -\frac{1}{R_E}$$




$R_E$  samples output current in 'series' and feedback a signal voltage in 'series' with the input voltage.

It is a trans-conductance amplifier with a gain of  $-1/R_E$ .

# Feedback Configuration

$$\begin{aligned}v_{out} &= v_{be} - (i_{in} - i_b)R_F \\&= i_b r_\pi - i_{in}R_F + i_b R_F \\&= i_b(r_\pi + R_F) - i_{in}R_F \\&\because i_{in} \gg i_b, \therefore v_{out} \approx -i_{in}R_F\end{aligned}$$


$$\frac{v_{out}}{i_{in}} = -R_F$$

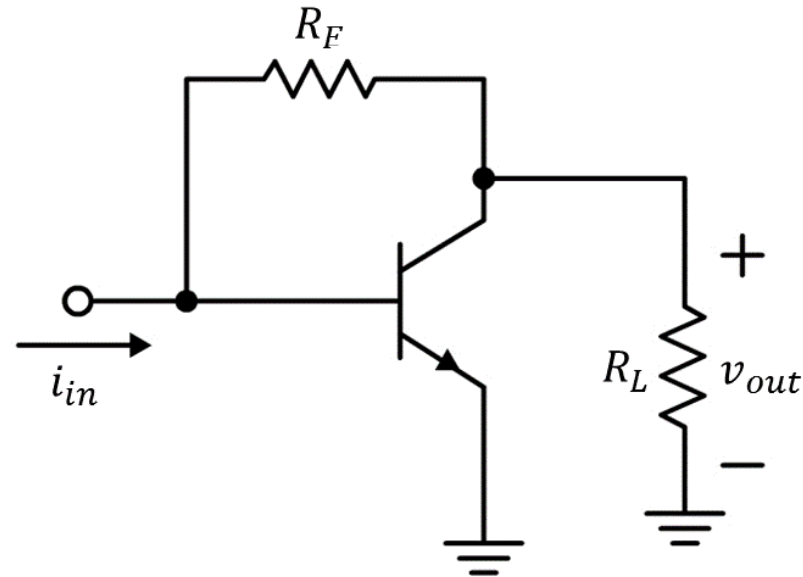

$R_F$  samples output voltage in 'shunt' and feedback a signal current in 'shunt' with the input current.

It is a trans-impedance amplifier with a gain of  $-R_F$ .

# Feedback Configuration

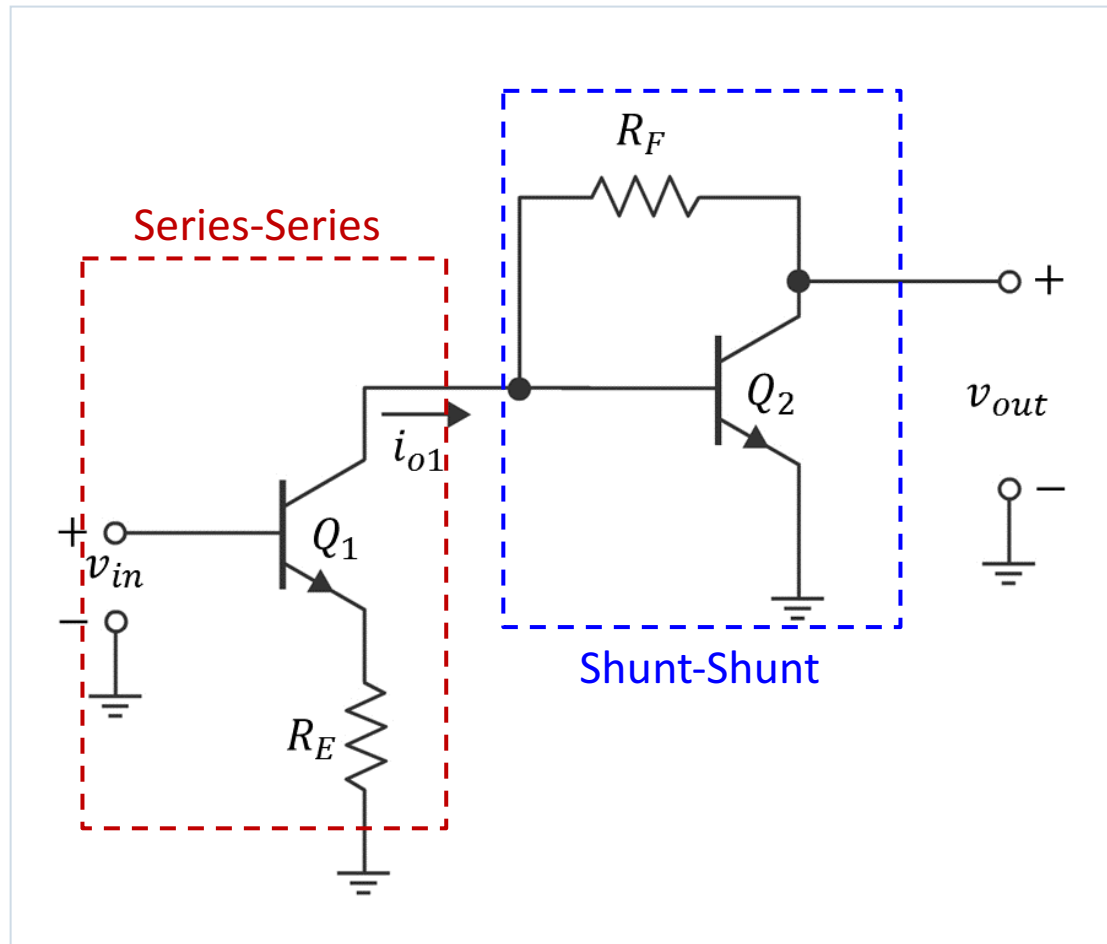


It is a voltage amplifier with series-shunt feedback configuration.

$$\frac{v_{out}}{v_{in}} = \left(-\frac{1}{R_E}\right)(-R_F) = \frac{R_F}{R_E}$$

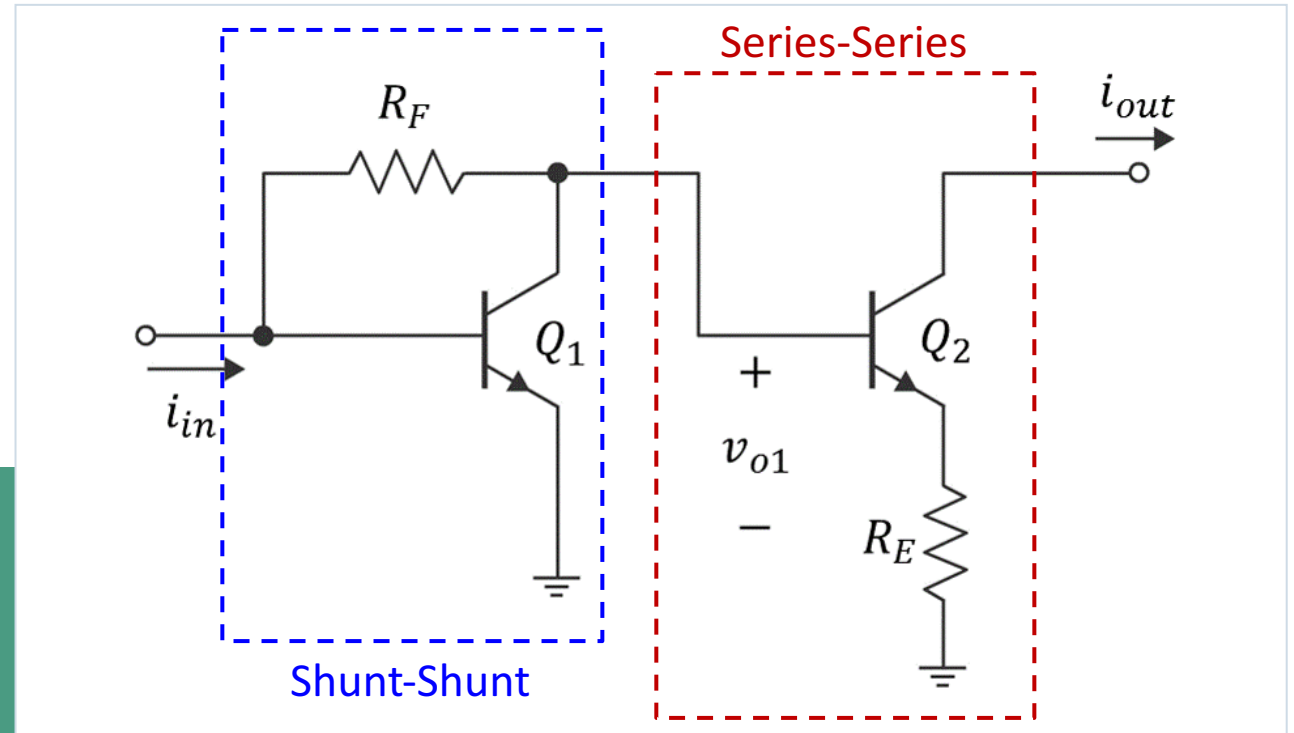
# Feedback Configuration

It is a current amplifier with shunt-series feedback configuration.

$$\frac{i_{out}}{i_{in}} = (-R_F) \left( -\frac{1}{R_E} \right) = \frac{R_F}{R_E}$$




# Differential Video Amplifier

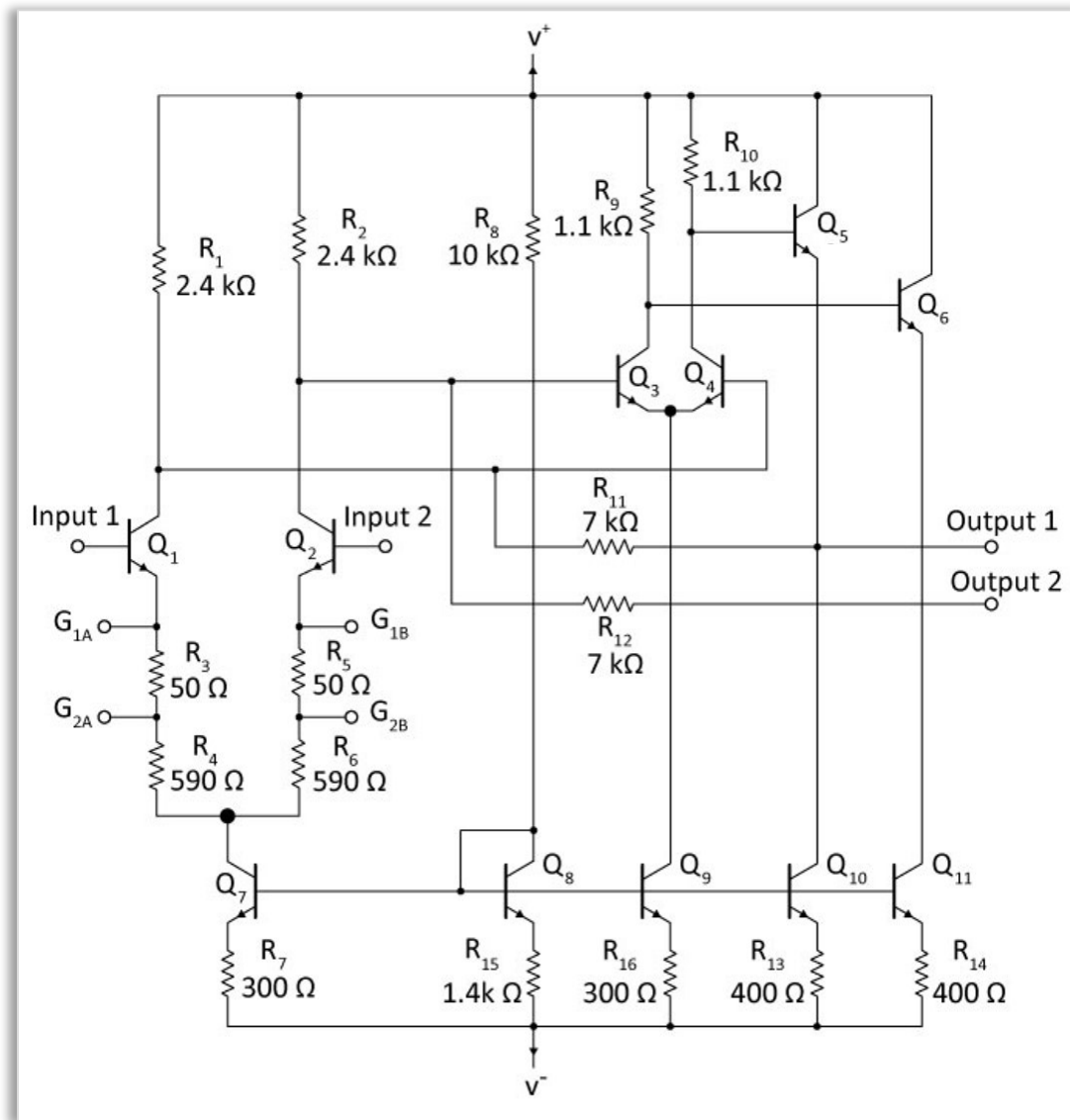

Circuit diagram of  $\mu A 733$  wideband differential video amplifier that uses the series-shunt cascade feedback topology.

The circuit has a good CMRR (Common-mode Rejection Ratio).


# Differential Video Amplifier

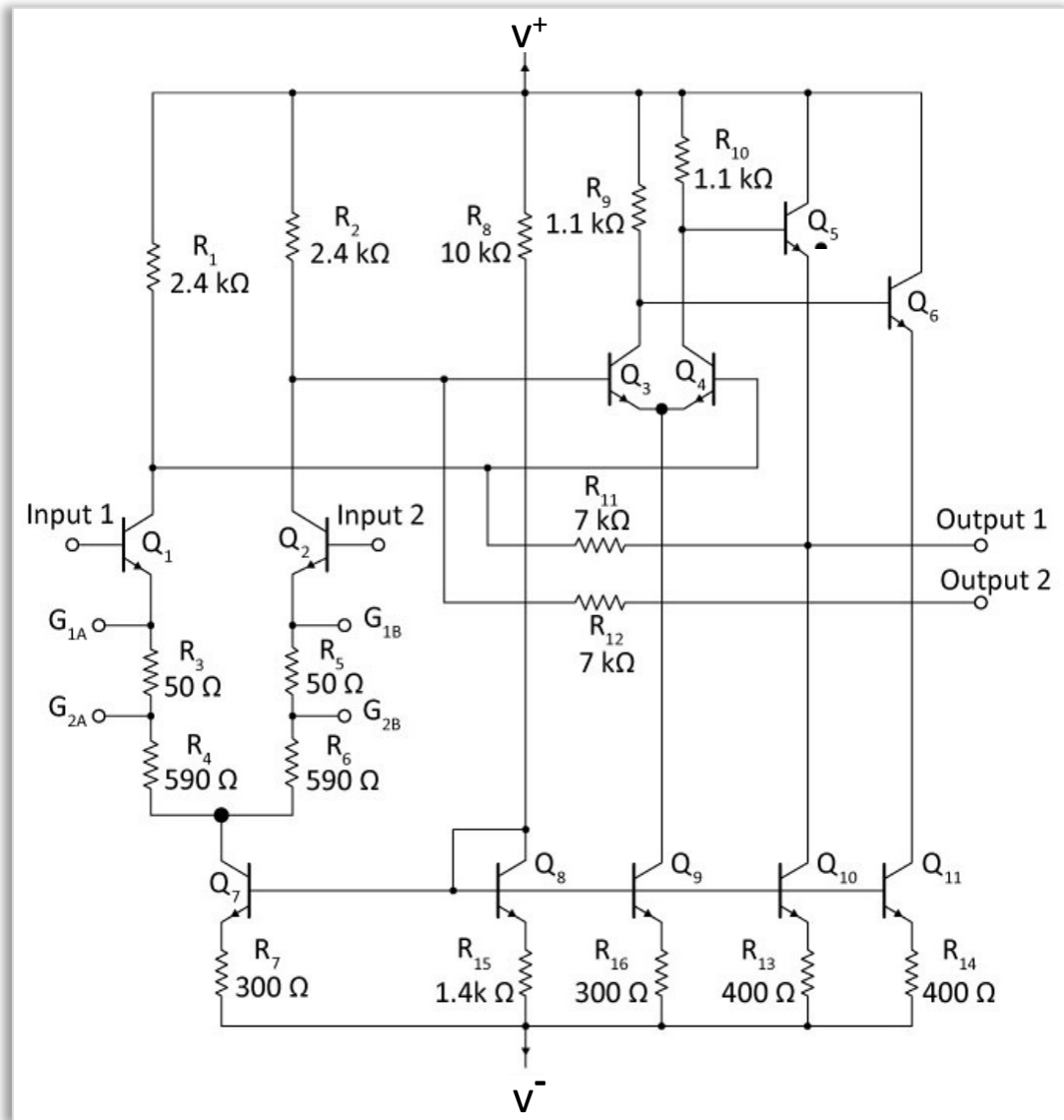

Series-shunt feedback

Current mirrors for DC biasing

# DC Biasing Analysis

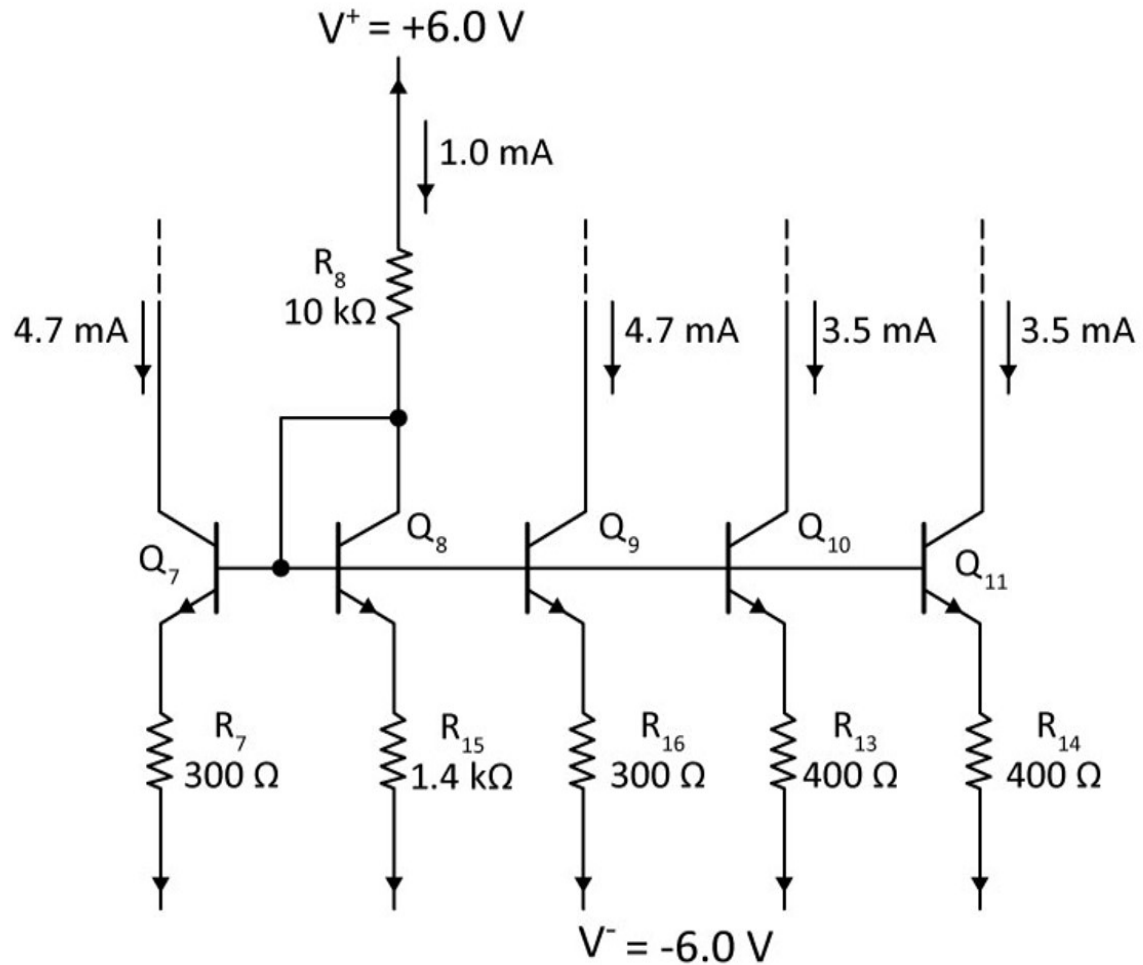

$$I_{C8} = \frac{(V^+ - V^-) - V_{BE8}}{R_8 + R_{15}}$$

$$= \frac{12 - 0.6}{(10 + 1.4) \times 10^3}$$

$$= 1\text{ mA}$$

$$V_{R15} = 1\text{ mA} \times 1.4\text{ k}\Omega = 1.4\text{ V}$$

$$I_{C7} = I_{C9} = \frac{1.4\text{ V}}{300\ \Omega} = 4.7\text{ mA}$$

$$I_{C10} = I_{C11} = \frac{1.4\text{ V}}{400\ \Omega} = 3.5\text{ mA}$$

# Voltage Gain Analysis


$$g_{f1} = \frac{i_{c1}}{v_{b1}} = \frac{i_{c1}}{i_{e1}(r_{e1} + R_E)} \approx \frac{i_{c1}}{i_{c1}(r_{e1} + R_E)} = \frac{1}{r_{e1} + R_E}$$

$$r_{e1} \approx \frac{V_T}{I_{C1}}$$

$$i_{c1} = g_{f1} v_{b1} = \frac{g_{f1} v_{in}}{2}$$

The voltage gain for second stage ( $Q_3$  or  $Q_4$ ) is:
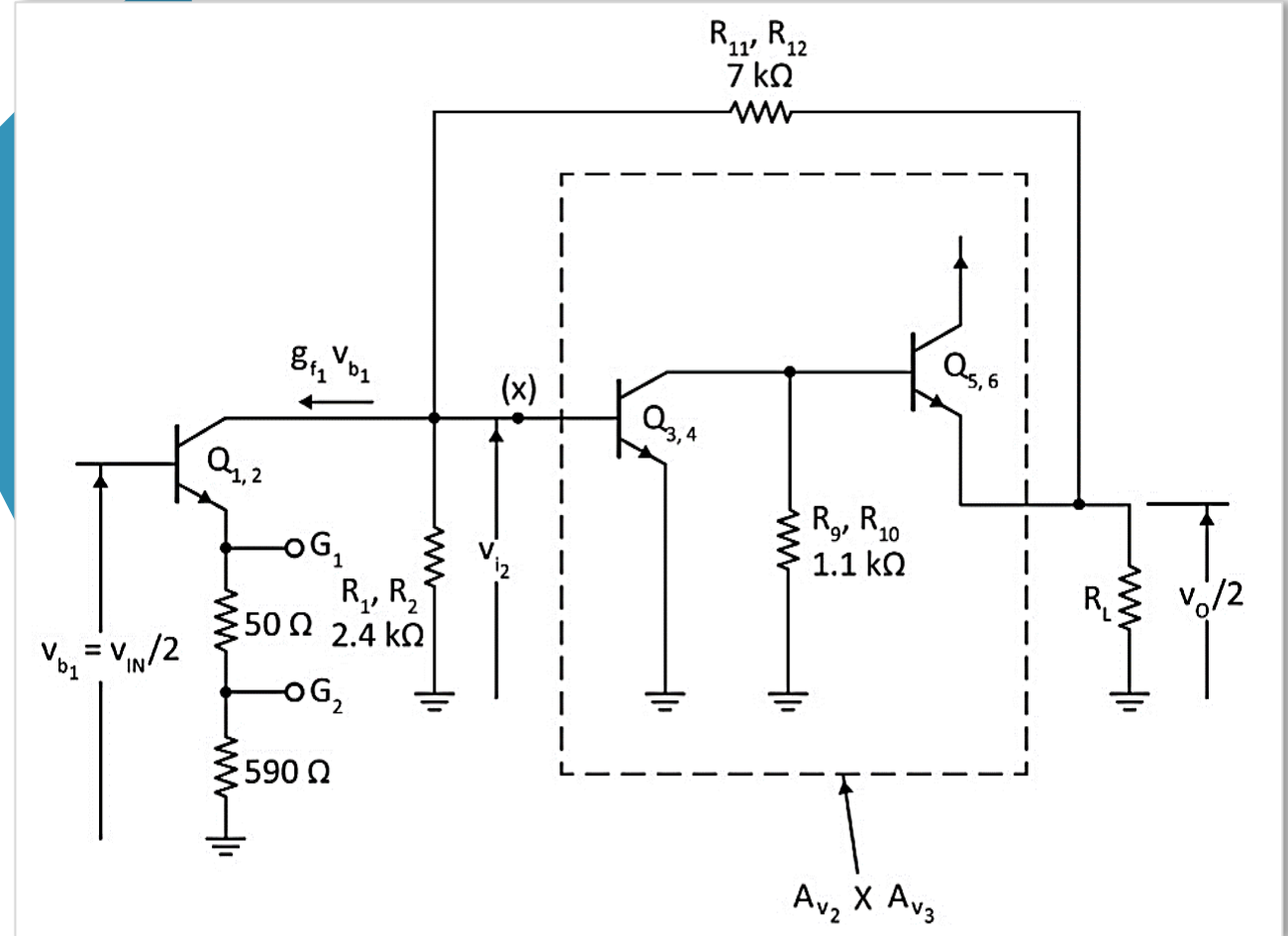
$$\begin{aligned} A_{v2} &= \frac{v_{c3}}{v_{i2}} = -\frac{g_{f3} v_{i2} R_9}{v_{i2}} = -\left(\frac{I_{C3}}{V_T}\right) R_9 \\ &= -\frac{4.7 \text{ mA}/2}{26 \text{ mV}} \times 1.1 \text{ k}\Omega = -103 \end{aligned}$$





# Voltage Gain Analysis

The voltage gain for third stage ( $Q_5$  or  $Q_6$ ) is:

$$A_{v3} = \frac{v_o/2}{v_{c3}} = \frac{i_{e5}R_L}{i_{e5}(R_L + r_{e5})} = \frac{R_L}{R_L + r_{e5}} \approx 1$$


$$\because R_L \gg r_{e5}$$

$$\therefore A_{v2} \times A_{v3} \approx -100$$

Applying KCL at node "x":

$$\frac{g_{f1}v_{in}}{2} + \frac{v_x}{R_1} = \left(\frac{v_o}{2} - v_x\right) \left(\frac{1}{R_{11}}\right) \Rightarrow$$
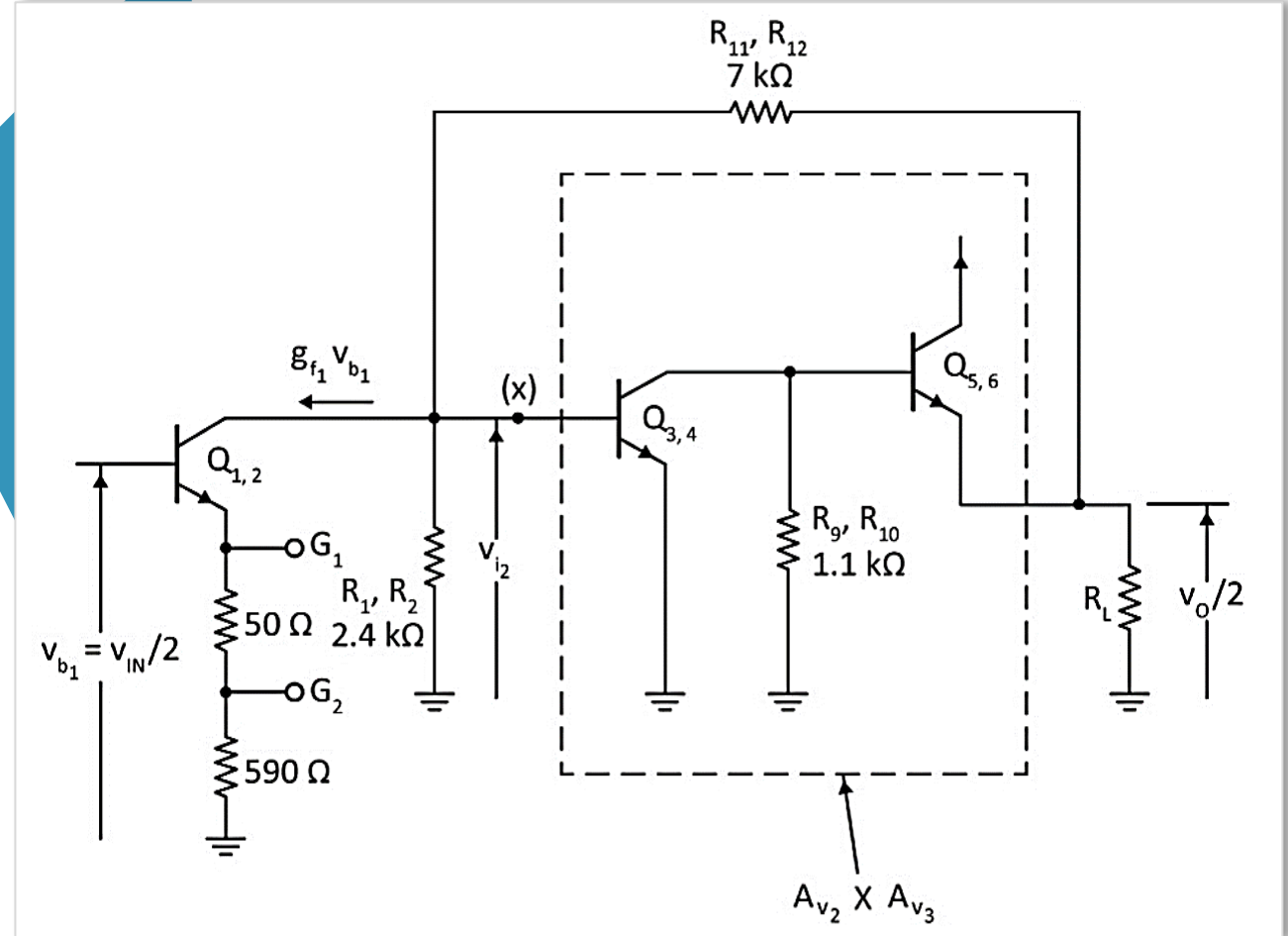
$$\frac{g_{f1}v_{in}}{2} = \frac{v_o}{2R_{11}} - v_x \left(\frac{1}{R_1} + \frac{1}{R_{11}}\right) \text{-----(1)}$$



# Voltage Gain Analysis

Note:  $\frac{v_o}{2} = A_{v2}A_{v3}v_x \Rightarrow v_x = -\frac{v_o}{200}$  --- (2)


Substituting (2) into (1):

$$\frac{g_{f1}v_{in}}{2} = \frac{v_o}{2R_{11}} + \left(\frac{v_o}{200}\right)\left(\frac{1}{R_1} + \frac{1}{R_{11}}\right)$$

$$A_v = \frac{v_o}{v_{in}} = \frac{g_{f1}}{1/R_{11} + (1/100)(1/R_1 + 1/R_{11})}$$

$$= \frac{g_{f1}}{1/7\text{ k} + (1/100)(1/7\text{ k} + 1/2.4\text{ k})} \approx g_{f1}(7\text{ k})$$
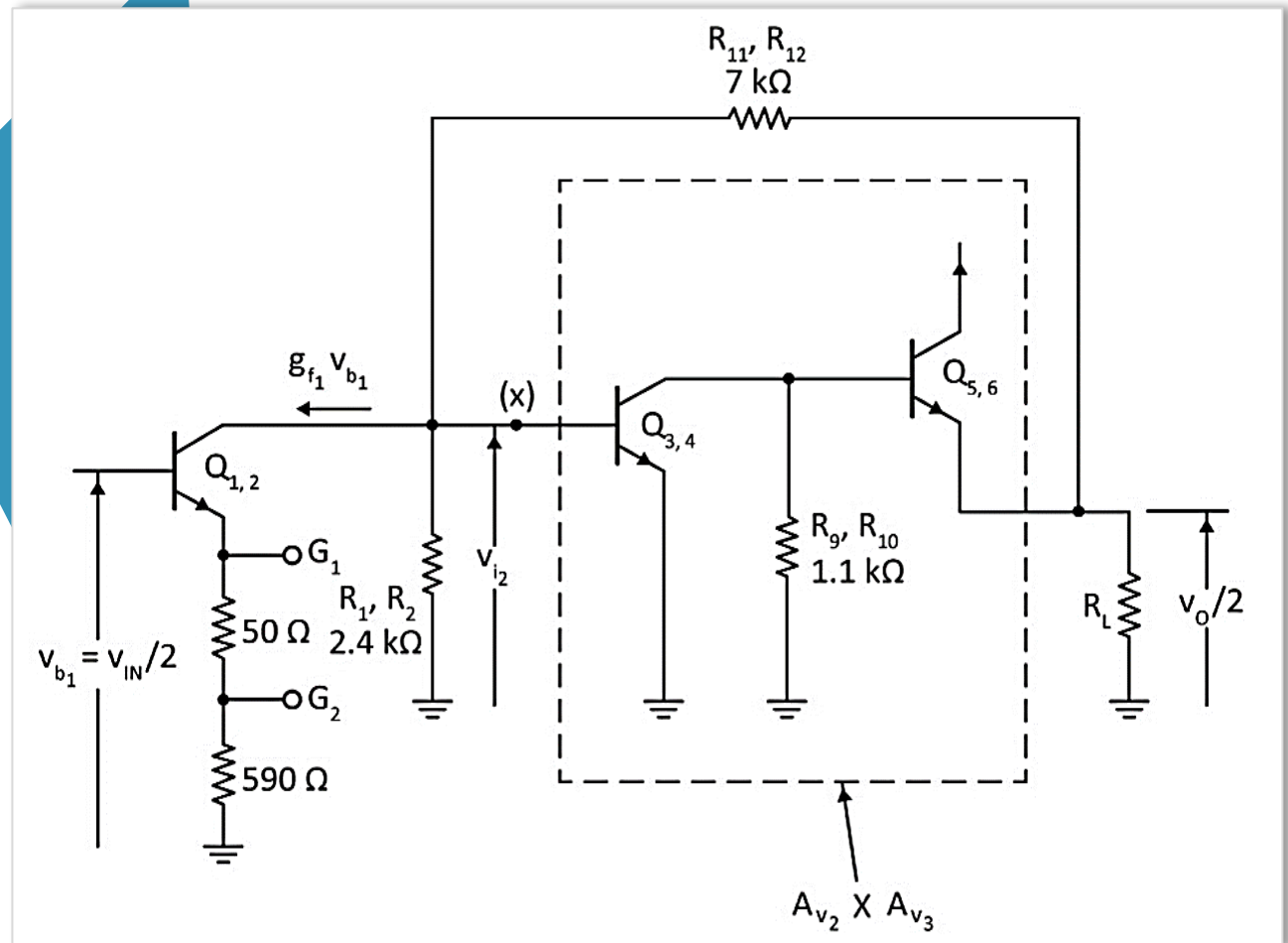
$$A_v = g_{f1}(7\text{ k}) = \frac{7\text{ k}}{r_{e1} + R_E} = \frac{7 \times 10^3}{11 + R_E}$$



# Voltage Gain Analysis

The gain for  $R_E = 0, 50 \Omega$  and  $640 \Omega$  are calculated as follows:

$$R_E = 0: A_v = \frac{7 \times 10^3}{11} = 640$$

$$R_E = 50 \Omega: A_v = \frac{7 \times 10^3}{11 + 50} = 115$$


$$R_E = 640 \Omega: A_v = \frac{7 \times 10^3}{11 + 640} = 10.8$$

The 3 dB bandwidth obtained from the data sheet:

$$R_E = 0: BW = 50 \text{ MHz (Typical)}$$

$$R_E = 50 \Omega: BW = 90 \text{ MHz (Typical)}$$
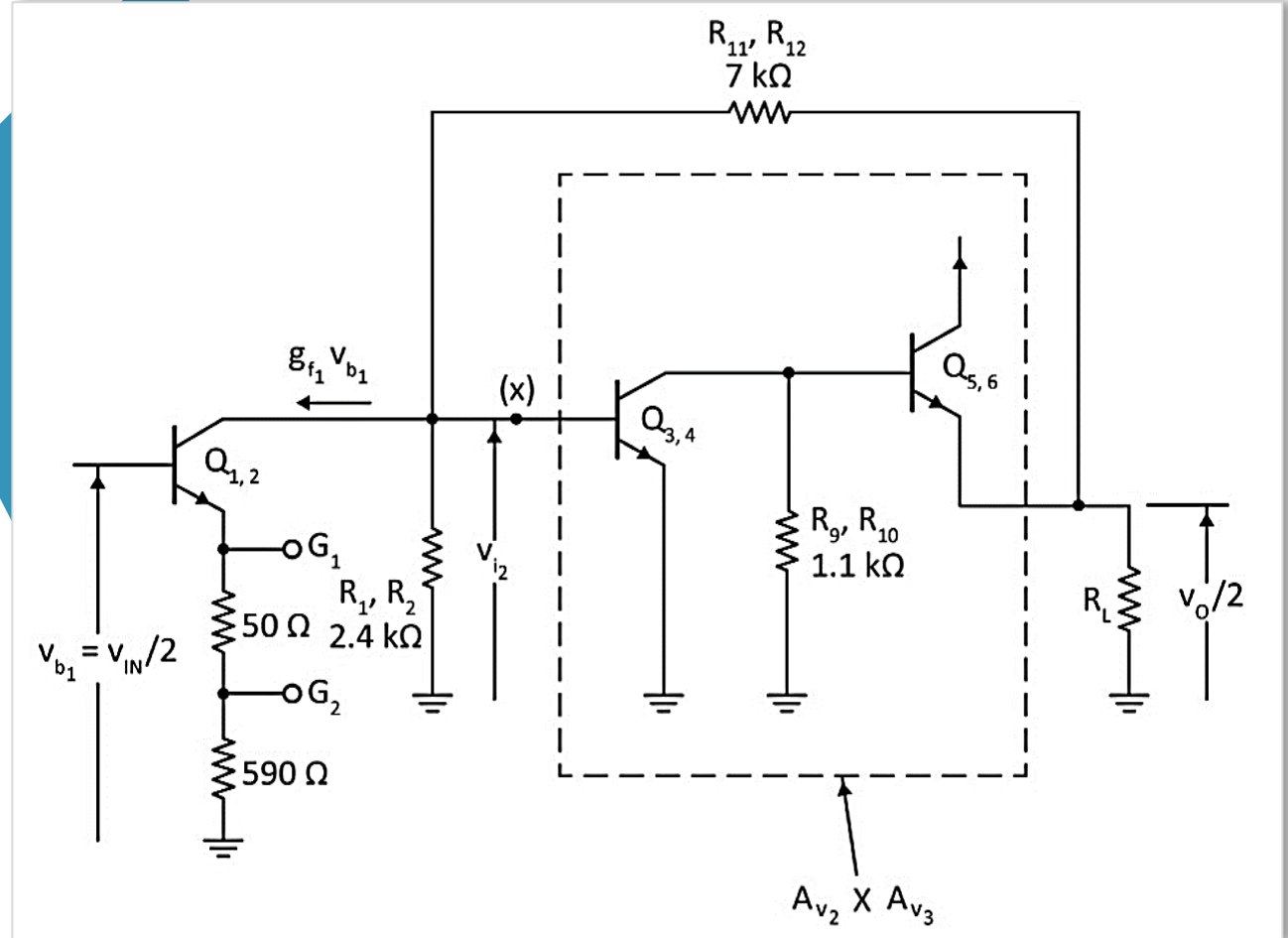
$$R_E = 640 \Omega: BW = 200 \text{ MHz (Typical)}$$



# Cascading Identical Stages

If a large voltage gain is required, it is convenient to cascade several identical amplifier stages.

The voltage transfer function of each stage is:

$$A_v = \frac{A}{1 + j \omega / \omega_p}$$

The overall voltage transfer function of  $n$  stage is:

$$A_T = \frac{A^n}{(1 + j \omega / \omega_p)^n}$$

The overall bandwidth  $\omega_1$  can be found by:

$$|A_T| = \frac{A^n}{|1 + j \omega_1 / \omega_p|^n} = \frac{A^n}{\sqrt{2}} \Rightarrow \left[ 1 + (\omega_1 / \omega_p)^2 \right]^{n/2} = 2^{1/2}$$

$$\therefore \omega_1 = \omega_p (2^{1/n} - 1)^{1/2} \Rightarrow f_1 = f_p \sqrt{2^{1/n} - 1}$$

# Cascading Identical Stages: Example

Three identical amplifiers, each with a voltage gain of 10 and a bandwidth of 10 MHz, are cascaded. What is the overall gain and bandwidth?

The overall voltage gain:

$$A^n = 10^3 = 1,000$$

The overall bandwidth:

$$\begin{aligned} f_1 &= f_p \sqrt{2^{1/n} - 1} \\ &= 10 \times 10^6 \sqrt{2^{1/3} - 1} \\ &= 5.1 \text{ MHz} \end{aligned}$$

# Wideband Amplifiers

## Summary

### EE4341: Advanced Analog Circuits

A/P Zheng Yuanjin

School of Electrical and Electronic Engineering

Email: [YJZHENG@ntu.edu.sg](mailto:YJZHENG@ntu.edu.sg)

# Summary



BJT Frequency Response

Amplifier Frequency Response for CE Amplifiers

CE-CB Amplifier Analysis

Feedback Circuit Analysis for Wideband Amplifiers

Cascaded Integrated Circuit Analysis