

EE4341/EE6341 Advanced Analog Circuits - Power Amplifiers

Dr See Kye Yak

Associate Professor

School of EEE

Last Revised: July 2023

Email: ekysee@ntu.edu.sg

Office: S2-B2C-112


All course materials, including but not limited to, lecture slides, handout and recordings, are for your own educational purposes only. All the contents of the materials are protected by copyright, trademark or other forms of proprietary rights.

All rights, title and interest in the materials are owned by, licensed to or controlled by the University, unless otherwise expressly stated. The materials shall not be uploaded, reproduced, distributed, republished or transmitted in any form or by any means, in whole or in part, without written approval from the University.

You are also not allowed to take any photograph, film, audio record or other means of capturing images or voice of any contents during lecture(s) and/or tutorial(s) and reproduce, distribute and/or transmit any form or by any means, in whole or in part, without the written permission from the University.

Appropriate action(s) will be taken against you including but not limited to disciplinary proceeding and/or legal action if you are found to have committed any of the above or infringed the University's copyright.


Power Amplifier

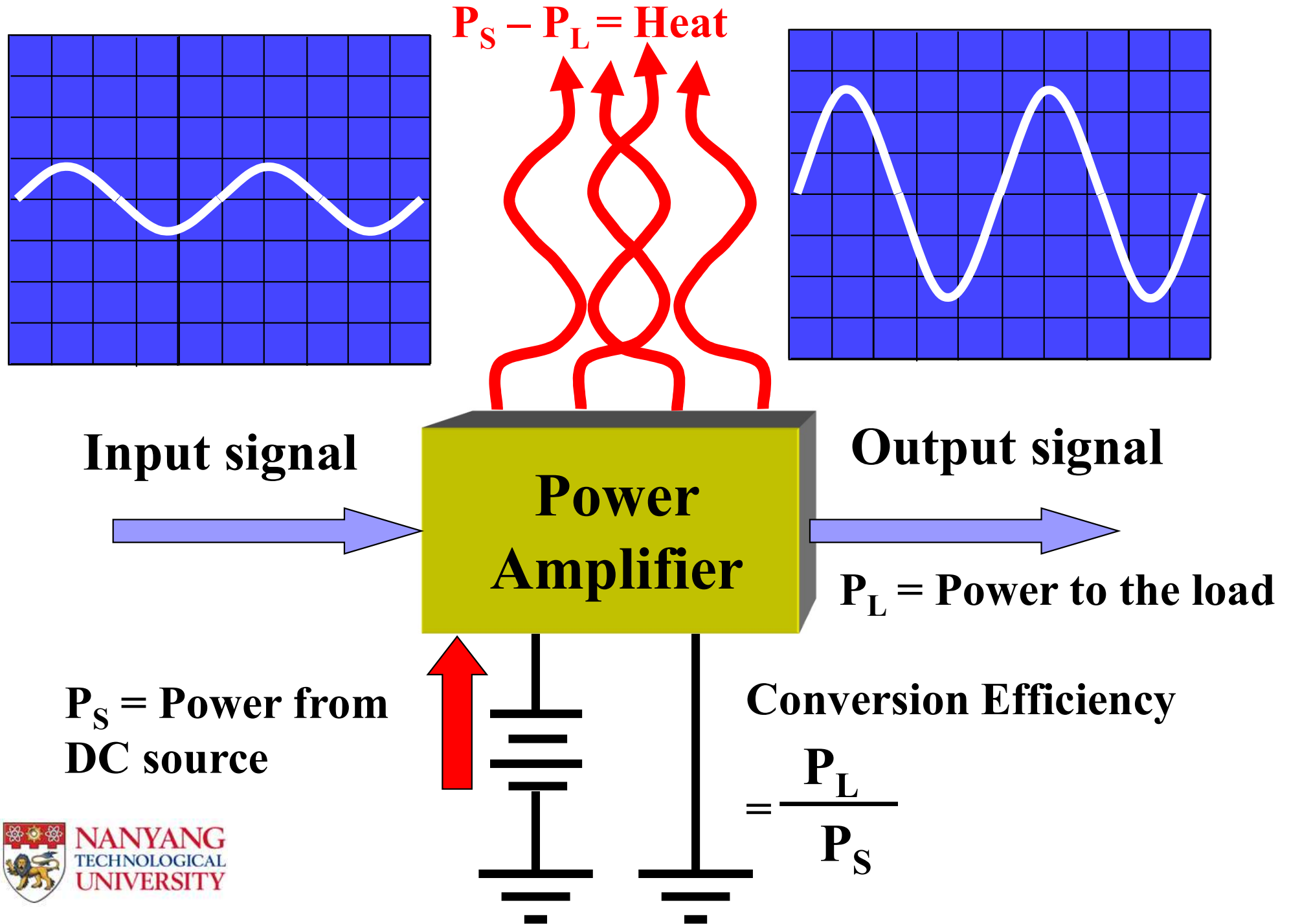

Power Amplifier



- To deliver a **large amount of power** to a load (for examples, audio amplifiers and RF transmitters).
- To deliver the required power to the load **efficiently** with lowest possible power dissipation in the power amplifier itself.
- To operate in the linear region to **minimize the distortion** of the output signal waveform, usually measured in terms of total harmonic distortion (THD).

Typical Amplifier Circuit

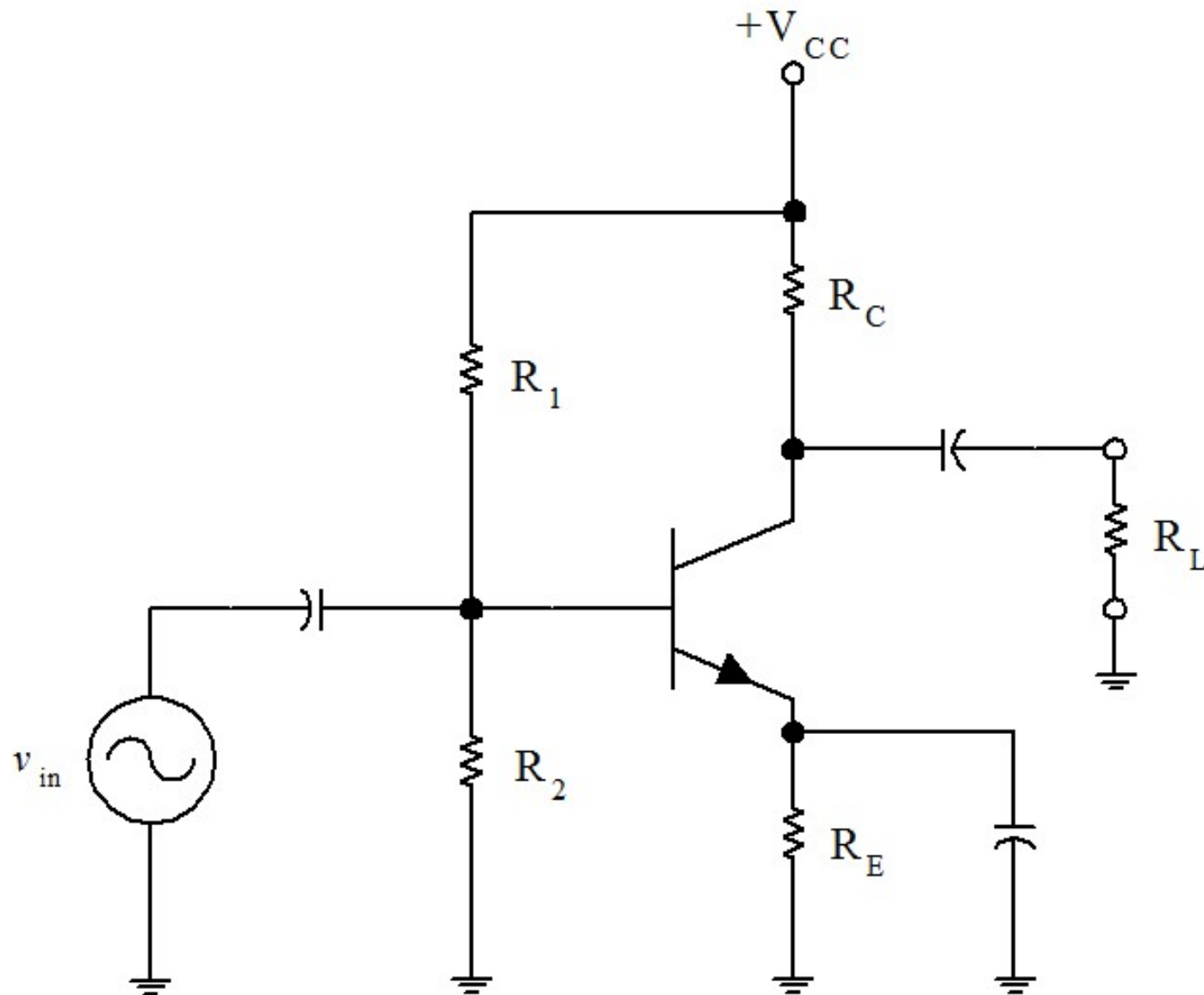

Under DC condition:

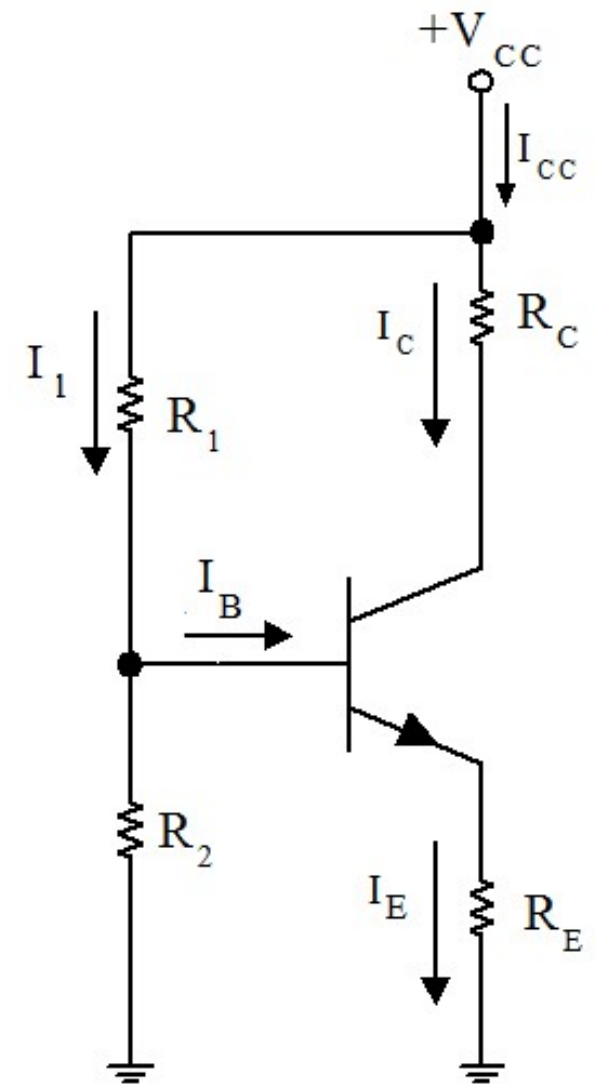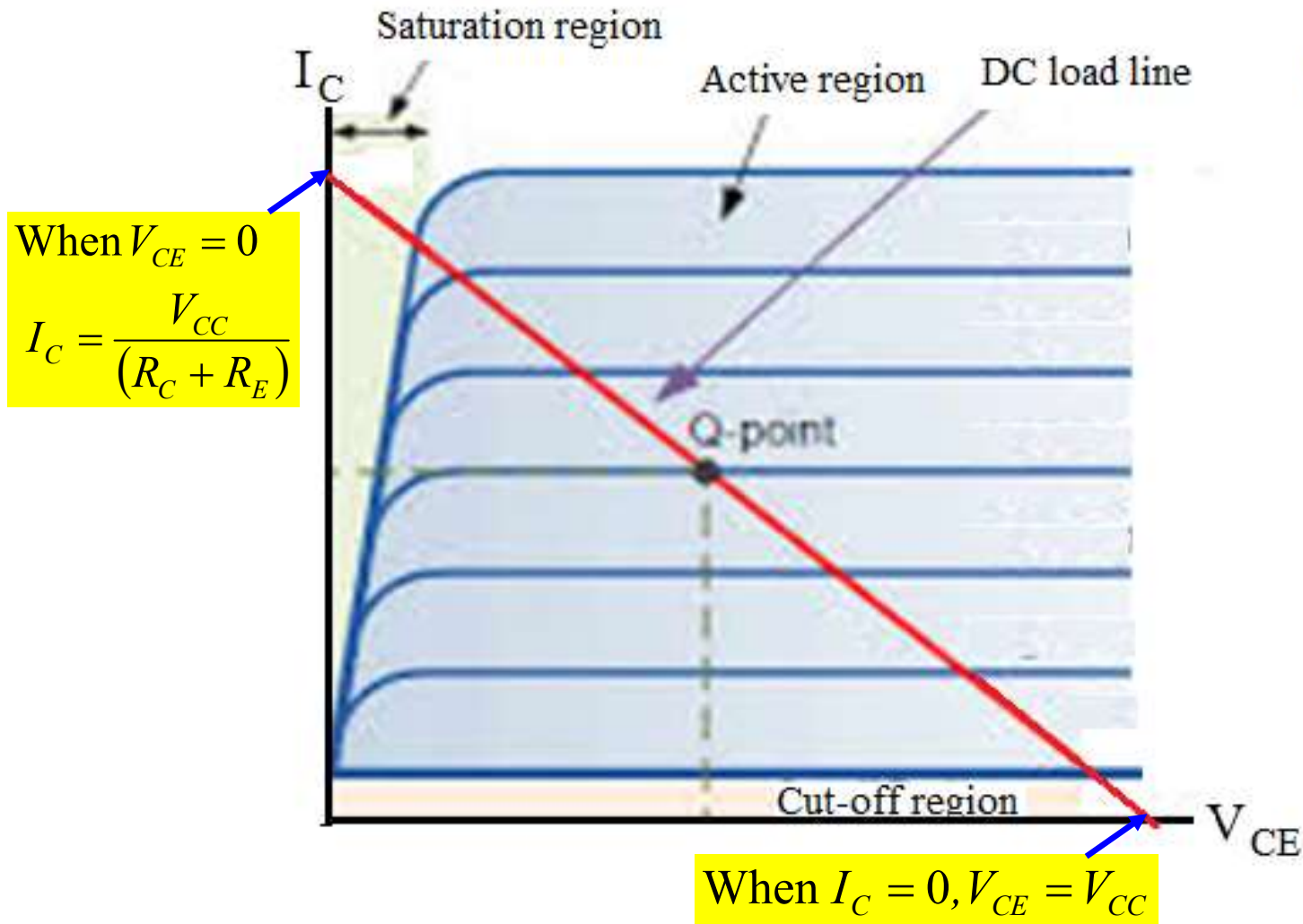If β is large, $I_C \approx I_E$ $V_{CE} = V_{CC} - I_C(R_C + R_E)$



For maximum output voltage swing, the biasing is chosen at the mid-point of the DC load line.

The Q-point is chosen so that:


$$V_{CEQ} = \frac{V_{CC}}{2} \quad I_{CQ} = \frac{1}{2} \times \frac{V_{CC}}{(R_C + R_E)}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{V_{CC}}{2\beta(R_C + R_E)}$$

$$V_{th} = V_{CC} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$
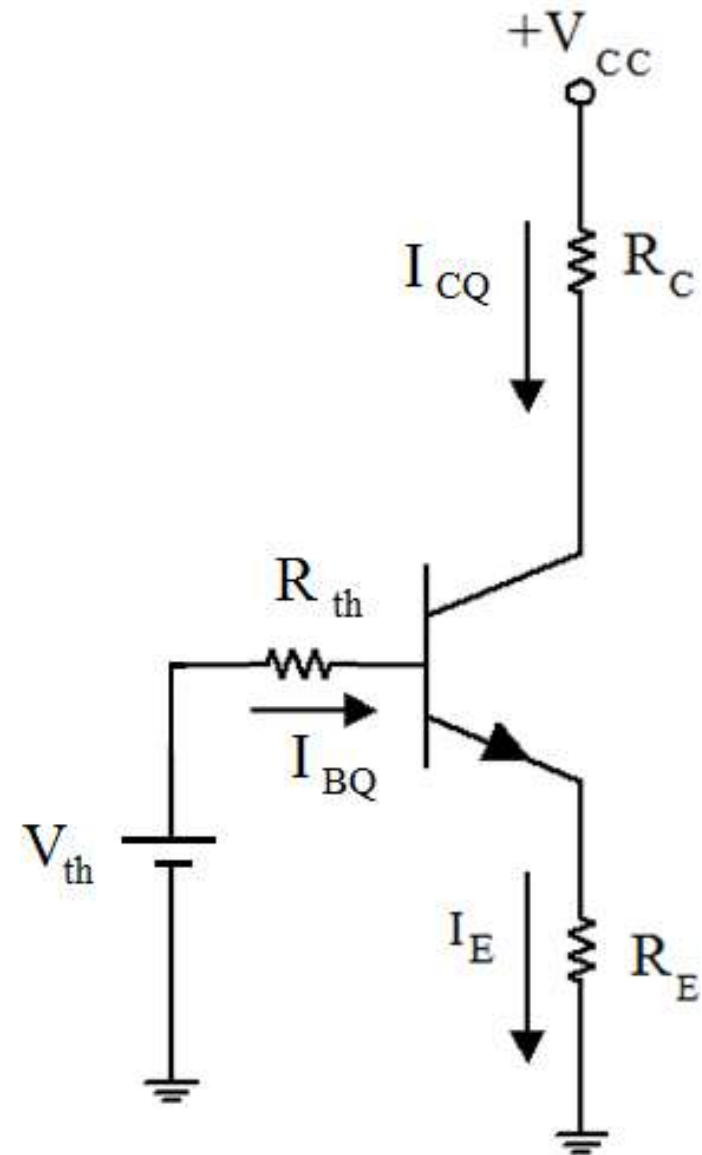
$$V_{th} = I_{BQ} R_{th} + V_{BE} + (\beta + 1) I_{BQ} R_E$$



From the above equations, R_1 and R_2 can be determined to provide the required Q-point.

Amplifier Efficiency

The **conversion efficiency** is defined as: $\eta = \frac{\overline{P_L}}{\overline{P_S}}$

where $\overline{P_L}$ = Average ac power delivered to the load

$\overline{P_S}$ = Average power supplied from dc power source

$$\overline{P_L}(max) = \frac{1}{2} V_p I_p = \frac{1}{2} \left(\frac{V_{CC}}{2} \right) (I_{CQ}) = \frac{V_{CC} I_{CQ}}{4}$$


Assuming that both maximum voltage and current swings are possible

$$\overline{P_S} = V_{CC} I_{CC} = V_{CC} (I_{CQ} + I_1) \approx V_{CC} I_{CQ} \quad \text{assume } I_1 \ll I_{CQ}$$

$$\eta(max) = \frac{\overline{P_L}(max)}{\overline{P_S}} = \left(\frac{V_{CC} I_{CQ}}{4} \right) \left(\frac{1}{V_{CC} I_{CQ}} \right) = 25\%$$

This is the highest efficiency that can be achieved

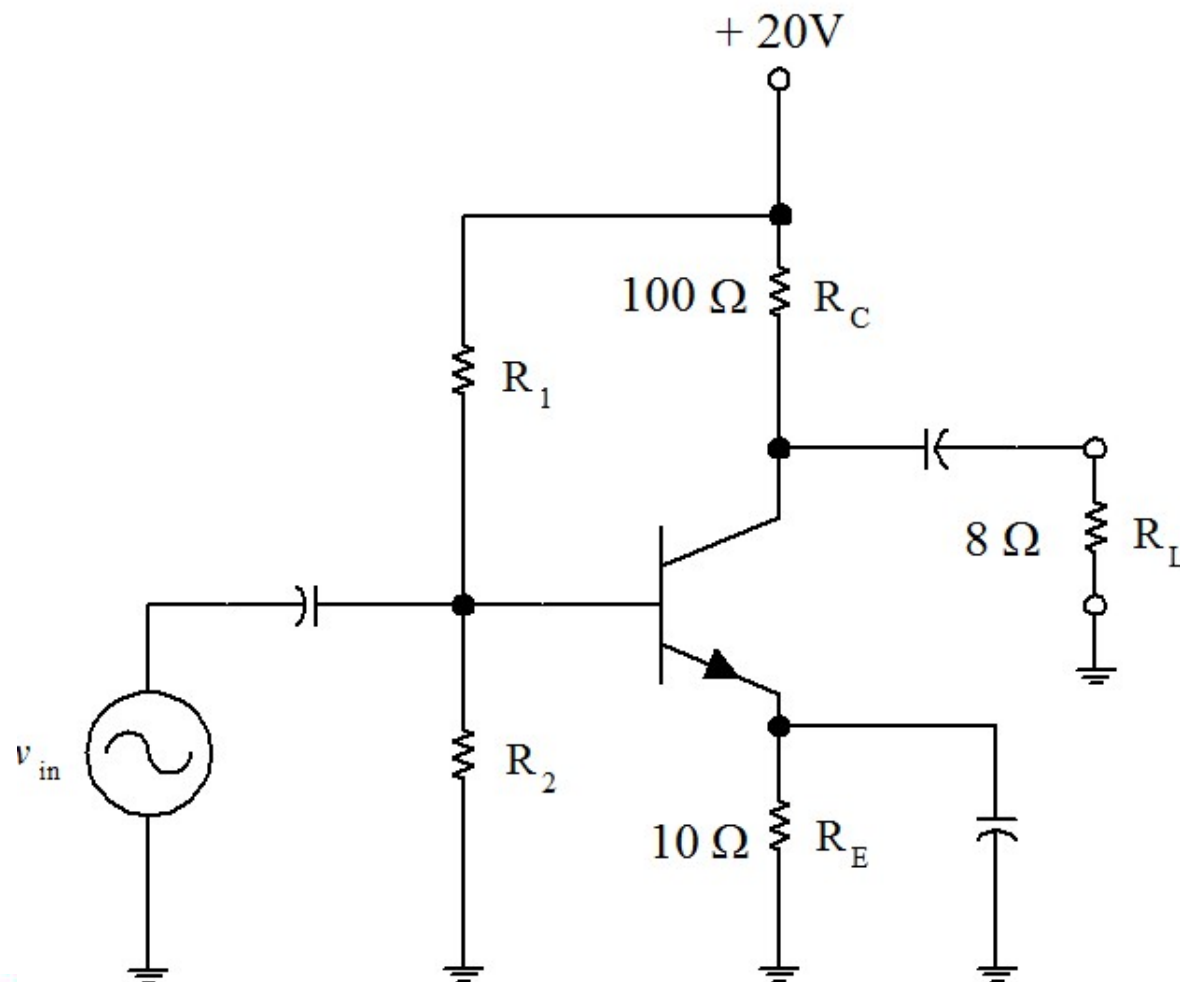Exercise #1: For the given amplifier circuit, determine the value of R_1 and R_2 to provide maximum output voltage swing. Calculate its conversion efficiency if $v_i = 0.2 V_{\text{peak}}$. Assume $\beta = 25$, $V_T = 26 \text{ mV}$, $V_{BE} = 0.7 \text{ V}$ and $V_{CE,\text{sat}} = 0.2 \text{ V}$.




DC biasing circuit:


$$V_{CEQ} = \frac{V_{CC}}{2} = 10 \text{ V}$$

$$V_{CC} = I_{CQ}R_C + V_{CEQ} + \left(\frac{\beta + 1}{\beta}\right)I_{CQ}R_E$$

$$\begin{aligned} I_{CQ} &= \frac{V_{CC} - V_{CEQ}}{R_C + \left(\frac{\beta + 1}{\beta}\right)R_E} \\ &= \frac{20 - 10}{100 + 1.04 \times 10} \\ &= 90.56 \text{ mA} \end{aligned}$$
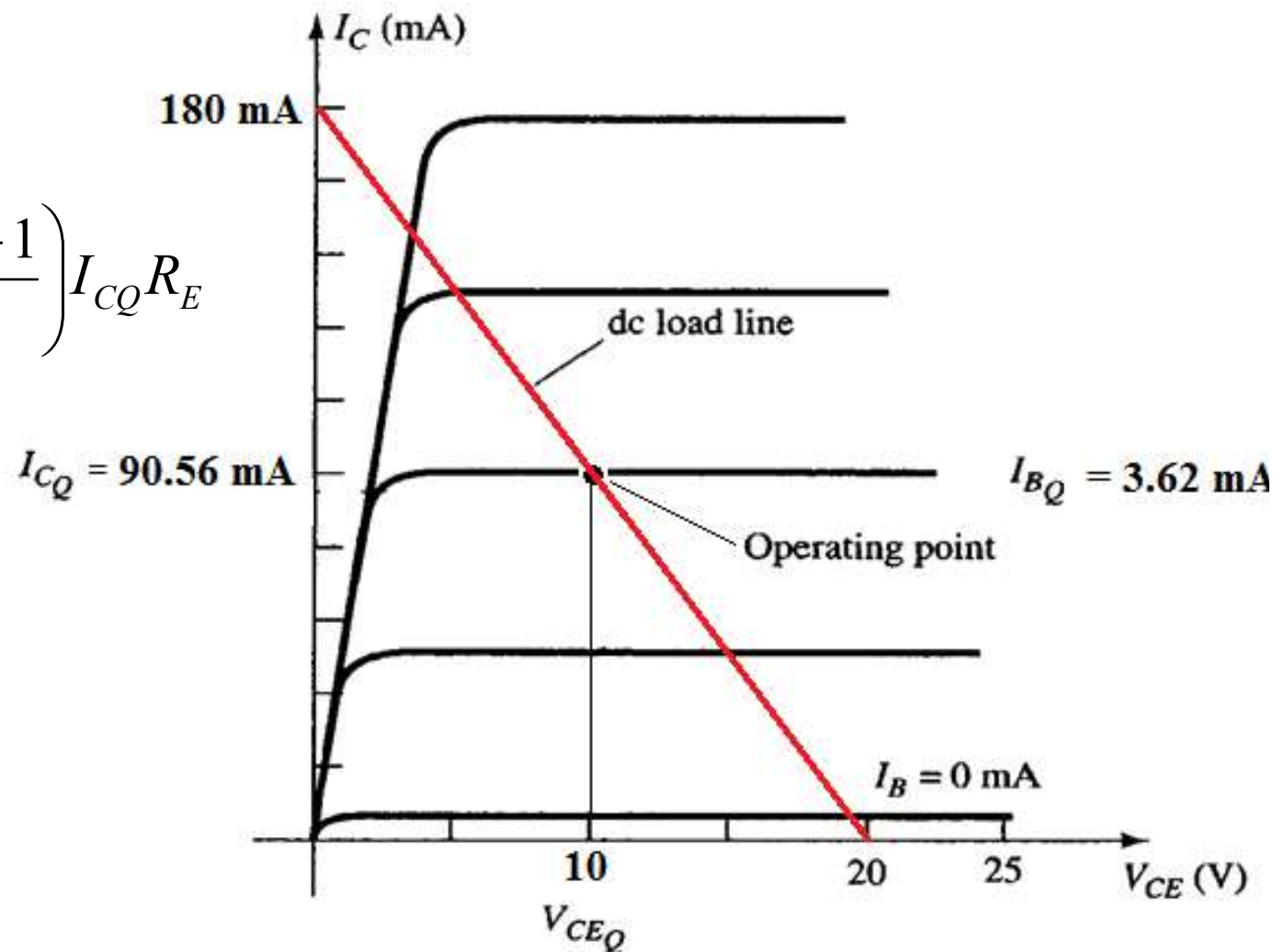
$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{90.56 \text{ mA}}{25} = 3.62 \text{ mA}$$



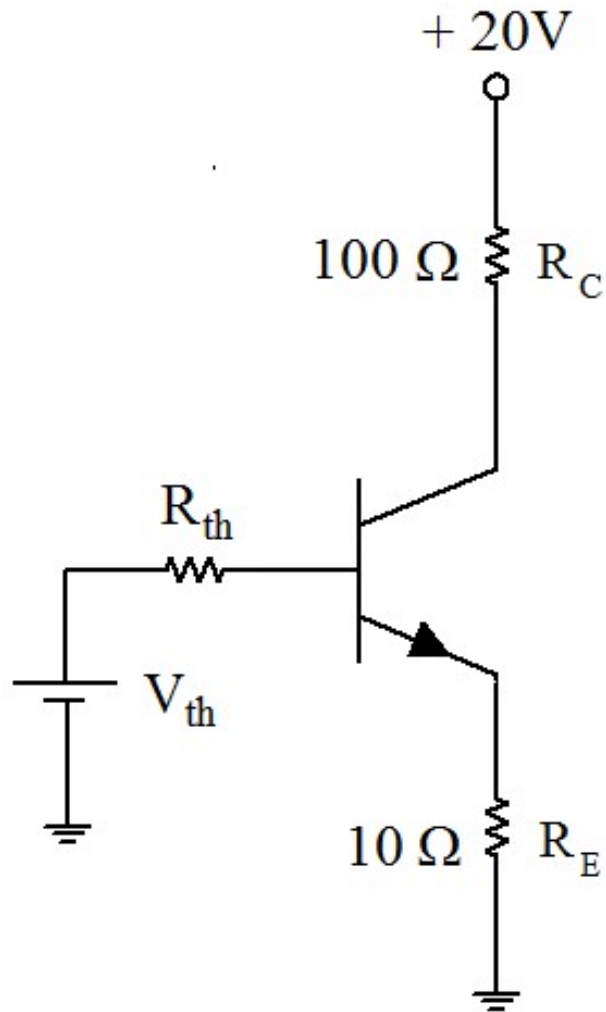

$$V_{th} = I_{BQ} R_{th} + V_{BE} + (\beta + 1) I_{BQ} R_E$$

$$I_{BQ} = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$


$$R_{th} = \frac{V_{th} - V_{BE}}{I_{BQ}} - (\beta + 1) R_E$$

Let make $R_1 = R_2$

$$\therefore V_{th} = 0.5 V_{CC} = 10 \text{ V}$$

$$R_{th} = \frac{10 - 0.7}{3.62 \times 10^{-3}} - 26 \times 10 = 2.31 \text{ k}\Omega$$

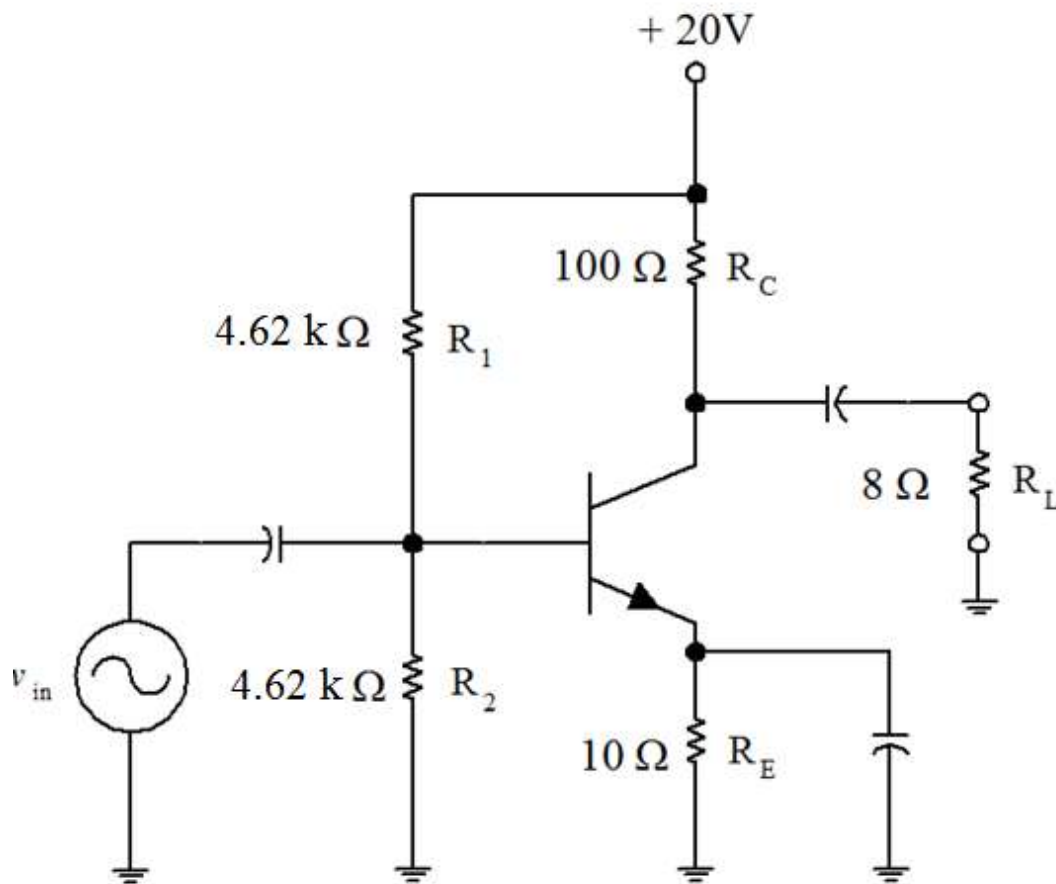
$$\therefore R_1 = R_2 = 2 \times 2.31 \text{ k}\Omega = 4.62 \text{ k}\Omega$$



$$g_m = \frac{I_{CQ}}{V_T} = \frac{90.56 \text{ mA}}{26 \text{ mV}} = 3.48 \text{ S}$$

$$\begin{aligned} v_{o,peak} &= g_m v_{i,peak} (R_L // R_C) \\ &= 3.48 \times 0.2 \times (7.41) \\ &= 5.15 \text{ V} \end{aligned}$$

AC small signal model:

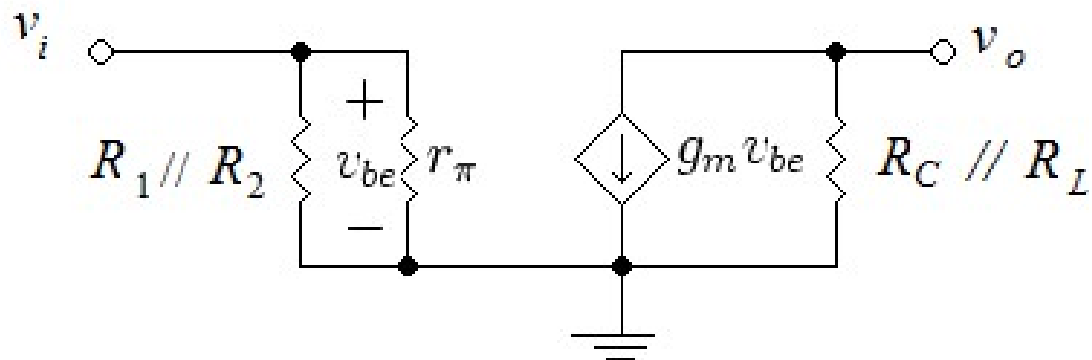

$$i_{o,peak} = \frac{v_{o,peak}}{R_L} = \frac{5.15}{8} = 643.75 \text{ mA}$$


Maximum peak current = $I_{CQ} \approx 90 \text{ mA}$, so it is impossible for the peak voltage to be 5.15 V!

Maximum peak current = $I_{CQ} \approx 90 \text{ mA}$

$$v_{o,peak} = i_{o,peak} (R_L // R_C) = 90 \text{ mA} \times (7.41) = 0.67 \text{ V}$$

Maximum peak voltage is limited to 0.67V not 10 V!
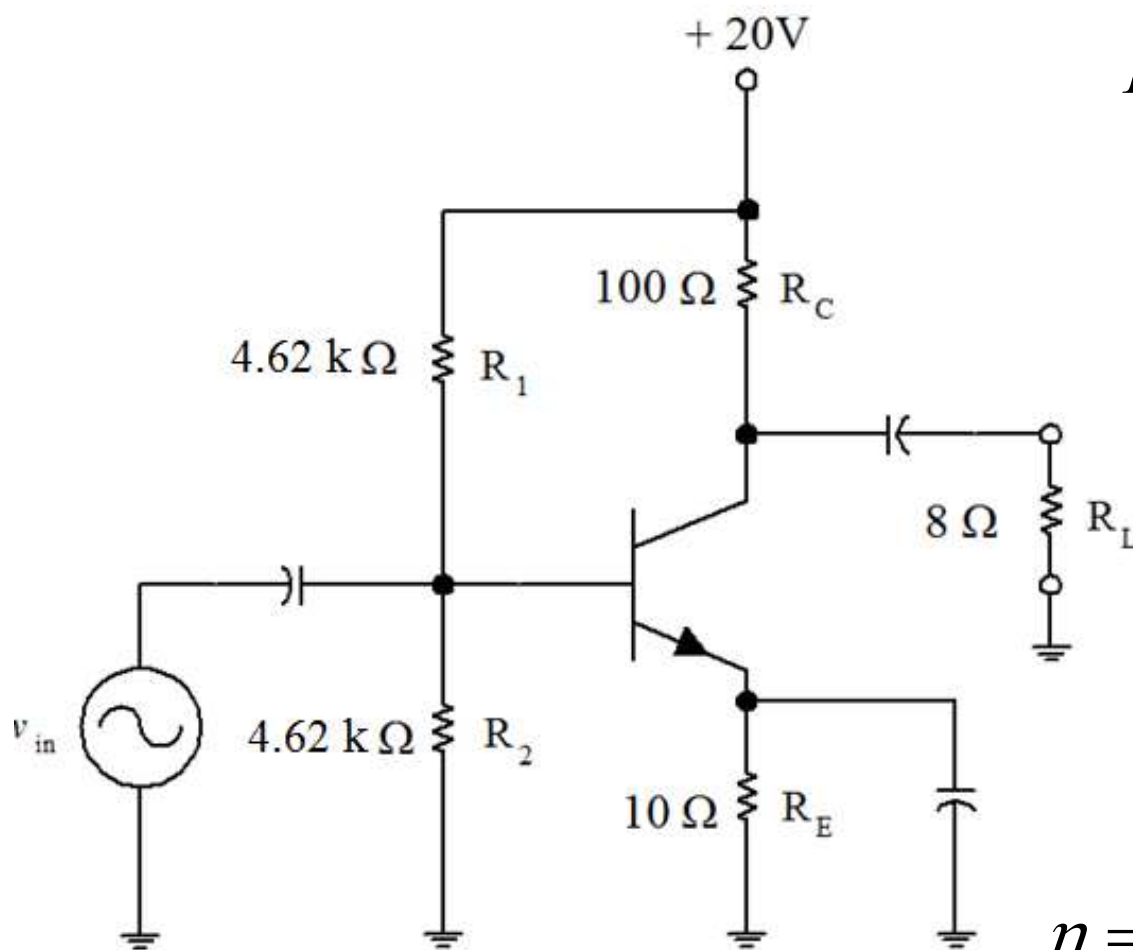
$$\overline{P}_L = \frac{1}{2} i_{o,peak} v_{o,peak} = 0.5 \times 90 \text{ mA} \times 0.67 \text{ V} = 0.03 \text{ W}$$



$$I_{R1} = \frac{V_{CC} - V_{BE} - (\beta + 1)I_{BQ}R_E}{R_1}$$

$$= \frac{20 - 0.7 - 26 \times 3.62m \times 10}{4.62k}$$

$$= 3.97 \text{ mA}$$

$$\overline{P}_S = V_{CC}(I_{CQ} + I_{R1})$$


$$= 20 \times (90.56 + 3.97)m$$

$$= 7.19 \text{ W}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} \times 100\% = \frac{0.03}{7.91} \times 100 = 0.38\%$$

- The output peak voltage and current are load-dependent.
- It is good for voltage amplification but unable to deliver the load current.

Power Amplifier Architecture

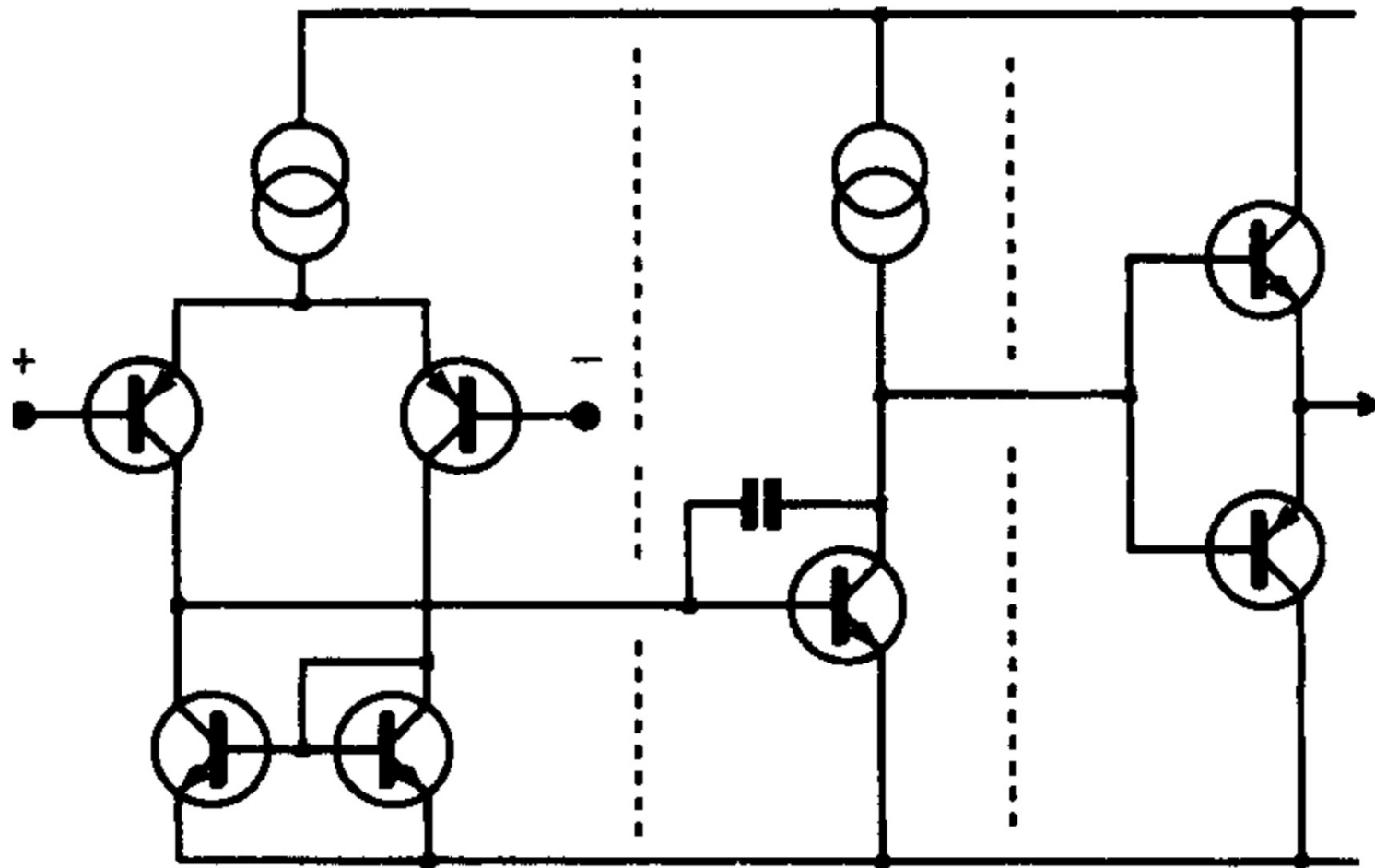


Differential input to reject common-mode noise

Voltage amplifier to achieve maximum voltage swing





Output stage to deliver maximum current swing

Classification of Power Amplifiers

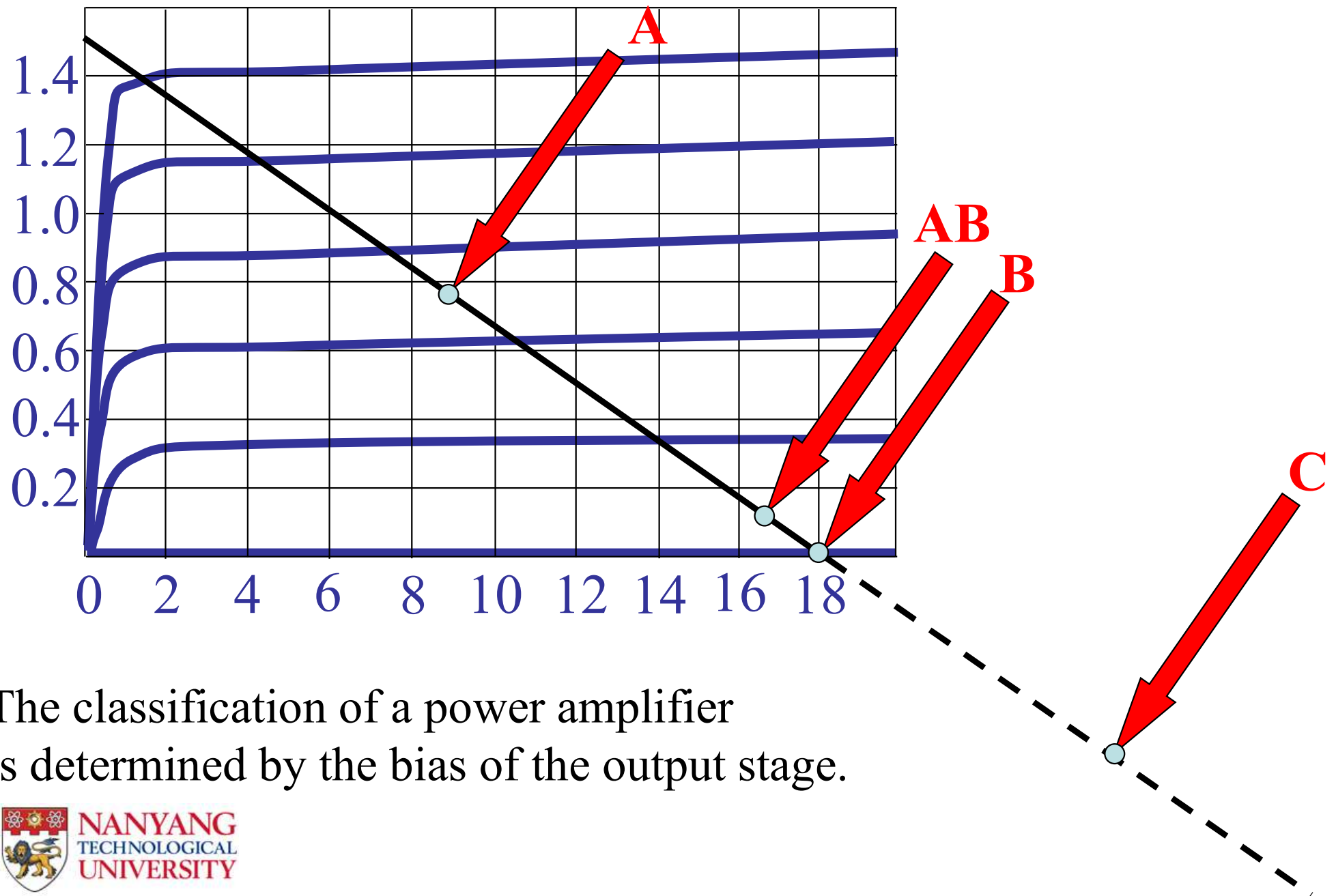


The classification of a power amplifier is determined by the bias of the output stage.

Classification of Power Amplifiers

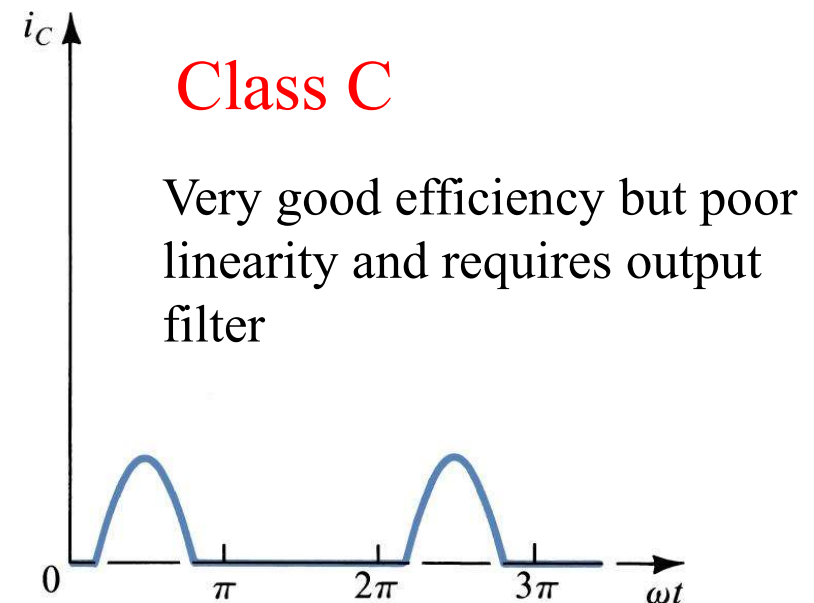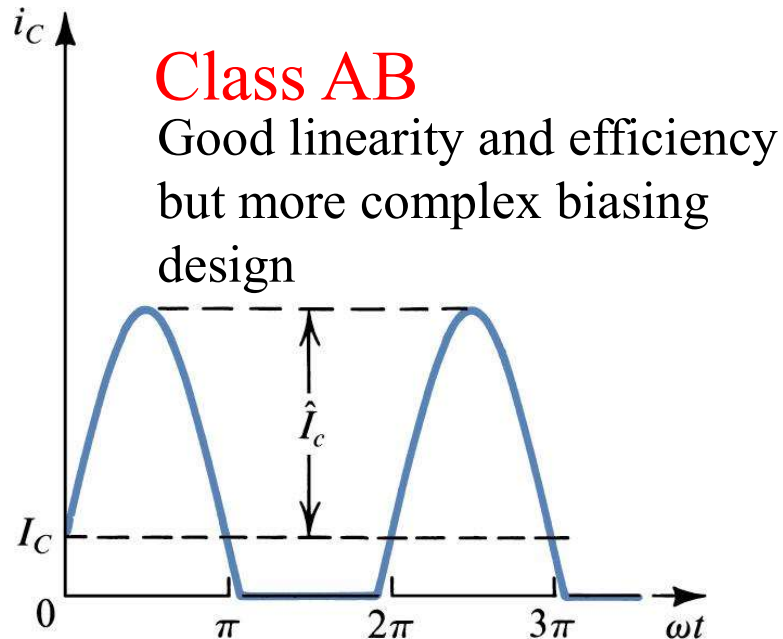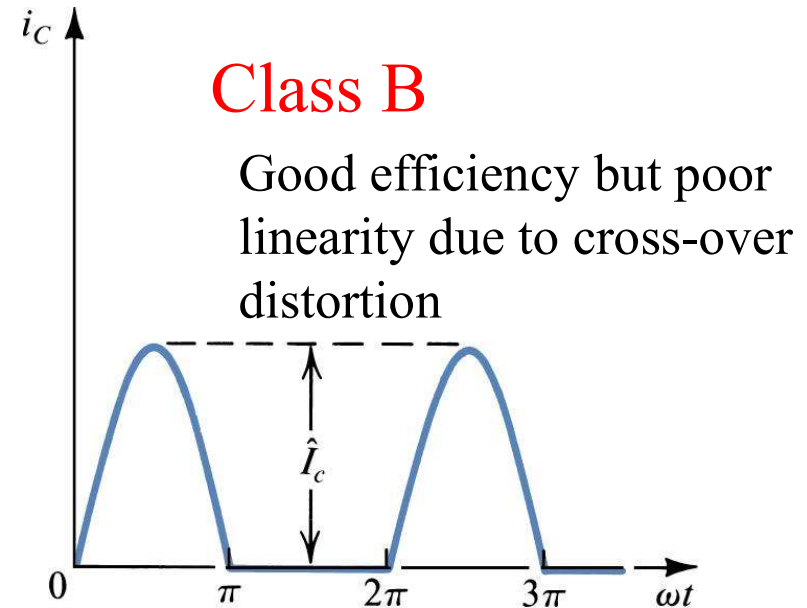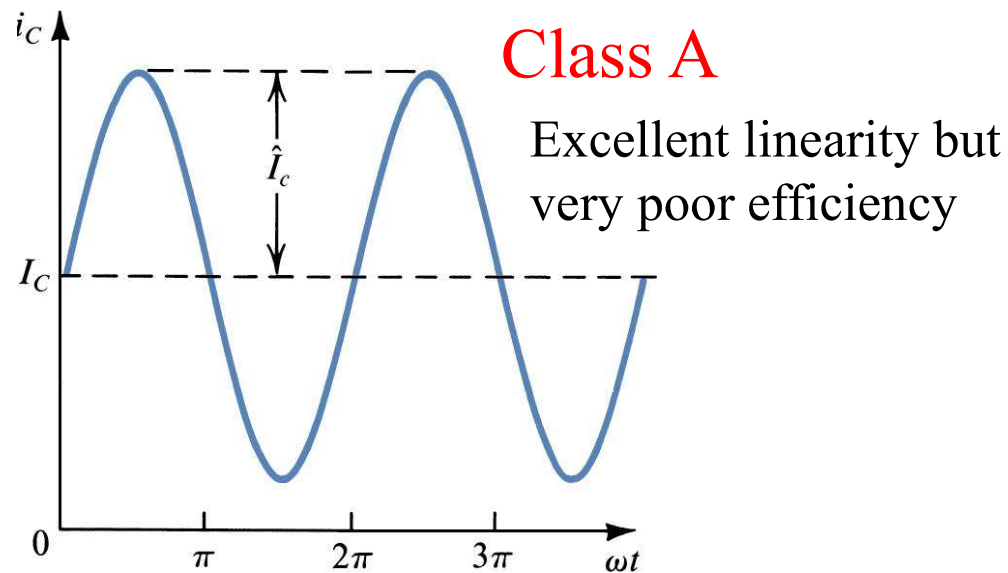

Power Amplifier using Digital Technique

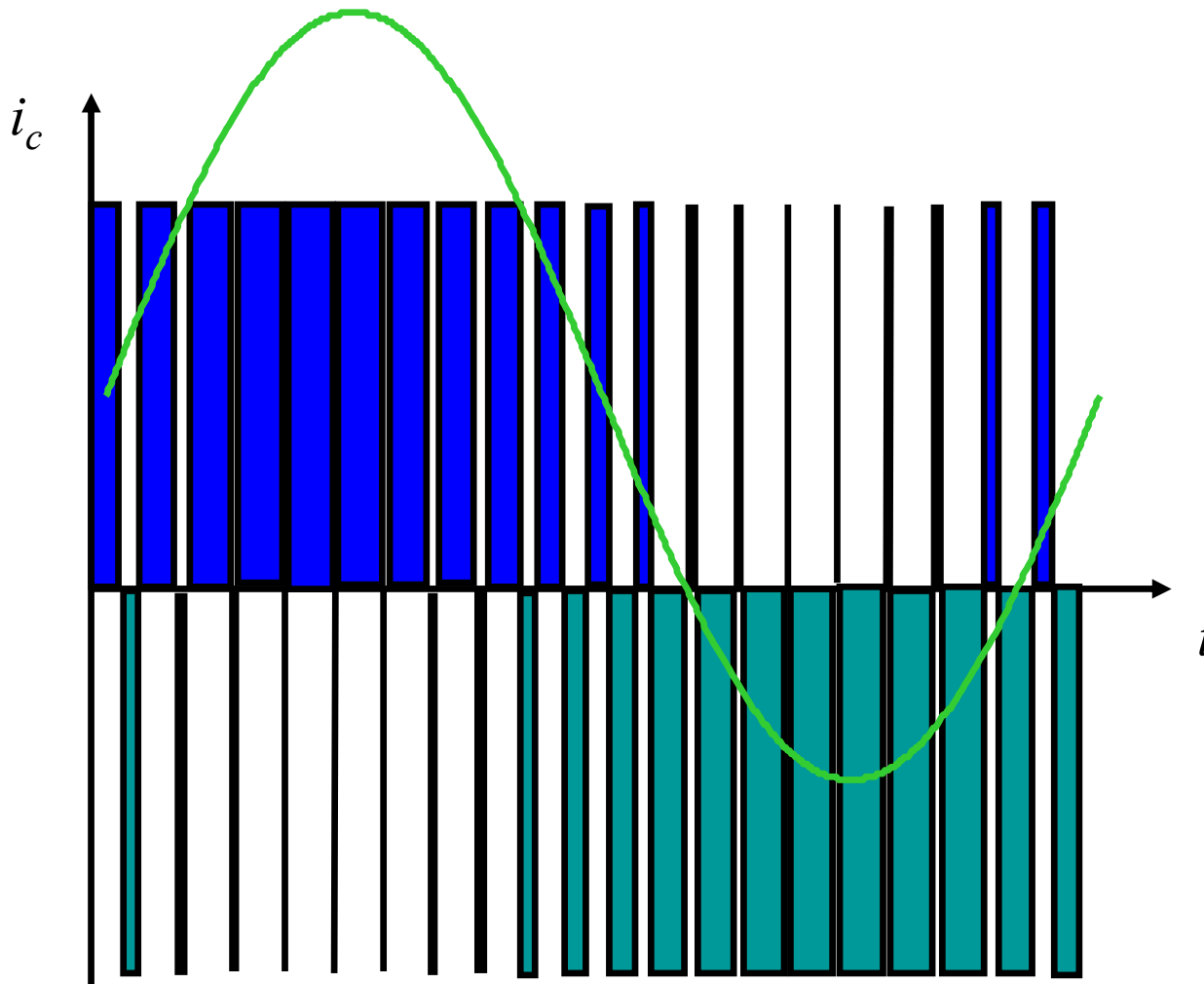There is another class of amplifier (**Class D**) which is based pulse-width modulation (PWM) technique.



- ❖ Superb efficiency
- ❖ More circuit blocks such as PWM, lower pass filter, etc.
- ❖ Generates significant electromagnetic interference (EMI) due to fast switching

Class A Emitter Follower


$$v_o = v_i - v_{be1}$$

$$v_{BE1} = \frac{kT}{q} \ln \left(\frac{i_{c1}}{I_S} \right)$$

Q_2 is in active region and provide the biasing current I_Q

$$i_{C1} \approx i_{E1} = I_Q + i_L = I_Q + \frac{v_o}{R_L}$$
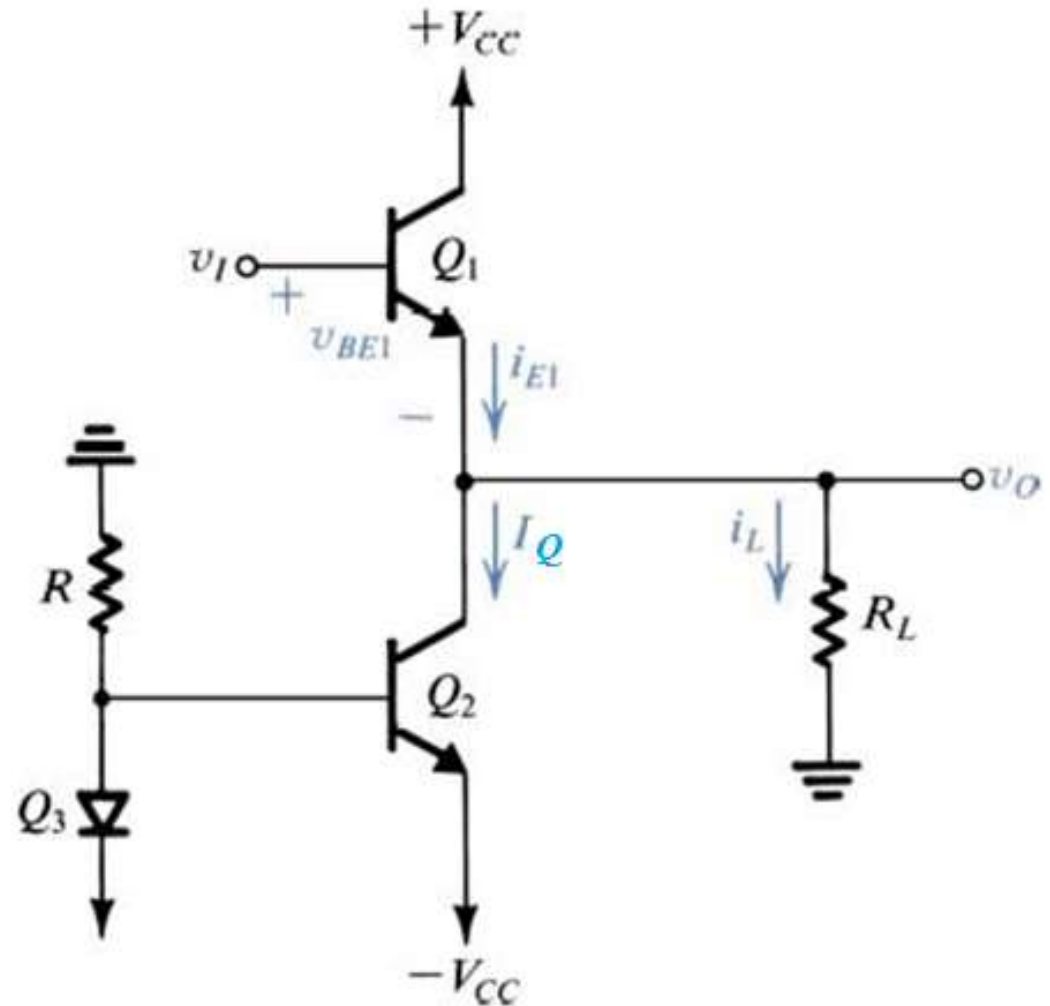
$$v_o = v_i - \frac{kT}{q} \ln \left(\frac{I_Q + \frac{v_o}{R_L}}{I_S} \right)$$



$$v_o = v_i - \frac{kT}{q} \ln \left(\frac{I_Q + \frac{v_o}{R_L}}{I_S} \right)$$

If $v_o > 0$:


$$i_{C1} = I_Q + \frac{v_o}{R_L} > 0$$

Then v_o and v_i are related by:

$$v_o = v_i - v_{BE1}$$

The maximum output voltage is limited by:

$$v_o = V_{CC} - V_{CE1,sat}$$

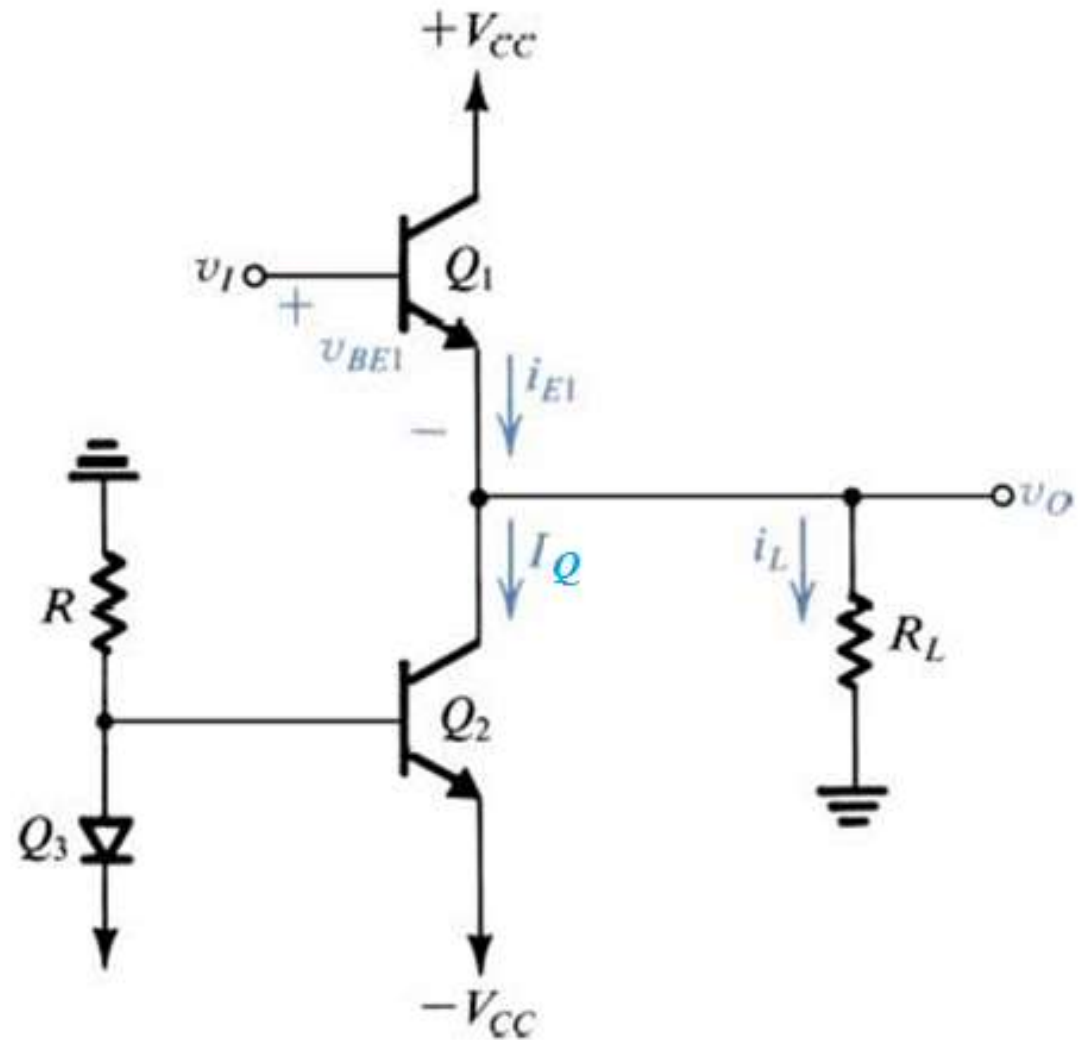

$$v_o = v_i - \frac{kT}{q} \ln \left(\frac{I_Q + \frac{v_o}{R_L}}{I_S} \right)$$

When $v_o < 0$, i_L will be -ve, the output will depend of the value of R_L .


If R_L is small, Q_1 will be in cut-off if:

$$i_{C1} = I_Q + \frac{v_o}{R_L} = 0, \therefore I_Q = -\frac{v_o}{R_L}$$

$$v_o = -I_Q R_L$$


If R_L is large, Q_1 will remain in active region and:

$$v_o = -V_{CC} + V_{CE2,sat}$$

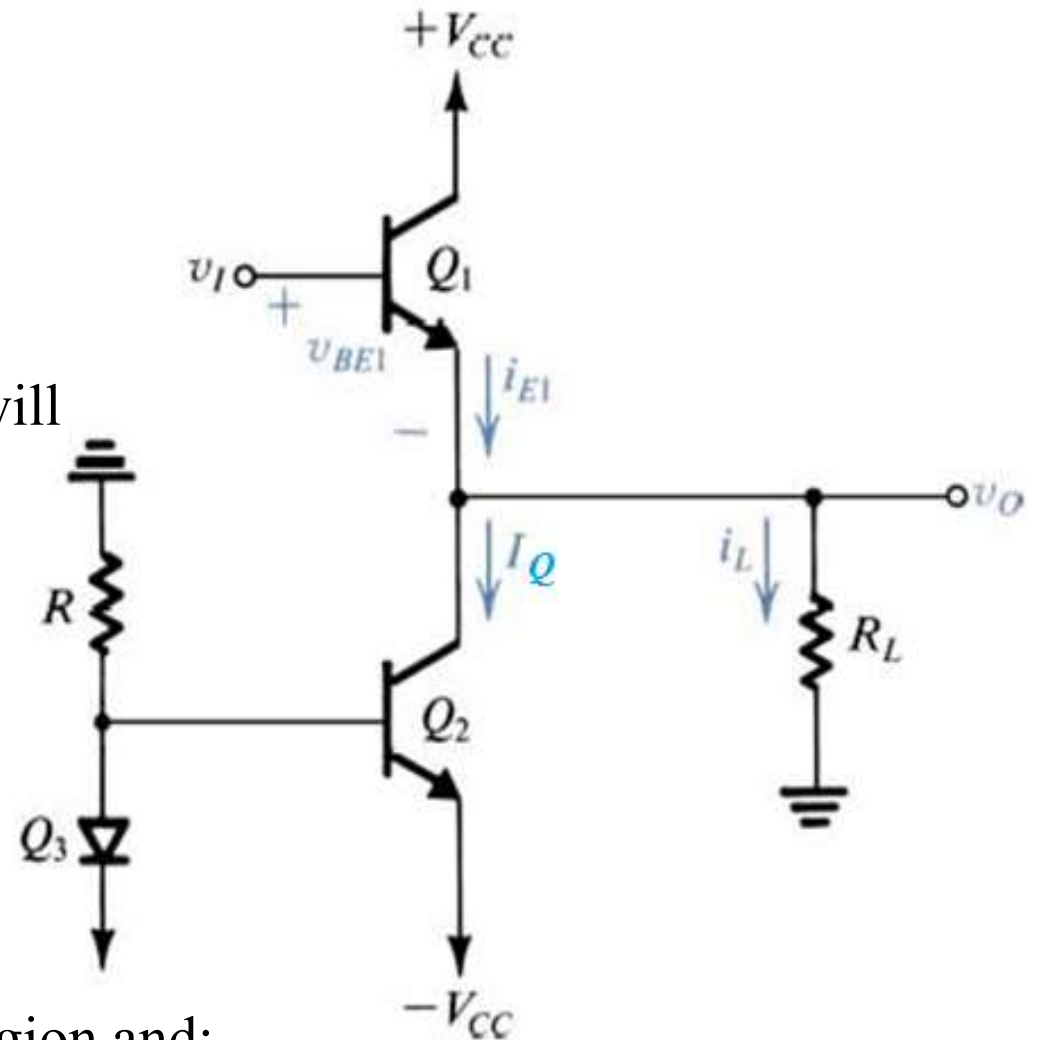


Transfer Characteristic

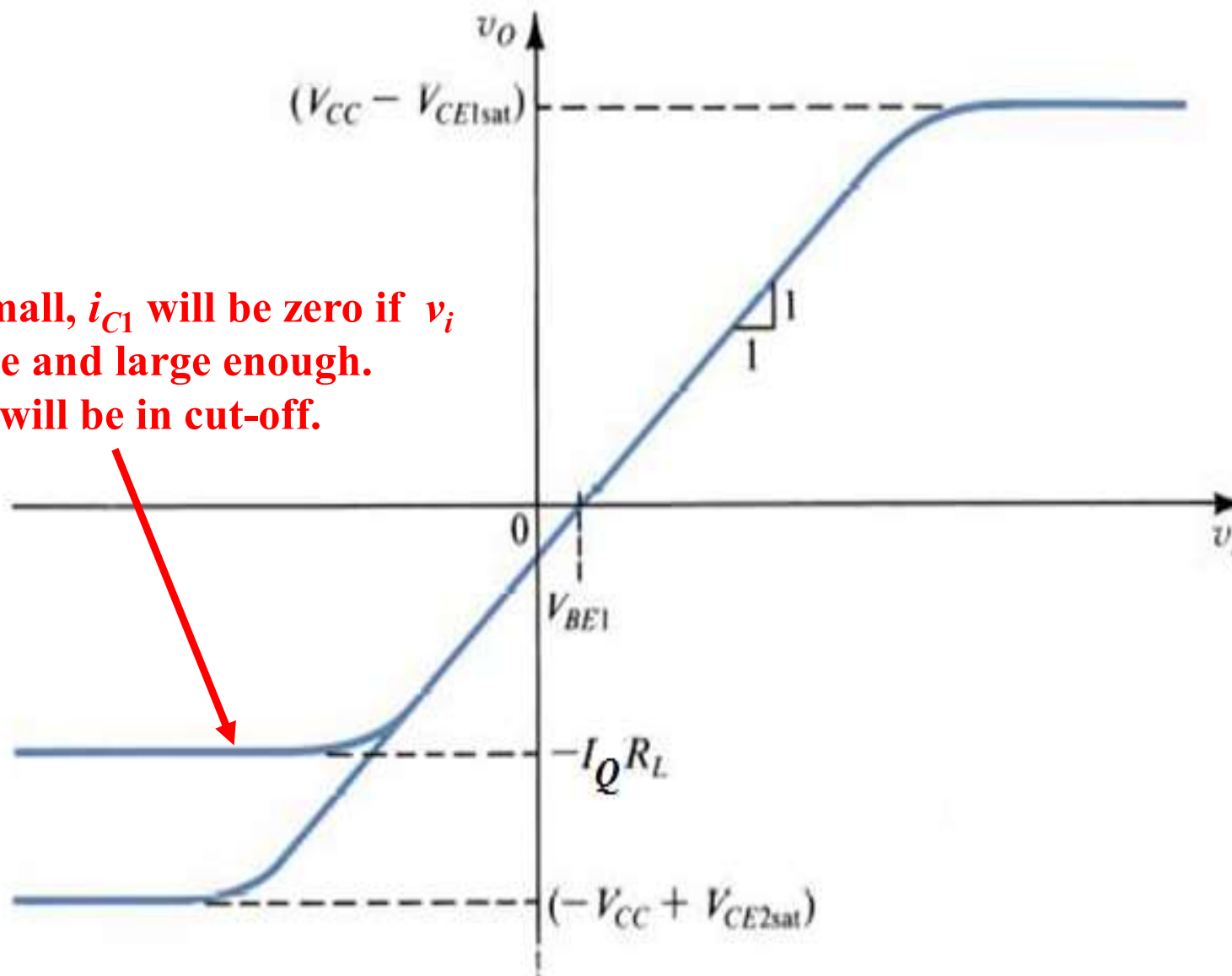If R_L is small, i_{C1} will be zero if v_i is negative and large enough.
Then Q1 will be in cut-off.




Class B Amplifiers

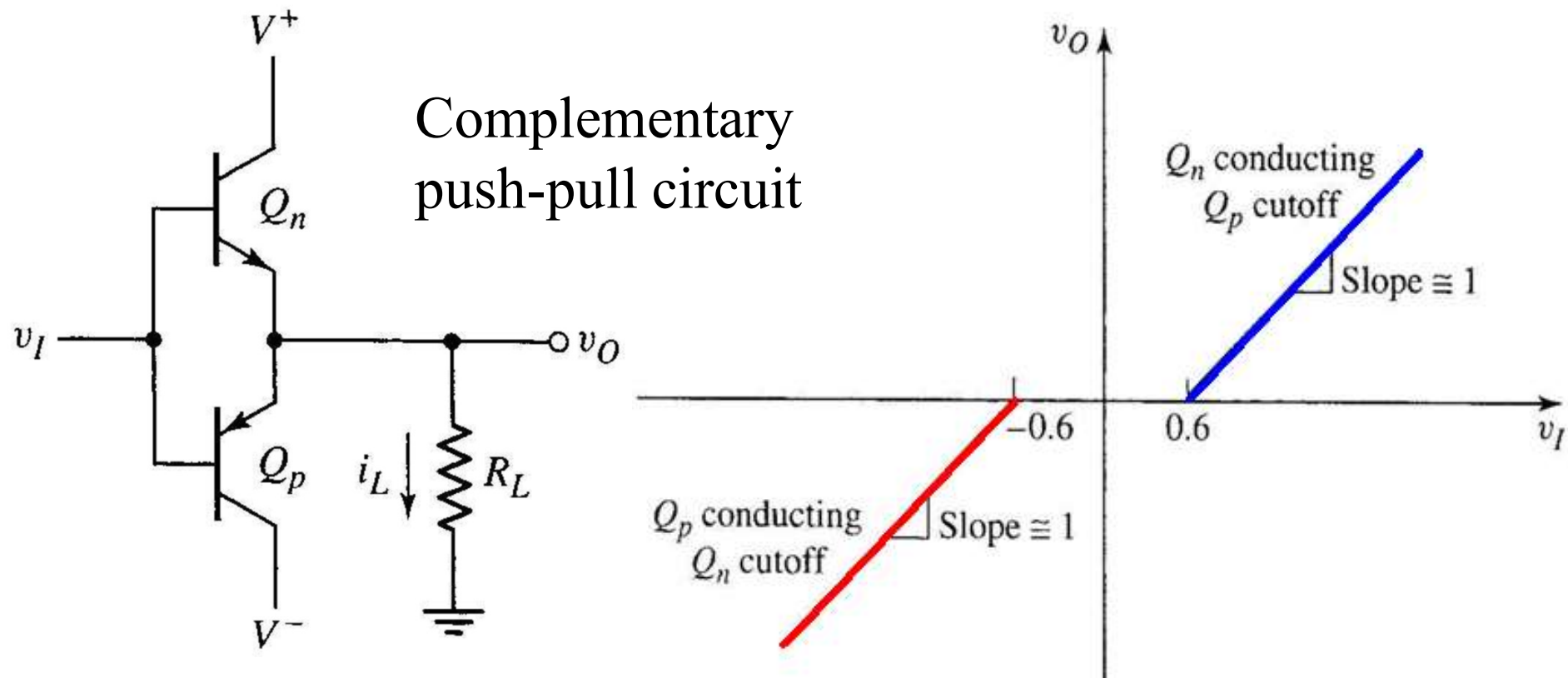

When $V_i > 0$ and greater than 0.6 V, Q_n turns on and operates as an emitter follower.

When $V_i < 0$ and less than -0.6 V, Q_p turns on and operates as an emitter follower.

Crossover Distortion

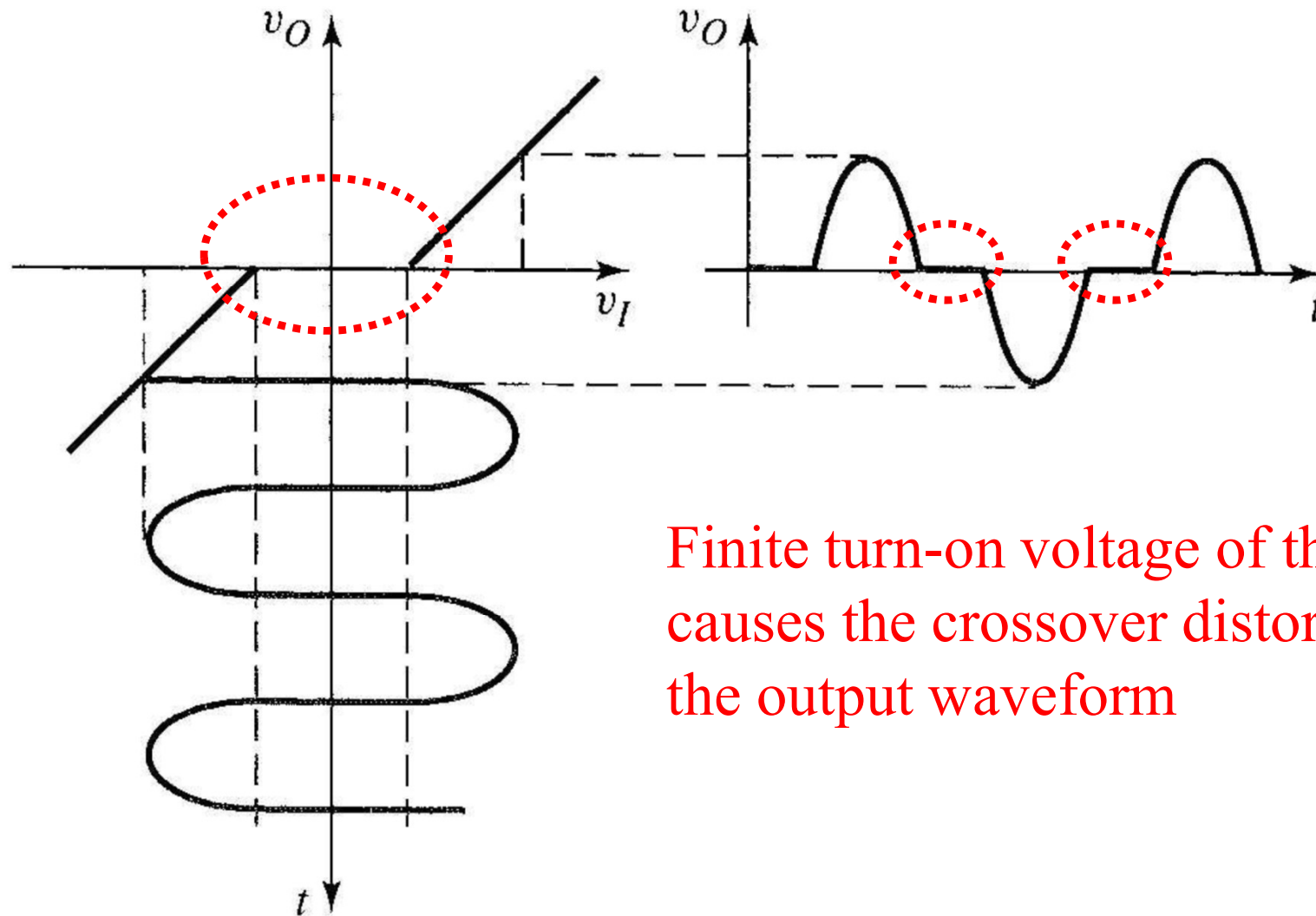

Finite turn-on voltage of the BJT causes the crossover distortion of the output waveform

Exercise #2: A 1 kHz sinusoidal signal with an amplitude of 2V was applied to the Class B amplifier. The supply voltage = $\pm 10\text{V}$. Due to crossover distortion, the output waveform is not a pure sinusoidal waveform. The harmonics measured as the output in frequency domain are recorded as follows. Please compute the total harmonic distortion (THD).


Frequency (Hz)	Fourier component	Normalized component
1.000E+03	1.151E+00	1.000E+00
2.000E+03	6.313E-03	5.485E-03
3.000E+03	2.103E-01	1.827E-01
4.000E+03	4.984E-03	4.331E-03
5.000E+03	8.064E-02	7.006E-02
6.000E+03	3.456E-03	3.003E-03
7.000E+03	2.835E-02	2.464E-02
8.000E+03	2.019E-03	1.754E-03
9.000E+03	6.679E-03	5.803E-03

Frequency (Hz)	Fourier component	Normalized component
1.000E+03	1.151E+00	1.000E+00
2.000E+03	6.313E-03	5.485E-03
3.000E+03	2.103E-01	1.827E-01
4.000E+03	4.984E-03	4.331E-03
5.000E+03	8.064E-02	7.006E-02
6.000E+03	3.456E-03	3.003E-03
7.000E+03	2.835E-02	2.464E-02
8.000E+03	2.019E-03	1.754E-03
9.000E+03	6.679E-03	5.803E-03


$$\begin{aligned}
 THD &= \frac{\sqrt{V_2^2 + V_3^2 + V_4^2 + \dots + V_n^2}}{V_1} \times 100 \\
 &= \frac{\sqrt{0.006313^2 + 0.2103^2 + 0.004984^2 + 0.08064^2 + \dots}}{1.151} \times 100 \\
 &= \frac{0.2273}{1.151} \times 100 \\
 &= 19.7\%
 \end{aligned}$$

THD is a gauge of how good a power amplifier amplifies a signal without distortion. $THD > 5\%$ is usually not acceptable for audio applications.

Class B Amplifier Efficiency

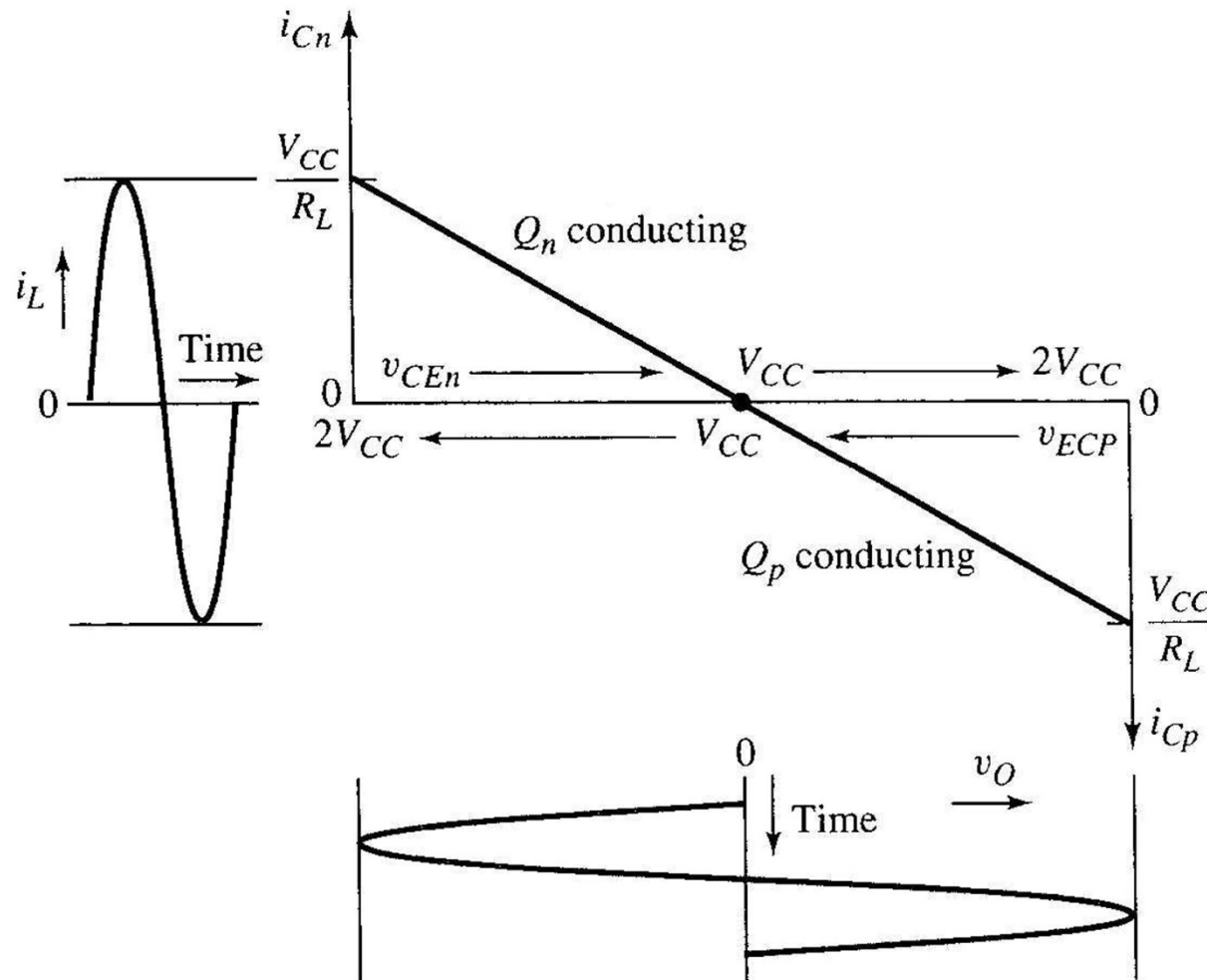

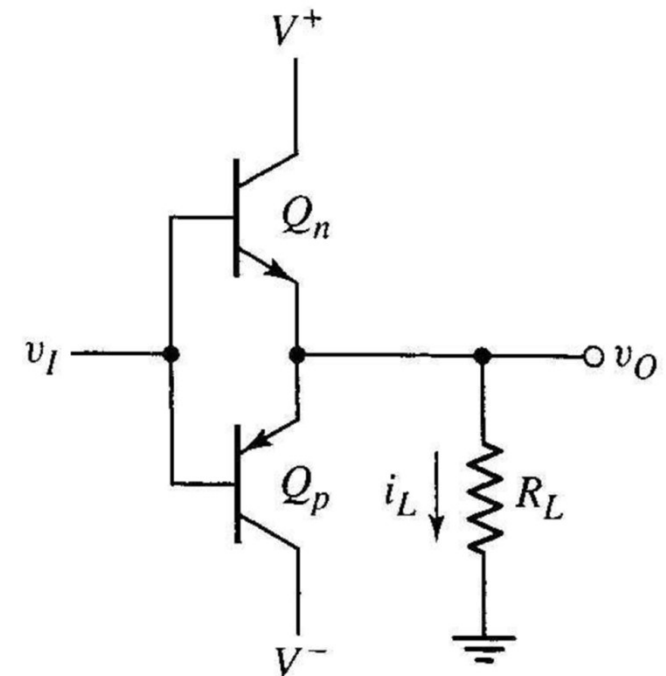For ease of analysis, assume the transistors are ideal with zero turn-on voltage.



$$v_o = V_p \sin \omega t$$

Average power to the load: $\overline{P}_L = \frac{1}{2} V_p I_p = \frac{1}{2} V_p \left(\frac{V_p}{R_L} \right) = \frac{V_p^2}{2R_L}$

Average power supplied by each voltage source:

$$\overline{P}_{S+} = \overline{P}_{S-} = V_{CC} \overline{I}_S = V_{CC} \left(\frac{V_p}{\pi R_L} \right)$$

Total average power supplied by two voltage sources:

$$\overline{P}_S = 2V_{CC} \left(\frac{V_p}{\pi R_L} \right)$$

Conversion efficiency: $\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{\frac{1}{2} \left(\frac{V_p^2}{R_L} \right)}{2V_{CC} \left(\frac{V_p}{\pi R_L} \right)} = \frac{\pi}{4} \left(\frac{V_p}{V_{CC}} \right)$

Maximum conversion efficiency occurs when $V_p = V_{CC}$:

$$\eta(max) = \frac{\pi}{4} = 78.5\% \quad \text{It is much higher than Class A amplifier.}$$

In reality, to avoid distortion of output signal, the actual voltage swing is smaller and therefore the conversion efficiency is less than 78.5%.

$$v_{CEn} = V_{CC} - v_o = V_{CC} - V_p \sin \omega t$$

$$i_{Cn} = \frac{V_p}{R_L} \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi, \quad i_{Cn} = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi$$

$$P_n = v_{CEn} i_{Cn} = (V_{CC} - V_p \sin \omega t) \left(\frac{V_p}{R_L} \sin \omega t \right) \quad \text{for } 0 \leq \omega t \leq \pi$$

$$P_n = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi$$

$$P_n = \frac{V_{CC}V_p}{R_L} \sin \omega t - \frac{V_p^2}{R_L} \sin^2 \omega t = \frac{V_{CC}V_p}{R_L} \sin \omega t - \frac{V_p^2}{R_L} \left(\frac{1 - \cos 2\omega t}{2} \right)$$

$$= \frac{V_{CC}V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} + \frac{V_p^2 \cos 2\omega t}{2R_L}$$

$$\overline{P_n} = \frac{1}{2\pi} \int_0^\pi \left(\frac{V_{CC}V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} + \frac{V_p^2 \cos 2\omega t}{2R_L} \right) d\omega t$$

$$= \frac{1}{2\pi} \left\{ \frac{V_{CC}V_p}{R_L} [-\cos \omega t]_0^\pi - \frac{V_p^2}{2R_L} [\omega t]_0^\pi + \frac{V_p^2}{2R_L} \left[\frac{1}{2} \sin 2\omega t \right]_0^\pi \right\}$$

$$= \frac{1}{2\pi} \left\{ \frac{2V_{CC}V_p}{R_L} - \frac{\pi V_p^2}{2R_L} + 0 \right\} = \frac{V_{CC}V_p}{\pi R_L} - \frac{V_p^2}{4R_L}$$

Note: The average power dissipated in transistor Q_p is the same.

To determine the maximum average power dissipated in transistor Q_n :


$$\frac{d\overline{P}_n}{dV_p} = \frac{V_{CC}}{\pi R_L} - \frac{V_p}{2R_L} = 0 \Rightarrow V_p = \frac{2V_{CC}}{\pi}$$

$$\overline{P}_n(max) = \frac{V_{CC}}{\pi R_L} \left(\frac{2V_{CC}}{\pi} \right) - \frac{1}{4R_L} \left(\frac{2V_{CC}}{\pi} \right)^2 = \frac{V_{CC}^2}{\pi^2 R_L}$$

Conversion efficiency when $V_p = \frac{2V_{CC}}{\pi}$:

$$\eta = \frac{\pi}{4} \left(\frac{2V_{CC}}{\pi V_{CC}} \right) = \frac{1}{2} = 50\%$$


Class B Amplifier Conversion Efficiency

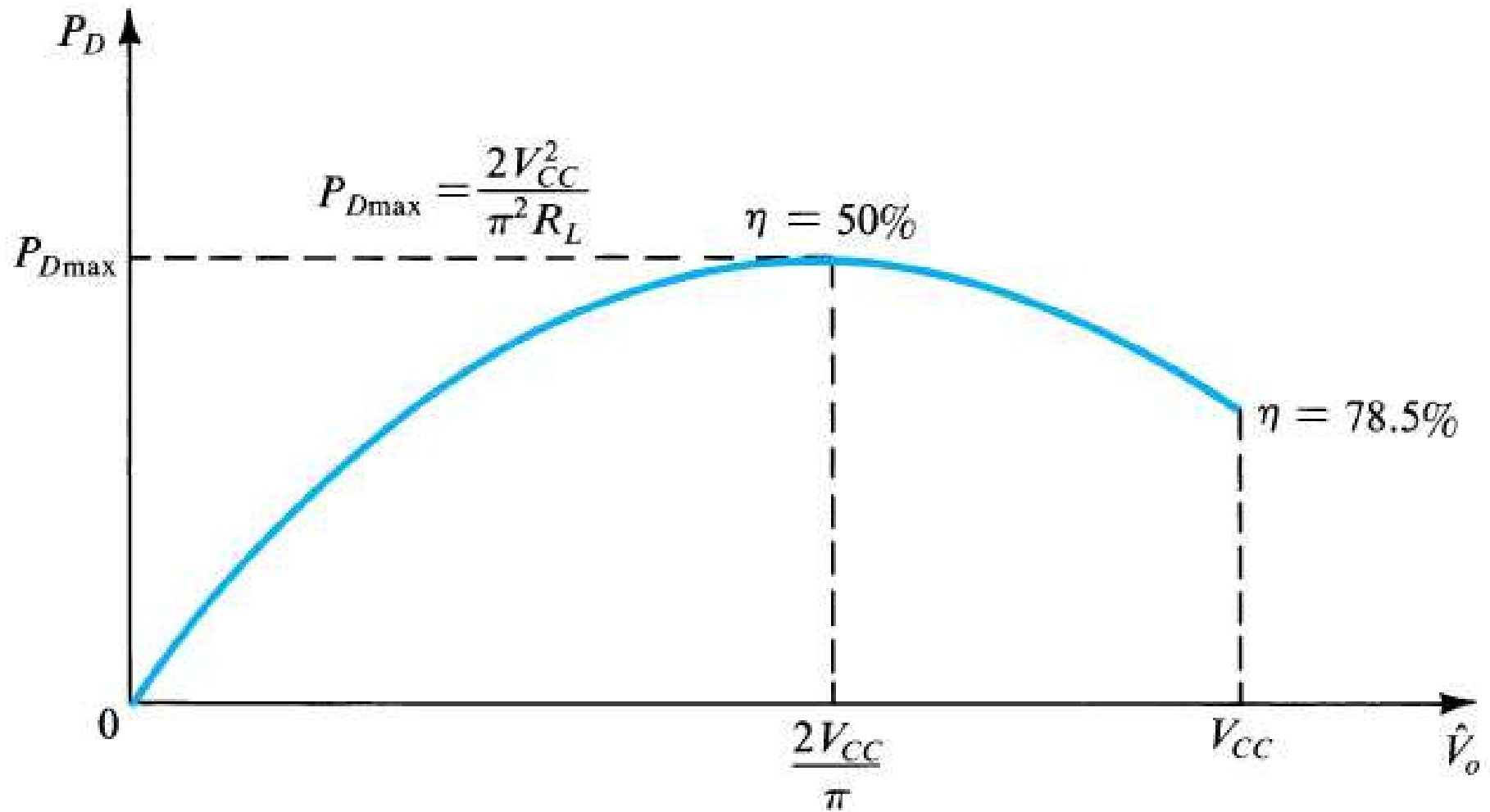

Class AB Amplifiers

Crossover distortion can be eliminated by applying a small bias on each transistor so that the transistor is already turn-on without an input signal.

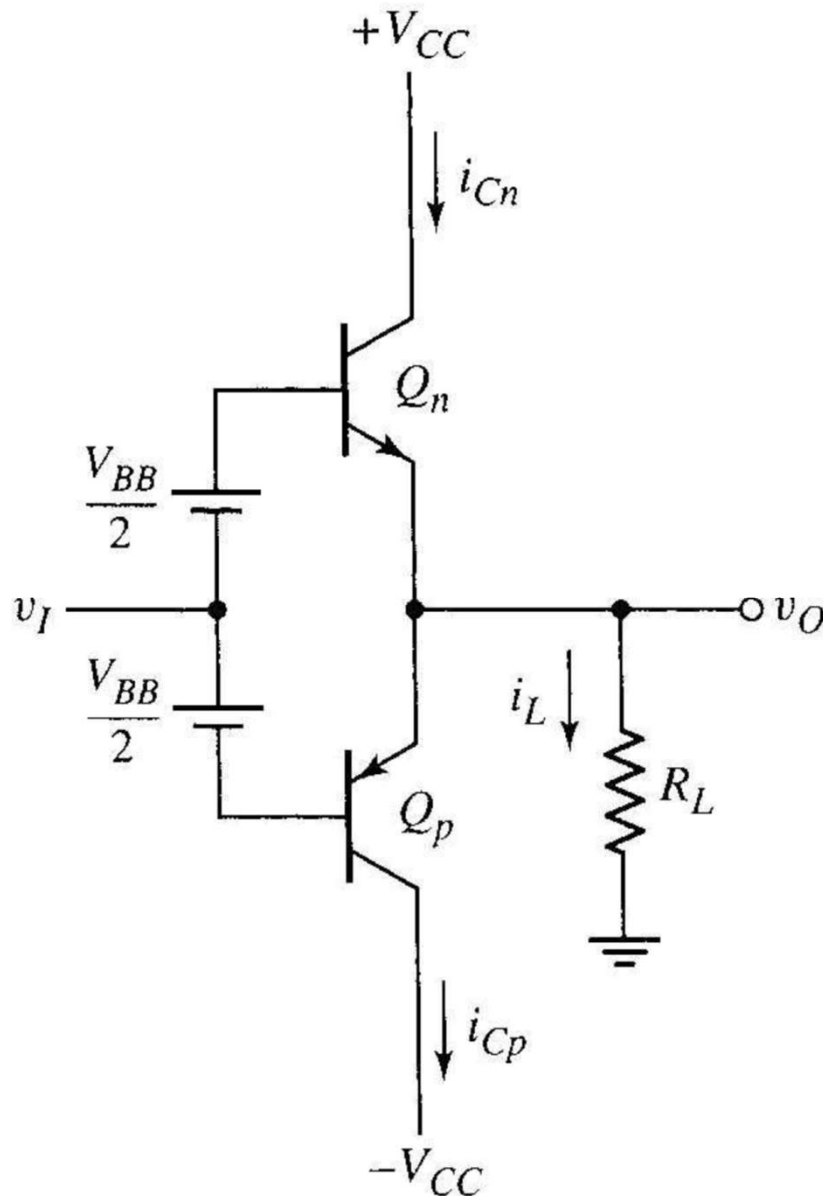When $v_i = 0$, $v_o = 0$, both Q_n and Q_p have the same biasing currents:



$$v_{BE_n} = v_{EB_p} = \frac{V_{BB}}{2}$$

$$i_{C_n} = i_{C_p} = I_{CQ}$$

$$I_{CQ} = I_S e^{\frac{V_{BB}}{2V_T}}$$

Class AB Amplifiers

When v_i is +ve, the output voltage increases and the collector current of Q_n also increases to supply the load current:

$$v_o = v_i + \frac{V_{BB}}{2} - v_{BE_n} \quad i_{Cn} = i_L + i_{Cp}$$

When v_i is -ve, Q_p turns on and sinking the current from the load and the output voltage goes -ve.

The collector currents of both transistors are governed by:

$$v_{BE_n} + v_{EB_p} = V_{BB}$$

$$V_T \ln\left(\frac{i_{Cn}}{I_S}\right) + V_T \ln\left(\frac{i_{Cp}}{I_S}\right) = 2V_T \ln\left(\frac{I_{CQ}}{I_S}\right)$$


$$i_{Cn} i_{Cp} = I_{CQ}^2$$


$$i_{Cn} i_{Cp} = I_{CQ}^2$$

$$i_{Cn} (i_{Cn} - i_L) = I_{CQ}^2$$

$$i_{Cn}^2 - i_L i_{Cn} = I_{CQ}^2$$

Exercise #3: Determine the required biasing for the MOSFET Class AB amplifier so that $I_{DQ} = 20\%$ of the load current when $v_o = 5\text{V}$. Power supply voltage = $\pm 10\text{V}$ and $R_L = 20\ \Omega$. Assume that both transistors are matched with $K_n = K_p = 0.2\text{ A/V}^2$ and $|V_{TN}| = |V_{TP}| = 1\text{ V}$.

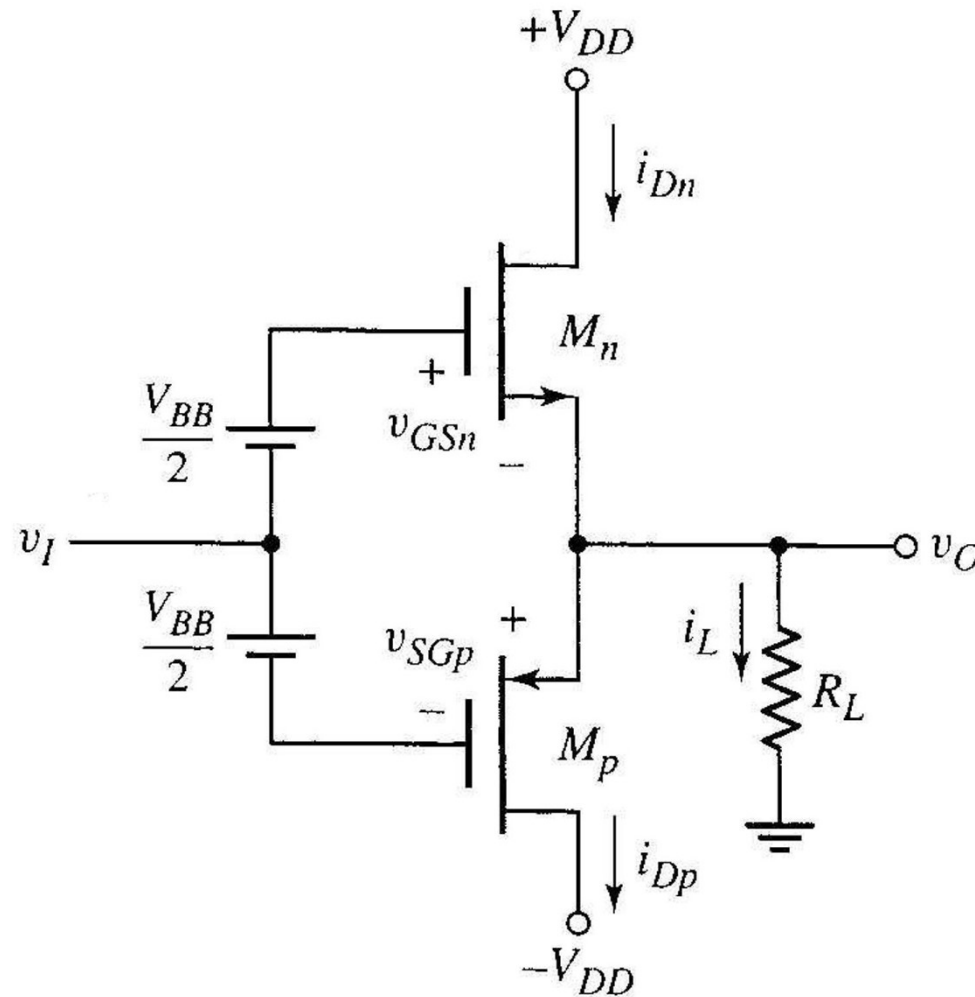

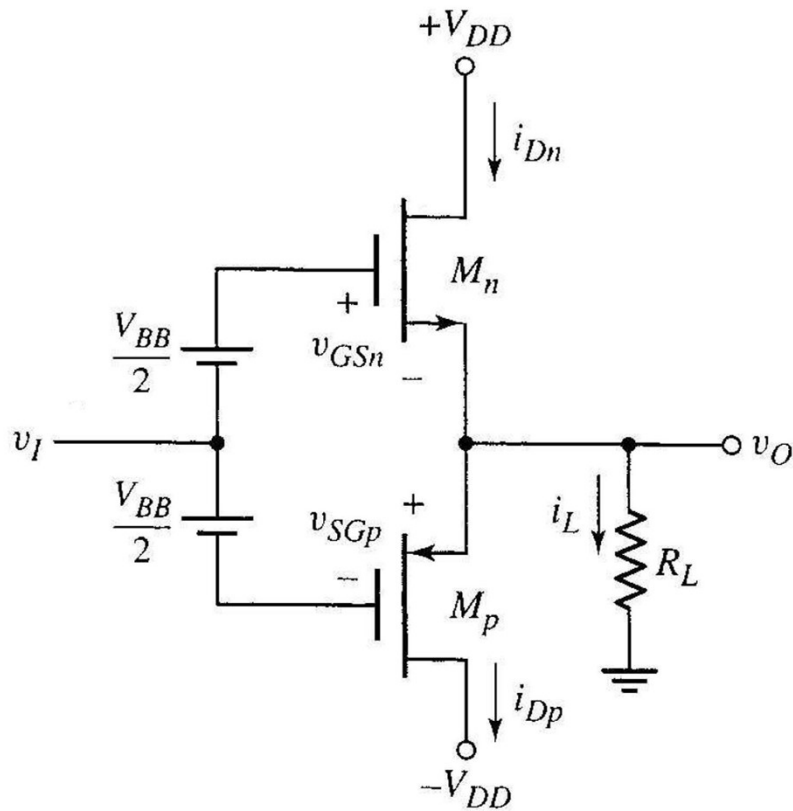

$$\text{When } v_o = 5 \text{ V}, i_L = \frac{v_o}{R_L} = \frac{5}{20} = 250 \text{ mA}$$

$$I_{DQ} = 0.2 \times 250 \text{ mA} = 50 \text{ mA}$$

$$\text{When } v_o = 0, i_L = 0, i_{Dn} = i_{Dp} = I_{DQ} = 50 \text{ mA}$$


$$\therefore v_{GSn} = v_{SGp} = \frac{V_{BB}}{2}$$

$$i_{Dn} = i_{Dp} = K \left(\frac{V_{BB}}{2} - |V_T| \right)^2 = 50 \text{ mA}$$

$$(0.2) \left(\frac{V_{BB}}{2} - 1 \right)^2 = 0.05 \text{ A} \Rightarrow \frac{V_{BB}}{2} = 1.5 \text{ V}$$

$$v_{GSn} = v_{SGp} = \frac{V_{BB}}{2} = 1.5 \text{ V}$$
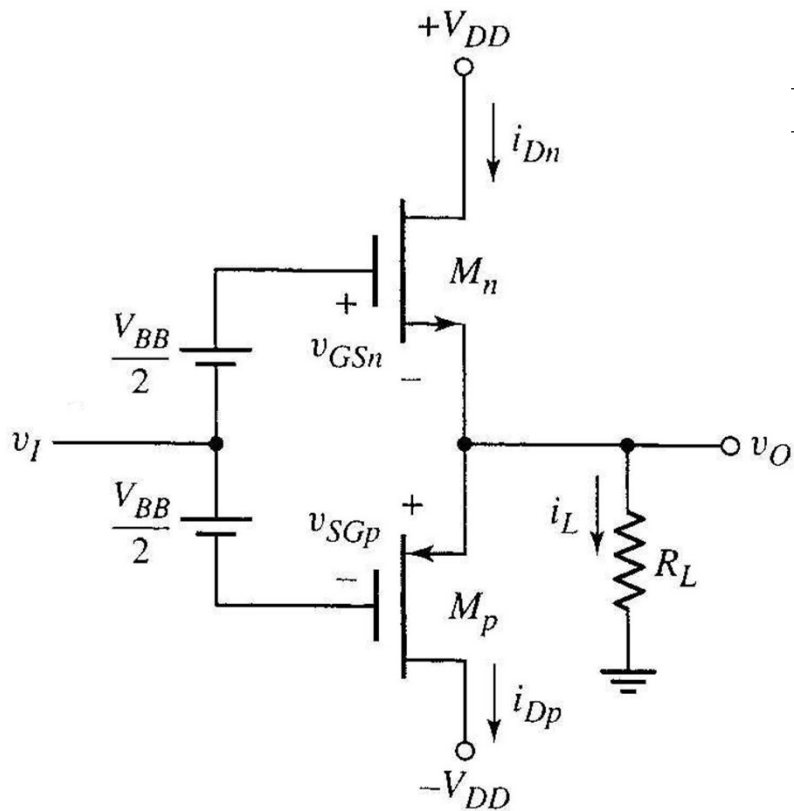
$$v_i = v_o + v_{GSn} - \frac{V_{BB}}{2} = 0 + 1.5 - 1.5 = 0 \text{ V}$$



For $v_o = 5\text{ V}$, $i_{Dp} \approx 0$, $i_{Dn} \approx i_L = 250\text{ mA}$

$$i_{Dn} = K(v_{GSn} - |V_T|)^2 = 0.25\text{ A}$$

$$v_{GSn} = \sqrt{\frac{i_{Dn}}{K}} + |V_T| = \sqrt{\frac{0.25}{0.2}} + 1 = 2.12\text{ V}$$


$$v_{SGp} = V_{BB} - v_{GSn} = 3 - 2.12 = 0.88\text{ V}$$

$$\because v_{SGp} = 0.88\text{ V} < V_T = 1\text{ V}$$

It confirms that M_p is in cut off, $i_{Dp} = 0$ and $i_{Dn} = i_L$.

$$v_i = v_o + v_{GSn} - \frac{V_{BB}}{2} = 5 + 2.12 - 1.5 = 5.62\text{ V}$$

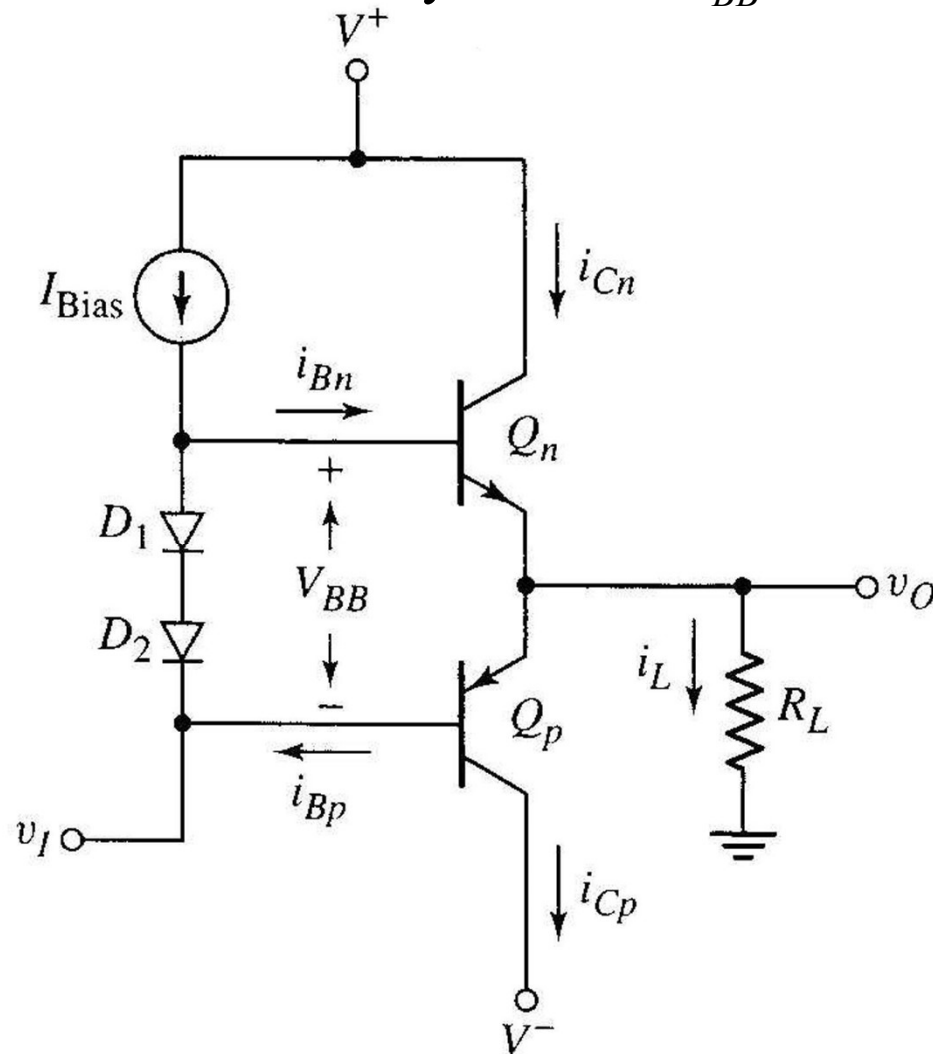Exercise #4: Design the following BJT Class AB amplifier so that the average power to the load is 5 W and $R_L = 8 \Omega$. The peak output voltage is not more than 80% of V_{CC} to ensure good linearity. The diode current cannot be less than 5 mA to maintain a nearly constant V_{BB} .



$$I_{SD} = 3 \times 10^{-14} \text{ A for } D_1 \text{ and } D_2$$

$$I_{SQ} = 10^{-13} \text{ A for } Q_n \text{ and } Q_p$$

$$\beta_n = \beta_p = 75$$

$$\bar{P}_L = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = \sqrt{2R_L \bar{P}_L} = \sqrt{2(8)(5)} = 8.94\text{V}$$

$$V_{CC} = \frac{V_p}{0.8} = \frac{8.94}{0.8} = 11.2\text{ V}$$

At the peak of output voltage,


$$i_L = \frac{V_p}{R_L} = \frac{8.94}{8} = 1.12\text{ A}$$

$$i_{En} = i_L + i_{Ep} = 1.12 + i_{Ep}$$

$$\frac{i_{Cn}}{\alpha} = i_L + \frac{i_{Cp}}{\alpha} \Rightarrow i_{Cn} = \alpha i_L + i_{Cp} \Rightarrow i_{Cn} \approx i_L + i_{Cp}$$

$$V_{BB} = v_{BE n} + v_{EB p} \Rightarrow 2V_D = v_{BE n} + v_{EB p}$$
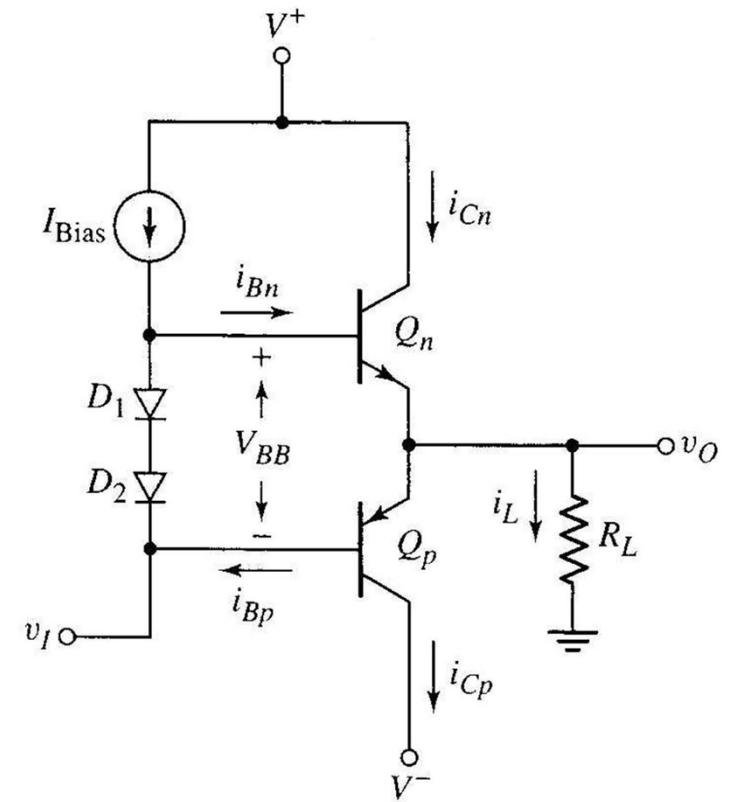
$$2V_T \ln\left(\frac{I_D}{I_{SD}}\right) = V_T \ln\left(\frac{i_{Cn}}{I_{SQ}}\right) + V_T \ln\left(\frac{i_{Cp}}{I_{SQ}}\right)$$



$$\therefore \frac{I_D^2}{I_{SD}^2} = \frac{i_{Cn} i_{Cp}}{I_{SQ}^2} \Rightarrow i_{Cn} i_{Cp} = \left(\frac{I_{SQ}}{I_{SD}}\right)^2 I_D^2$$

$$i_{Cn} i_{Cp} = \left(\frac{10^{-13}}{3 \times 10^{-14}}\right)^2 I_D^2$$

$$i_{Cn} i_{Cp} = 11.11 I_D^2$$

$$i_{Cn}i_{Cp} = 11.11I_D^2$$

$$i_{Cn}(i_{Cn} - i_L) = 11.11I_D^2$$

$$i_{Cn}(i_{Cn} - 1.12) = 11.11(5 \times 10^{-3})^2 = 2.78 \times 10^{-4} \approx 0$$

$$i_{Cn} = 0 \text{ or } i_{Cn} = 1.12 \text{ A (take } i_{Cn} = 1.12 \text{ A)}$$


$$i_{Cp} = i_{Cn} - i_L = 1.12 - 1.12 = 0$$

$$i_{Bn} = \frac{i_{Cn}}{\beta} = \frac{1.12}{75} = 14.93 \text{ mA}$$

$$I_{Bias} = I_D + i_{Bn} = 5 \text{ mA} + 14.93 \text{ mA} \approx 20 \text{ mA}$$

$$V_{BB} = 2V_T \ln\left(\frac{I_D}{I_{SD}}\right) = 2(0.026) \ln\left(\frac{5 \times 10^{-3}}{3 \times 10^{-14}}\right) = 1.344 \text{ V}$$
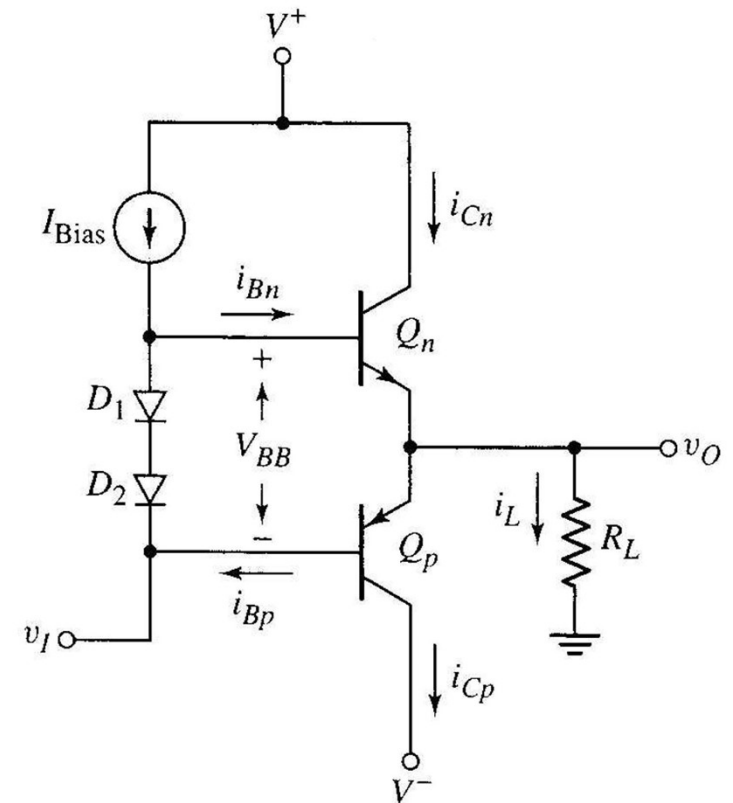
$$v_{BE_n} = V_T \ln\left(\frac{i_{Cn}}{I_{SQ}}\right) = (0.026) \ln\left(\frac{1.12}{10^{-13}}\right) = 0.781 \text{ V}$$



$$\begin{aligned} v_{EBp} &= V_{BB} - v_{BE_n} \\ &= 1.344 - 0.781 \\ &= 0.563 \text{ V} \end{aligned}$$

$$i_{Cp} = I_{SQ} e^{\frac{v_{EBp}}{V_T}} = 10^{-13} e^{\frac{0.563}{0.026}} = 0.25 \text{ mA}$$

When $v_o = 0$:

$$i_{Cn}(i_{Cn} - i_L) = 11.11 I_D^2$$

$$i_{Cn}(i_{Cn} - 0) = 11.11 \left(20 \times 10^{-3} - \frac{i_{Cn}}{75} \right)^2$$

$$i_{Cn}^2 = 0.0044 - 0.006 i_{Cn} - 0.002 i_{Cn}^2$$

$$0.998 i_{Cn}^2 + 0.006 i_{Cn} - 0.0044 = 0$$


$$i_{Cn} = \frac{-0.006 \pm \sqrt{0.006^2 - 4 \times 0.998 \times 0.0044}}{2 \times 0.998}$$

$$i_{Cn} = 63.46 \text{ mA (take + ve value)}$$

$$i_{Cp} = i_{Cn} = 63.46 \text{ mA}$$

$$i_{Bn} = \frac{i_{Cn}}{\beta} = \frac{63.46 \text{ mA}}{75} = 0.846 \text{ mA}$$
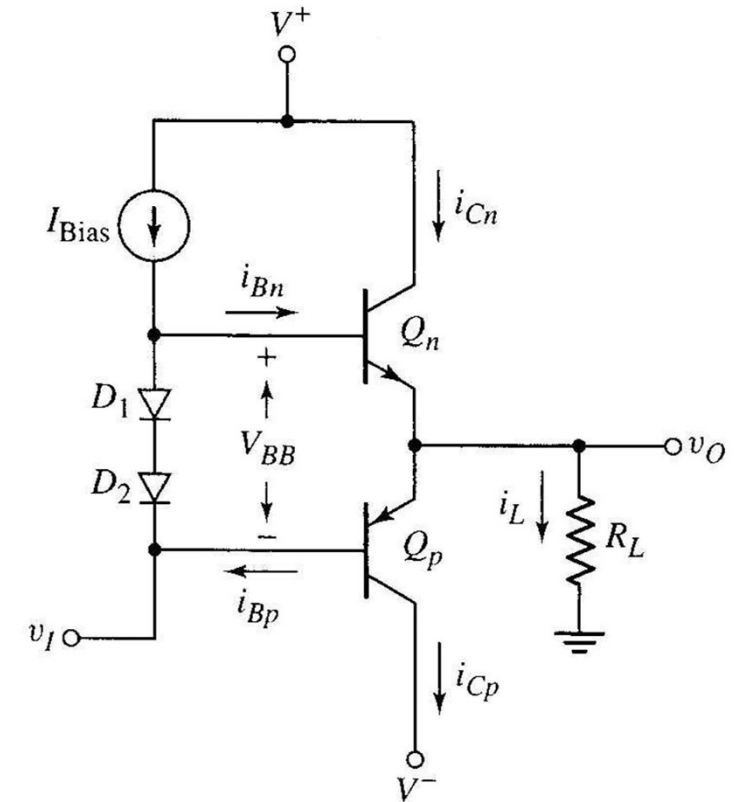
$$I_D = I_{Bias} - i_{Bn} = 20 \text{ mA} - 0.846 \text{ mA} \approx 19.15 \text{ mA}$$




$$V_{BB} = 2(0.026) \ln \left(\frac{19.15 \times 10^{-3}}{3 \times 10^{-14}} \right) = 1.413 \text{ V}$$

$$v_{BE} = (0.026) \ln \left(\frac{63.46 \times 10^{-3}}{10^{-13}} \right) = 0.707 \text{ V}$$

$$v_{EB} = 1.413 - 0.707 = 0.707 \text{ V}$$

Class C Amplifiers

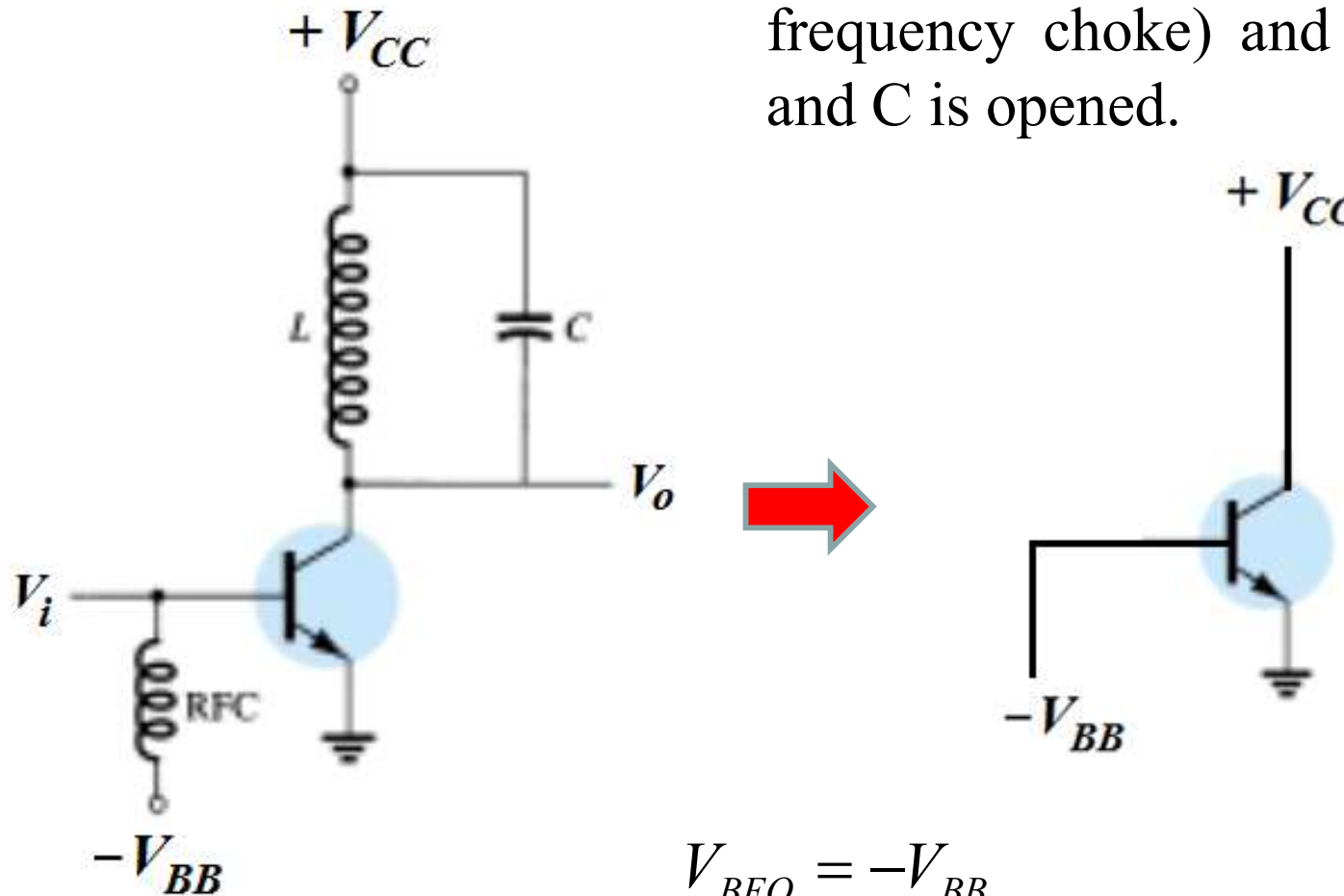
Under DC condition, both RFC (radio frequency choke) and L are shorted and C is opened.




$$V_{BEQ} = -V_{BB}$$

\therefore The BJT is reversed biased.

Class C Amplifiers

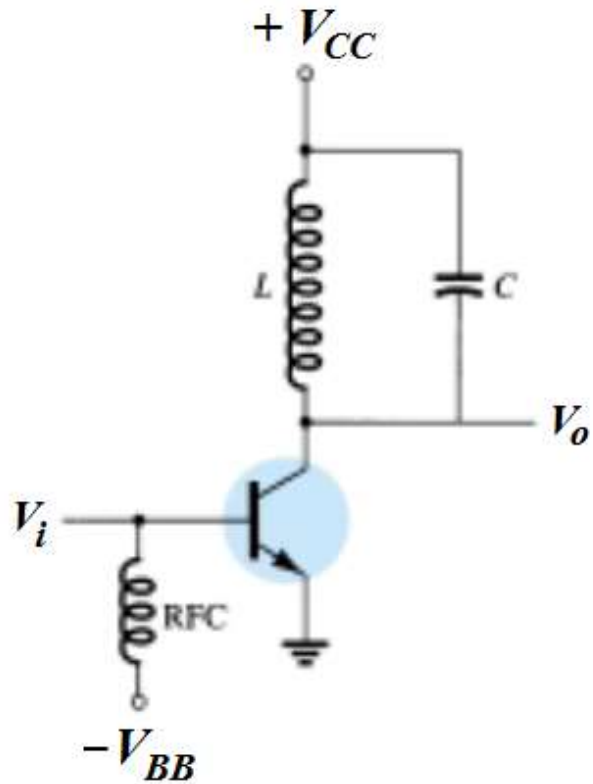

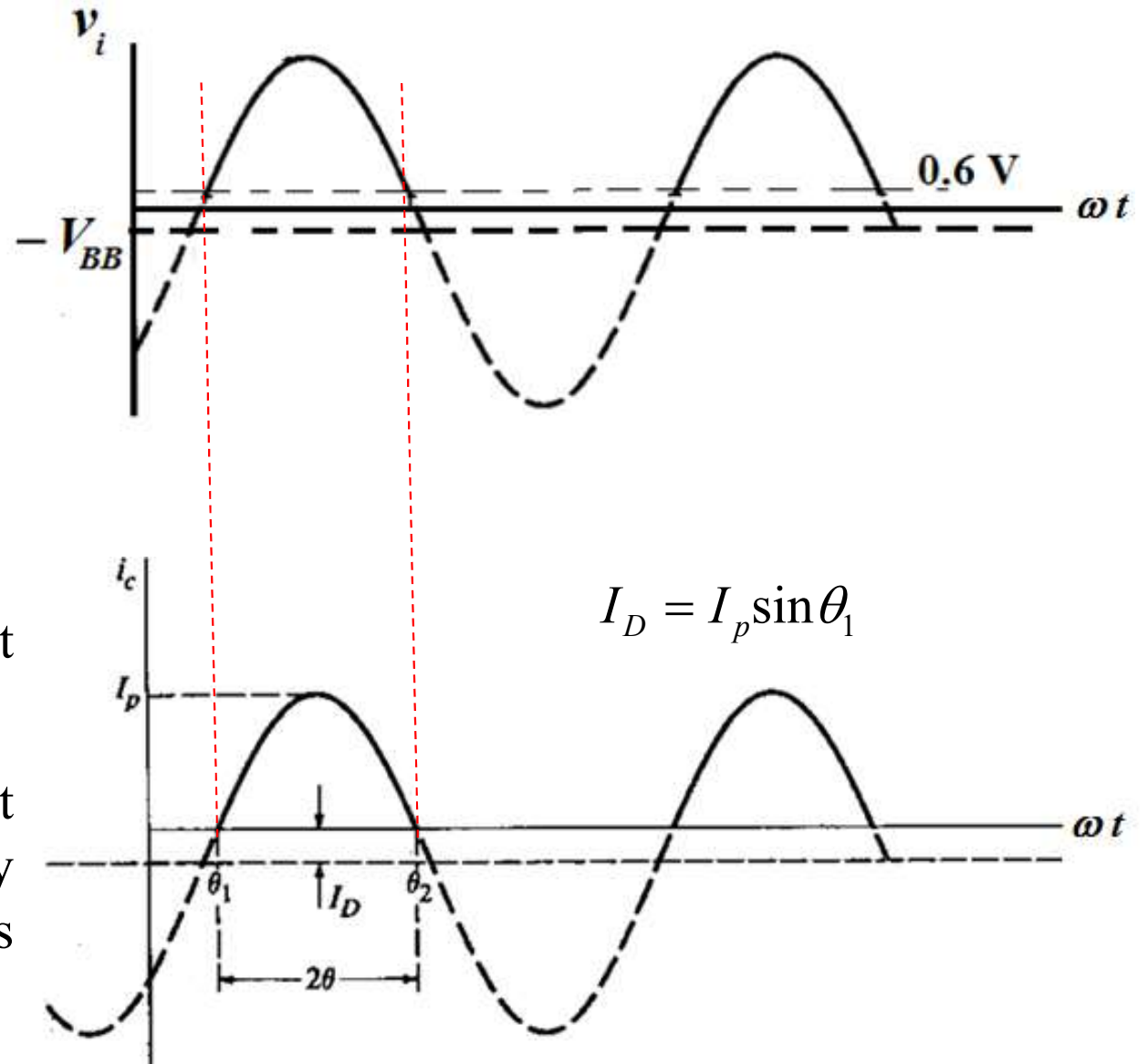- The transistor is reversed bias at the Q point
- It conducts only when the input signal becomes sufficiently positive, i.e. it conducts less than half a cycle.



Fourier Series

For any periodic function, it can be expressed in terms of a DC component and a series of harmonics:

$$f(x) = a_o + \sum_{n=1}^{\infty} (a_n \cos nx + b_n \sin nx)$$


Its average component is given by:

$$a_o = \frac{1}{2\pi} \int_{-\pi}^{\pi} f(x) dx$$

Its harmonics, $n = 1, 2, 3 \dots$ can be determined by:

$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos nxdx$$
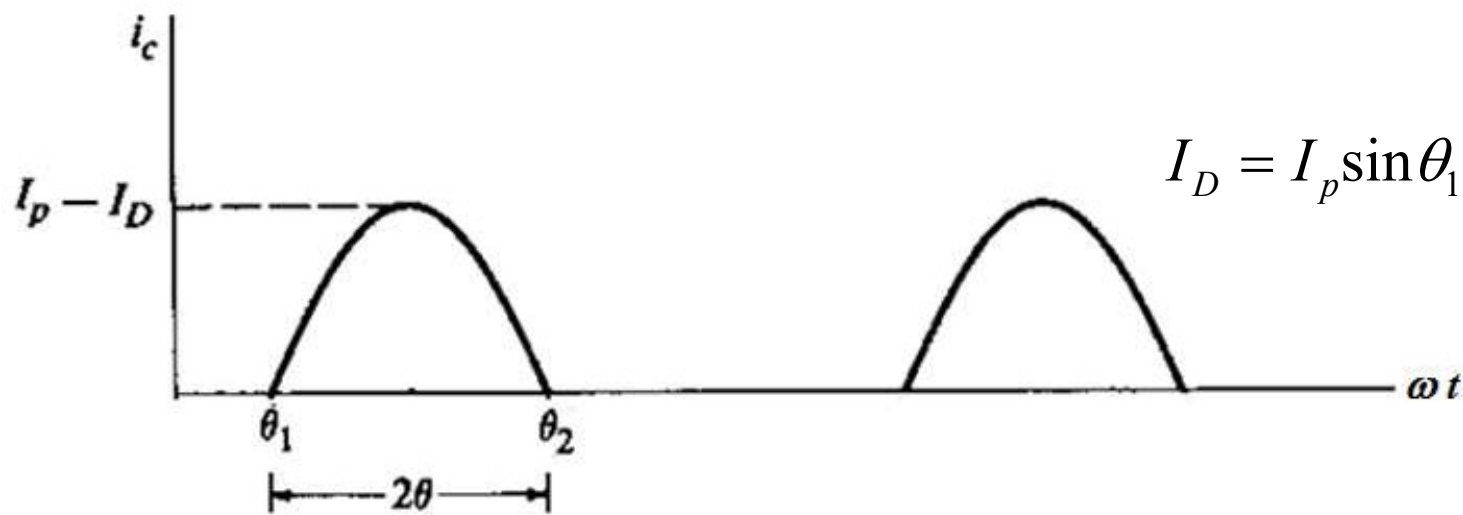
$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin nxdx$$



The collector current is given by:
$$i_c = \begin{cases} I_p \sin \omega t - I_D & \theta_1 \leq \omega t \leq \theta_2 \\ 0 & \text{otherwise} \end{cases}$$


For any periodic function, it can be expressed mathematically by:

$$i_c(\omega t) = a_o + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

Its average component is given by:
$$a_o = \frac{1}{2\pi} \int_{-\pi}^{\pi} i_c(\omega t) d\omega t$$


Its harmonic components ($n = 1, 2, 3 \dots$) are given by:
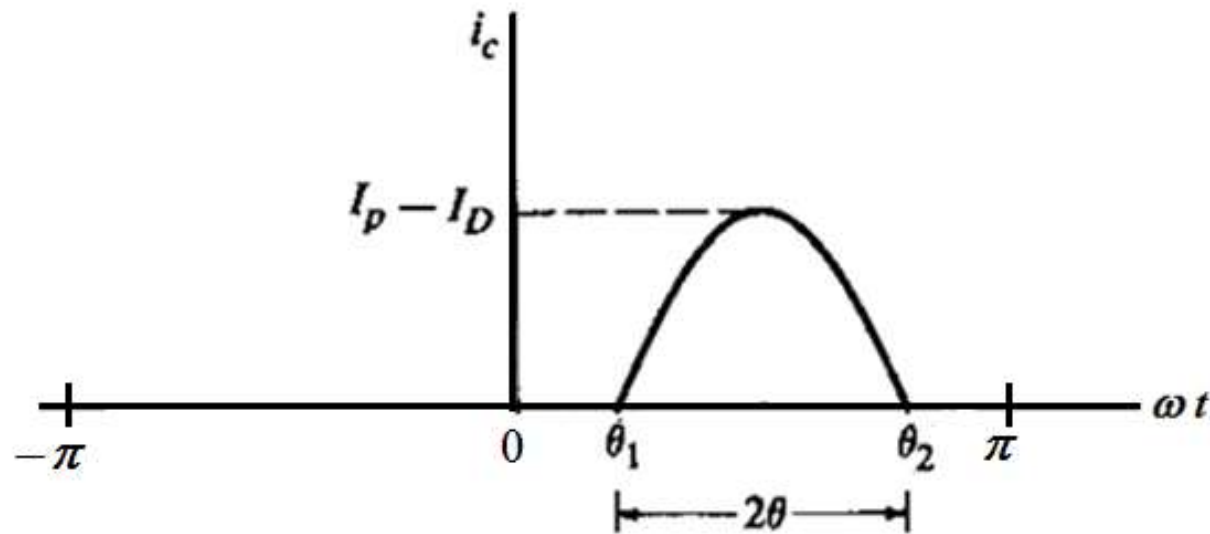
$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} i_c(\omega t) \cos n\omega t d\omega t \quad b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} i_c(\omega t) \sin n\omega t d\omega t$$



The average collector current:
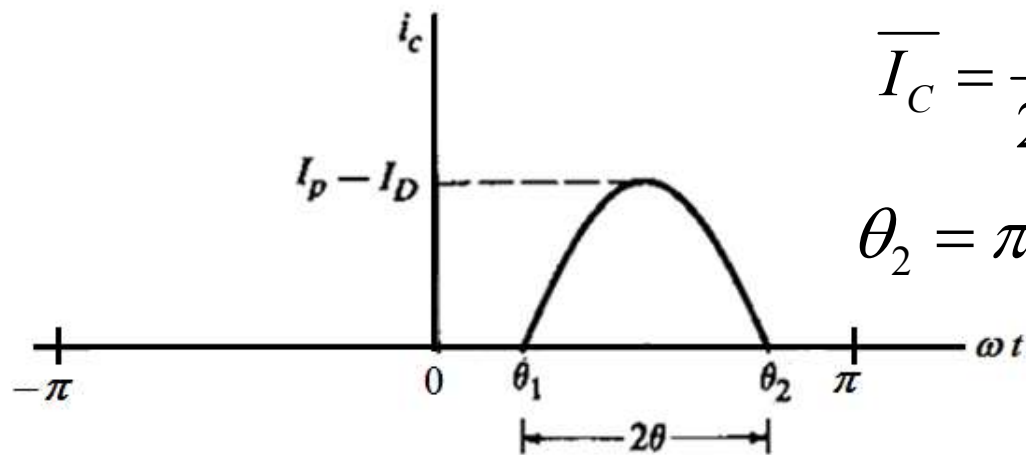
$$\begin{aligned}
 \overline{I_C} &= a_o = \frac{1}{2\pi} \int_{-\pi}^{\pi} (I_p \sin \omega t - I_D) d\omega t \\
 &= \frac{1}{2\pi} \int_{\theta_1}^{\theta_2} (I_p \sin \omega t - I_D) d\omega t = \frac{1}{2\pi} [-I_p \cos \omega t - I_D \omega t]_{\theta_1}^{\theta_2} \\
 &= \frac{1}{2\pi} [I_p (\cos \theta_1 - \cos \theta_2) - I_D (\theta_2 - \theta_1)]
 \end{aligned}$$



$$\overline{I_C} = \frac{1}{2\pi} [I_p (\cos \theta_1 - \cos \theta_2) - I_D (\theta_2 - \theta_1)]$$

$$\theta_2 = \pi - \theta_1, \cos \theta_2 = \cos(\pi - \theta_1) = -\cos \theta_1$$

$$I_D = I_p \sin \theta_1$$

$$\therefore \overline{I_C} = \frac{1}{2\pi} [2I_p \cos \theta_1 - I_p \sin \theta_1 (\theta_2 - \theta_1)]$$

The conduction angle can be defined as:

$$2\theta = \theta_2 - \theta_1 \quad \text{or} \quad \theta_1 = \frac{\pi}{2} - \theta$$

$$\overline{I_C} = \frac{1}{2\pi} \left[2I_p \cos \left(\frac{\pi}{2} - \theta \right) - 2\theta I_p \sin \left(\frac{\pi}{2} - \theta \right) \right] = \frac{I_p}{\pi} (\sin \theta - \theta \cos \theta)$$

If I_1 is the amplitude of the fundamental current components which is determined by the trigonometric Fourier series:

$$\begin{aligned}
 a_1 &= \frac{1}{\pi} \int_{-\pi}^{\pi} (I_p \sin \omega t - I_D) \cos \omega t d\omega t \\
 &= \frac{1}{\pi} \int_{\theta_1}^{\theta_2} (I_p \sin \omega t - I_D) \cos \omega t d\omega t = \frac{1}{\pi} \int_{\theta_1}^{\theta_2} (I_p \sin \omega t \cos \omega t - I_D \cos \omega t) d\omega t \\
 &= \frac{1}{\pi} \int_{\theta_1}^{\theta_2} \left(\frac{I_p \sin 2\omega t}{2} - I_D \cos \omega t \right) d\omega t = \frac{1}{\pi} \left[\frac{-I_p \cos 2\omega t}{4} - I_D \sin \omega t \right]_{\theta_1}^{\theta_2} \\
 &= \frac{1}{4\pi} [I_p (\cos 2\theta_1 - \cos 2\theta_2) - I_D (\sin \theta_2 - \sin \theta_1)]
 \end{aligned}$$

$$\theta_2 = \pi - \theta_1 :$$

$$\cos 2\theta_2 = \cos(2\pi - 2\theta_1) = \cos 2\theta_1, \quad \sin \theta_2 = \sin(\pi - \theta_1) = \sin \theta_1$$

$$\therefore a_1 = 0$$

$$\begin{aligned}
b_1 &= \frac{1}{\pi} \int_{-\pi}^{\pi} (I_p \sin \omega t - I_D) \sin \omega t d\omega t \\
&= \frac{1}{\pi} \int_{\theta_1}^{\theta_2} (I_p \sin \omega t - I_D) \sin \omega t d\omega t = \frac{1}{\pi} \int_{\theta_1}^{\theta_2} (I_p \sin^2 \omega t - I_D \sin \omega t) d\omega t \\
&= \frac{1}{\pi} \int_{\theta_1}^{\theta_2} \left(\frac{I_p (1 - \cos 2\omega t)}{2} - I_D \sin \omega t \right) d\omega t = \frac{1}{\pi} \left[\frac{I_p \omega t}{2} - \frac{I_p \sin 2\omega t}{4} + I_D \cos \omega t \right]_{\theta_1}^{\theta_2} \\
&= \frac{1}{\pi} \left[\frac{I_p}{2} (\theta_2 - \theta_1) - \frac{I_p}{4} (\sin 2\theta_2 - \sin 2\theta_1) + I_D (\cos \theta_2 - \cos \theta_1) \right]
\end{aligned}$$

$$\theta_2 = \pi - \theta_1 \text{ and } \theta_2 - \theta_1 = 2\theta$$

$$\sin 2\theta_2 = \sin(2\pi - 2\theta_1) = -\sin 2\theta_1, \quad \cos \theta_2 = \cos(\pi - \theta_1) = -\cos \theta_1$$

$$\therefore b_1 = \frac{1}{\pi} \left[I_p \theta + \frac{I_p}{2} \sin 2\theta_1 - 2I_D \cos \theta_1 \right]$$

$$\begin{aligned}
b_1 &= \frac{1}{\pi} \left[I_p \theta + \frac{I_p}{2} \sin 2\theta_1 - 2I_D \cos \theta_1 \right] \\
&= \frac{1}{\pi} \left[I_p \theta + \frac{I_p}{2} \sin 2\theta_1 - 2I_p \sin \theta_1 \cos \theta_1 \right] \\
&= \frac{I_p}{\pi} [\theta + \sin \theta_1 \cos \theta_1 - 2 \sin \theta_1 \cos \theta_1] \\
&= \frac{I_p}{\pi} [\theta - \sin \theta_1 \cos \theta_1] = \frac{I_p}{\pi} \left(\theta - \sin \left(\frac{\pi}{2} - \theta \right) \cos \left(\frac{\pi}{2} - \theta \right) \right) \\
&= \frac{I_p}{\pi} (\theta - \cos \theta \sin \theta) = \frac{I_p}{\pi} \left(\theta - \frac{\sin 2\theta}{2} \right) = \frac{I_p}{2\pi} (2\theta - \sin 2\theta)
\end{aligned}$$

The fundamental current component is: $I_1 = \frac{I_p}{2\pi} (2\theta - \sin 2\theta)$

$$i_c(\omega t) = \underbrace{\frac{I_p}{\pi} (\sin \theta - \theta \cos \theta)}_{\text{DC current}} + \underbrace{\frac{I_p}{2\pi} (2\theta - \sin 2\theta) \sin \omega t}_{\text{Fundamental component of the current}}$$

$$I_1 = \frac{I_p}{2\pi} (2\theta - \sin 2\theta) \quad \overline{I_C} = \frac{I_p}{\pi} (\sin \theta - \theta \cos \theta)$$

▣ The output power to load:

$$\overline{P_L} = \frac{1}{2} V_{CC} I_1 = \frac{V_{CC} I_p}{4\pi} (2\theta - \sin 2\theta)$$


▣ The power drawn from supply:

$$\overline{P_S} = V_{CC} \overline{I_C} = \frac{V_{CC} I_p}{\pi} (\sin \theta - \theta \cos \theta)$$

▣ Conversion efficiency:

$$\begin{aligned} \eta = \frac{\overline{P_L}}{\overline{P_S}} &= \frac{V_{CC} I_p (2\theta - \sin 2\theta)}{4\pi} \times \frac{\pi}{V_{CC} I_p (\sin \theta - \theta \cos \theta)} \\ &= \frac{2\theta - \sin 2\theta}{4(\sin \theta - \theta \cos \theta)} \end{aligned}$$


Class C Amplifier Conversion Efficiency

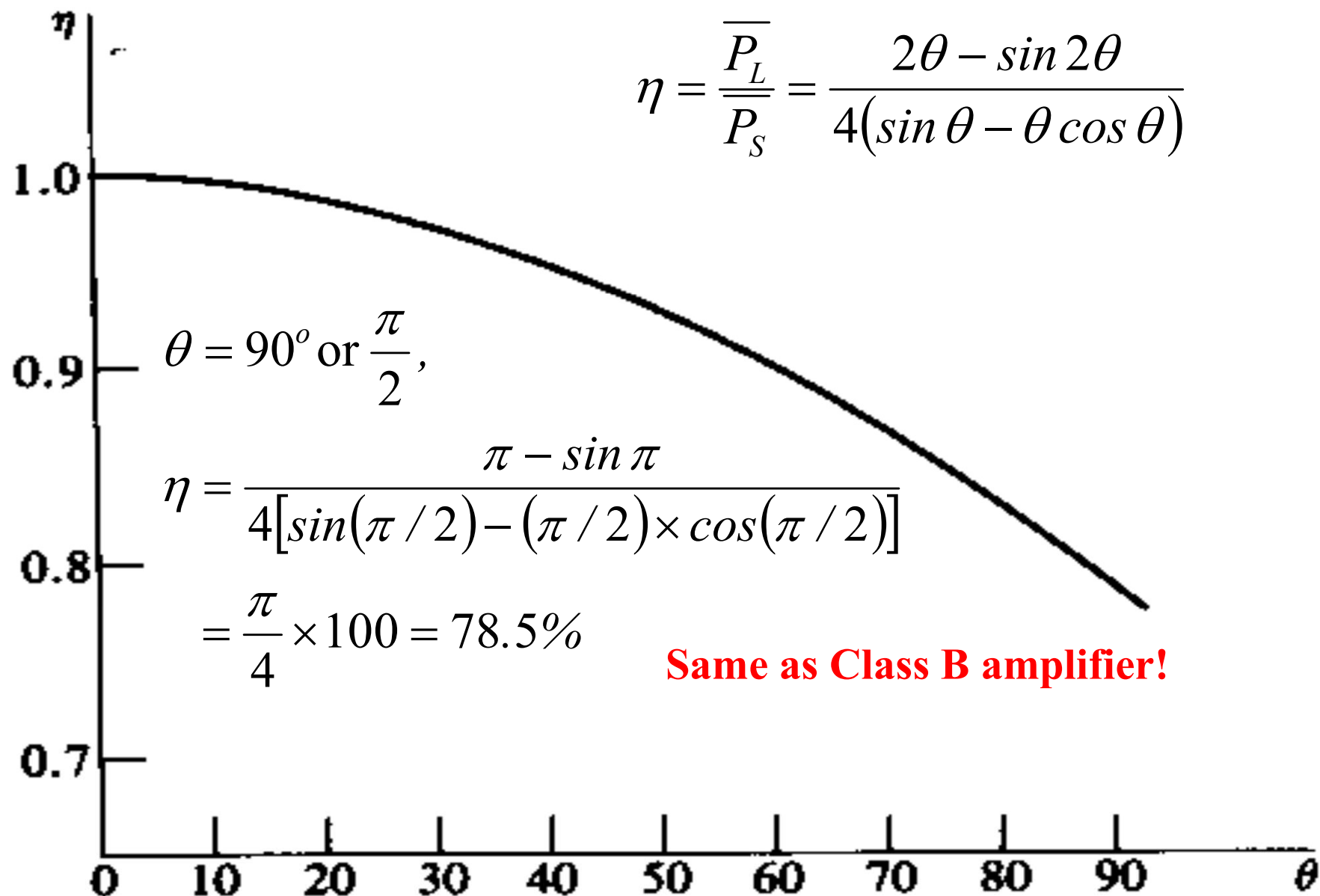

Class D Amplifiers

- ❖ Class D amplifier is a pulse-width modulated (PWM) circuit.
- ❖ Conversion efficiency as high as 90% is achievable and therefore commonly used for very high power (400-600 W) amplifier stage.
- ❖ As PWM requires switching frequencies of 200-500 kHz, electromagnetic interference (EMI) issue has to be considered in the design.

Concept of PWM

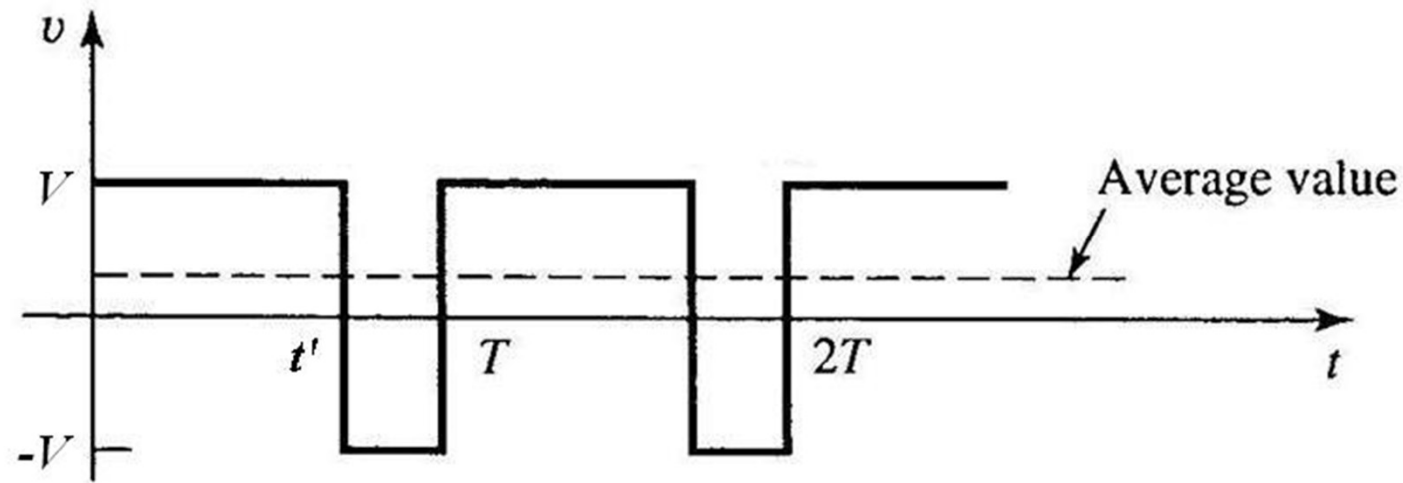


$$d = \frac{t'}{T}$$
$$\therefore t' = dT$$


$$V_{av} = \frac{1}{T} \left[\int_0^{dT} V dt + \int_{dT}^T (-V) dt \right] = \frac{1}{T} [VdT + (-VT + VdT)]$$
$$= \frac{1}{T} [2VdT - VT] = \frac{VT}{T} [2d - 1] = V[2d - 1]$$

Concept of PWM


$$V_{av} = V[2d - 1]$$

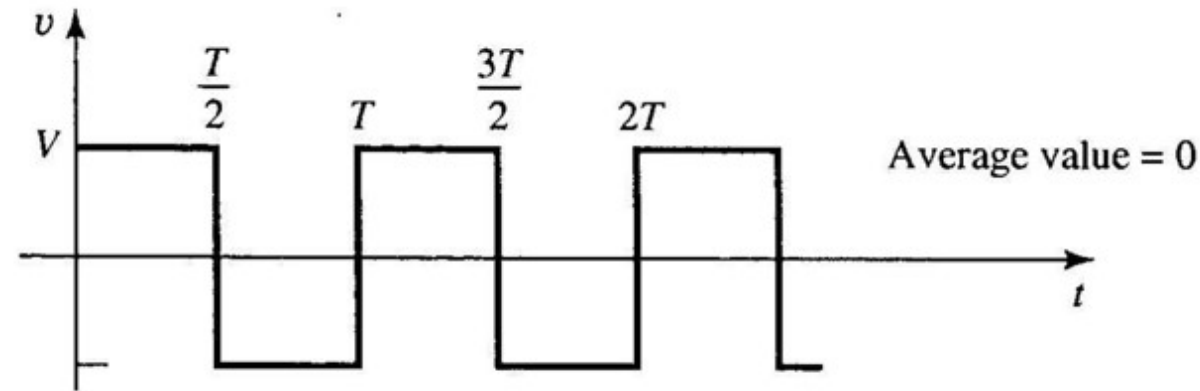

$$V_{av} = V[2(0.5) - 1] = 0$$

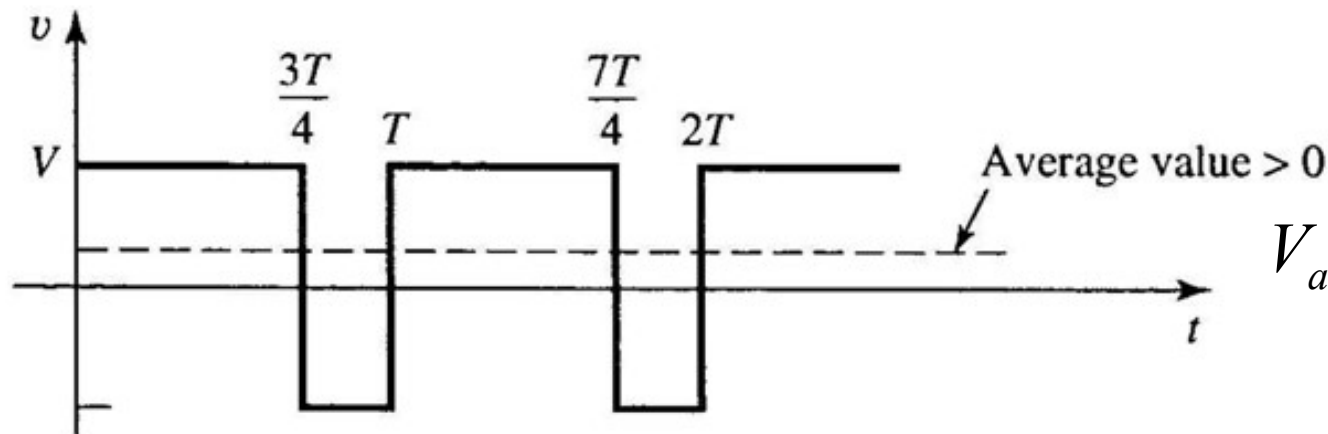


$$V_{av} = V[2(0.75) - 1] = 0.5V$$

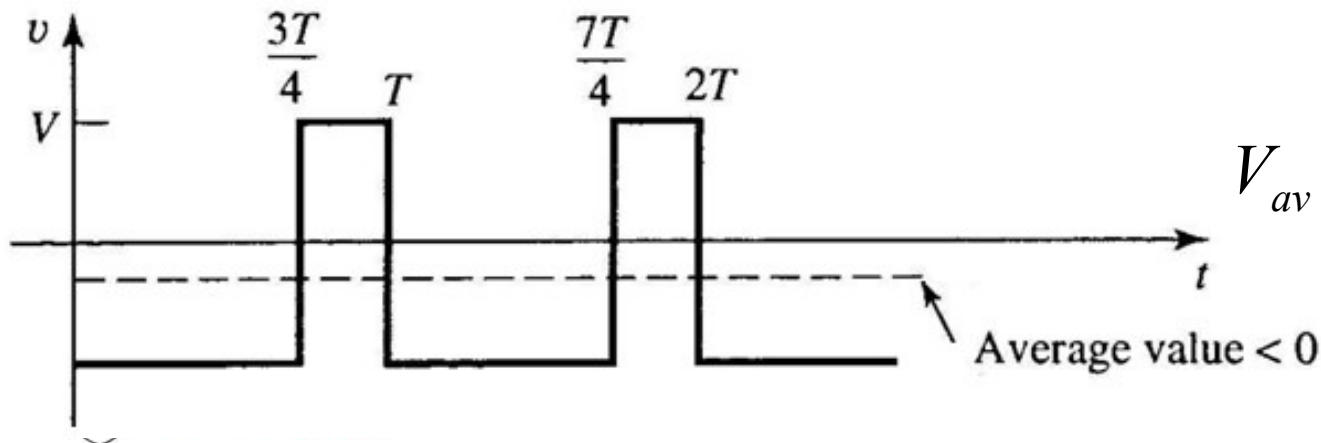

$$V_{av} = V[2(0.25) - 1] = -0.5V$$

Generation of PWM Signal

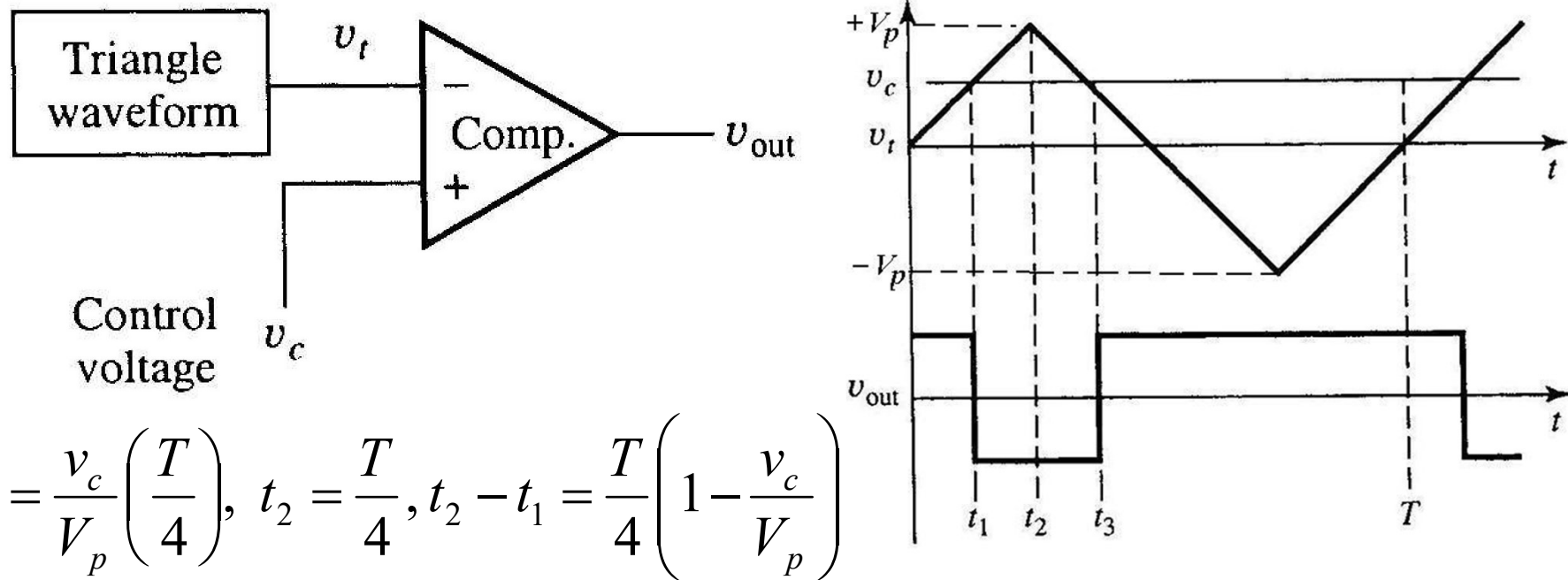

$$t_1 = \frac{v_c}{V_p} \left(\frac{T}{4} \right), \quad t_2 = \frac{T}{4}, \quad t_2 - t_1 = \frac{T}{4} \left(1 - \frac{v_c}{V_p} \right)$$

$$t^- = 2(t_2 - t_1) = \frac{T}{2} \left(1 - \frac{v_c}{V_p} \right) \quad t^+ = T - t^- = \frac{T}{2} \left(1 + \frac{v_c}{V_p} \right)$$

$$d = \frac{t^+}{T} = \frac{(T/2)(1 + v_c/V_p)}{T} = 0.5 + \frac{v_c}{2V_p} = 0.5 + kv_c \quad k = \frac{1}{2V_p}$$

$$V_{av} = V(2d - 1)$$


$$d = 0.5 + kv_c$$

If $v_c = \sin \omega t$, then : $d = 0.5 + k \sin \omega t$

$$V_{av} = V(2d - 1) = V[2(0.5 + k \sin \omega t) - 1] = 2Vk \sin \omega t$$

- ❖ d can be varied sinusoidally by making v_c a sinusoidal signal instead of a constant DC voltage
- ❖ then the average signal of the PWM signal will be a sinusoidal signal too.

Class D Amplifier


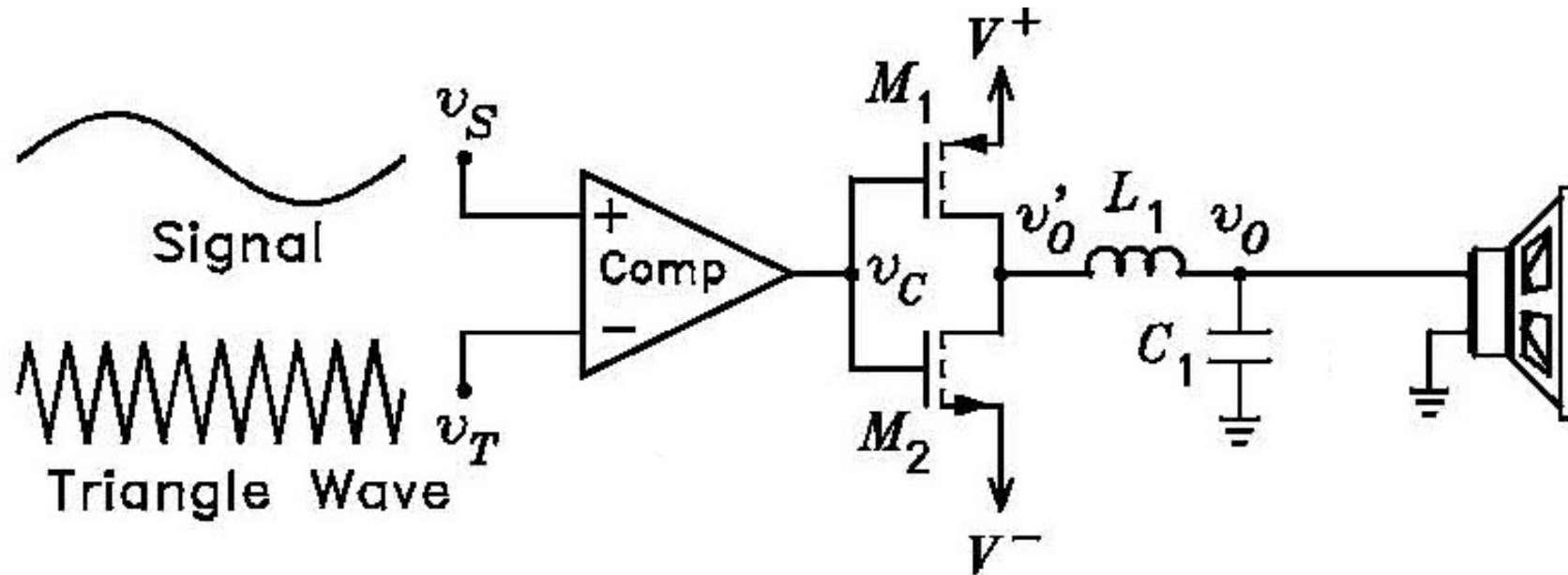


If $d = 0.5 + k \sin \omega t$


$$V_{av} = V(2d - 1) = V(1 + 2k \sin \omega t - 1) = 2kV \sin \omega t$$

By having the low-pass filter, only the average component of the PWM waveform appeared at the load and other higher harmonics of ω are eliminated. Note: when there is no input sinusoidal signal to the PWM circuit, $d = 0.5$ and $V_{av} = 0$.

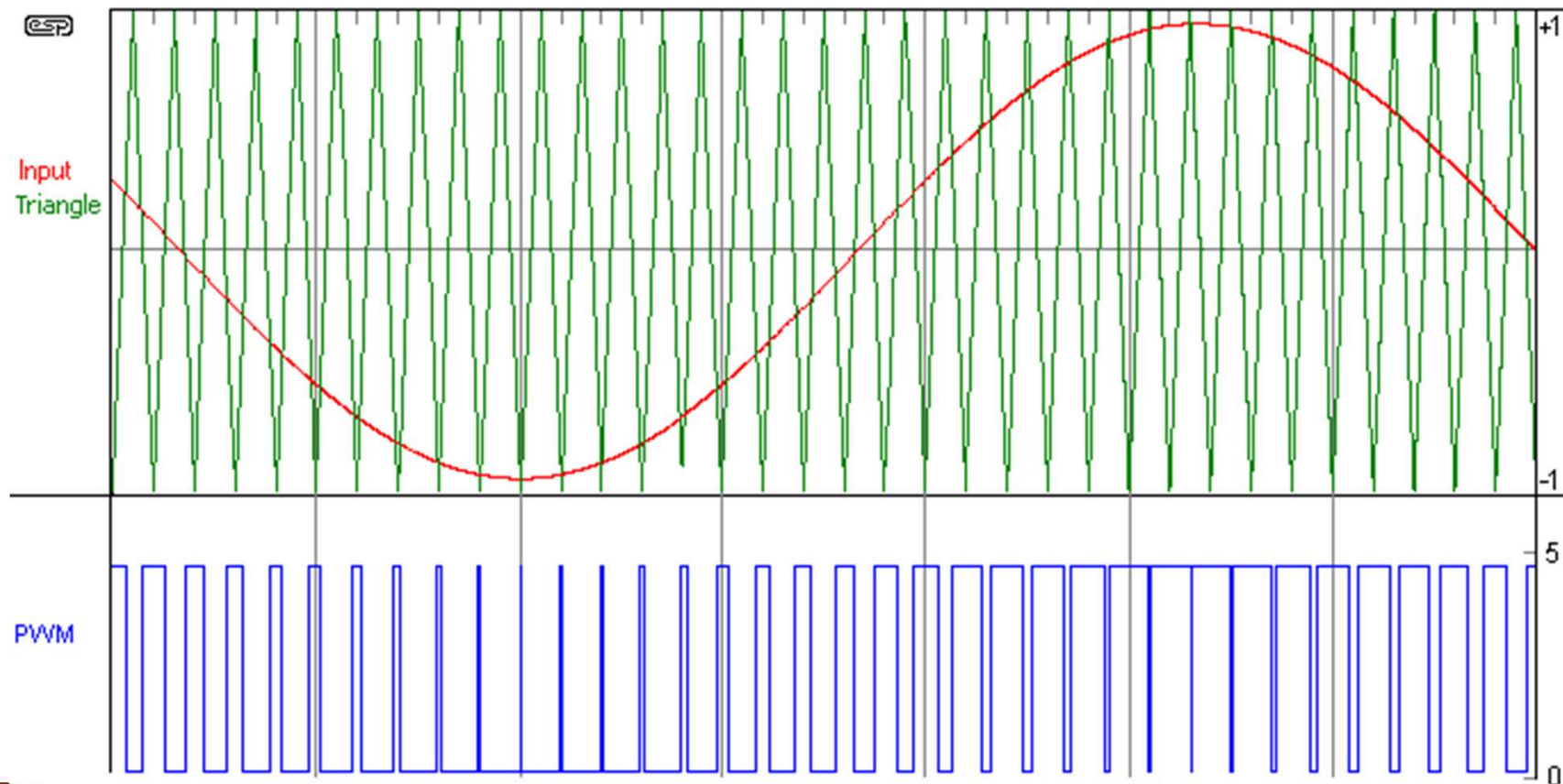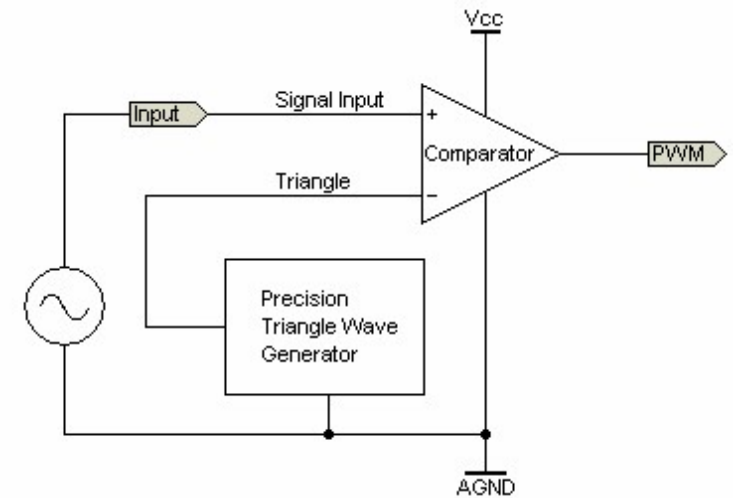- ❖ The sine wave swings between -1 and $+1$ V.
- ❖ It will produce 0% to 100% duty cycles
- ❖ 0% and 100% duty cycles correspond to -1 V and $+1$ V, respectively. 50% corresponds to 0V input.



Class D Amplifier

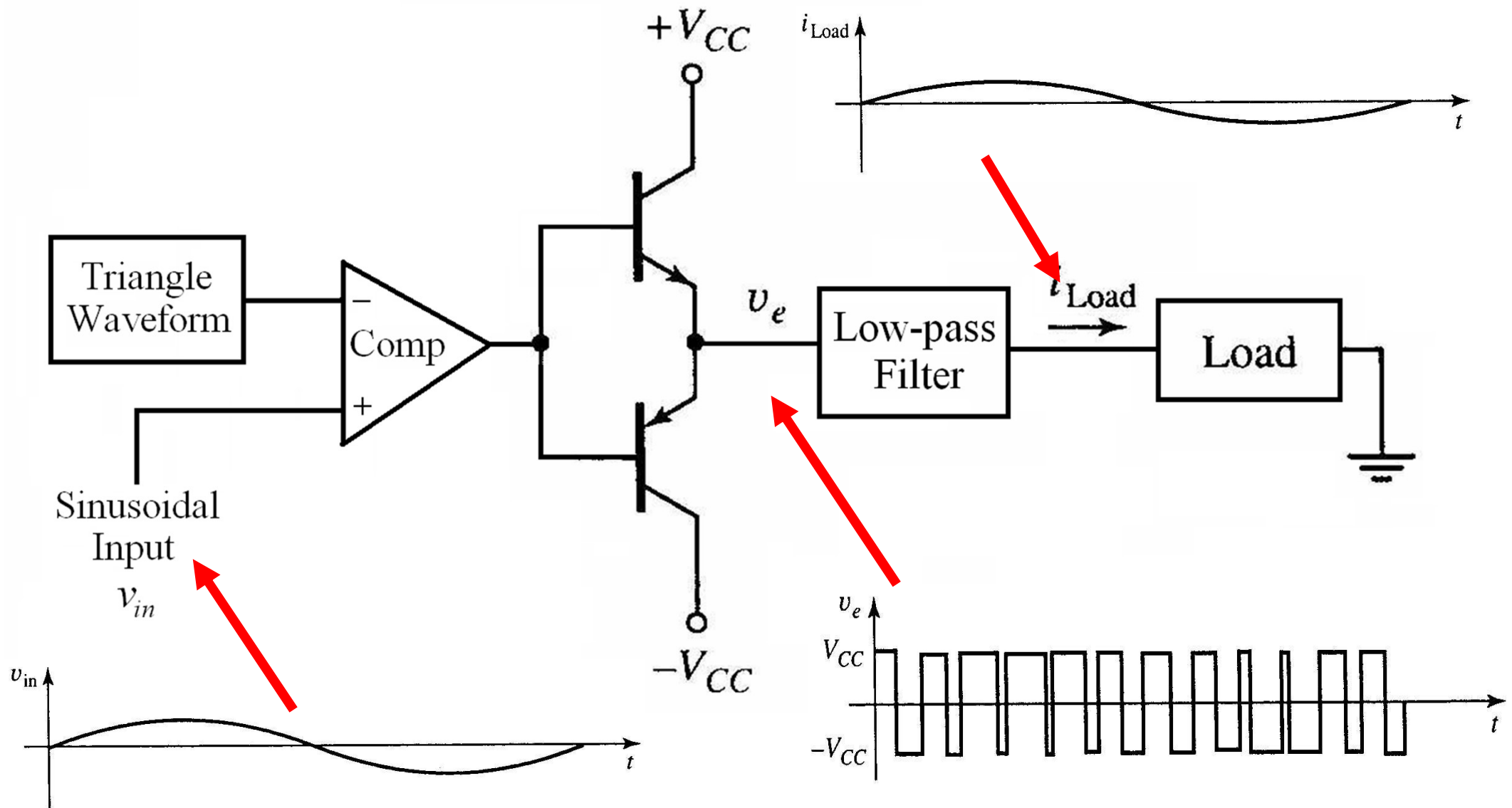

Class D Amplifier Efficiency


For 50% duty cycle ($d = 0.5$), the time-domain repetitive pulses with amplitude of $\pm V_{CC}$ has the following Fourier components in frequency-domain:

$$v_e = \frac{4V_{CC}}{\pi} \left(\sin \omega_s t + \frac{1}{3} \sin 3\omega_s t + \frac{1}{5} \sin 5\omega_s t + \dots \right)$$

where ω_s is the switching frequency.

When a sinusoidal inputs signal is applied, d is modulated sinusoidally about the Q-point of 0.5. The maximum possible output load voltage and current are:

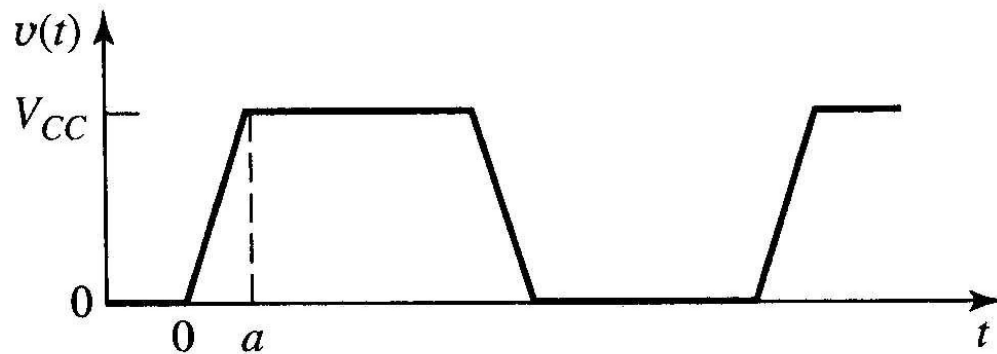
$$V_{max} = V_{CC} \quad I_{max} = \frac{V_{CC}}{R_L} \quad P_L = \frac{V_{CC}^2}{2R_L}$$



The voltage across the transistor and the current through the transistor from $t = 0$ to $t = a$:

$$v(t) = \frac{t}{a} V_{CC}$$
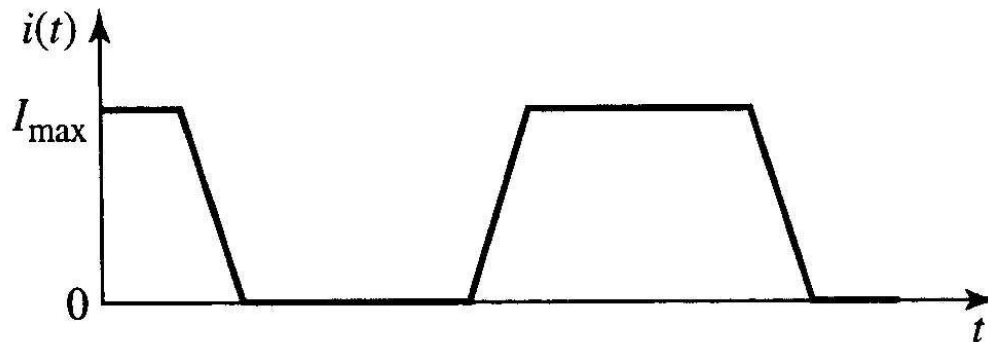
$$i(t) = I_{max} - \frac{t}{a} I_{max} = \frac{V_{CC}}{R_L} \left(1 - \frac{t}{a} \right)$$



The power dissipation for each transistor over the transition from $t = 0$ to $t = a$:

$$p(t) = v(t)i(t) = \frac{V_{CC}^2}{R_L} \left(\frac{t}{a} - \frac{t^2}{a^2} \right)$$

Each transistor makes two transitions in one period of the switching frequency. The average power dissipation for each transistor is:

$$P_T = 2 \times \frac{1}{T} \int_0^a \frac{V_{CC}^2}{R_L} \left(\frac{t}{a} - \frac{t^2}{a^2} \right) dt = \frac{2}{T} \left(\frac{V_{CC}^2}{R_L} \right) \left[\frac{t^2}{2a} - \frac{t^3}{3a^2} \right]_0^a = \frac{a}{T} \left(\frac{V_{CC}^2}{3R_L} \right)$$

The total power dissipation for two transistors:

$$2P_T = \frac{a}{T} \left(\frac{2V_{CC}^2}{3R_L} \right)$$

The conversion efficiency:

$$\eta = \frac{P_L}{P_L + 2P_T}$$

Note: the actual conversion efficiency is lower because of additional power dissipation in the low-pass filter and non-zero saturation voltage of the transistor.

Exercise #5: Determine the conversion efficiency for a Class D amplifier. Each switching transition is 5% of the period of the switching frequency. The power supplies are ± 24 V and the load resistance is $50\ \Omega$. Neglect the power dissipation in the low-pass filter.

$$2P_T = \frac{a}{T} \left(\frac{2V_{CC}^2}{3R_L} \right) = (0.05) \left(\frac{2 \times 24^2}{3 \times 50} \right) = 0.384\ \text{W}$$

$$P_L = \frac{V_{CC}^2}{2R_L} = \frac{24^2}{100} = 5.76\ \text{W}$$

$$\eta = \frac{P_L}{P_L + 2P_T} = \frac{5.76}{5.76 + 0.384} = 93.8\%$$

If considering finite saturation voltage of the transistor $V_{CE(sat)} = 0.4\text{V}$,

$$V_{max} = V_{CC} - V_{CE(sat)} = 24 - 0.4 = 23.6 \text{ V}$$


$$P_L = \frac{V_{max}^2}{2R_L} = \frac{(23.6)^2}{100} = 5.57 \text{ W}$$

$$I_{max} = \frac{V_{max}}{R_L} = \frac{23.6}{50} = 0.472 \text{ A}$$

$$2P_T = \frac{a}{T} \left(\frac{2V_{max}^2}{3R_L} \right) = (0.05) \left(\frac{2 \times 23.6^2}{3 \times 50} \right) = 0.371$$

$$\eta = \frac{P_L}{P_L + 2P_T + 0.9I_{max}V_{CE(sat)}} = \frac{5.57}{5.57 + 0.371 + 0.9 \times 0.472 \times 0.4} = 91.15\%$$

Heat Sinks

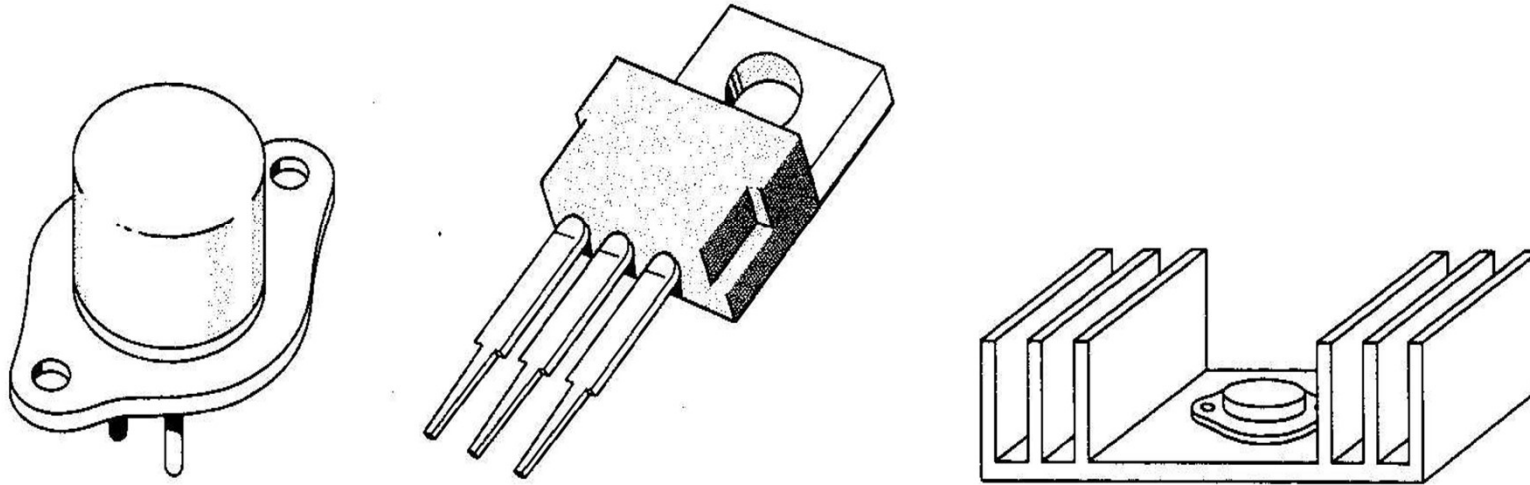

Heat sink removes the heat from the device's junction to prevent permanent damage.

$$T_2 - T_1 = P \theta$$

where $(T_2 - T_1)$ is the temperature difference across an element, θ is the **thermal resistance** of the element in unit of $^{\circ}\text{C}/\text{W}$ and P is the thermal power through the element.

Exercise #6: Determine the maximum power dissipation in a transistor without and with heat sink. With the heat sink, determine the temperature of the transistor case and heat sink. The ambient temperature is 30°C and the maximum device temperature is 150°C. The transistor and the heat sink thermal resistance parameters are:


$$\theta_{dev-case} = 1.75^{\circ} \text{ C/W}$$

$$\theta_{case-sink} = 1^{\circ} \text{ C/W}$$

$$\theta_{sink-amb} = 5^{\circ} \text{ C/W}$$

$$\theta_{case-amb} = 50^{\circ} \text{ C/W}$$

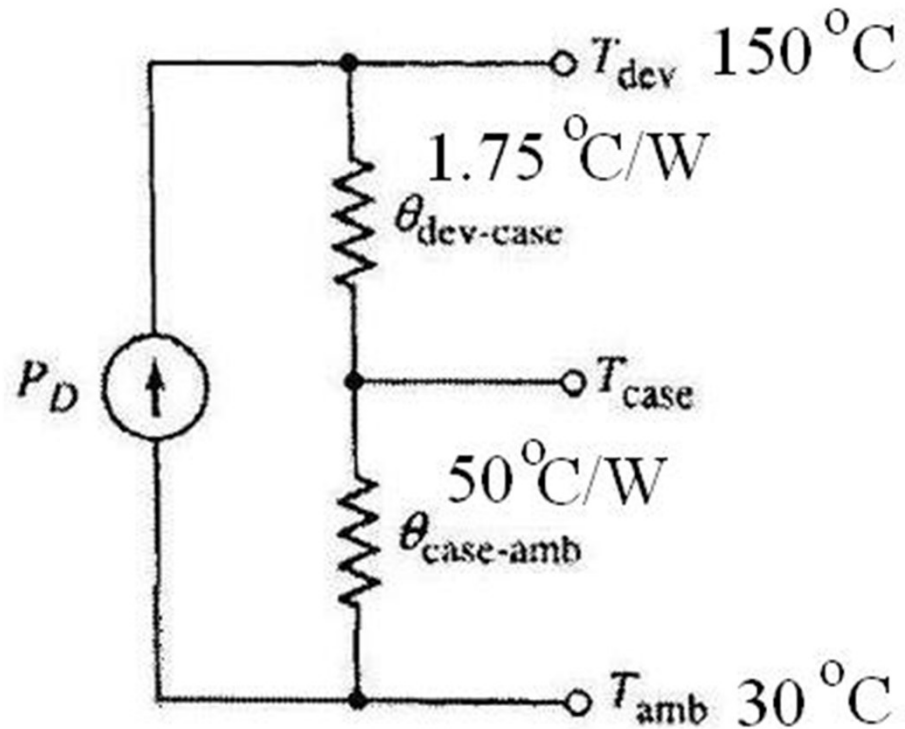When no heat sink is used, the maximum allowable power dissipation is:



$$\begin{aligned} P_{D,max} &= \frac{T_{j,max} - T_{amb}}{\theta_{dev-case} + \theta_{case-amb}} \\ &= \frac{150 - 30}{1.75 + 50} \\ &= 2.32 \text{ W} \end{aligned}$$

When a heat sink is used, the maximum allowable power dissipation is:

$$P_{D,max} = \frac{T_{j,max} - T_{amb}}{\theta_{dev-case} + \theta_{case-sink} + \theta_{sink-amb}}$$

$$= \frac{150 - 30}{1.75 + 1 + 5}$$

$$= 15.5 \text{ W}$$

Note: The use of heat sink allows more power to be dissipated (increased from 2.32 W to 15.5W)


$$T_{sink} - T_{amb} = P_D \theta_{sink-amb}$$

$$T_{sink} = P_D \theta_{sink-amb} + T_{amb}$$

$$= (15.5)(5) + 30 = 107.5^\circ \text{C}$$


$$T_{case} - T_{amb} = P_D (\theta_{case-sink} + \theta_{sink-amb})$$
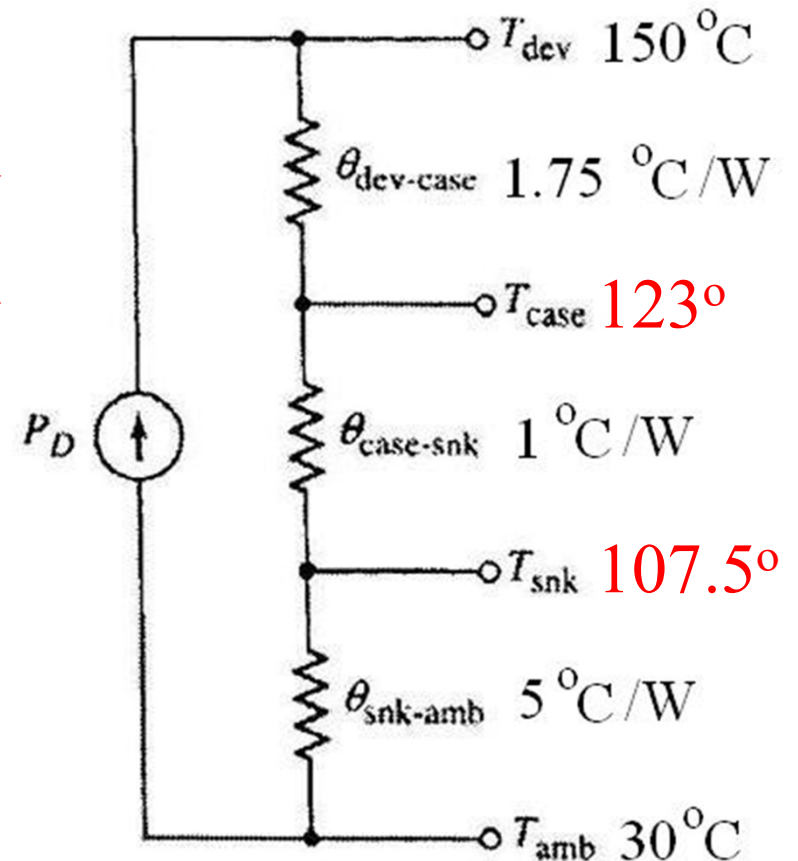
$$T_{case} = (15.5)(1 + 5) + 30 = 123^\circ \text{C}$$



Power Derating

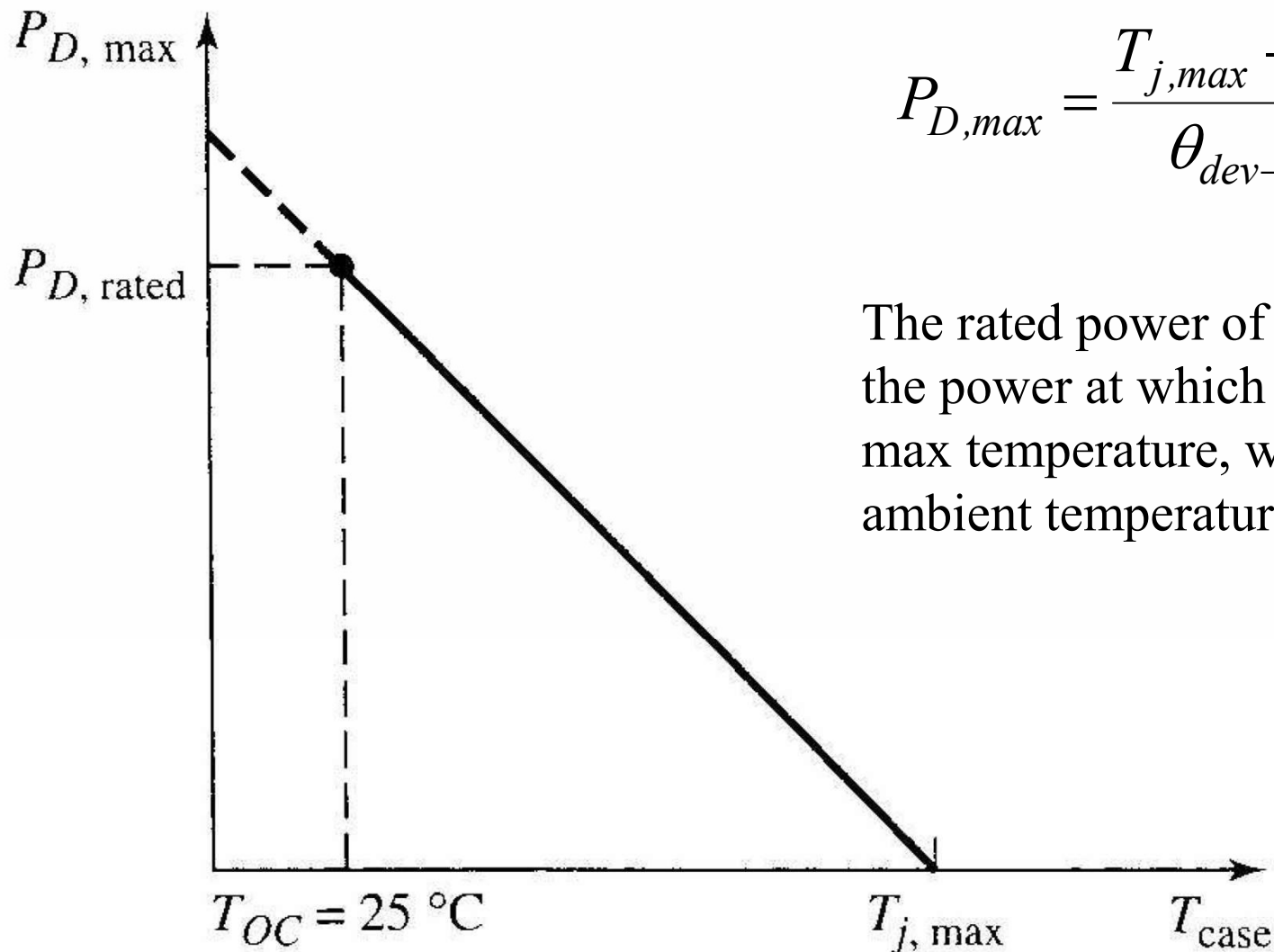The max safe power dissipation is determined by:



$$P_{D, \max} = \frac{T_{j, \max} - T_{\text{case}}}{\theta_{\text{dev-case}}}$$

The rated power of a device is defined as the power at which the device reaches its max temperature, while the case remains at ambient temperature.