
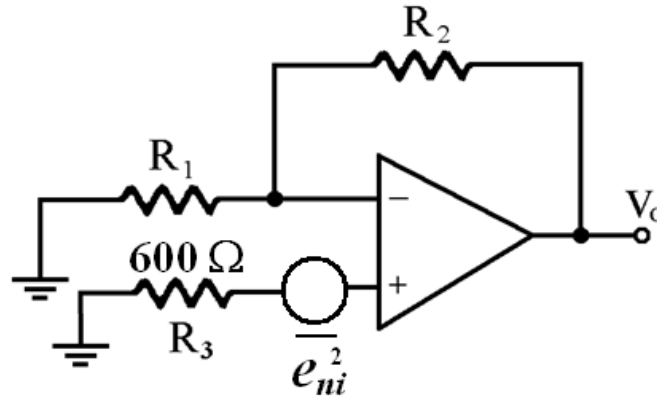


## EE4341 TUTORIAL 4 SOLUTION

1a. (i) Non-inverting amplifier

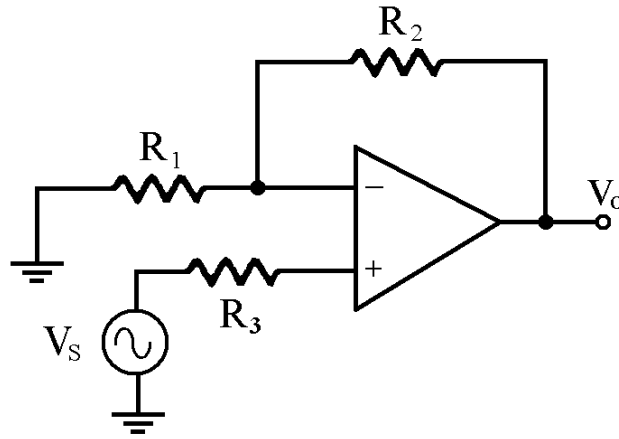


$R_1$  and  $R_2$  are chosen such that  $R_1 // R_2 = R_3$  for DC offset cancellation.

$$\begin{aligned}
 \overline{e_{ni}^2} &= \overline{v_n^2} + \overline{i_n^2} (R_3^2 + (R_1 // R_2)^2) + 4kT(R_3 + R_1 // R_2) \\
 &= \overline{v_n^2} + \overline{i_n^2} (2R_3^2) + 8kTR_3 \\
 &= 8 \times 10^{-16} + 9 \times 10^{-25} (2 \times 600^2) + 2 \times 1.656 \times 10^{-22} \times 600 \\
 &= 8 \times 10^{-16} + 6.48 \times 10^{-19} + 2 \times 10^{-17} \\
 &= 8.2 \times 10^{-16} \text{ V}^2 / \text{Hz}
 \end{aligned}$$

$$E_{ni} = \sqrt{\overline{e_{ni}^2} \Delta f} = \sqrt{8.2 \times 10^{-16} \times 20k} = 4.05 \text{ } \mu\text{V}$$

$$SNR(\text{dB}) = 20 \log \frac{V_s}{E_{ni}} = 20 \log \frac{5\text{mV}}{4.05 \mu\text{V}} = 61.8 \text{ dB}$$

1a. (ii) Inverting amplifier

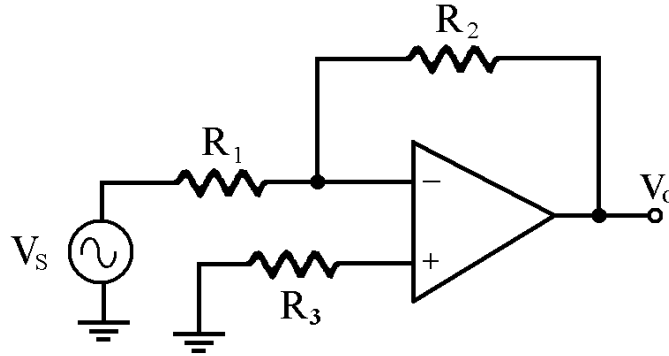

The voltage gain for the noise voltage is non-inverting amplifier gain:

$$\therefore \overline{e_{no}^2} = \overline{e_{ni+}^2} \left( 1 + \frac{R_2}{R_1} \right)^2 = \overline{e_{ni+}^2} \left( \frac{R_1 + R_2}{R_1} \right)^2$$

To reflect the noise at the inverting input:

$$\begin{aligned} \therefore \overline{e_{ni-}^2} &= \frac{\overline{e_{no}^2}}{(R_2/R_1)^2} = \overline{e_{ni+}^2} \left( \frac{R_1 + R_2}{R_1} \right)^2 \left( \frac{R_1}{R_2} \right)^2 \\ &= \overline{e_{ni+}^2} \left( \frac{R_1 + R_2}{R_2} \right)^2 = \overline{e_{ni+}^2} \left( 1 + \frac{R_1}{R_2} \right)^2 \end{aligned}$$

$$E_{ni-} = \left( 1 + \frac{R_1}{R_2} \right) E_{ni+} = \left( 1 + \frac{1}{10} \right) \times 4.05 = 4.46 \mu V$$

$$SNR(dB) = 20 \log \frac{V_s}{E_{ni}} = 20 \log \frac{5mV}{4.46 \mu V} = 61 \text{ dB}$$

1b. (i) Non-inverting amplifier

$$\begin{aligned}\overline{e_{ni}^2} &= \overline{v_n^2} + \overline{i_n^2} (2R_3^2) + 8kTR_3 \\ &= 16 \times 10^{-18} + 0 + 2 \times 1.656 \times 10^{-22} \times 600 \\ &= 3.6 \times 10^{-17} \text{ V}^2 / \text{Hz}\end{aligned}$$

$$E_{ni} = \sqrt{\overline{e_{ni}^2} \Delta f} = \sqrt{3.6 \times 10^{-17} \times 20k} = 0.85 \text{ } \mu\text{V}$$


$$SNR(\text{dB}) = 20 \log \frac{V_s}{E_{ni}} = 20 \log \frac{5\text{mV}}{0.85 \mu\text{V}} = 75.4 \text{ dB}$$

(ii) Inverting amplifier:

$$E_{ni-} = \left(1 + \frac{R_1}{R_2}\right) E_{ni+} = \left(1 + \frac{1}{10}\right) \times 0.85 = 0.94 \mu\text{V}$$

$$SNR(\text{dB}) = 20 \log \frac{V_s}{E_{ni}} = 20 \log \frac{5\text{mV}}{0.94 \mu\text{V}} = 74.5 \text{ dB}$$

2.

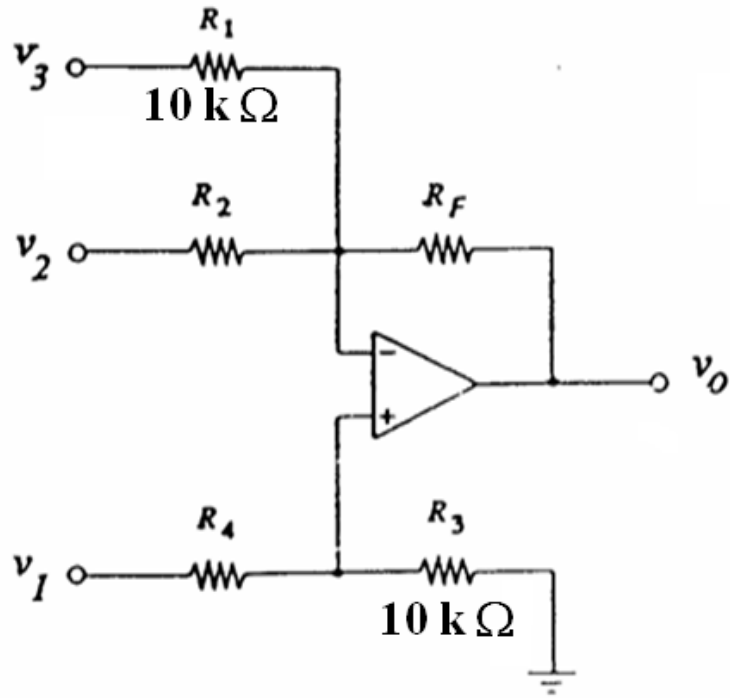

$$v_o = 2(v_1 - v_2 - v_3) = 2v_1 - 2v_2 - 2v_3$$

$$v_{o3} = -\frac{R_F}{R_1} v_3 = -2v_3$$

$$\therefore \frac{R_F}{R_1} = 2 \Rightarrow R_F = 2R_1 = 20\text{k}\Omega$$

$$v_{o2} = -\frac{R_F}{R_2} v_2 = -2v_2$$

$$\therefore \frac{R_F}{R_2} = 2 \Rightarrow R_2 = \frac{R_F}{2} = 10\text{k}\Omega$$

$$\begin{aligned} v_{o1} &= \left( \frac{R_3}{R_3 + R_4} \right) v_1 \left( 1 + \frac{R_F}{R_1 // R_2} \right) = \left( \frac{R_3}{R_3 + R_4} \right) v_1 \left( 1 + \frac{20k}{5k} \right) \\ &= 5v_1 \left( \frac{R_3}{R_3 + R_4} \right) = 2v_1 \end{aligned}$$

$$\therefore \frac{5R_3}{R_3 + R_4} = 2 \Rightarrow R_4 = \frac{3R_3}{2} = 15k\Omega$$

$$R_n = R_1 // R_2 // R_F = 10k // 10k // 20k = 4k\Omega$$

$$R_p = R_4 // R_3 = 15k // 10k = 6k\Omega$$

The non-inverting amplifier gain for the noise:

$$A_v = 1 + \frac{R_F}{R_1 // R_2} = 1 + \frac{20k}{5k} = 5$$

The -3dB bandwidth of the non-inverting amplifier:

$$f_A = \frac{GBW}{A_v} = \frac{10^6}{5} = 200kHz$$

$$\begin{aligned} E_{no} &= A_v \left[ e_{nw}^2 \left( f_{ce} \ln \frac{1.57 f_A}{f_L} + 1.57 f_A - f_L \right) + \right. \\ &\quad \left. (R_p^2 + R_n^2) i_{nw}^2 \left( f_{ci} \ln \frac{1.57 f_A}{f_L} + 1.57 f_A - f_L \right) + 4kT(R_p + R_n)(1.57 f_A - f_L) \right]^{\frac{1}{2}} \\ &= 5 \left[ (20 \times 10^{-9})^2 \left( 200 \ln \frac{314k}{1} + 314k - 1 \right) + \right. \\ &\quad \left. ((6k)^2 + (4k)^2) (0.5 \times 10^{-12})^2 \left( 2000 \ln \frac{314k}{1} + 314k - 1 \right) + \right. \\ &\quad \left. 1.656 \times 10^{-20} (6k + 4k)(314k - 1) \right]^{\frac{1}{2}} \end{aligned}$$

$$E_{no} = 5 \left[ 1.27 \times 10^{-10} + 4.41 \times 10^{-12} + 5.20 \times 10^{-11} \right]^{\frac{1}{2}} = 67.64 \mu V$$

$$E_{no,p-p} = 6.6 E_{no, rms} = 6.6 \times 67.64 \mu V = 0.45 mV$$