

NANYANG TECHNOLOGICAL UNIVERSITY
SCHOOL OF ELECTRICAL & ELECTRONIC ENGINEERING
EE4341 ADVANCED ANALOG CIRCUITS
TUTORIAL 2

1. Calculate the mean-squared noise-voltage spectral density in V^2/Hz at v_o for the circuit in Fig. 1 and then calculate the rms noise voltage in a 100 kHz equivalent noise bandwidth. Neglect capacitive effects, flicker noise and series resistance in the diode. Assume that $V_D = 0.60\text{V}$. Boltzmann's constant $k = 1.38 \times 10^{-23} \text{ J/K}$, $q = 1.6 \times 10^{-19} \text{ C}$ and $T = 300\text{K}$. If a 1000 pF capacitor is now connected across the diode, including flicker noise, calculate and plot the output mean-squared noise voltage spectral density at v_o in V^2/Hz on log scales from $f = 1\text{Hz}$ to $f = 10 \text{ MHz}$. Flicker noise spectral density $= 3 \times 10^{-16} (I_D/f) \text{ A}^2/\text{Hz}$.

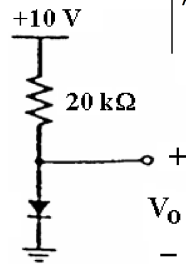


Fig. 1

$$\text{Answer } \overline{v_o^2} = \left(4.6 \times 10^{-19} + \frac{4.3 \times 10^{-16}}{f} \right) \frac{1}{1 + \left(\frac{f}{f_o} \right)^2} \text{ V}^2/\text{Hz}$$

2. The amplifier circuit in Fig. 2 has a -3dB bandwidth of 10 kHz (single-pole response). Boltzmann's constant $k = 1.38 \times 10^{-23} \text{ J/K}$, $q = 1.6 \times 10^{-19} \text{ C}$ and $T = 300\text{K}$. Ignoring flicker noise and the thermal noise of the load resistance, determine the value of v_s so that $\text{SNR} = 0 \text{ dB}$. Show that if a BJT is driven from a signal source with a source resistance R_s , the value of biasing collector current for maximum sensitivity is given by the following expression.

$$I_c = \frac{V_T \sqrt{\beta}}{R_s + r_{bb'}}, \text{ where } V_T = kT/q.$$

Determine the value of I_c for max SNR for the amplifier circuit shown in Fig. 2. What is v_s for $\text{SNR} = 0 \text{ dB}$ under the new biasing condition? | Answer $I_c = 2.9 \text{ mA}$ $V_s = 176 \text{ nV}$ |

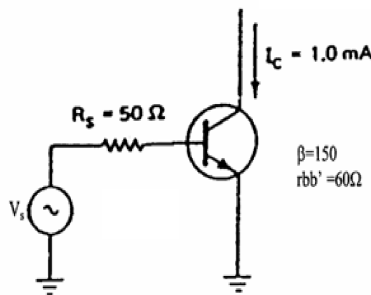


Fig. 2